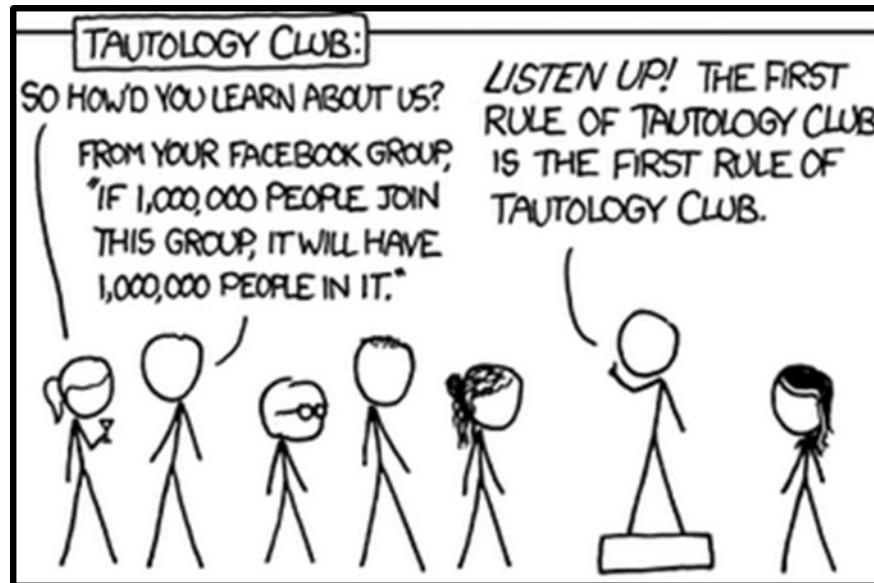


CSE 311: Foundations of Computing

Lecture 3: Digital Circuits



HW1 section out
sol's posted
OH posted
COTY

Review: Propositional Logic

Propositions

- atomic propositions are T/F-valued variables
- combined using logical connectives (not, and, or, etc.)
- can be described by a truth table
 - shows the truth value of the proposition in each combination of truth values of the atomic propositions

p	q	$p \wedge q$
T	T	T
T	F	F
F	T	F
F	F	F

Logical equivalence

- used to simplify logical expressions



First application

- Simplifying English sentences

Truth Table to show tautology

Option 1

$$(p \wedge r) \rightarrow (r \vee p)$$

$$(p \wedge r) \rightarrow (r \vee p) \equiv T$$

p	r	$p \wedge r$	$r \vee p$	$(p \wedge r) \rightarrow (r \vee p)$
T	T	T	T	T
T	F	F	T	T
F	T	F	T	T
F	F	F	F	T

Logical Proofs of Equivalence

Option 2

$$(p \wedge r) \rightarrow (r \vee p) \equiv \top$$

Use a series of equivalences like so:

$$\begin{aligned} (p \wedge r) \rightarrow (r \vee p) &\equiv \neg(p \wedge r) \vee (r \vee p) \\ &\equiv (\neg p \vee \neg r) \vee (r \vee p) \\ &\equiv \neg p \vee (\neg r \vee (r \vee p)) \\ &\equiv \neg p \vee ((\neg r \vee r) \vee p) \\ &\equiv \neg p \vee (p \vee (\neg r \vee r)) \\ &\equiv (\neg p \vee p) \vee (\neg r \vee r) \\ &\equiv (p \vee \neg p) \vee (r \vee \neg r) \\ &\equiv \top \vee \top \\ &\equiv \top \end{aligned}$$



Identity

- $p \wedge \top \equiv p$
- $p \vee \text{F} \equiv p$

Domination

- $p \vee \top \equiv \top$
- $p \wedge \text{F} \equiv \text{F}$

Idempotent

- $p \vee p \equiv p$
- $p \wedge p \equiv p$

Commutative

- $p \vee q \equiv q \vee p$
- $p \wedge q \equiv q \wedge p$

Law of Implication

De Morgan

Associative

Associative

Commutative

Associative

Commutative (twice)

Negation (twice)

Domination/Identity

Logical Proofs of Equivalence/Tautology

- Not smaller than truth tables when there are only a few propositional variables...
 - ...but usually *much shorter* than truth table proofs when there are many propositional variables
- A big advantage will be that we can extend them to a more in-depth understanding of logic for which truth tables don't apply.

Another key application: Digital Circuits

351?

Computing With Logic


- T corresponds to 1 or “high” voltage
- F corresponds to 0 or “low” voltage

Gates

- Take inputs and produce outputs (functions)
- Several kinds of gates
- Correspond to propositional connectives (most of them)

Circuits: AND, OR, NOT Gates


AND Gate

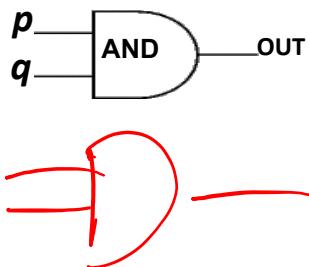

p	q	OUT
1	1	1
1	0	0
0	1	0
0	0	0

p	q	$p \wedge q$
T	T	T
T	F	F
F	T	F
F	F	F


OR Gate

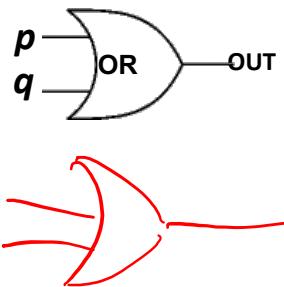

p	q	OUT
1	1	1
1	0	1
0	1	1
0	0	0

p	q	$p \vee q$
T	T	T
T	F	T
F	T	T
F	F	F


NOT Gate

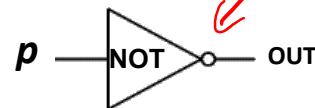

p	OUT
1	0
0	1


p	$\neg p$
T	F
F	T

Combinational Logic Circuits

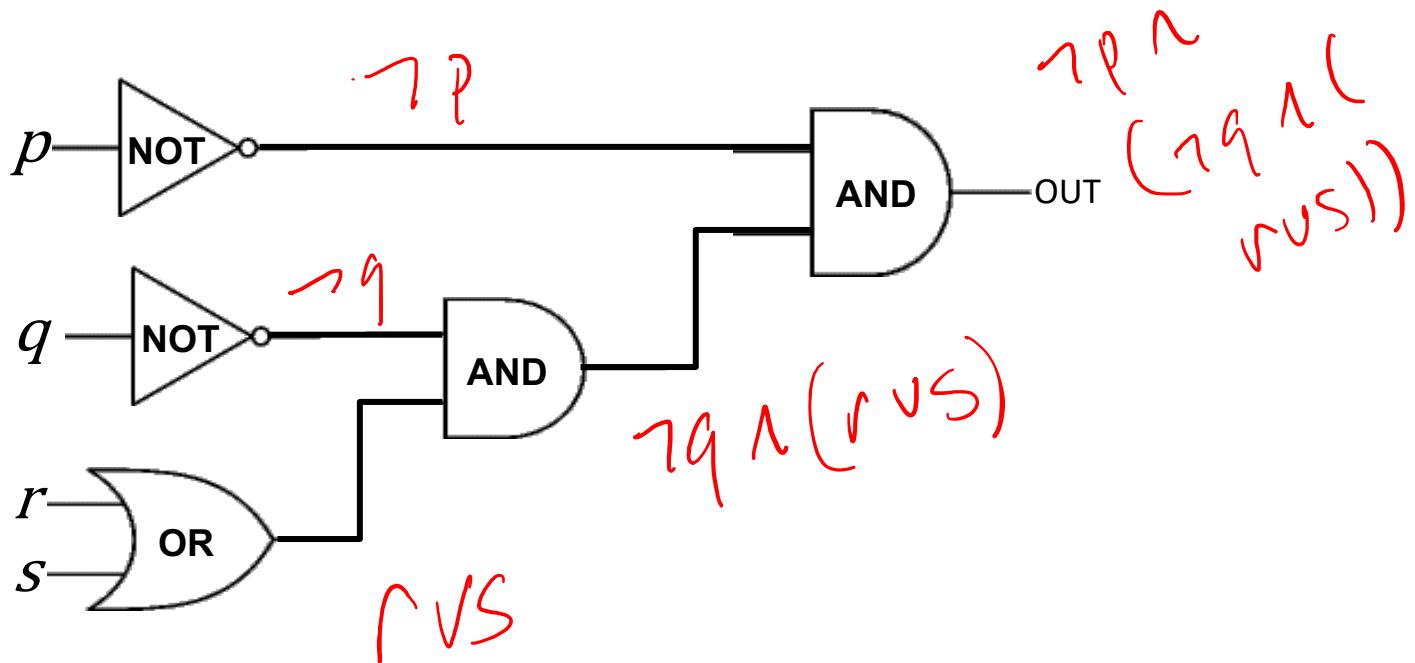

Values get sent along wires connecting gates


Combinational Logic Circuits

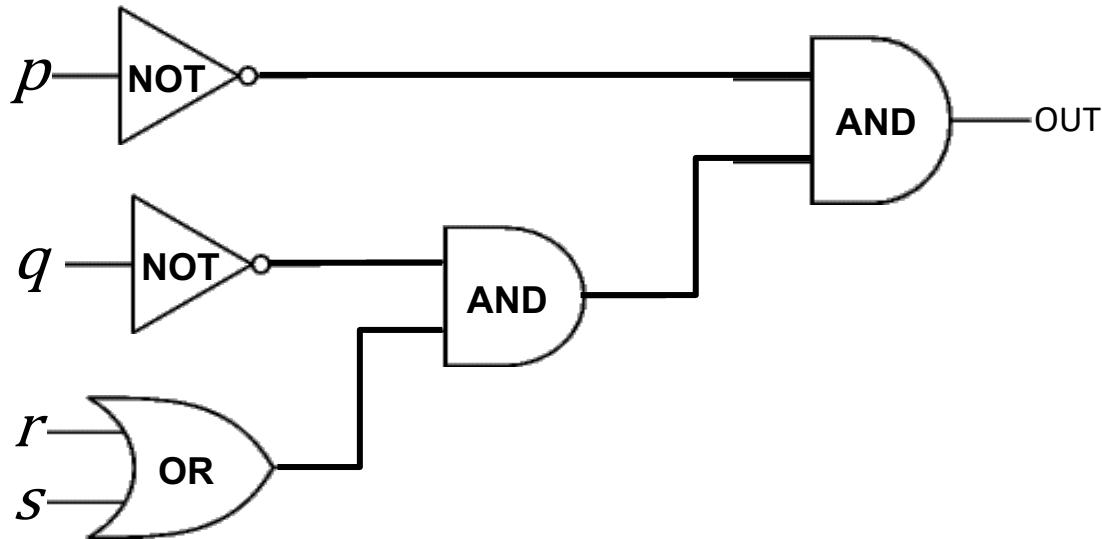

Values get sent along wires connecting gates


$$\neg p \wedge (\neg q \wedge (r \vee s))$$

Combinational Logic Circuits

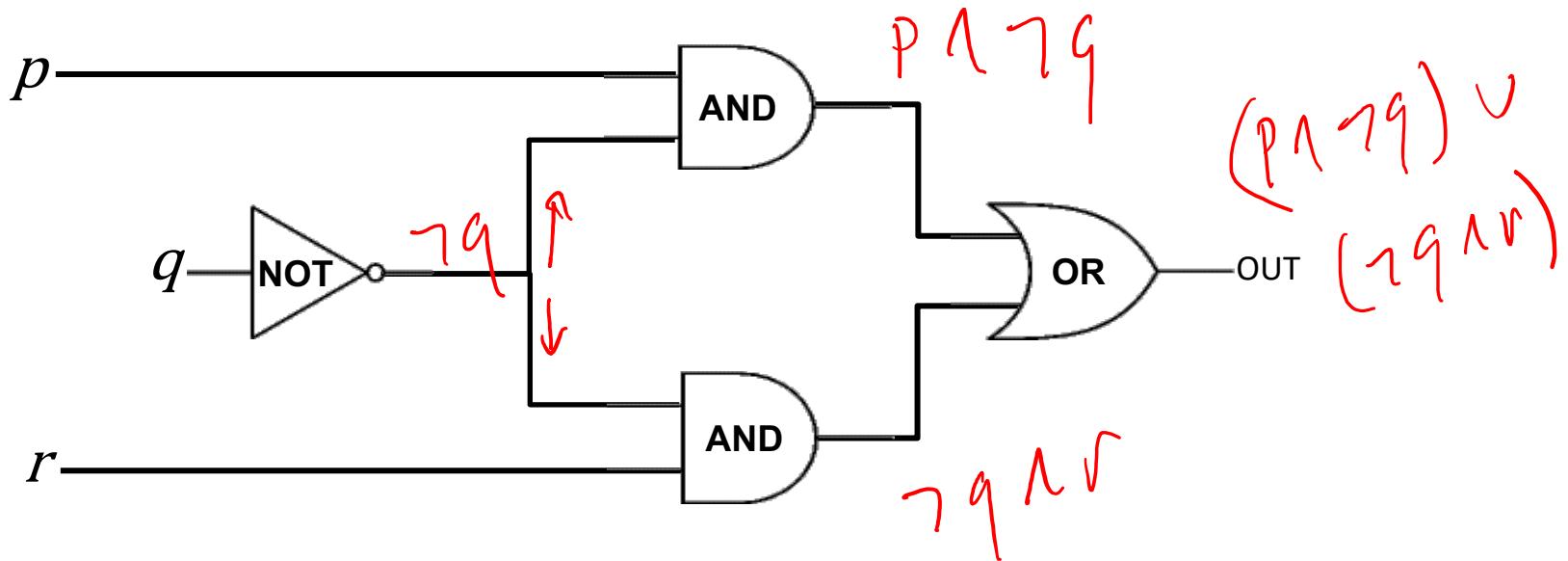

Wires can send one value to multiple gates!

Combinational Logic Circuits

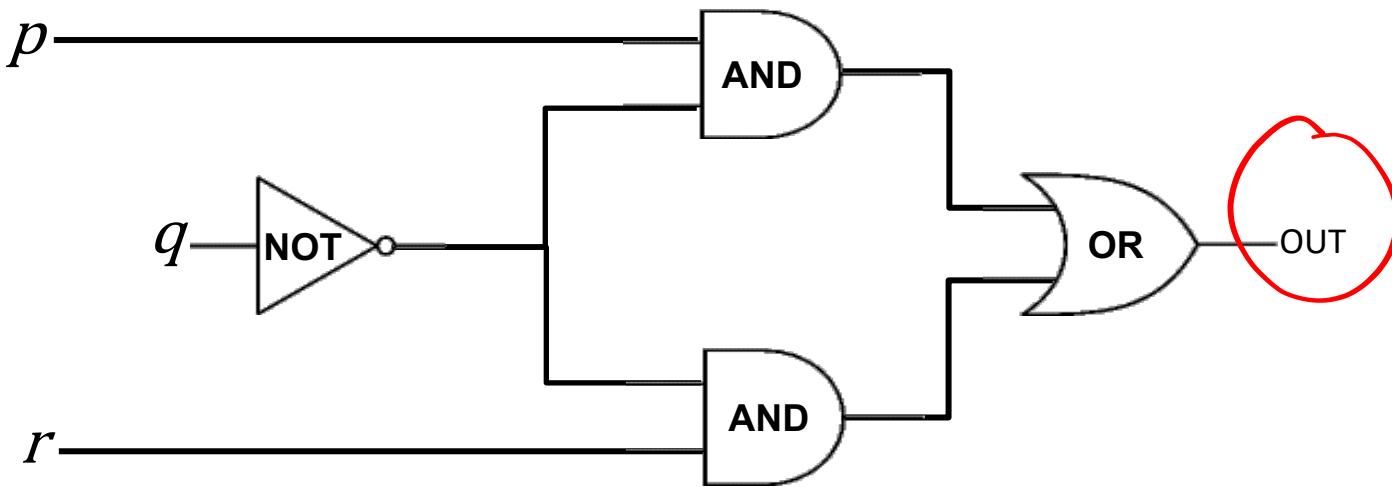

Wires can send one value to multiple gates!


$$(p \wedge \neg q) \vee (\neg q \wedge r)$$

Other Useful Gates



NAND


$$\neg(p \wedge q)$$

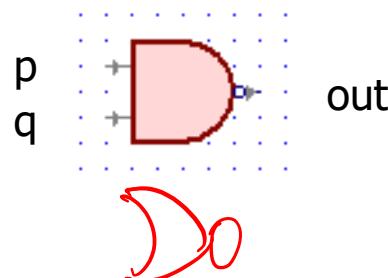

p	q	out
0	0	1
0	1	1
1	0	1
1	1	0

NOR


$$\neg(p \vee q)$$

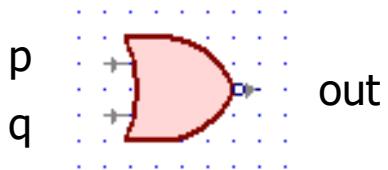

p	q	out
0	0	1
0	1	0
1	0	0
1	1	0

XOR


$$p \oplus q$$

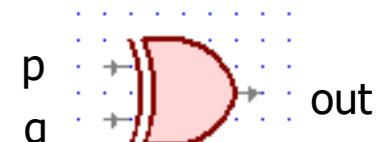

p	q	out
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

$$p \leftrightarrow q$$

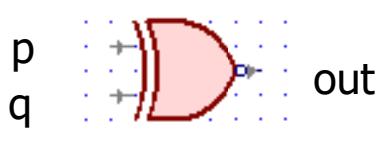

p	q	out
0	0	1
0	1	0
1	0	0
1	1	1

$$\neg(p \oplus q)$$

Boolean Logic

Combinational Logic

- $\underline{\text{output}} = F(\underline{\text{input}})$

Sequential Logic

- $\text{output}_t = F(\text{output}_{t-1}, \text{input}_t)$
 - output dependent on history
 - concept of a time step (clock, t)
- Covered in CSE 369

Boolean Logic

Combinational Logic

- output = $F(\text{input})$



Boolean Algebra: another notation for logic consisting of...

- a set of elements $B = \{0, 1\}$
- binary operations $\{ +, \cdot \}$ (OR, AND)
- and a unary operation $\{ '\}$ (NOT)


x' $\neg x$

\vee \wedge
 \neg

Boolean Algebra

= vs ≡

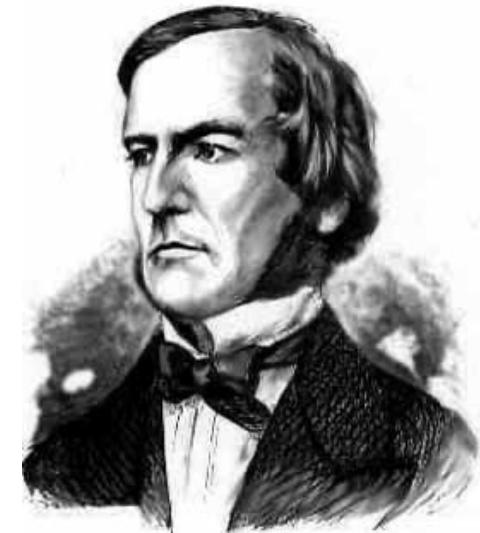- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing {0, 1}
 - binary operations { + , • }
 - and a unary operation { ' }
 - such that the following axioms hold:



For any a, b, c in B :

1. closure:
2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned} & a + b \text{ is in } B \\ & a + b = b + a \\ & a + (b + c) = (a + b) + c \\ & a + (b \cdot c) = (a + b) \cdot (a + c) \\ & a + 0 = a \\ & a + a' = 1 \\ & a + 1 = 1 \\ & a + a = a \\ & (a')' = a \end{aligned}$$

$$\begin{aligned} & a \cdot b \text{ is in } B \\ & a \cdot b = b \cdot a \\ & a \cdot (b \cdot c) = (a \cdot b) \cdot c \\ & a \cdot (b + c) = (a \cdot b) + (a \cdot c) \\ & a \cdot 1 = a \\ & a \cdot a' = 0 \\ & a \cdot 0 = 0 \\ & a \cdot a = a \end{aligned}$$

Proving Theorems

Using truth table:

For example, de Morgan's Law:

$$(X + Y)' = X' \bullet Y'$$

NOR is equivalent to AND
with inputs complemented

X	Y	X'	Y'	(X + Y)'	X' • Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(X \bullet Y)' = X' + Y'$$

NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	(X • Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

More generally $(a + b + c + \dots)' = a' \bullet b' \bullet c' \bullet \dots$

$(a \bullet b \bullet c \bullet \dots)' = a' + b' + c' + \dots$

Proving Theorems

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned} a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a = a & \\ (a')' = a & \end{aligned}$$

$$\begin{aligned} a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a = a & \end{aligned}$$

Using the laws of Boolean Algebra:

prove the “Uniting theorem”:

$$\begin{aligned} X \cdot Y + \underline{X \cdot Y'} &= X \\ X \cdot Y + X \cdot Y' &= \cancel{X} \cdot (Y + Y') \\ &= X \cdot 1 \\ &= X \end{aligned}$$

prove the “Absorption theorem”:

$$\begin{aligned} X + X \cdot Y &= X \\ X + X \cdot Y &= \end{aligned}$$

Proving Theorems

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned} a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a = a & \\ (a')' = a & \end{aligned}$$

$$\begin{aligned} a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a = a & \end{aligned}$$

Using the laws of Boolean Algebra:

prove the “Uniting theorem”:

$$X \cdot Y + X \cdot Y' = X$$

distributivity

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\ &= X \cdot 1 \\ &= X \end{aligned}$$

complementarity

identity

prove the “Absorption theorem”:

$$X + X \cdot Y = X$$

identity

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y \\ &= X \cdot (1 + Y) \\ &= X \cdot (Y + 1) \\ &= X \cdot 1 \\ &= X \end{aligned}$$

distributivity

commutativity

null

identity

A Combinational Logic Example

Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**
Input: (Monday, Section) Output: **1**

Implementation in Software


```
public int classesLeftInMorning(int weekday, boolean isLecture) {  
    switch (weekday) {  
        case SUNDAY:  
        case MONDAY:  
            return isLecture ? 3 : 1;  
        case TUESDAY:  
        case WEDNESDAY:  
            return isLecture ? 2 : 1;  
        case THURSDAY:  
            return isLecture ? 1 : 1;  
        case FRIDAY:  
            return isLecture ? 1 : 0;  
        case SATURDAY:  
            return isLecture ? 0 : 0;  
    }  
}
```

Implementation with Combinational Logic

Encoding:

- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output

one hot

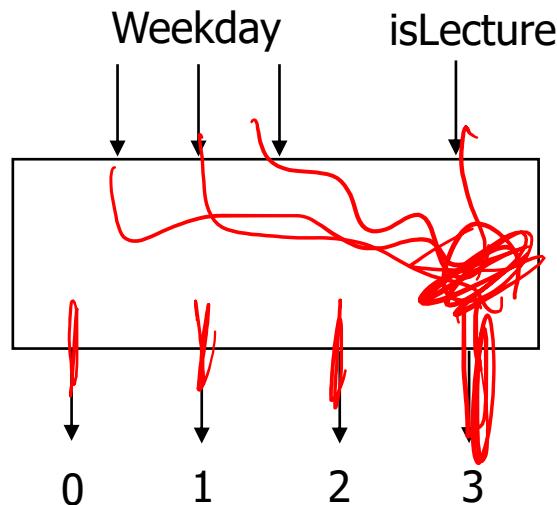

Defining Our Inputs!

Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	(000) ₂
Monday	1	(001) ₂
Tuesday	2	(010) ₂
Wednesday	3	(011) ₂
Thursday	4	(100) ₂
Friday	5	(101) ₂
Saturday	6	(110) ₂

Converting to a Truth Table!

```
case SUNDAY or MONDAY:  
    return isLecture ? 3 : 1;  
  
case TUESDAY or WEDNESDAY:  
    return isLecture ? 2 : 1;  
  
case THURSDAY:  
    return isLecture ? 1 : 1;  
  
case FRIDAY:  
    return isLecture ? 1 : 0;  
  
case SATURDAY:  
    return isLecture ? 0 : 0;
```

Weekday	isLecture	c ₀	c ₁	c ₂	c ₃
SUN	000	0			
SUN	000	1			
MON	001	0			
MON	001	1	0	0	0
TUE	010	0			
TUE	010	1			
WED	011	0			
WED	011	1			
THU	100	-			
FRI	101	0			
FRI	101	1			
SAT	110	-			
-	111	-			

Converting to a Truth Table!

```
case SUNDAY or MONDAY:  
    return isLecture ? 3 : 1;  
  
case TUESDAY or WEDNESDAY:  
    return isLecture ? 2 : 1;  
  
case THURSDAY:  
    return isLecture ? 1 : 0;  
  
case FRIDAY:  
    return isLecture ? 1 : 0;  
  
case SATURDAY:  
    return isLecture ? 0 : 0;
```

Weekday	isLecture	c_0	c_1	c_2	c_3
SUN	000	0	1	0	0
SUN	000	1	0	0	1
MON	001	0	1	0	0
MON	001	1	0	0	1
TUE	010	0	1	0	0
TUE	010	1	0	1	0
WED	011	0	1	0	0
WED	011	1	0	1	0
THU	100	-	0	1	0
FRI	101	0	1	0	0
FRI	101	1	0	1	0
SAT	110	-	1	0	0
	-	111	-	1	0
					1

Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Let's begin by finding an expression for c_3 . To do this, we look at the rows where $c_3 = 1$ (true).

$$d_2' \cdot d_1' \cdot d_0' \cdot L + \\ d_2' \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	1	0	0
SUN	000	1	0	0	1
MON	001	0	1	0	0
MON	001	1	0	0	1
TUE	010	0	1	0	0
TUE	010	1	0	1	0
WED	011	0	1	0	0
WED	011	1	0	1	0
THU	100	-	0	1	0
FRI	101	0	1	0	0
FRI	101	1	0	1	0
SAT	110	-	1	0	0
-	111	-	1	0	0

DAY == SUN && L == 1

DAY == MON && L == 1

Truth Table to Logic (Part 1)

$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN	000	0	1	0	0
SUN	000	1	0	0	1
MON	001	0	1	0	0
MON	001	1	0	0	1
TUE	010	0	1	0	0
TUE	010	1	0	0	1
WED	011	0	1	0	0
WED	011	1	0	0	1
THU	100	-	0	1	0
FRI	101	0	1	0	0
FRI	101	1	0	1	0
SAT	110	-	1	0	0
-	111	-	1	0	0

$d_2d_1d_0 == 000 \&& L == 1$

$d_2d_1d_0 == 001 \&& L == 1$

Substituting DAY for the binary representation.

Truth Table to Logic (Part 1)

$d_2d_1d_0$	L	c_0	c_1	c_2	c_3
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

→ $d_2 == 0 \&& d_1 == 0 \&& d_0 == 0 \&& L == 1$

→ $d_2 == 0 \&& d_1 == 0 \&& d_0 == 1 \&& L == 1$

Splitting up the bits of the day;
so, we can write a formula.

Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Replacing with
Boolean Algebra...

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

How do we combine them?

Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Either situation causes c_3 to be true. So, we “or” them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 2)

	$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	
TUE	010	1	0	0	1	0	$d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
WED	011	0	0	1	0	0	
WED	011	1	0	0	1	0	$d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
THU	100	-	0	1	0	0	
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do c_2 .

$$d_2' \cdot d_1' \cdot d_0' \cdot L +$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Now, we do c_1 :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2 \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3	
SUN 000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN 000	1	0	0	0	1	
MON 001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON 001	1	0	0	0	1	
TUE 010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE 010	1	0	0	1	0	
WED 011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED 011	1	0	0	1	0	
THU 100	-	0	1	0	0	???
FRI 101	0	1	0	0	0	
FRI 101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT 110	-	1	0	0	0	
- 111	-	1	0	0	0	

Now, we do c_1 :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3	
SUN 000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN 000	1	0	0	0	1	
MON 001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON 001	1	0	0	0	1	
TUE 010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE 010	1	0	0	1	0	
WED 011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED 011	1	0	0	1	0	
THU 100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI 101	0	1	0	0	0	
FRI 101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT 110	-	1	0	0	0	
- 111	-	1	0	0	0	

Now, we do c_1 :

$$d_2' \cdot d_1' \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L'$$

$$d_2 \cdot d_1' \cdot d_0'$$

$$d_2 \cdot d_1' \cdot d_0 \cdot L$$

No matter what L is,
we always say it's 1.
So, we don't need L
in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2 \cdot d_1 \cdot d_0' \cdot L + d_2 \cdot d_1 \cdot d_0 \cdot L$$

Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3	
SUN 000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN 000	1	0	0	0	1	
MON 001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON 001	1	0	0	0	1	
TUE 010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE 010	1	0	0	1	0	
WED 011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED 011	1	0	0	1	0	
THU 100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI 101	0	1	0	0	0	
FRI 101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT 110	-	1	0	0	0	
- 111	-	1	0	0	0	

Now, we do c_1 :

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2 \cdot d_1 \cdot d_0' \cdot L + d_2 \cdot d_1 \cdot d_0 \cdot L$$

No matter what L is,
we always say it's 1.
So, we don't need L
in the expression.

Truth Table to Logic (Part 4)

	$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3	
SUN	000	0	0	1	0	0	$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' +$ $d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' +$ $d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$
SUN	000	1	0	0	0	1	$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$
MON	001	0	0	1	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	
FRI	101	0	1	0	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L'$
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	$d_2 \cdot d_1 \cdot d_0'$
-	111	-	1	0	0	0	$d_2 \cdot d_1 \cdot d_0$

Finally, we do c_0 :


Truth Table to Logic (Part 4)

$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$



$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' \cdot L' + d_2 \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$
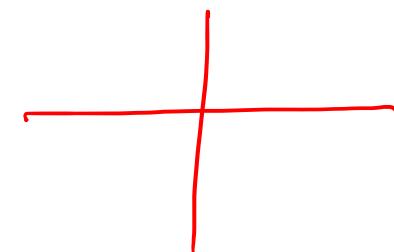
$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$



Here's c_3 as a circuit:

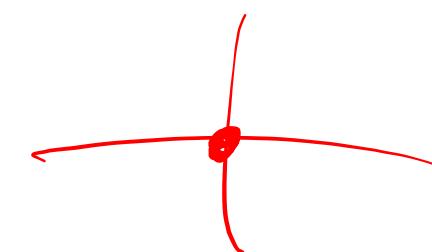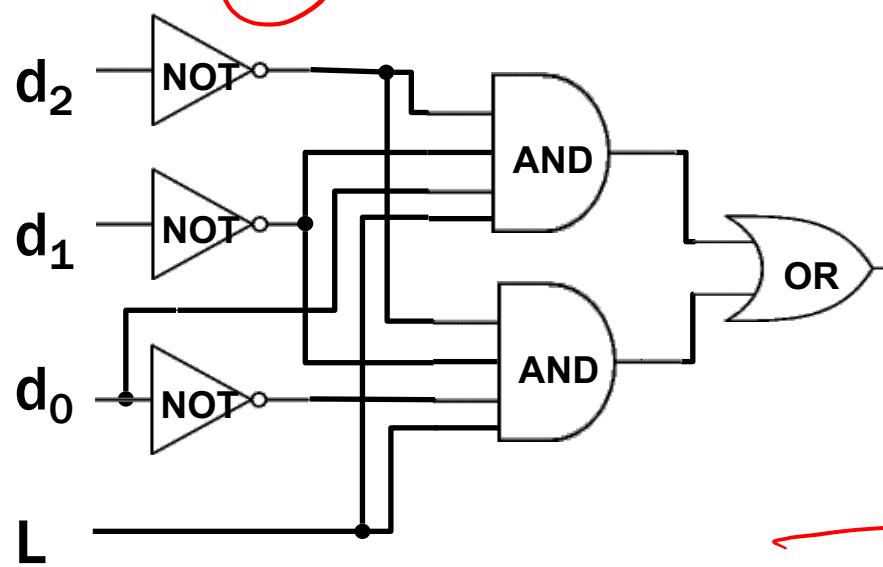

Simplifying using Boolean Algebra

$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\&= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\&= d2' \cdot d1' \cdot 1 \cdot L \\&= d2' \cdot d1' \cdot L\end{aligned}$$

