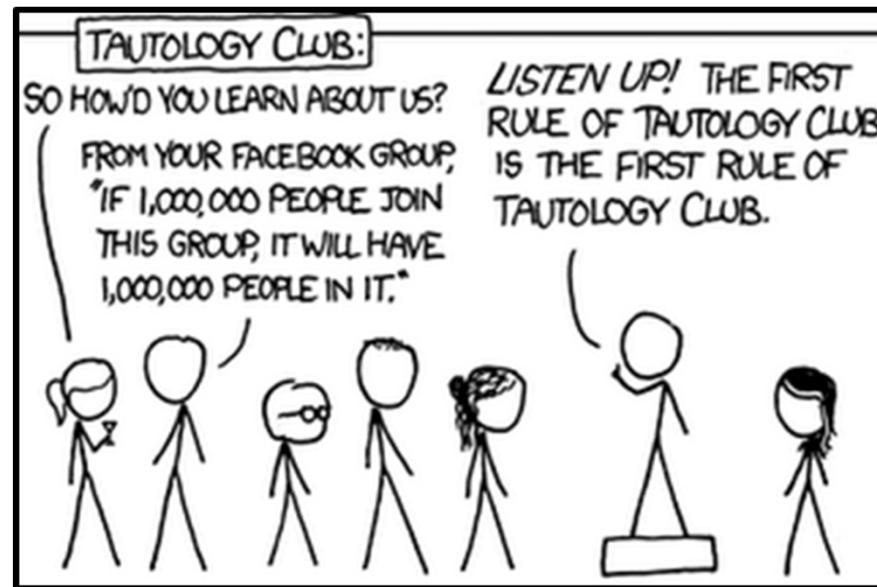


# CSE 311: Foundations of Computing

## Lecture 3: Digital Circuits



1<sup>st</sup> HW out

Section materials  
& solutions  
posted.  
OH posted.

# Review: Propositional Logic

---

## Propositions

- atomic propositions are T/F-valued variables
- combined using logical connectives (not, and, or, etc.)
- can be described by a truth table
  - shows the truth value of the proposition in each combination of truth values of the atomic propositions

$p$	$q$	$p \wedge q$
T	T	T
T	F	F
F	T	F
F	F	F

## Logical equivalence

- used to simplify logical expressions

## First application

- Simplifying English sentences

# Truth Table to show tautology

---

$$(p \wedge r) \rightarrow (r \vee p)$$

$$(p \wedge r) \rightarrow (r \vee p) \equiv \mathbf{T}$$

        ↴

$p$	$r$	$p \wedge r$	$r \vee p$	$(p \wedge r) \rightarrow (r \vee p)$
T	T	T	T	T
T	F	F	T	T
F	T	F	T	T
F	F	F	F	T

↑      ↪      ↴

# Logical Proofs of Equivalence

$$(p \wedge r) \rightarrow (r \vee p)$$

Use a series of equivalences like so:

$$\begin{aligned} (p \wedge r) \rightarrow (r \vee p) &\equiv \neg(p \wedge r) \vee (r \vee p) \\ &\equiv (\neg p \vee \neg r) \vee (r \vee p) \\ &\equiv \neg p \vee (\neg r \vee (r \vee p)) \\ &\equiv \neg p \vee ((\neg r \vee r) \vee p) \\ &\equiv \neg p \vee (p \vee (\neg r \vee r)) \\ &\equiv (\neg p \vee p) \vee (\neg r \vee r) \\ &\equiv (p \vee \neg p) \vee (r \vee \neg r) \\ &\equiv T \vee T \\ &\equiv T \end{aligned}$$

Law of Implication

De Morgan

Associative

Associative

Commutative

Associative

Commutative (twice)

Negation (twice)

Domination/Identity

## Identity

- $p \wedge T \equiv p$
- $p \vee F \equiv p$

## Domination

- $p \vee T \equiv T$
- $p \wedge F \equiv F$

## Idempotent

- $p \vee p \equiv p$
- $p \wedge p \equiv p$

## Commutative

- $p \vee q \equiv q \vee p$
- $p \wedge q \equiv q \wedge p$

# Logical Proofs of Equivalence/Tautology

---

- Not smaller than truth tables when there are only a few propositional variables...
- ...but usually *much shorter* than truth table proofs when there are many propositional variables
- A big advantage will be that we can extend them to a more in-depth understanding of logic for which truth tables don't apply.

# Another key application: Digital Circuits

---

## Computing With Logic


- T corresponds to 1 or “high” voltage
- F corresponds to 0 or “low” voltage

## Gates

- Take inputs and produce outputs (functions)
- Several kinds of gates
- Correspond to propositional connectives (most of them)

# Circuits: AND, OR, NOT Gates

## AND Gate

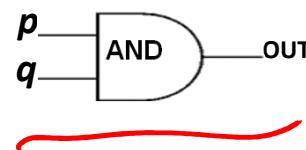


$p$	$q$	OUT
1	1	1
1	0	0
0	1	0
0	0	0

$\overleftarrow{1 \rightarrow T}$   
 $\overleftarrow{0 \leftrightarrow F}$   
 $\overrightarrow{0 \rightarrow F}$

$p$	$q$	$p \wedge q$
T	T	T
T	F	F
F	T	F
F	F	F

## OR Gate

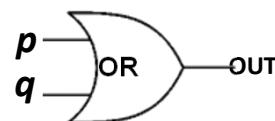


V

$p$	$q$	OUT
1	1	1
1	0	1
0	1	1
0	0	0

$p$	$q$	$p \vee q$
T	T	T
T	F	T
F	T	T
F	F	F

## NOT Gate

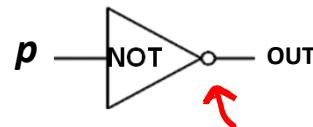


$p$	OUT
1	0
0	1

$p$	$\neg p$
T	F
F	T

# Combinational Logic Circuits


---

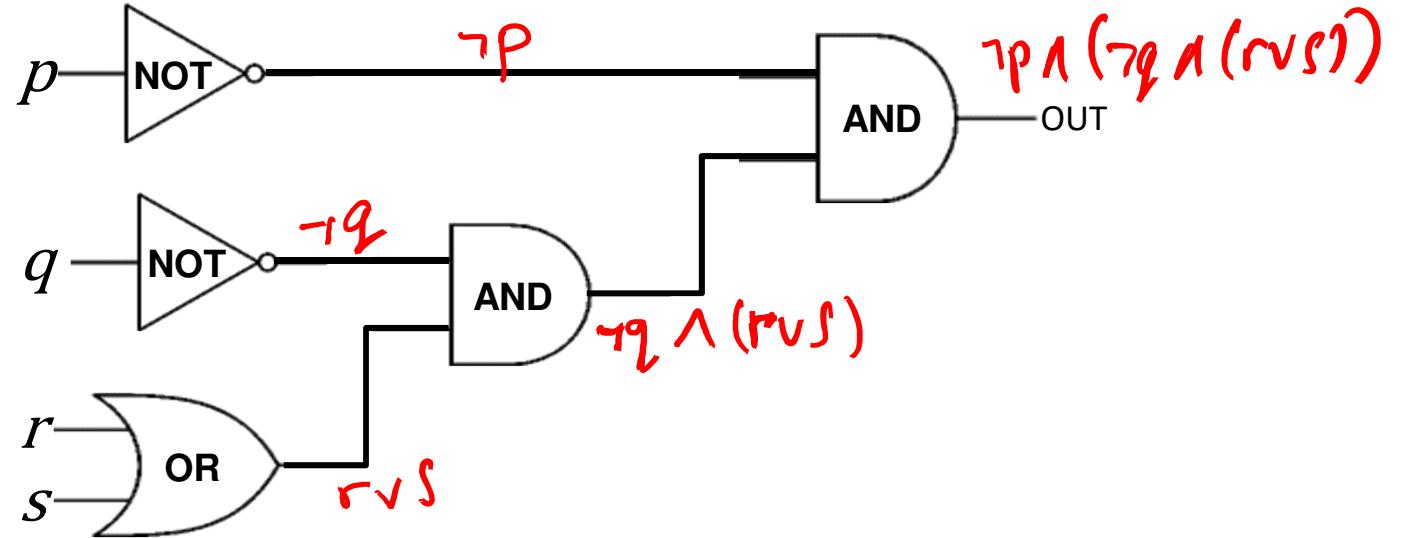

Values get sent along wires connecting gates

# Combinational Logic Circuits

---

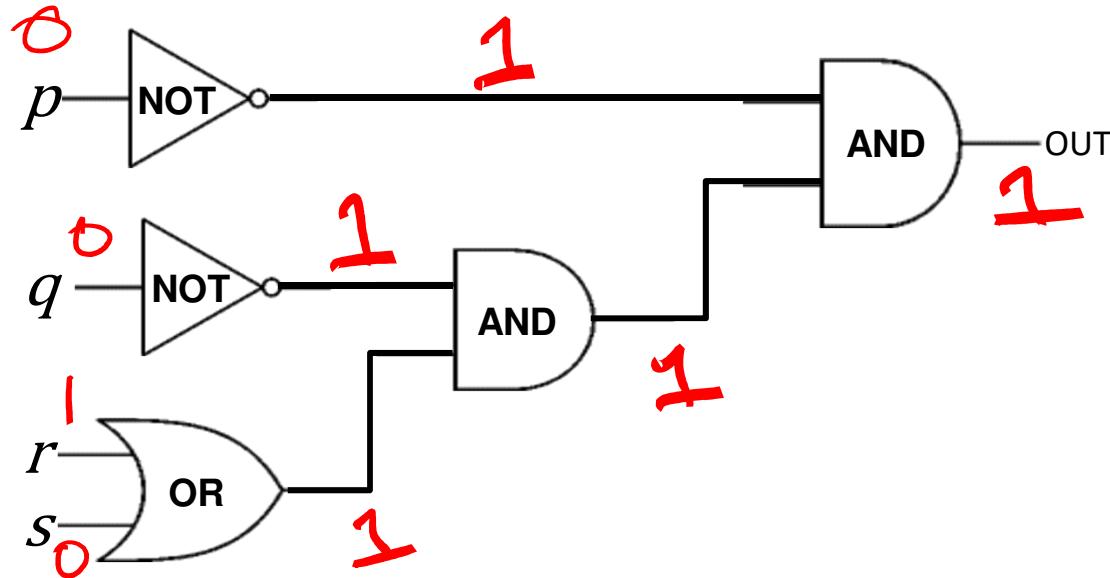


Values get sent along wires connecting gates

$$\neg p \wedge (\neg q \wedge (r \vee s))$$

# Combinational Logic Circuits

---

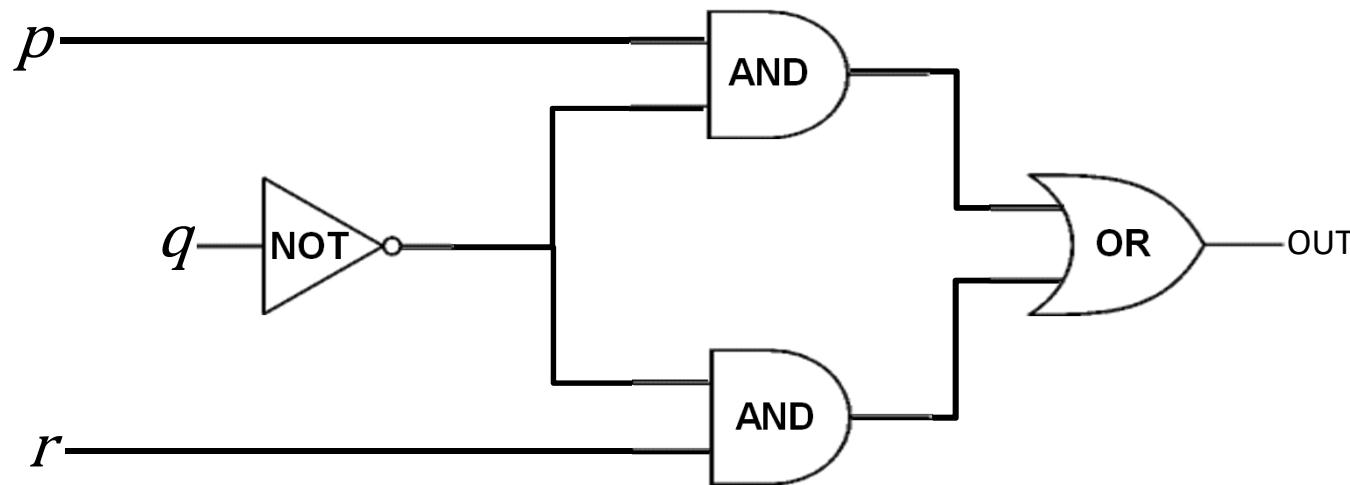

Wires can send one value to multiple gates!


$$(p \wedge \neg q) \vee (\neg q \wedge r) \quad \checkmark$$

$$(p \wedge \neg q) \vee (r \wedge \neg q) \quad \checkmark$$

$$\equiv (p \vee r) \wedge \neg q \quad \checkmark$$

# Combinational Logic Circuits

---

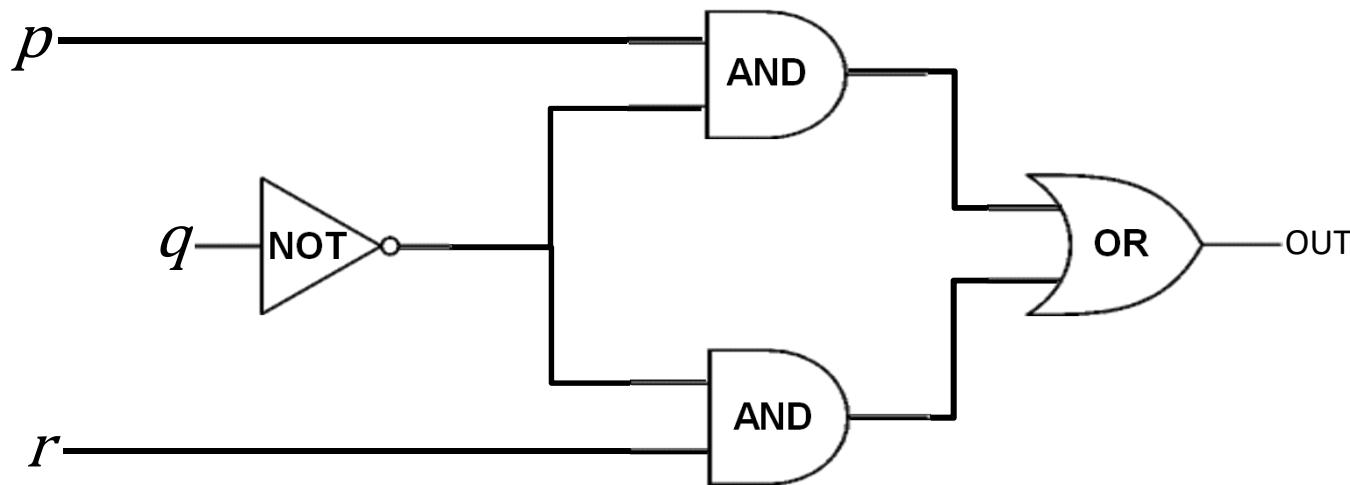

Wires can send one value to multiple gates!


$$(p \wedge \neg q) \vee (\neg q \wedge r)$$

# Other Useful Gates

---

**NAND**


$$\neg(p \wedge q)$$

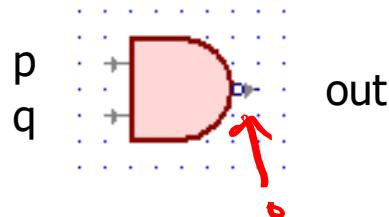p	q	out
0	0	1
0	1	1
1	0	1
1	1	0

**NOR**


$$\neg(p \vee q)$$

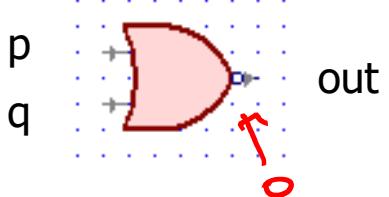

p	q	out
0	0	1
0	1	0
1	0	0
1	1	0

**XOR**


$$p \oplus q$$

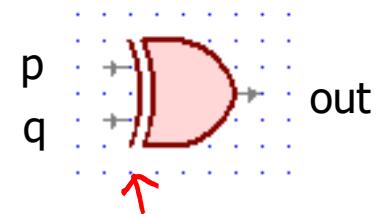

p	q	out
0	0	0
0	1	1
1	0	1
1	1	0

**XNOR**

$$p \leftrightarrow q$$

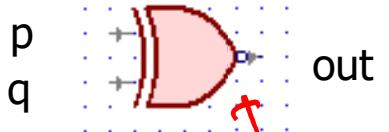p	q	out
0	0	1
0	1	0
1	0	0
1	1	1

# Boolean Logic

---

## Combinational Logic

- $\text{output} = F(\text{input})$

## Sequential Logic

- $\text{output}_t = F(\text{output}_{t-1}, \text{input}_t)$ 
  - output dependent on history
  - concept of a time step (clock, t)
  - Covered in CSE 369



# Boolean Logic

---

## Combinational Logic

- output =  $F(\text{input})$



## Boolean Algebra: another notation for logic consisting of...

- a set of elements  $B = \{0, 1\}$
- binary operations  $\{ +, \cdot, - \}$  (OR, AND)
- and a unary operation  $\{ ' \}$  (NOT)

$x'$

$\neg x$

# Boolean Algebra

---

- Usual notation used in circuit design
- Boolean algebra
  - a set of elements  $B$  containing  $\{0, 1\}$
  - binary operations  $\{ +, \cdot \}$
  - and a unary operation  $\{ '\}$
  - such that the following axioms hold:



For any  $a, b, c$  in  $B$ :

1. closure:
2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned} & a + b \text{ is in } B \\ & a + b = b + a \\ & a + (b + c) = (a + b) + c \\ & \boxed{a + (b \cdot c) = (a + b) \cdot (a + c)} \\ & a + 0 = a \\ & a + a' = 1 \\ & a + 1 = 1 \\ & \boxed{a + a = a} \\ & (a')' = a \end{aligned}$$

$$\begin{aligned} & a \cdot b \text{ is in } B \\ & a \cdot b = b \cdot a \\ & a \cdot (b \cdot c) = (a \cdot b) \cdot c \\ & a \cdot (b + c) = (a \cdot b) + (a \cdot c) \\ & a \cdot 1 = a \\ & a \cdot a' = 0 \\ & \boxed{a \cdot 0 = 0} \\ & \boxed{a \cdot a = a} \end{aligned}$$

# Proving Theorems

---

Using truth table:

For example, de Morgan's Law:

$$(X + Y)' = X' \cdot Y'$$

NOR is equivalent to AND  
with inputs complemented

X	Y	X'	Y'	(X + Y)'	X' · Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$(X \cdot Y)' = X' + Y'$$

NAND is equivalent to OR  
with inputs complemented

X	Y	X'	Y'	(X · Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

More generally  $(a + b + c + \dots)' = a' \cdot b' \cdot c' \cdot \dots$

$(a \cdot b \cdot c \cdot \dots)' = a' + b' + c' + \dots$

# Proving Theorems

---

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned} a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a &= a \\ (a')' &= a \end{aligned}$$

$$\begin{aligned} a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a &= a \end{aligned}$$

Using the laws of Boolean Algebra:

**prove the “Uniting theorem”:**

$$X \cdot Y + X \cdot Y' = X$$

Dit

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\ &= X \cdot \end{aligned}$$

**prove the “Absorption theorem”:**

$$X + X \cdot Y = X$$

$$X + X \cdot Y =$$

# Proving Theorems

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned} a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a &= a \\ (a')' &= a \end{aligned}$$

$$\begin{aligned} a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a &= a \end{aligned}$$

Using the laws of Boolean Algebra:

**prove the “Uniting theorem”:**

$$X \cdot Y + X \cdot Y' = X \quad \text{←}$$

distributivity

$$\begin{aligned} X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\ &= X \cdot 1 \quad \text{←} \\ &= X \quad \text{—} \end{aligned}$$

complementarity

identity

**prove the “Absorption theorem”:**

$$X + X \cdot Y = X \quad \text{←}$$

identity

distributivity

commutativity

null

identity

$$\begin{aligned} X + X \cdot Y &= X \cdot 1 + X \cdot Y \\ &= X \cdot (1 + Y) \\ &= X \cdot (Y + 1) \\ &= X \cdot 1 \\ &= X \end{aligned}$$

# A Combinational Logic Example

---

## Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.



- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**  
Input: (Monday, Section) Output: **1**

# Implementation in Software

---


```
public int classesLeftInMorning(int weekday, boolean isLecture) {  
    switch (weekday) {  
        case SUNDAY:  
        case MONDAY:  
            return isLecture ? 3 : 1;  
        case TUESDAY:  
        case WEDNESDAY:  
            return isLecture ? 2 : 1;  
        case THURSDAY:  
            return isLecture ? 1 : 1;  
        case FRIDAY:  
            return isLecture ? 1 : 0;  
        case SATURDAY:  
            return isLecture ? 0 : 0;  
    }  
}
```

# Implementation with Combinational Logic

---
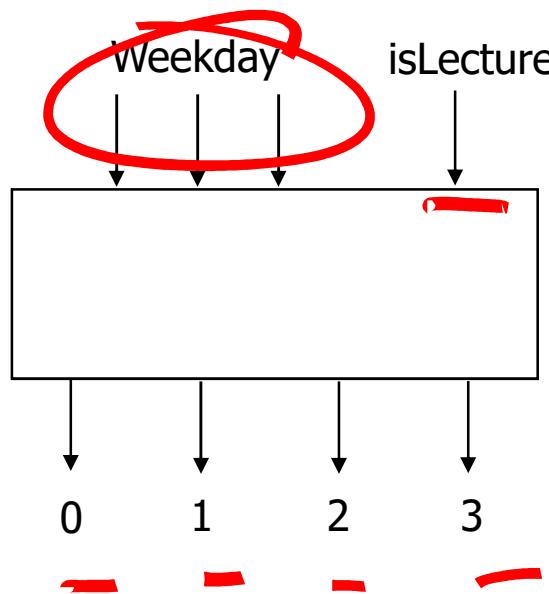
## Encoding:

- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



# Defining Our Inputs!

---

## Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	$(000)_2$
Monday	1	$(001)_2$
Tuesday	2	$(010)_2$
Wednesday	3	$(011)_2$
Thursday	4	$(100)_2$
Friday	5	$(101)_2$
Saturday	6	$(110)_2$

# Converting to a Truth Table!

---

```
case SUNDAY or MONDAY:  
    return isLecture ? 3 : 1;  
case TUESDAY or WEDNESDAY:  
    return isLecture ? 2 : 1;  
case THURSDAY:  
    return isLecture ? 1 : 1;  
case FRIDAY:  
    return isLecture ? 1 : 0;  
case SATURDAY:  
    return isLecture ? 0 : 0;
```

Weekday	isLecture	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
SUN	000	0	-	-	-
SUN	000	1	-	-	-
MON	001	0	-	-	-
MON	001	1	-	-	-
TUE	010	0	-	-	-
TUE	010	1	-	-	-
WED	011	0	-	-	-
WED	011	1	-	-	-
THU	100	-	-	-	-
FRI	101	0	-	-	-
FRI	101	1	-	-	-
SAT	110	-	-	-	-
-	111	-	-	-	-

# Converting to a Truth Table!

---

```
case SUNDAY or MONDAY:  
    return isLecture ? 3 : 1;  
case TUESDAY or WEDNESDAY:  
    return isLecture ? 2 : 1;  
case THURSDAY:  
    return isLecture ? 1 : 1;  
case FRIDAY:  
    return isLecture ? 1 : 0;  
case SATURDAY:  
    return isLecture ? 0 : 0;
```

	Weekday	isLecture	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
	SUN	000	0	1	0	0
	SUN	000	1	0	0	1
	MON	001	0	1	0	0
	MON	001	1	0	0	1
	TUE	010	0	1	0	0
	TUE	010	1	0	1	0
	WED	011	0	1	0	0
	WED	011	1	0	0	1
	THU	100	-	1	0	0
	FRI	101	0	0	1	0
	FRI	101	1	0	1	0
	SAT	110	-	1	0	0
	-	111	-	1	0	0

# Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Let's begin by finding an expression for  $c_3$ . To do this, we look at the rows where  $c_3 = 1$  (true).

# Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

DAY == SUN && L == 1

DAY == MON && L == 1

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2d_1d_0 == 000 \&& L == 1$   
 $d_2d_1d_0 == 001 \&& L == 1$

Substituting DAY for the binary representation.

# Truth Table to Logic (Part 1)

$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

→  $d_2 == 0 \&\& d_1 == 0 \&\& d_0 == 0 \&\& L == 1$

→  $d_2 == 0 \&\& d_1 == 0 \&\& d_0 == 1 \&\& L == 1$

**Splitting up the bits of the day;  
so, we can write a formula.**

# Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Replacing with  
Boolean Algebra...

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

How do we combine them?

# Truth Table to Logic (Part 1)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

$$d_2' \cdot d_1' \cdot d_0' \cdot L$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L$$

Either situation causes  $c_3$  to be true. So, we “or” them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$


# Truth Table to Logic (Part 2)

	$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
SUN	000	1	0	0	0	1	Now, we do $c_2$ .
MON	001	0	0	1	0	0	
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	
TUE	010	1	0	0	1	0	$d_2' \cdot d_1 \cdot d_0' \cdot L$
WED	011	0	0	1	0	0	
WED	011	1	0	0	1	0	$d_2' \cdot d_1 \cdot d_0 \cdot L$
THU	100	-	0	1	0	0	
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

# Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Now, we do c<sub>1</sub>:

$$d_2' \cdot d_1' \cdot d_0' \cdot L'$$

$$d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$\underline{c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L}$$

# Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN 000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN 000	1	0	0	0	1	
MON 001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON 001	1	0	0	0	1	
TUE 010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE 010	1	0	0	1	0	
WED 011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED 011	1	0	0	1	0	
THU 100	-	0	1	0	0	$???$
FRI 101	0	1	0	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI 101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT 110	-	1	0	0	0	
- 111	-	1	0	0	0	

Now, we do  $c_1$ :

$$d_2' \cdot d_1' \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L'$$

$$d_2 \cdot d_1' \cdot d_0'$$

$$d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Now, we do  $c_1$ :

$$d_2' \cdot d_1' \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1' \cdot d_0 \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0' \cdot L'$$

$$d_2' \cdot d_1 \cdot d_0 \cdot L'$$

$$d_2 \cdot d_1' \cdot d_0'$$

$$d_2 \cdot d_1' \cdot d_0 \cdot L$$

No matter what L is,  
we always say it's 1.  
So, we don't need L  
in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN 000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN 000	1	0	0	0	1	
MON 001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON 001	1	0	0	0	1	
TUE 010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE 010	1	0	0	1	0	
WED 011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED 011	1	0	0	1	0	
THU 100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI 101	0	1	0	0	0	
FRI 101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT 110	-	1	0	0	0	
- 111	-	1	0	0	0	

Now, we do  $c_1$ :

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

No matter what L is,  
we always say it's 1.  
So, we don't need L  
in the expression.

# Truth Table to Logic (Part 4)

	$d_2 d_1 d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' +$ $d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' +$ $d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$
SUN	000	1	0	0	0	1	$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$
MON	001	0	0	1	0	0	$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	
FRI	101	0	1	0	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L'$
FRI	101	1	0	1	0	0	
SAT	110	-	1	0	0	0	$d_2 \cdot d_1 \cdot d_0'$
-	111	-	1	0	0	0	$d_2 \cdot d_1 \cdot d_0$

Finally, we do  $c_0$ :

# Truth Table to Logic (Part 4)


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Here's  $c_3$  as a circuit:

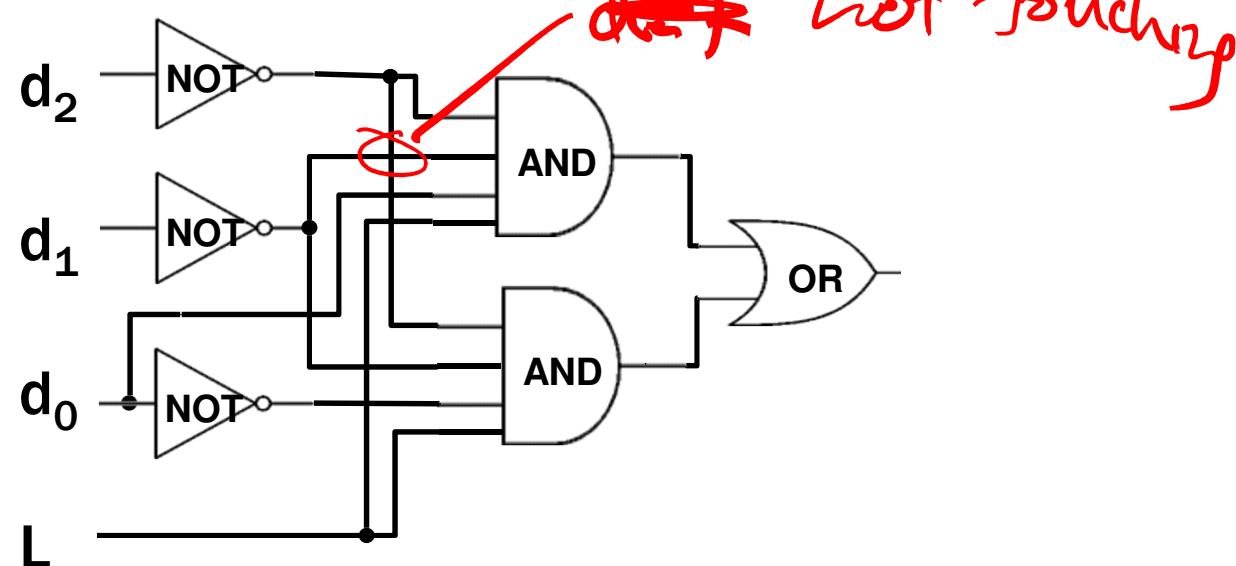

# Simplifying using Boolean Algebra

---

$$\begin{aligned}c3 &= \overline{d2'} \cdot \overline{d1'} \cdot \overline{d0'} \cdot L + \overline{d2'} \cdot \overline{d1'} \cdot d0 \cdot L \\&= \overline{d2'} \cdot \overline{d1'} \cdot (\overline{d0'} + d0) \cdot L \quad \text{distribution} \\&= \overline{d2'} \cdot \overline{d1'} \cdot 1 \cdot L \\&= \overline{d2'} \cdot \overline{d1'} \cdot L\end{aligned}$$

