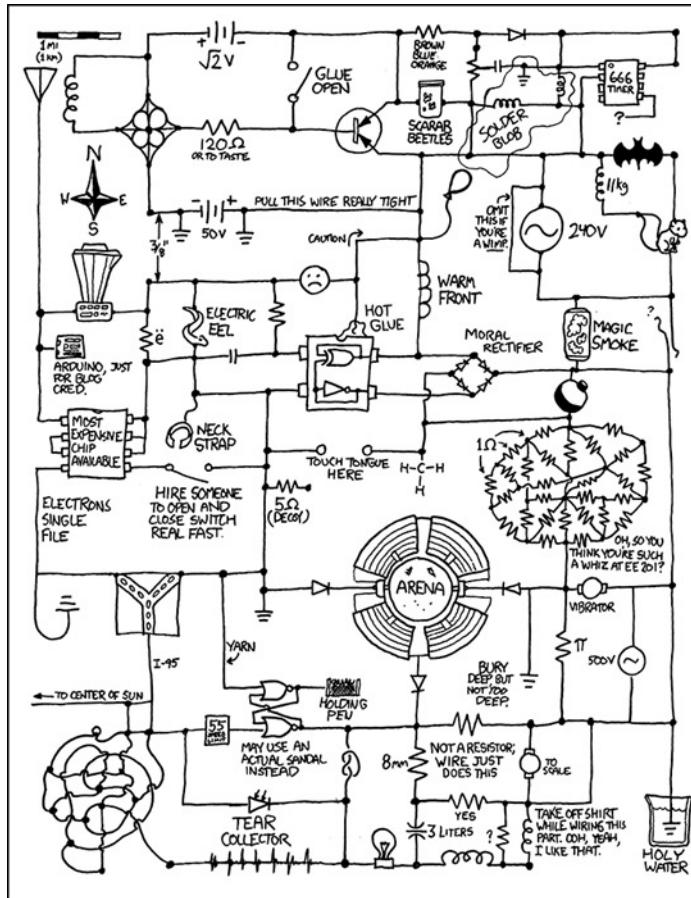


CSE 311: Foundations of Computing

Lecture 4: Boolean Algebra, Circuits, Canonical Forms



HW
COTY

Last Time: Boolean Algebra

- Usual notation used in circuit design
- Boolean algebra
 - a set of elements B containing $\{0, 1\}$
 - binary operations $\{ +, \cdot \}$
 - and a unary operation $\{ '\}$
 - such that the following axioms hold:



For any a, b, c in B :

1. closure:
2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$a + b$ is in B	$a + b = b + a$	$a + (b + c) = (a + b) + c$	$a + (b \cdot c) = (a + b) \cdot (a + c)$
$a + 0 = a$		$a + 1 = 1$	$a + a' = 0$
$a + a' = 1$		$a + a = a$	$a \cdot 0 = 0$
		$(a')' = a$	$a \cdot a = a$

$a \cdot b$ is in B	$a \cdot b = b \cdot a$	$a \cdot (b \cdot c) = (a \cdot b) \cdot c$	$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
		$a \cdot 1 = a$	
		$a \cdot a' = 0$	
		$a \cdot 0 = 0$	

Warm-up Exercise

- Create a Boolean Algebra expression for C below in terms of the variables a and b

Inputs ↗ *Output*

a	b	$C(a, b)$
1	1	0
1	0	1
0	1	1
0	0	0

$\leftarrow a \cdot b'$
 $\leftarrow a' \cdot b^+$

$$ab' + a'b$$


Warm-up Exercise

- Create a Boolean Algebra expression for “c” below in terms of the variables a and b

$$a \cdot b'$$

$$c = ab' + a'b$$

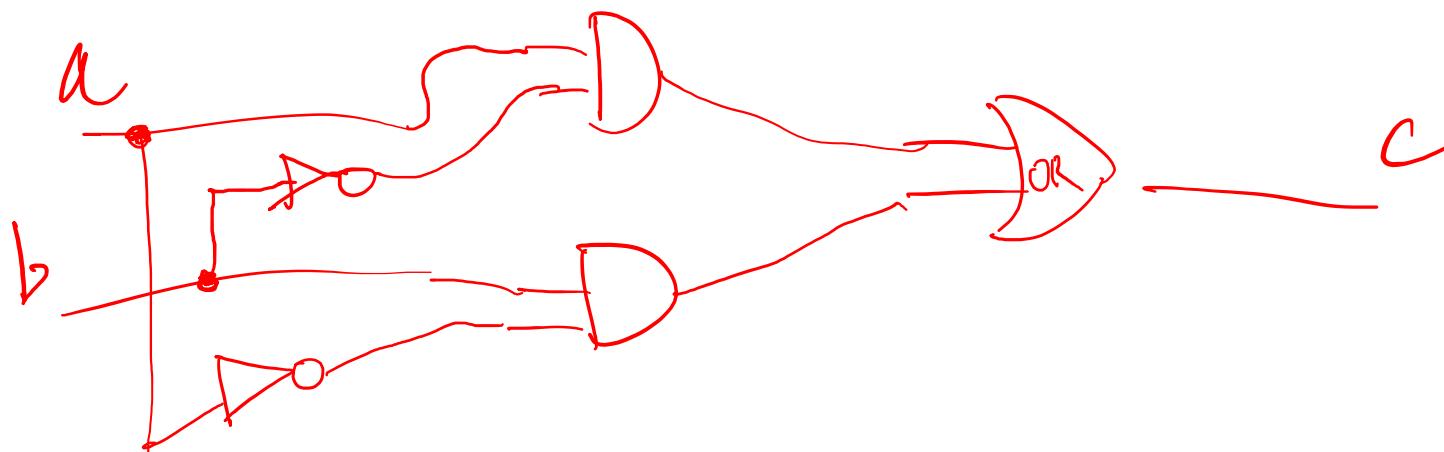
- Draw this as a circuit (using AND, OR, NOT)



Last Time: Combinational Logic

Encoding:

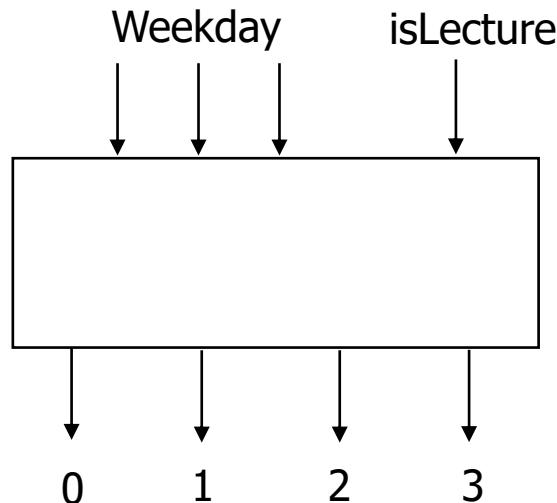- Binary number for weekday (Binary encoding)
- One bit for each possible output (“1-Hot” encoding)



Last Time: Truth Table to Logic

$d_2 d_1 d_0$	L	c_0	c_1	c_2	c_3
SUN 000	0	0	1	0	0
SUN 000	1	0	0	0	1
MON 001	0	0	1	0	0
MON 001	1	0	0	0	1
TUE 010	0	0	1	0	0
TUE 010	1	0	0	1	0
WED 011	0	0	1	0	0
WED 011	1	0	0	1	0
THU 100	-	0	1	0	0
FRI 101	0	1	0	0	0
FRI 101	1	0	1	0	0
SAT 110	-	1	0	0	0
- 111	-	1	0	0	0

Either situation causes c_3 to be true. So, we “or” them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Last Time: Truth Table to Logic


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' \cdot L' + d_2 \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$


$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Here's c_3 as a circuit:

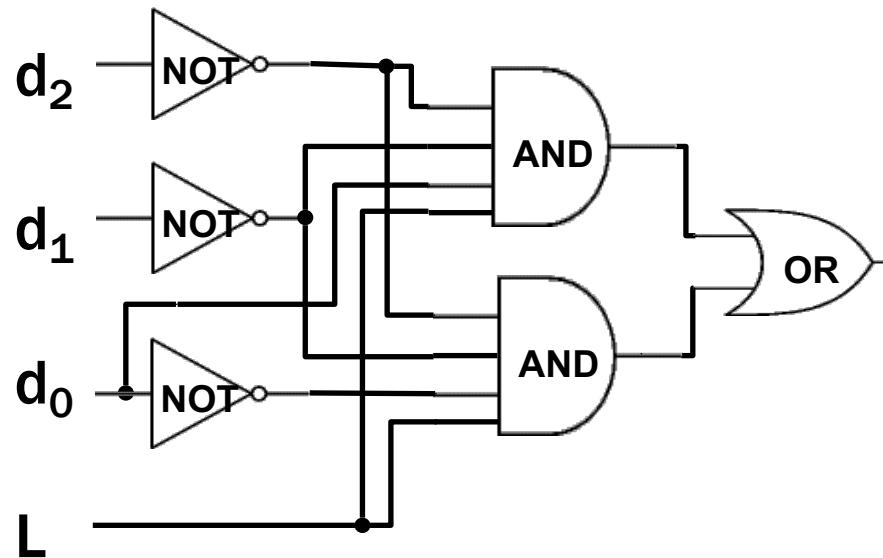

Simplifying using Boolean Algebra
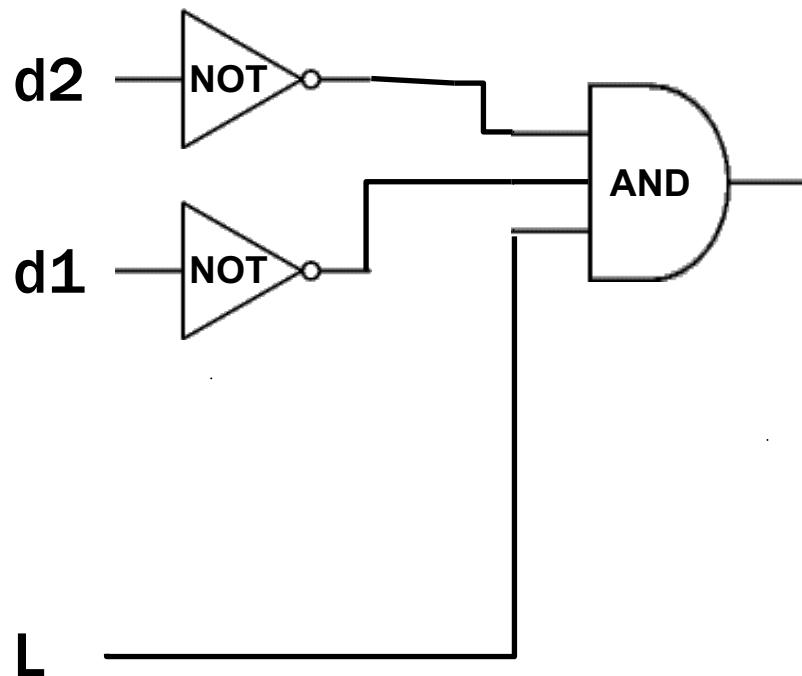
$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\&= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\&= d2' \cdot d1' \cdot 1 \cdot L \\&= d2' \cdot d1' \cdot L\end{aligned}$$



Important Corollaries of this Construction


- \neg, \wedge, \vee can implement any Boolean function
we didn't need any others to do this

- Actually, just \neg, \wedge (or \neg, \vee) are enough

follows by De Morgan's laws

$$a \vee b$$


- Actually, just NAND (or NOR)

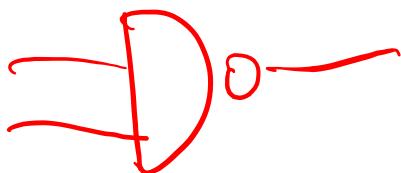

$$\begin{aligned} & \equiv \neg a \vee \neg b \\ & \equiv \neg(\neg a \wedge \neg b) \end{aligned}$$

1-bit Binary Adder

39
+ 1
—
0

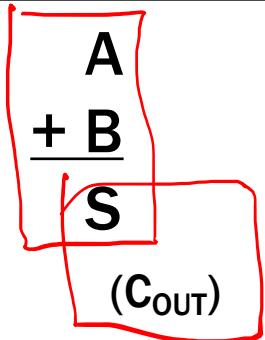


$$0 + 0 = 0 \text{ (with } C_{OUT} = 0\text{)}$$

$$0 + 1 = 1 \text{ (with } C_{OUT} = 0\text{)}$$

$$1 + 0 = 1 \text{ (with } C_{OUT} = 0\text{)}$$

$$1 + 1 = 0 \text{ (with } C_{OUT} = 1\text{)}$$

1 + 1 = 10

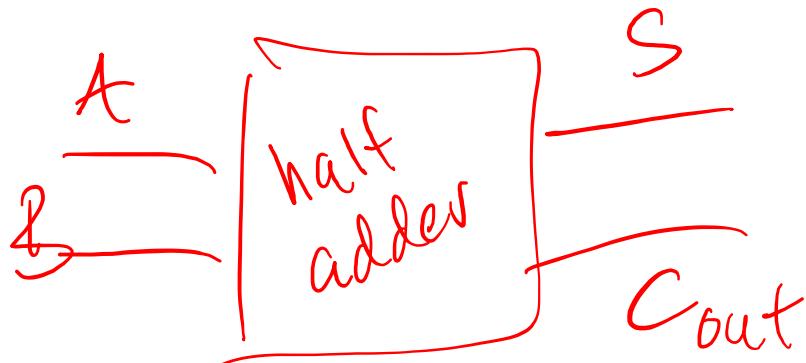

1
39
+ 01
—
0

1-bit Binary Adder

A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

Idea: chain these together to add larger numbers

Recall from
elementary school:


$$\begin{array}{r} 248 \\ + 375 \\ \hline \end{array}$$

1-bit Binary Adder

A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

Idea: These are chained together with a carry-in
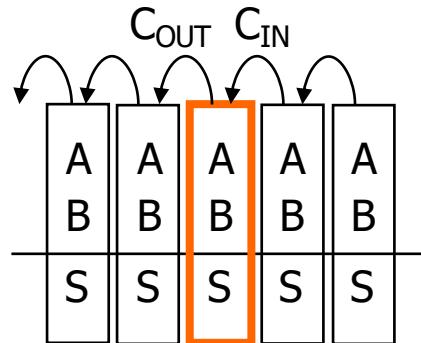
$$\begin{array}{r} (C_{IN}) \\ A \\ + B \\ \hline S \\ (C_{OUT}) \end{array}$$





C _{OUT} C _{IN}		0	0	0	0
1	1	0	1	1	0
0	0	1	1	0	1
0	0	1	1	0	1

1-bit Binary Adder

Full adder


- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out

A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

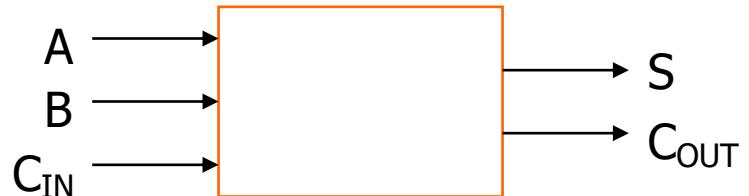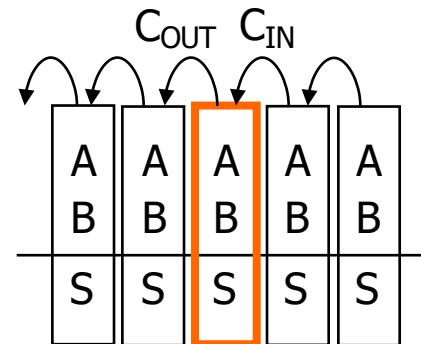

1-bit Binary Adder

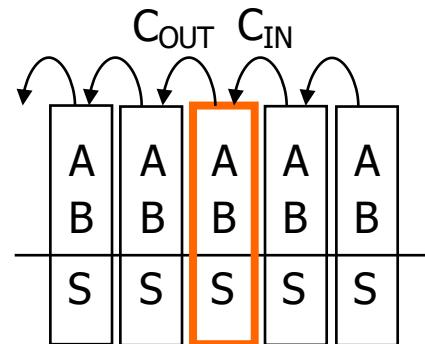- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C_{IN}	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for S

$$A' \cdot B' \cdot C_{IN}$$

$$A' \cdot B \cdot C_{IN}'$$


$$A \cdot B' \cdot C_{IN}'$$

$$A \cdot B \cdot C_{IN}$$

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + \\ A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$


1-bit Binary Adder

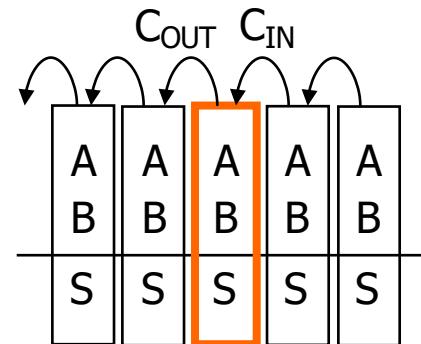- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Derive an expression for C_{OUT}

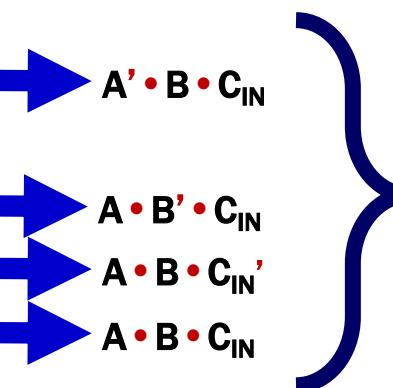


$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}'$$

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

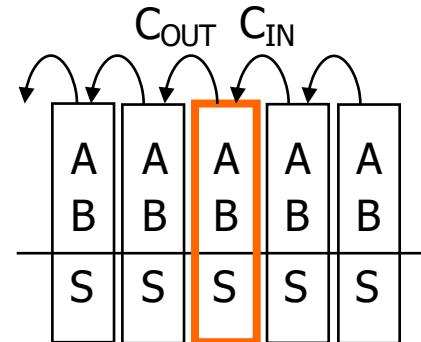- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

Apply Theorems to Simplify Expressions

The theorems of Boolean algebra can simplify expressions

- e.g., full adder's carry-out function

14 gates

$$\begin{aligned} \text{Cout} &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} + A B \text{ Cin} \\ &= (A' B \text{ Cin} + A B \text{ Cin}) + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= (A' + A) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= (1) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} + A B \text{ Cin} \\ &= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A (B' + B) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A (1) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\ &= B \text{ Cin} + A \text{ Cin} + A B (\text{Cin}' + \text{Cin}) \\ &= B \text{ Cin} + A \text{ Cin} + A B (1) \\ &= B \text{ Cin} + A \text{ Cin} + A B \end{aligned}$$

5 gates

Apply Theorems to Simplify Expressions


The theorems of Boolean algebra can simplify expressions

- e.g., full adder's carry-out function

$$\begin{aligned}\text{Cout} &= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= A' B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin} + A B \text{ Cin}} \\&= A' B \text{ Cin} + A B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= (A' + A) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= (1) B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin}' + \boxed{A B \text{ Cin} + A B \text{ Cin}} \\&= B \text{ Cin} + A B' \text{ Cin} + A B \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A (B' + B) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A (1) \text{ Cin} + A B \text{ Cin}' + A B \text{ Cin} \\&= B \text{ Cin} + A \text{ Cin} + A B (\text{Cin}' + \text{Cin}) \\&= B \text{ Cin} + A \text{ Cin} + A B (1) \\&= B \text{ Cin} + A \text{ Cin} + A B\end{aligned}$$

adding extra terms
creates new factoring
opportunities

A 3-bit Ripple-Carry Adder

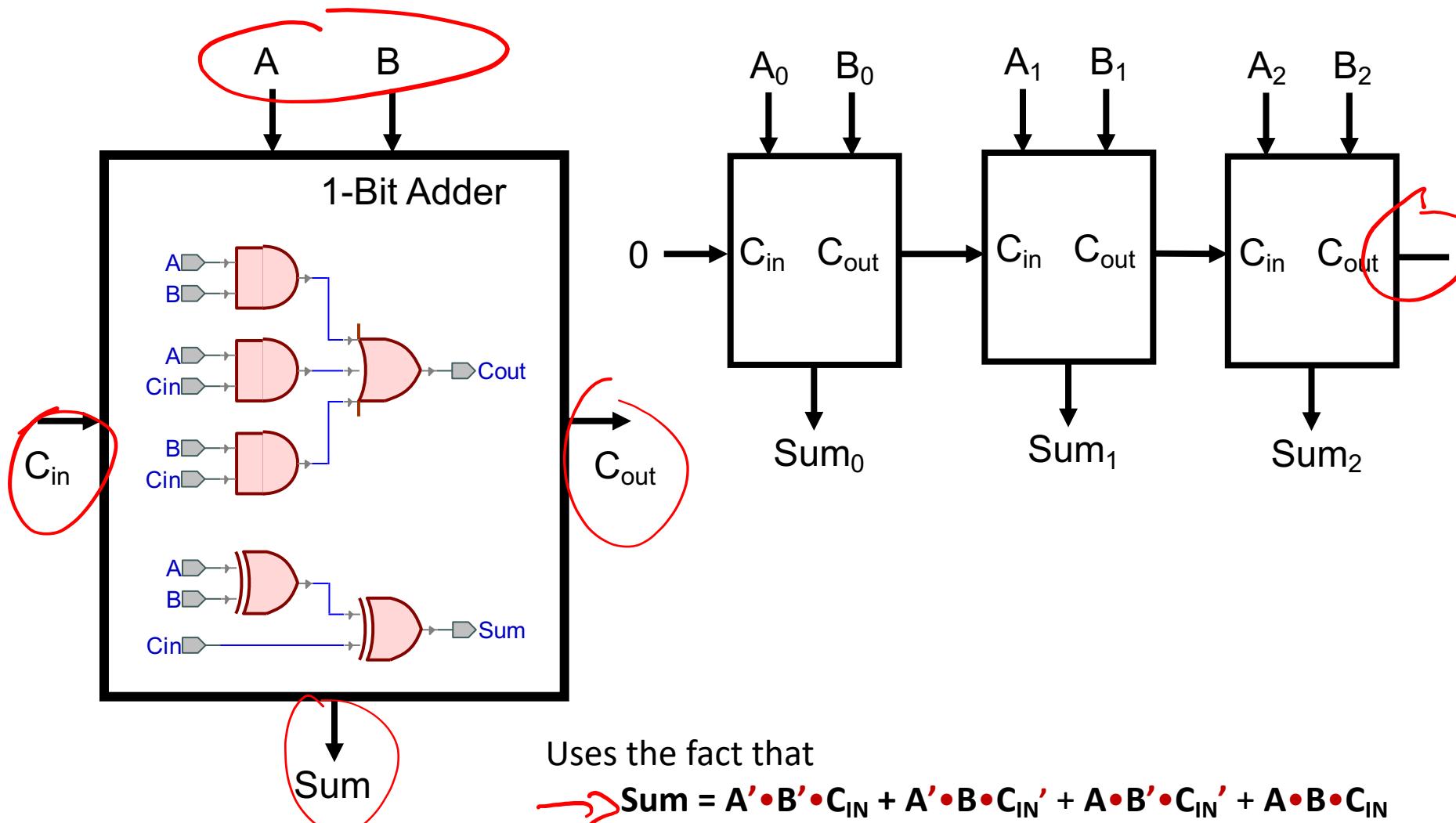

Mapping Truth Tables to Logic Gates


Given a truth table:

- 1. Write the output in a table
- 2. Write the Boolean expression
- 3. Minimize the Boolean expression
- 4. Draw as gates
- 5. Map to available gates


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(3)
$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$

(2)

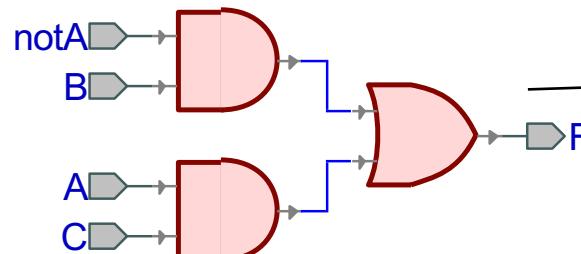

(5)

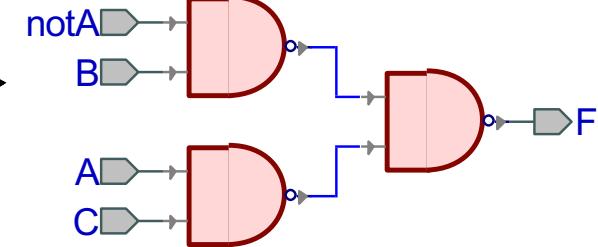

Canonical Forms

- Truth table is the **unique signature** of a 0/1 function
- The same truth table can have many gate realizations
 - We've seen this already
 - Depends on how good we are at Boolean simplification
- Canonical forms
 - Standard forms for a Boolean expression
 - We all produce the same expression

Sum-of-Products Canonical Form

- AKA Disjunctive Normal Form (DNF)
- AKA Minterm Expansion

$A'BC$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

①
Read T rows off
truth table

001

②
Convert to
Boolean Algebra

$A'B'C$

011

$A'BC$

101

$AB'C$

110

ABC'

111

ABC

Add the minterms together

$$F = \cancel{A'B'C} + A'BC + AB'C + ABC' + \cancel{ABC}$$

③

$A'BC$

F

Sum-of-Products Canonical Form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'BC'$
0	1	1	$A'BC$
1	0	0	$AB'C'$
1	0	1	$AB'C$
1	1	0	ABC'
1	1	1	ABC

F in canonical form:

$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$

Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

① Read F rows off truth table

④ Multiply the maxterms together

$F =$

② Negate all bits

③ Convert to Boolean Algebra

F

Product-of-Sums Canonical Form

- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

① Read F rows off
truth table

1

000

② Negate all
bits

2

111

③ Convert to
Boolean Algebra

4

$A + B + C$

010

101

$A + B' + C$

100

011

$A' + B + C$

Multiply the maxterms together

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

F

Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a minterm expansion for F'

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F' = A'B'C' + A'BC' + AB'C'$$

Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a minterm expansion for F'

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F' = A'B'C' + A'BC' + AB'C'$$

Taking the complement of both sides...

$$(F')' = (A'B'C' + A'BC' + AB'C)'$$

And using DeMorgan/Comp....

$$F = (A'B'C')' (A'BC')' (AB'C')'$$

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

Product-of-Sums Canonical Form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	$A+B+C$
0	0	1	$A+B+C'$
0	1	0	$A+B'+C$
0	1	1	$A+B'+C'$
1	0	0	$A'+B+C$
1	0	1	$A'+B+C'$
1	1	0	$A'+B'+C$
1	1	1	$A'+B'+C'$

F in canonical form:

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$