 



Question 1) CMOS transistor level circuits

Part 1 (20 points): Draw the CMOS transistor level circuit that implements the following function: $\sim(A + C)B$. Use as few transistors as possible. Make sure to label ground, Vdd and the input and output signals. This problem will be graded on the quality of the circuit as well as its correctness.



Question 2) Flip-flops

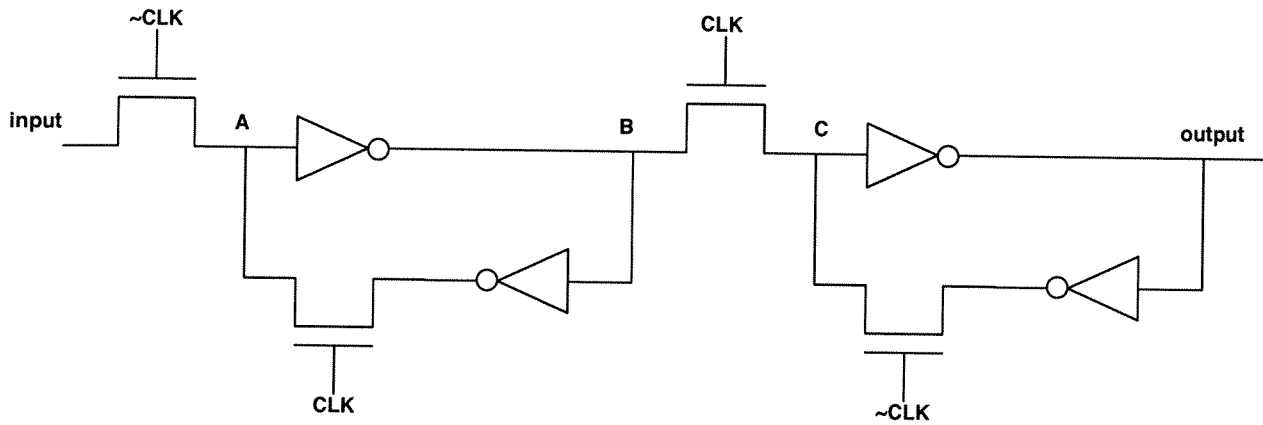Part 1 (15 points): Given the following flip-flop (PMOS transistors are not shown for simplicity):






Fill in the following table. If something cannot be known, place an X in that region.

CLK	
input	
A	
B	
C	
output	

Part 2 (5 points): Is this a positive edge triggered flip flop or negative edge triggered flip flop?



Question 3) Full Adders

   Part 1 (10 points): Draw the gate-level circuit for a full adder. Clearly label the inputs, and outputs.



ALTERNATIVE DESIGN
less gates BUT higher delay

  Part 2 (10 points): Implement a full adder using two 8:1 multiplexers. The inputs of the multiplexers can only be connected to Vdd, GND or the inputs of your full adder.



1 ~ connect to Vdd



0 ~ connect to GND

Question 4) Arithmetic Circuits (2 pages!)

Part 1 (10 points): Design a circuit using only full adders (FA) and half adders (HA) that computes the sum of three unsigned 3-bit integers $A[2:0]$, $B[2:0]$, $C[2:0]$. **You will be graded based on correctness and efficiency.**

Your full adders and half adders can be represented as block diagrams. For each adder, indicate which output is the sum, and which output is the carry. Make sure to clearly label your circuit to leave no room for ambiguity.

Soln 1

  


critical path ~~xxxxxxxxxxxx~~
 $A_0 B_0 \rightarrow S_0 S_4$

HA: delay from input to C_0 : 1×2 -input gate \therefore delay $HA-C = 3F_01$
 delay from input to S : 1×2 -input gate \therefore delay $HA-S = 3F_01$

FA: delay from input to S : 1×3 -input gate \therefore delay $FA-S = 5F_01$
 delay from input to C_0 : 1×2 -input gate + 1×3 -input gate \therefore delay $FA-C = 8F_01$

we assume the following adder:

 

\therefore critical path delay is delay $HA-C$ + delay $FA-S$ + delay $FA-C$ + delay $FA-C$ + delay $HA-C$

$$= 3 + 5 + 8 + 8 + 3 = 27F_01$$

Part 2 (10 points):

Based on the following delays:

1 input gate = 1 FO1


2 input gate = 3 FO1

3 input gate = 5 FO1

(4 points) What is the critical path of your circuit (indicate on your diagram)?

(6 points) What is the critical path **delay** of your circuit? Show your work and state your assumptions.

Soln 2

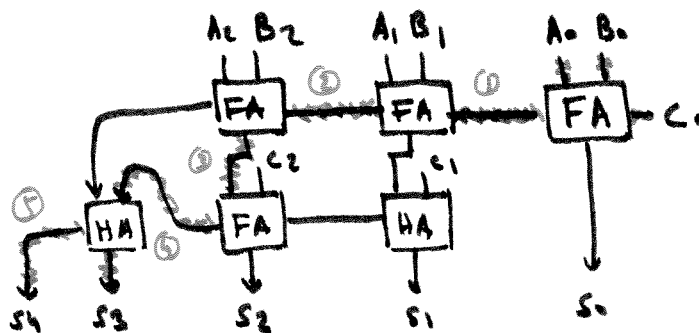

critical path
delay ~~is~~

A₀ B₀ → c₀
→ s₀ s₄

∴ critical path delay is :

$$\text{delay}_{\text{FA-C}}^{①} + \text{delay}_{\text{FA-C}}^{②} + \text{delay}_{\text{FA-S}}^{③} + \text{delay}_{\text{FA-C}}^{④} + \text{delay}_{\text{HA-C}}^{⑤}$$


$$= 2 + 8 + 5 + 8 + 3$$

$$= 32 \text{ FO1}$$

∴ slower than Soln 1

but 1 less HA used!

Soln 3

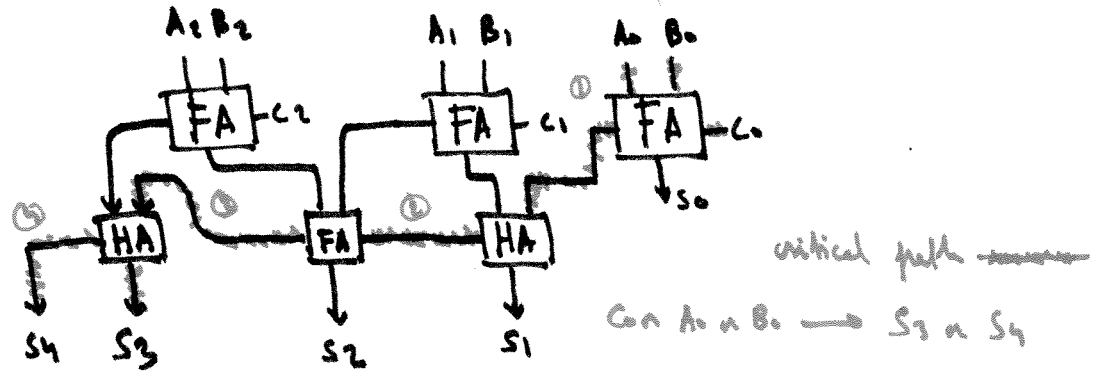

$$\begin{aligned}
 \text{critical path delay} &= \overset{①}{\text{delay FA-c}} + \overset{②}{\text{delay HA-c}} + \overset{③}{\text{delay FA-c}} + \overset{④}{\text{delay HA-c}} \\
 &= 8 + 3 + 8 + 3 \\
 &= 22 \text{ FOI}
 \end{aligned}$$

\therefore Faster than Soln 1 & soln 2!

Same resources as soln 1

Question 5) Short answer (2 pages!)

4.1) (3 points) Order SRAM, DRAM and flip-flop by increasing number of transistors used per bit cell?

less DRAM, SRAM, flip-flop more

4.2) (3 points) Provide *one* reason for using FPGAs vs. ASIC to implement a product.

- lower up-front cost
- faster time to market
- simpler design cycle
- field reprogrammability

4.3) (3 points) Why are glitches undesirable?


glitches consume power

4.4) (3 points) Discuss the area and delay trade-offs between using a ripple-carry adder vs. a carry-select adder:

Ripple carry adder: smaller area but longer delay

Carry select adder: larger area but shorter delay

 4.5) (4 points) What does this circuit implement?



A 2:1 MUX

4.6) (4 points) This is the LFSR that you put together in Lab 3:

Derives the values of A, B, C, D at every clock tick for 4 consecutive clock ticks.

Time	A	B	C	D
t=0	1	0	0	1
t=1	1	1	0	0
t=2	0	1	1	0
t=3	1	0	1	1
t=4	0	1	0	1

