

CSE352 Spring 2013 Homework Assignment #3 [updated]
Due in class Wednesday, May 1st 2013

Q1) Multiplexers:

Consider the function given by the following truth table:

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Table 1: Truth table

Implement that function using:

- An 8:1 multiplexer
- A 4:1 multiplexer and one inverter
- A 2:1 multiplexer, one NOR gate and one AND gate

You can use the ground and Vdd as inputs to the multiplexer. Signal fanouts are allowed.

Q2) Adders:

- a) An incrementer adds 1 to an N-bit number. Build a 4-bit incrementer using *only* half adders. You can connect input ports of the half adder to Vdd or GND. The circuit you will compose will have 5 labeled inputs and 5 labeled outputs:

- 1-bit input M – Mode: when set to 0, $S=A$, and when set to 1 $S=A+1$.
- 4 bit input $A[3:0]$ – Input of the incrementer
- 4-bit output $S[3:0]$ – Output of the incrementer
- 1-bit output O – Overflow: 1 if incrementer overflows, 0 otherwise

Recall: half adders have two inputs (A,B) and two outputs (Co and S) given by:

- $Co = A \cdot B$
- $S = A \oplus B$

You can represent the half adder using the following representation:

 


Figure 1: Half adder block diagram

- b) If an **AND** gate delay is 500ps and an XOR gate delay is 1.5ns. What is the delay of a half adder? Of the 4-bit incrementer?
- c) Let's build a 16-bit counter. In part a), you built the following 4-bit incrementer:

 


Figure 2: Block diagram for 4-bit incrementer

Using 4-bit incrementers, and pos-edge triggered flip-flops with active-high asynchronous reset, design a 16-bit counter that adds 1 at each positive clock edge. The counter has a clock input and an asynchronous reset input. The outputs should include the 16-bit counter value, and an overflow bit. Note: you can represent your 16 flip flops as one monolithic register which assumes all clocks and reset signals are wired together.

 


Figure 3: 16-bit register

Change log:

EDIT 4/24/2013: in Q2 fixed the Co equation to AND. Also updated the gate delays.

EDIT 4/25/2013: in Q2 part c, labeled the input of the 4-bit incrementer correctly