

Combinational Logic Technologies

- ⌘ Standard gates
 - ☒ gate packages
 - ☒ cell libraries
- ⌘ Regular logic
 - ☒ multiplexers
 - ☒ decoders
- ⌘ Two-level programmable logic
 - ☒ PALs
 - ☒ PLAs
 - ☒ ROMs

Random logic

- ⌘ Transistors quickly integrated into logic gates (1960s)
- ⌘ Catalog of common gates (1970s)
 - ☒ Texas Instruments Logic Data Book – the yellow bible
 - ☒ all common packages listed and characterized (delays, power)
 - ☒ typical packages:
 - ☒ in 14-pin IC: 6-inverters, 4 NAND gates, 4 XOR gates
- ⌘ Today, very few parts are still in use
- ⌘ However, parts libraries exist for chip design
 - ☒ designers reuse already characterized logic gates on chips
 - ☒ same reasons as before
 - ☒ difference is that the parts don't exist in physical inventory – created as needed

Random logic


- ⌘ Too hard to figure out exactly what gates to use
 - ☒ map from logic to NAND/NOR networks
 - ☒ determine minimum number of packages
 - ☒ slight changes to logic function could decrease cost
- ⌘ Changes to difficult to realize
 - ☒ need to rewire parts
 - ☒ may need new parts
 - ☒ design with spares (few extra inverters and gates on every board)

Regular logic

- ⌘ Need to make design faster
- ⌘ Need to make engineering changes easier to make
- ⌘ Simpler for designers to understand and map to functionality
 - ☒ harder to think in terms of specific gates
 - ☒ better to think in terms of a large multi-purpose block


Making connections

 - ⌘ Direct point-to-point connections between gates
 - ☐ wires we've seen so far
- ⌘ Route one of many inputs to a single output --- multiplexer
- ⌘ Route a single input to one of many outputs --- demultiplexer




Mux and demux

 - ⌘ Switch implementation of multiplexers and demultiplexers
 - ☐ can be composed to make arbitrary size switching networks
 - ☐ used to implement multiple-source/multiple-destination interconnections



Mux and demux (cont'd)

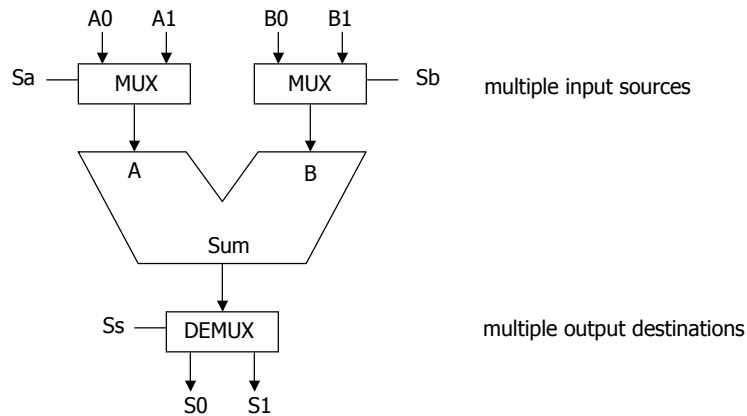⌘ Uses of multiplexers/demultiplexers in multi-point connections



Multiplexers/selectors

⌘ Multiplexers/selectors: general concept

- ☑ 2^n data inputs, n control inputs (called "selects"), 1 output
- ☑ used to connect 2^n points to a single point
- ☑ control signal pattern forms binary index of input connected to output

$$Z = A' I_0 + A I_1$$

A	Z
0	I_0
1	I_1

I_1	I_0	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

functional form → (points to the first table)

logical form → (points to the second table)

two alternative forms for a 2:1 Mux truth table

Multiplexers/selectors (cont'd)


⌘ 2:1 mux: $Z = A' I_0 + A I_1$

⌘ 4:1 mux: $Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$

⌘ 8:1 mux: $Z = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$


⌘ In general: $Z = \sum_{k=0}^{2^n-1} (m_k I_k)$

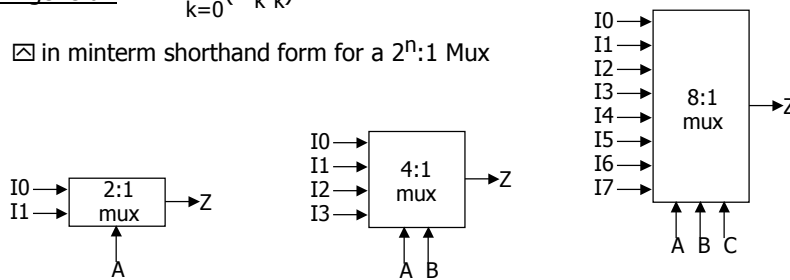☒ in minterm shorthand form for a $2^n:1$ Mux




Gate level implementation of muxes

⌘ 2:1 mux

 


⌘ 4:1 mux

 


Cascading multiplexers

 ⌘ Large multiplexers can be implemented by cascading smaller ones



control signals B and C simultaneously choose one of I0, I1, I2, I3 and one of I4, I5, I6, I7

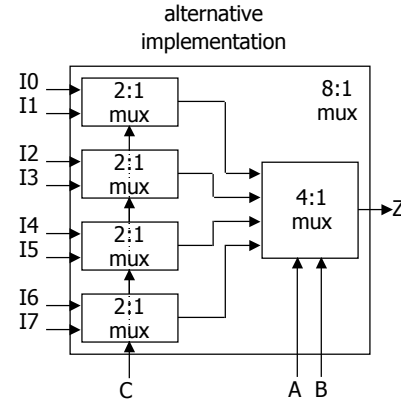control signal A chooses which of the upper or lower mux's output to gate to Z




Multiplexers as general-purpose logic

⌘ A $2^n:1$ multiplexer can implement any function of n variables

- ☒ with the variables used as control inputs and
- ☒ the data inputs tied to 0 or 1
- ☒ in essence, a lookup table

⌘ Example:
 
$$\begin{aligned} \square F(A,B,C) &= m_0 + m_2 + m_6 + m_7 \\ &= A'B'C' + A'BC' + ABC' + ABC \\ &= A'B'(C') + A'B(C') + AB'(0) + AB(1) \end{aligned}$$




Multiplexers as general-purpose logic (cont'd)


- ⌘ A $2^{n-1}:1$ multiplexer can implement any function of n variables
 - ☐ with $n-1$ variables used as control inputs and
 - ☐ the data inputs tied to the last variable or its complement

⌘ Example:
 
$$\begin{aligned} \square F(A,B,C) &= m_0 + m_2 + m_6 + m_7 \\ &= A'B'C' + A'BC' + ABC' + ABC \\ &= A'B'(C') + A'B(C') + AB'(0) + AB(1) \end{aligned}$$



A	B	C	F
0	0	0	1 C'
0	0	1	0
0	1	0	1 C'
0	1	1	0
1	0	0	0 0
1	0	1	0
1	1	0	1 1
1	1	1	1

 

Multiplexers as general-purpose logic (cont'd)

⌘ Generalization

$n-1$ mux control variables

single mux data variable

I_0	I_1	...	I_{n-1}	I_n	F
.	.	.	.	0	0
.	.	.	.	1	1

F	I_n	I_n'	1
0	0	1	1
1	1	0	1


four possible configurations of truth table rows can be expressed as a function of I_n

⌘ Example: $G(A,B,C,D)$ can be implemented by an 8:1 MUX

choose A,B,C as control variables

multiplexer implementation

A	B	C	D	G
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

 

Activity

- ⌘ Map the following equation to an 4:1 multiplexer using a minimum of external gates:



Demultiplexers/decoders

- ⌘ Decoders/demultiplexers: general concept
- single data input, n control inputs, 2^n outputs
 - control inputs (called "selects" (S)) represent binary index of output to which the input is connected
 - data input usually called "enable" (G)

1:2 Decoder:

$$O0 = G \cdot S'$$

$$O1 = G \cdot S$$

2:4 Decoder:

$$O0 = G \cdot S1' \cdot S0'$$

$$O1 = G \cdot S1' \cdot S0$$

$$O2 = G \cdot S1 \cdot S0'$$

$$O3 = G \cdot S1 \cdot S0$$

3:8 Decoder:

$$O0 = G \cdot S2' \cdot S1' \cdot S0'$$

$$O1 = G \cdot S2' \cdot S1' \cdot S0$$

$$O2 = G \cdot S2' \cdot S1 \cdot S0'$$

$$O3 = G \cdot S2' \cdot S1 \cdot S0$$

$$O4 = G \cdot S2 \cdot S1' \cdot S0'$$

$$O5 = G \cdot S2 \cdot S1' \cdot S0$$


$$O6 = G \cdot S2 \cdot S1 \cdot S0'$$

$$O7 = G \cdot S2 \cdot S1 \cdot S0$$


Gate level implementation of demultiplexers

⌘ 1:2 decoders



active-high enable

 

active-low enable

 


⌘ 2:4 decoders

  

Demultiplexers as general-purpose logic

⌘ A $n:2^n$ decoder can implement any function of n variables

 - ☑ with the variables used as control inputs
- ☑ the enable inputs tied to 1 and
- ☑ the appropriate minterms summed to form the function




demultiplexer generates appropriate minterm based on control signals (it "decodes" control signals)

Demultiplexers as general-purpose logic (cont'd)

⌘ $F1 = A' B C' D + A' B' C D + A B C D$

⌘ $F2 = A B C' D' + A B C$

⌘ $F3 = (A' + B' + C' + D')$

 


Cascading decoders

⌘ 5:32 decoder


☐ 1x2:4 decoder

☐ 4x3:8 decoders

 

Programmable logic arrays

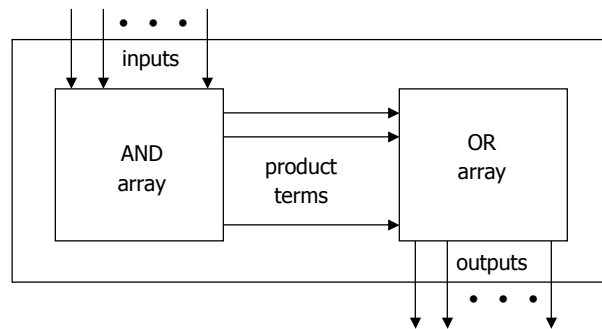- ⌘ Pre-fabricated building block of many AND/OR gates
 - ☒ actually NOR or NAND
 - ☒ "personalized" by making or breaking connections among the gates
 - ☒ programmable array block diagram for sum of products form



Enabling concept

- ⌘ Shared product terms among outputs

example:

$$\begin{aligned}
 F0 &= A + B' C' \\
 F1 &= A C' + A B \\
 F2 &= B' C' + A B \\
 F3 &= B' C + A
 \end{aligned}$$

personality matrix

product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

input side:

1 = uncomplemented in term
 0 = complemented in term
 - = does not participate


output side:

1 = term connected to output
 0 = no connection to output

reuse of terms

Before programming

- ⌘ All possible connections are available before "programming"
 - ☐ in reality, all AND and OR gates are NANDs

 


Autumn 2000

CSE370 - III - Combinational Logic Technologies

23

After programming

- ⌘ Unwanted connections are "blown"
 - ☑ fuse (normally connected, break unwanted ones)
 - ☑ anti-fuse (normally disconnected, make wanted connections)

 

Autumn 2000


CSE370 - III - Combinational Logic Technologies

24

Alternate representation for high fan-in structures

⌘ Short-hand notation so we don't have to draw all the wires

 
☒ × signifies a connection is present and perpendicular signal is an input to gate



notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

 

Programmable logic array example

⌘ Multiple functions of A, B, C

☒ $F1 = A B C$

☒ $F2 = A + B + C$


☒ $F3 = A' B' C'$

☒ $F4 = A' + B' + C'$

☒ $F5 = A \text{ xor } B \text{ xor } C$

☒ $F6 = A \text{ xnor } B \text{ xnor } C$


A	B	C	F1	F2	F3	F4	F5	F6
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	1	1	1
0	1	0	0	1	0	1	1	1
0	1	1	0	1	0	1	0	0
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	0
1	1	0	0	1	0	1	0	0
1	1	1	1	1	0	0	1	1

 

PALs and PLAs

- ⌘ Programmable logic array (PLA)
 - ☒ what we've seen so far
 - ☒ unconstrained fully-general AND and OR arrays
- ⌘ Programmable array logic (PAL)
 - ☒ constrained topology of the OR array
 - ☒ innovation by Monolithic Memories
 - ☒ faster and smaller OR plane

 a given column of the OR array has access to only a subset of the possible product terms



PALs and PLAs: design example

- ⌘ BCD to Gray code converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	-	-	-	-	-
1	1	-	-	-	-	-	-

minimized functions:

$$W = A + B D + B C$$


$$X = B C'$$

$$Y = B + C$$

$$Z = A'B'C'D + B C D + A D' + B' C D'$$

PALs and PLAs: design example (cont'd)

⌘ Code converter: programmed PLA

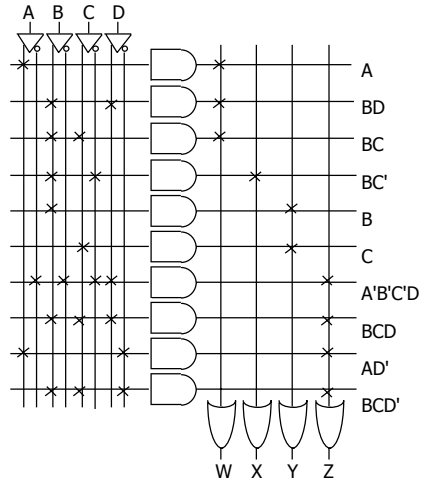

minimized functions:

$$\begin{aligned} W &= A + B D + B C \\ X &= B C' \\ Y &= B + C \\ Z &= A'B'C'D + B C D + A D' + B' C D' \end{aligned}$$


not a particularly good candidate for PAL/PLA implementation since no terms are shared among outputs

however, much more compact and regular implementation when compared with discrete AND and OR gates

PALs and PLAs: design example (cont'd)

⌘ Code converter: programmed PAL


4 product terms per each OR gate

 

PALs and PLAs: design example (cont'd)

⌘ Code converter: NAND gate implementation

 - ☒ loss of regularity, harder to understand
- ☒ harder to make changes



PALs and PLAs: another design example

⌘ Magnitude comparator

A	B	C	D	EQ	NE	LT	GT
0	0	0	0	1	0	0	0
0	0	0	1	0	1	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	1	0	0	0
0	1	1	0	0	1	1	0
0	1	1	1	0	1	1	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	0	1
1	0	1	0	1	0	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	1
1	1	0	1	0	1	0	1
1	1	1	0	0	1	0	1
1	1	1	1	1	0	0	0


minimized functions:

$$EQ = A'B'C'D' + A'BC'D + ABCD + AB'CD'$$

$$LT = A'C + A'B'D + B'CD$$

$$NE = AC' + A'C + B'D + BD'$$

$$GT = AC' + ABC + BC'D'$$

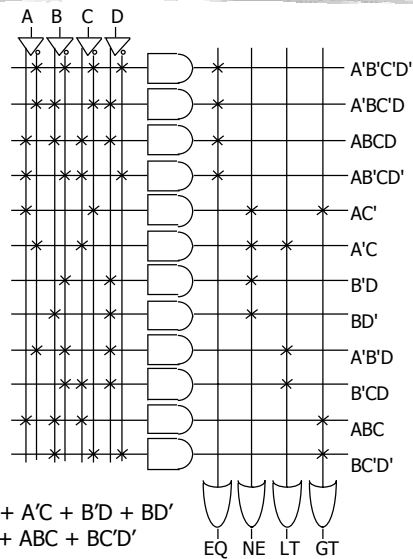


Activity

⌘ Map the following functions to the PLA below:


$$\square W = AB + A'C' + BC'$$

$$\square X = ABC + AB' + A'B$$

$$\square Y = ABC' + BC + B'C'$$

 

Activity (cont'd)

 


Read-only memories

⌘ Two dimensional array of 1s and 0s

- ☒ entry (row) is called a "word"
- ☒ width of row = word-size
- ☒ index is called an "address"
- ☒ address is input
- ☒ selected word is output

internal organization

 

ROMs and combinational logic

⌘ Combinational logic implementation (two-level canonical form) using a ROM

$$F_0 = A' B' C + A' B C' + A B' C$$


$$F_1 = A' B' C + A' B C' + A B C$$

$$F_2 = A' B' C' + A' B' C + A B' C'$$

$$F_3 = A' B C + A B' C' + A B C'$$

A	B	C	F0	F1	F2	F3
0	0	0	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	1	0	0
0	1	1	0	0	0	1
1	0	0	1	0	1	1
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	1	0	1	0	0


truth table

 

block diagram

ROM structure

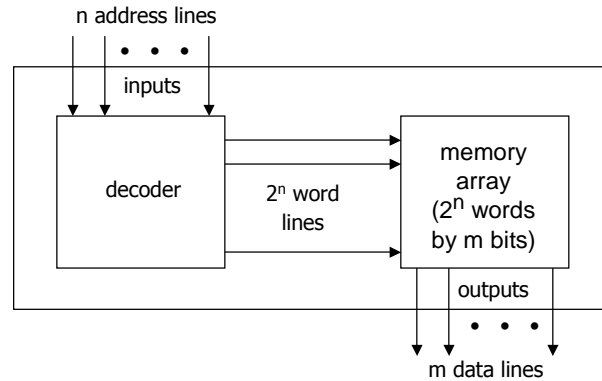- ⌘ Similar to a PLA structure but with a fully decoded AND array
 - ☒ completely flexible OR array (unlike PAL)



ROM vs. PLA

- ⌘ ROM approach advantageous when
 - ☒ design time is short (no need to minimize output functions)
 - ☒ most input combinations are needed (e.g., code converters)
 - ☒ little sharing of product terms among output functions
- ⌘ ROM problems
 - ☒ size doubles for each additional input
 - ☒ can't exploit don't cares
- ⌘ PLA approach advantageous when
 - ☒ design tools are available for multi-output minimization
 - ☒ there are relatively few unique minterm combinations
 - ☒ many minterms are shared among the output functions
- ⌘ PAL problems
 - ☒ constrained fan-ins on OR plane

Regular logic structures for two-level logic

- ⌘ ROM – full AND plane, general OR plane
 - ☒ cheap (high-volume component)
 - ☒ can implement any function of n inputs
 - ☒ medium speed
- ⌘ PAL – programmable AND plane, fixed OR plane
 - ☒ intermediate cost
 - ☒ can implement functions limited by number of terms
 - ☒ high speed (only one programmable plane that is much smaller than ROM's decoder)
- ⌘ PLA – programmable AND and OR planes
 - ☒ most expensive (most complex in design, need more sophisticated tools)
 - ☒ can implement any function up to a product term limit
 - ☒ slow (two programmable planes)

Regular logic structures for multi-level logic

- ⌘ Difficult to devise a regular structure for arbitrary connections between a large set of different types of gates
 - ☒ efficiency/speed concerns for such a structure
 - ☒ in 467 you'll learn about field programmable gate arrays (FPGAs) that are just such programmable multi-level structures
 - ☒ programmable multiplexers for wiring
 - ☒ lookup tables for logic functions (programming fills in the table)
 - ☒ multi-purpose cells (utilization is the big issue)
- ⌘ Use multiple levels of PALs/PLAs/ROMs
 - ☒ output intermediate result
 - ☒ make it an input to be used in further logic

Combinational logic technology summary

⌘ Random logic

- ☒ Single gates or in groups
- ☒ conversion to NAND-NAND and NOR-NOR networks
- ☒ transition from simple gates to more complex gate building blocks
- ☒ reduced gate count, fan-ins, potentially faster
- ☒ more levels, harder to design

⌘ Time response in combinational networks

- ☒ gate delays and timing waveforms
- ☒ hazards/glitches (what they are and why they happen)

⌘ Regular logic

- ☒ multiplexers/decoders
- ☒ ROMs
- ☒ PLAs/PALs
- ☒ advantages/disadvantages of each