

Combinational logic design case studies

- ⌘ General design procedure
- ⌘ Case studies
 - ☒ BCD to 7-segment display controller
 - ☒ logical function unit
 - ☒ process line controller
 - ☒ calendar subsystem
- ⌘ Arithmetic circuits
 - ☒ integer representations
 - ☒ addition/subtraction
 - ☒ arithmetic/logic units

General design procedure for combinational logic


- ⌘ 1. Understand the problem
 - ☒ what is the circuit supposed to do?
 - ☒ write down inputs (data, control) and outputs
 - ☒ draw block diagram or other picture
- ⌘ 2. Formulate the problem using a suitable design representation
 - ☒ truth table or waveform diagram are typical
 - ☒ may require encoding of symbolic inputs and outputs
- ⌘ 3. Choose implementation target
 - ☒ ROM, PAL, PLA
 - ☒ mux, decoder and OR-gate
 - ☒ discrete gates
- ⌘ 4. Follow implementation procedure
 - ☒ K-maps for two-level, multi-level
 - ☒ design tools and hardware description language (e.g., Verilog)

BCD to 7-segment display controller

⌘ Understanding the problem

- input is a 4 bit bcd digit (A, B, C, D)
- output is the control signals for the display (7 outputs C0 – C6)

⌘ Block diagram

 

Formalize the problem

⌘ Truth table

- show don't cares

⌘ Choose implementation target

- if ROM, we are done
- don't cares imply PAL/PLA may be attractive

⌘ Follow implementation procedure

- minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	-	-	-	-	-	-	-	-
1	1	-	-	-	-	-	-	-	-	-

Implementation as minimized sum-of-products

⌘ 15 unique product terms when minimized individually

A			
1	0	X	1
0	1	X	1
1	1	X	X
1	1	X	X
B			

A			
1	1	X	1
1	0	X	1
1	1	X	X
1	0	X	X
B			

A			
1	1	X	1
1	1	X	1
1	1	X	X
0	1	X	X
B			

A			
1	0	X	1
0	1	X	0
1	0	X	X
1	1	X	X
B			

A			
1	0	X	1
0	0	X	0
0	0	X	X
1	1	X	X
B			

A			
1	1	X	1
0	1	X	1
0	0	X	X
0	1	X	X
B			

A			
0	1	X	1
0	1	X	1
1	0	X	X
1	1	X	X
B			

$$C0 = A + B D + C + B' D'$$

$$C1 = C' D' + C D + B'$$

$$C2 = B + C' + D$$

$$C3 = B' D' + C D' + B C' D + B' C$$

$$C4 = B' D' + C D'$$



$$C5 = A + C' D' + B D' + B C'$$

$$C6 = A + C D' + B C' + B' C$$

Implementation as minimized S-o-P (cont'd)

⌘ Can do better

  - ☑ 9 unique product terms (instead of 15)
- ☑ share terms among outputs
- ☑ each output not necessarily in minimized form



$$C0 = A + B D + C + B' D'$$

$$C1 = C' D' + C D + B'$$

$$C2 = B + C' + D$$

$$C3 = B' D' + C D' + B C' D + B' C$$

$$C4 = B' D' + C D'$$

$$C5 = A + C' D' + B D' + B C'$$

$$C6 = A + C D' + B C' + B' C$$

$$C0 = B C' D + C D + B' D' + B C D' + A$$

$$C1 = B' D + C' D' + C D + B' D'$$

$$C2 = B' D + B C' D + C' D' + C D + B C D'$$


$$C3 = B C' D + B' D + B' D' + B C D'$$

$$C4 = B' D' + B C D'$$

$$C5 = B C' D + C' D' + A + B C D'$$

$$C6 = B' C + B C' + B C D' + A$$

PLA implementation

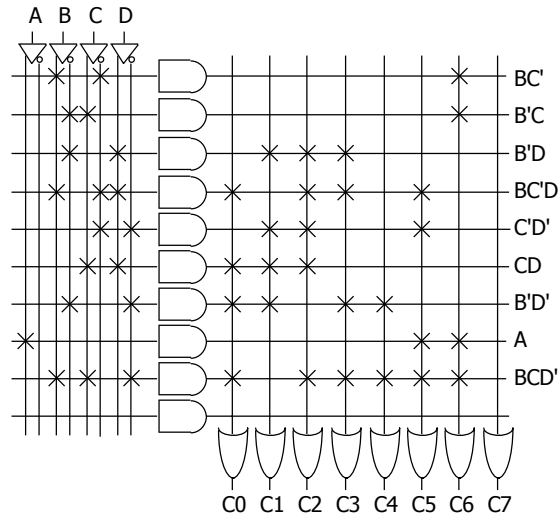

PAL implementation/Discrete gate implementation

⌘ Limit of 4 product terms per output

- ☒ decomposition of functions with larger number of terms
- ☒ do not share terms in PAL anyway
(although there are some with some shared terms)

$$C2 = B + C' + D$$

$$C2 = B'D + B'C'D + C'D' + CD + BCD'$$

$$C2 = B'D + B'C'D + C'D' + W \quad \leftarrow \text{need another input and another output}$$

$$W = CD + BCD'$$

⌘ decompose into multi-level logic (hopefully with CAD support)

- ☒ find common sub-expressions among functions

$$C0 = C3 + A'BX' + ADY$$

$$C1 = Y + A'C5' + C'D'C6$$

$$C2 = C5 + A'B'D + A'CD$$

$$C3 = C4 + BDC5 + A'B'X'$$

$$C4 = D'Y + A'CD'$$

$$C5 = C'C4 + AY + A'BX$$

$$C6 = AC4 + CC5 + C4'C5 + A'B'C$$

$$X = C' + D'$$

$$Y = B'C'$$

Logical function unit

⌘ Multi-purpose function block

- ☒ 3 control inputs to specify operation to perform on operands
- ☒ 2 data inputs for operands
- ☒ 1 output of the same bit-width as operands


C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \cdot B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \cdot B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0

3 control inputs: C0, C1, C2
2 data inputs: A, B
1 output: F

Formalize the problem

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

 choose implementation technology
5-variable K-map to discrete gates
multiplexor implementation




Production line control

- ⌘ Rods of varying length (+/-10%) travel on conveyor belt
 - ☒ mechanical arm pushes rods within spec (+/-5%) to one side
 - ☒ second arm pushes rods too long to other side
 - ☒ rods that are too short stay on belt
 - ☒ 3 light barriers (light source + photocell) as sensors
 - ☒ design combinational logic to activate the arms
- ⌘ Understanding the problem
 - ☒ inputs are three sensors
 - ☒ outputs are two arm control signals
 - ☒ assume sensor reads "1" when tripped, "0" otherwise
 - ☒ call sensors A, B, C

Sketch of problem

 - ⌘ Position of sensors
 - ☒ A to B distance = specification - 5%
 - ☒ A to C distance = specification + 5%



Formalize the problem

⌘ Truth table

show don't cares

A	B	C	Function
0	0	0	do nothing
0	0	1	do nothing
0	1	0	do nothing
0	1	1	do nothing
1	0	0	too short
1	0	1	don't care
1	1	0	in spec
1	1	1	too long

logic implementation now straightforward
just use three 3-input AND gates

"too short" = $AB'C$
(only first sensor tripped)

"in spec" = $AB C'$
(first two sensors tripped)

"too long" = $A B C$
(all three sensors tripped)

Calendar subsystem

⌘ Determine number of days in a month (to control watch display)

used in controlling the display of a wrist-watch LCD screen

inputs: month, leap year flag

outputs: number of days

⌘ Use software implementation to help understand the problem


```
integer number_of_days ( month, leap_year_flag) {
    switch (month) {
        case 1: return (31);
        case 2: if (leap_year_flag == 1)
                then return (29)
                else return (28);
        case 3: return (31);
        case 4: return (30);
        case 5: return (31);
        case 6: return (30);
        case 7: return (31);
        case 8: return (31);
        case 9: return (30);
        case 10: return (31);
        case 11: return (30);
        case 12: return (31);
        default: return (0);
    }
}
```

Formalize the problem

⌘ Encoding:

- ☒ binary number for month: 4 bits
- ☒ 4 wires for 28, 29, 30, and 31
one-hot – only one true at any time

⌘ Block diagram:

 

month	leap	28	29	30	31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
0101	-	0	0	0	1
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-

Choose implementation target and perform mapping

⌘ Discrete gates

- ☒ $28 = m8' m4' m2 m1' leap'$
- ☒ $29 = m8' m4' m2 m1' leap$
- ☒ $30 = m8' m4 m1' + m8 m1$
- ☒ $31 = m8' m1 + m8 m1'$

⌘ Can translate to S-o-P or P-o-S

month	leap	28	29	30	31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
0101	-	0	0	0	1
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-

Leap year flag

- ⌘ Determine value of leap year flag given the year
 - ☒ For years after 1582 (Gregorian calendar reformation),
 - ☒ leap years are all the years divisible by 4,
 - ☒ except that years divisible by 100 are not leap years,
 - ☒ but years divisible by 400 are leap years.
- ⌘ Encoding the year:
 - ☒ binary – easy for divisible by 4,
but difficult for 100 and 400 (not powers of 2)
 - ☒ BCD – easy for 100,
but more difficult for 4, what about 400?
- ⌘ Parts:
 - ☒ construct a circuit that determines if the year is divisible by 4
 - ☒ construct a circuit that determines if the year is divisible by 100
 - ☒ construct a circuit that determines if the year is divisible by 400
 - ☒ combine the results of the previous three steps to yield the leap year flag

Activity: divisible-by-4 circuit

- ⌘ BCD coded year
 - ☒ YM8 YM4 YM2 YM1 – YH8 YH4 YH2 YH1 – YT8 YT4 YT2 YT1 – YO8 YO4 YO2 YO1
- ⌘ Only need to look at low-order two digits of the year
all years ending in 00, 04, 08, 12, 16, 20, etc. are divisible by 4
 - ☒ if tens digit is even, then divisible by 4 if ones digit is 0, 4, or 8
 - ☒ if tens digit is odd, then divisible by 4 if the ones digit is 2 or 6.
- ⌘ Translates into the following Boolean expression
(where YT1 is the year's tens digit low-order bit,
YO8 is the high-order bit of year's ones digit, etc.):
$$YT1' (YO8' YO4' YO2' YO1' + YO8' YO4' YO2' YO1' + YO8' YO4' YO2' YO1')$$
$$+ YT1 (YO8' YO4' YO2' YO1' + YO8' YO4' YO2' YO1')$$
- ⌘ Digits with values of 10 to 15 will never occur, simplify further to yield:
$$YT1' YO2' YO1' + YT1 YO2 YO1'$$

Divisible-by-100 and divisible-by-400 circuits

- ⌘ Divisible-by-100 just requires checking that all bits of two low-order digits are all 0:

$$YT8' YT4' YT2' YT1'$$

$$\bullet YO8' YO4' YO2' YO1'$$

- ⌘ Divisible-by-400 combines the divisible-by-4 (applied to the thousands and hundreds digits) and divisible-by-100 circuits

$$(YM1' YH2' YH1' + YM1 YH2 YH1')$$

$$\bullet (YT8' YT4' YT2' YT1' \bullet YO8' YO4' YO2' YO1')$$

Combining to determine leap year flag


- ⌘ Label results of previous three circuits: D4, D100, and D400

$$\text{leap_year_flag} = D4 (D100 \bullet D400')'$$

$$= D4 \bullet D100' + D4 \bullet D400$$

$$= D4 \bullet D100' + D400$$

Implementation of leap year flag

 

Arithmetic circuits


- ⌘ Excellent examples of combinational logic design
- ⌘ Time vs. space trade-offs
 - ☒ doing things fast may require more logic and thus more space
 - ☒ example: carry lookahead logic
- ⌘ Arithmetic and logic units
 - ☒ general-purpose building blocks
 - ☒ critical components of processor datapaths
 - ☒ used within most computer instructions

Number systems

- ⌘ Representation of positive numbers is the same in most systems
- ⌘ Major differences are in how negative numbers are represented
- ⌘ Representation of negative numbers come in three major schemes
 - ☒ sign and magnitude
 - ☒ 1s complement
 - ☒ 2s complement
- ⌘ Assumptions
 - ☒ we'll assume a 4 bit machine word
 - ☒ 16 different values can be represented
 - ☒ roughly half are positive, half are negative

Sign and magnitude

 - ⌘ One bit dedicate to sign (positive or negative)
 - ☒ sign: 0 = positive (or zero), 1 = negative
- ⌘ Rest represent the absolute value or magnitude
 - ☒ three low order bits: 0 (000) thru 7 (111)
- ⌘ Range for n bits
 - ☒ $\pm 2^{n-1} - 1$ (two representations for 0)
- ⌘ Cumbersome addition/subtraction
 - ☒ must compare magnitudes to determine sign of result



1s complement

⌘ If N is a positive number, then the negative of N (its 1s complement or N') is $N' = (2^n - 1) - N$

☒ example: 1s complement of 7

$$\begin{array}{rcl}
 2^4 & = & 10000 \\
 1 & = & \underline{00001} \\
 2^4 - 1 & = & 1111 \\
 7 & = & \underline{0111} \\
 & & 1000 = -7 \text{ in 1s complement form}
 \end{array}$$

☒ shortcut: simply compute bit-wise complement (0111 -> 1000)

1s complement (cont'd)

⌘ Subtraction implemented by 1s complement and then addition


⌘ Two representations of 0

☒ causes some complexities in addition

⌘ High-order bit can act as sign bit

$$0\ 100 = +4$$

$$1\ 011 = -4$$

 


2s complement

- ⌘ 1s complement with negative numbers shifted one position clockwise
 - ☑ only one representation for 0
 - ☑ one more negative number than positive number
 - ☑ high-order bit can act as sign bit

$$0\ 100 = +4$$

$$1\ 100 = -4$$

 

2s complement (cont'd)

- ⌘ If N is a positive number, then the negative of N (its 2s complement or N*) is $N^* = 2n - N$

- ☑ example: 2s complement of 7

$$2^4 = 10000$$

$$\text{subtract } 7 = \underline{0111}$$

- ☑ example: 2s complement of -7

$$1001 = \text{repr. of } -7$$

$$2^4 = 10000$$

$$\text{subtract } -7 = \underline{1001}$$

$$0111 = \text{repr. of } 7$$

- ☑ shortcut: 2s complement = bit-wise complement + 1
 - ☑ 0111 -> 1000 + 1 -> 1001 (representation of -7)
 - ☑ 1001 -> 0110 + 1 -> 0111 (representation of 7)

2s complement addition and subtraction

⌘ Simple addition and subtraction

- ☑ simple scheme makes 2s complement the virtually unanimous choice for integer number systems in computers

$$\begin{array}{r}
 4 \quad 0100 \\
 + 3 \quad 0011 \\
 \hline
 7 \quad 0111
 \end{array}
 \qquad
 \begin{array}{r}
 -4 \quad 1100 \\
 + (-3) \quad 1101 \\
 \hline
 -7 \quad 11001
 \end{array}$$

$$\begin{array}{r}
 4 \quad 0100 \\
 - 3 \quad 1101 \\
 \hline
 1 \quad 10001
 \end{array}
 \qquad
 \begin{array}{r}
 -4 \quad 1100 \\
 + 3 \quad 0011 \\
 \hline
 -1 \quad 1111
 \end{array}$$

Why can the carry-out be ignored?

⌘ Can't ignore it completely

- ☑ needed to check for overflow (see next two slides)

⌘ When there is no overflow, carry-out may be true but can be ignored

– $M + N$ when $N > M$:

$$M^* + N = (2n - M) + N = 2n + (N - M)$$

ignoring carry-out is just like subtracting $2n$

– $M + -N$ where $N + M \leq 2n-1$


$$(-M) + (-N) = M^* + N^* = (2n - M) + (2n - N) = 2n - (M + N) + 2n$$

ignoring the carry, it is just the 2s complement representation for $-(M + N)$

Overflow in 2s complement addition/subtraction

⌘ Overflow conditions


- ☒ add two positive numbers to get a negative number
- ☒ add two negative numbers to get a positive number

 

Autumn 2000

CSE370 - V - Combinational Logic Case Studies

31

 

Overflow conditions

⌘ Overflow when carry into sign bit position is not equal to carry-out

$$\begin{array}{r}
 5 \quad 0111 \\
 -3 \quad 0101 \\
 \hline
 -8 \quad 0011 \\
 \hline
 -8 \quad 1000
 \end{array}$$

overflow

$$\begin{array}{r}
 -7 \quad 1000 \\
 -2 \quad 1001 \\
 \hline
 -7 \quad 1110 \\
 \hline
 -7 \quad 10111
 \end{array}$$

overflow

$$\begin{array}{r}
 5 \quad 0000 \\
 -2 \quad 0101 \\
 \hline
 7 \quad 0010 \\
 \hline
 7 \quad 0111
 \end{array}$$

no overflow

$$\begin{array}{r}
 -3 \quad 1111 \\
 -5 \quad 1101 \\
 \hline
 -8 \quad 1011 \\
 \hline
 -8 \quad 11000
 \end{array}$$

no overflow

Autumn 2000

CSE370 - V - Combinational Logic Case Studies

32

Circuits for binary addition

⌘ Half adder (add 2 1-bit numbers)

☑ Sum = $A_i' B_i + A_i B_i' = A_i \text{ xor } B_i$

☑ Cout = $A_i B_i$

⌘ Full adder (carry-in to cascade for multi-bit adders)

☑ Sum = $C_i \text{ xor } A \text{ xor } B$

☑ Cout = $B C_i + A C_i + A B = C_i (A + B) + A B$

A _i	B _i	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1


A _i	B _i	C _{in}	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full adder implementations

⌘ Standard approach

☑ 6 gates

☑ 2 XORs, 2 ANDs, 2 ORs

 


⌘ Alternative implementation

☑ 5 gates

☑ half adder is an XOR gate and AND gate

☑ 2 XORs, 2 ANDs, 1 OR
 
$$\text{Cout} = A B + C_{in} (A \text{ xor } B) = A B + B C_{in} + A C_{in}$$




Adder/subtractor

⌘ Use an adder to do subtraction thanks to 2s complement representation

$$\square A - B = A + (-B) = A + B' + 1$$

\square control signal selects B or 2s complement of B

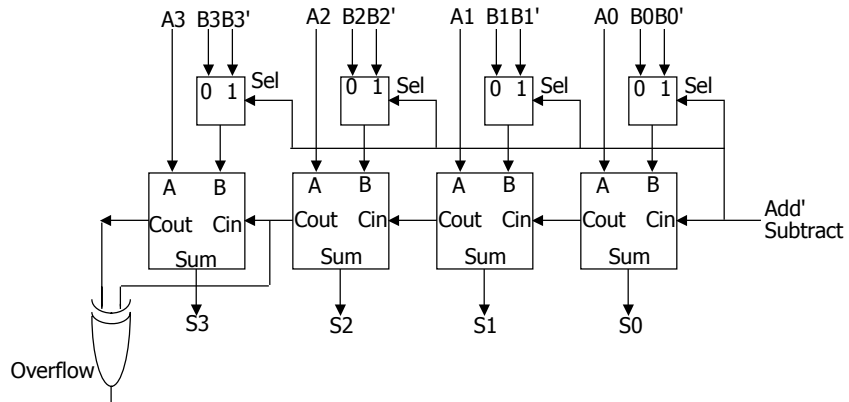

Autumn 2000


CSE370 - V - Combinational Logic Case Studies

35

Ripple-carry adders

⌘ Critical delay

\square the propagation of carry from low to high order stages

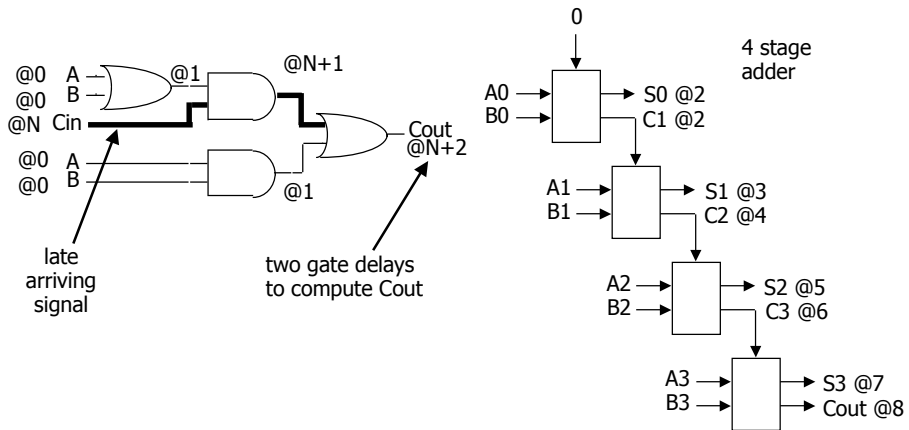

Autumn 2000


CSE370 - V - Combinational Logic Case Studies

36

Ripple-carry adders (cont'd)

⌘ Critical delay

 - ☒ the propagation of carry from low to high order stages
- ☒ 1111 + 0001 is the worst case addition
- ☒ carry must propagate through all bits



Carry-lookahead logic

⌘ Carry generate: $G_i = A_i B_i$

- ☒ must generate carry when $A = B = 1$

⌘ Carry propagate: $P_i = A_i \oplus B_i$

- ☒ carry-in will equal carry-out here

⌘ Sum and Cout can be re-expressed in terms of generate/propagate:

- ☒ $S_i = A_i \oplus B_i \oplus C_i$
 $= P_i \oplus C_i$
- ☒ $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$
 $= A_i B_i + C_i (A_i + B_i)$
 $= A_i B_i + C_i (A_i \oplus B_i)$
 $= G_i + C_i P_i$

Carry-lookahead logic (cont'd)

⌘ Re-express the carry logic as follows:

$$\square C1 = G0 + P0 C0$$

$$\square C2 = G1 + P1 C1 = G1 + P1 G0 + P1 P0 C0$$

$$\square C3 = G2 + P2 C2 = G2 + P2 G1 + P2 P1 G0 + P2 P1 P0 C0$$

$$\square C4 = G3 + P3 C3 = G3 + P3 G2 + P3 P2 G1 + P3 P2 P1 G0 + P3 P2 P1 P0 C0$$





⌘ Each of the carry equations can be implemented with two-level logic

☒ all inputs are now directly derived from data inputs and not from intermediate carries


☒ this allows computation of all sum outputs to proceed in parallel

Carry-lookahead implementation

    ⌘ Adder with propagate and generate outputs




increasingly complex
logic for carries

 

Carry-lookahead implementation (cont'd)

- ⌘ Carry-lookahead logic generates individual carries
 - ☒ sums computed much more quickly in parallel
 - ☒ however, cost of carry logic increases with more stages

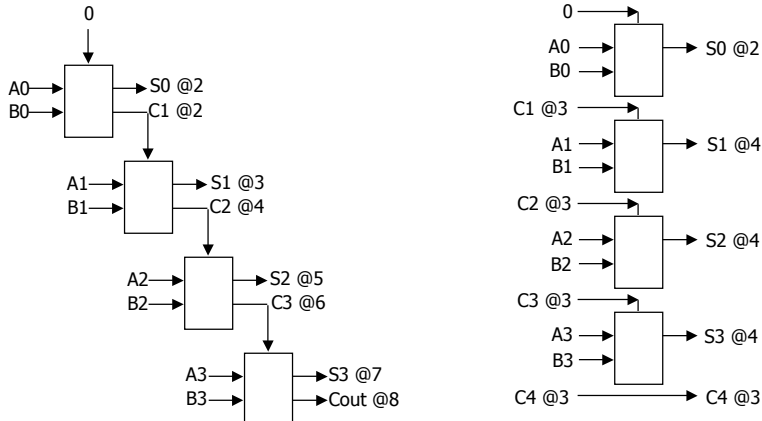


Autumn 2000

CSE370 - V - Combinational Logic Case Studies

41

Carry-lookahead adder with cascaded carry-lookahead logic

- ⌘ Carry-lookahead adder
 - ☒ 4 four-bit adders with internal carry lookahead
 - ☒ second level carry lookahead unit extends lookahead to 16 bits

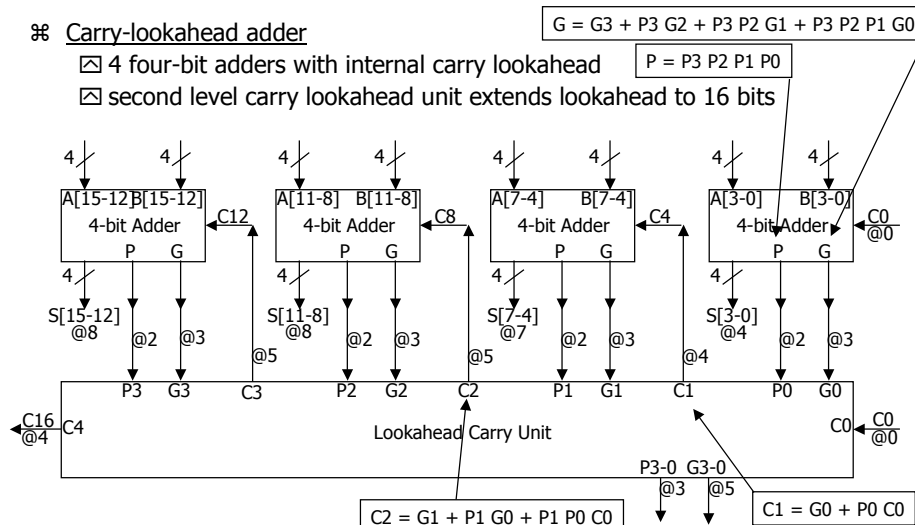


Autumn 2000

CSE370 - V - Combinational Logic Case Studies

42

Carry-select adder

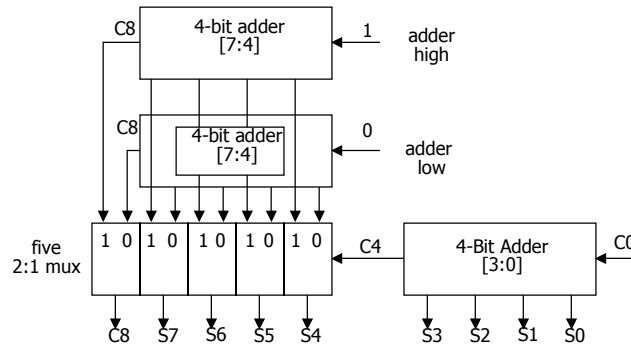- ⌘ Redundant hardware to make carry calculation go faster
 - ☑ compute two high-order sums in parallel while waiting for carry-in
 - ☑ one assuming carry-in is 0 and another assuming carry-in is 1
 - ☑ select correct result once carry-in is finally computed



Arithmetic logic unit design specification

M = 0, logical bitwise operations

S1	S0	Function	Comment
0	0	$F_i = A_i$	input A_i transferred to output
0	1	$F_i = \text{not } A_i$	complement of A_i transferred to output
1	0	$F_i = A_i \text{ xor } B_i$	compute XOR of A_i, B_i
1	1	$F_i = A_i \text{ xnor } B_i$	compute XNOR of A_i, B_i

M = 1, C0 = 0, arithmetic operations

0	0	$F = A$	input A passed to output
0	1	$F = \text{not } A$	complement of A passed to output
1	0	$F = A \text{ plus } B$	sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	sum of B and complement of A

M = 1, C0 = 1, arithmetic operations

0	0	$F = A \text{ plus } 1$	increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

logical and arithmetic operations
not all operations appear useful, but "fall out" of internal logic


Arithmetic logic unit design (cont'd)

⌘ Sample ALU – truth table

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
	0	1	X	1	X	1	X
	1	0	X	0	X	0	X
			X	0	0	1	X
			X	1	1	1	X
	1	1	X	0	1	1	X
			X	0	1	0	X
			X	1	1	0	X
1	0	0	0	0	X	0	X
	0	1	0	1	X	1	X
	1	0	0	0	X	0	X
			0	0	0	1	0
			0	1	1	1	0
	1	1	0	0	1	1	0
			0	0	1	0	0
			0	1	1	0	0
1	0	0	1	0	X	1	0
	0	1	1	1	X	0	1
	1	0	1	0	X	0	1
			1	0	0	1	0
			1	1	1	0	0
			1	1	0	1	1
	1	1	1	0	1	1	1
			1	1	1	0	1
			1	1	0	1	0
			1	1	1	0	1

Arithmetic logic unit design (cont'd)

 
⌘ Sample ALU – multi-level discrete gate logic implementation



12 gates

Arithmetic logic unit design (cont'd)

 ⌘ Sample ALU – clever multi-level implementation



first-level gates

use S0 to complement Ai

S0 = 0 causes gate X1 to pass Ai

S0 = 1 causes gate X1 to pass Ai'

use S1 to block Bi

S1 = 0 causes gate A1 to make Bi go forward as 0
(don't want Bi for operations with just A)

S1 = 1 causes gate A1 to pass Bi

use M to block Ci

M = 0 causes gate A2 to make Ci go forward as 0
(don't want Ci for logical operations)

M = 1 causes gate A2 to pass Ci

other gates

for M=0 (logical operations, Ci is ignored)

$$F_i = S_1 B_i \text{ xor } (S_0 \text{ xor } A_i)$$

$$= S_1 S_0' (A_i) + S_1 S_0 (A_i')$$

$$+ S_1 S_0' (A_i B_i' + A_i' B_i) + S_1 S_0 (A_i' B_i' + A_i B_i)$$

for M=1 (arithmetic operations)

$$F_i = S_1 B_i \text{ xor } ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

$$C_{i+1} = C_i (S_0 \text{ xor } A_i) + S_1 B_i ((S_0 \text{ xor } A_i) \text{ xor } C_i) =$$

just a full adder with inputs S0 xor Ai, S1 Bi, and Ci

Summary for examples of combinational logic

⌘ Combinational logic design process

- ☑ formalize problem: encodings, truth-table, equations
- ☑ choose implementation technology (ROM, PAL, PLA, discrete gates)
- ☑ implement by following the design procedure for that technology

⌘ Binary number representation

- ☑ positive numbers the same
- ☑ difference is in how negative numbers are represented
- ☑ 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition

⌘ Circuits for binary addition

- ☑ basic half-adder and full-adder
- ☑ carry lookahead logic
- ☑ carry-select

⌘ ALU Design

- ☑ specification, implementation