

Sequential logic examples

- ⌘ Basic design approach: a 4-step design process
- ⌘ Hardware description languages and finite state machines
- ⌘ Implementation examples and case studies
 - ☒ finite-string pattern recognizer
 - ☒ complex counter
 - ☒ traffic light controller
 - ☒ door combination lock

General FSM design procedure

- ⌘ (1) Determine inputs and outputs
- ⌘ (2) Determine possible states of machine
 - ☒ – state minimization
- ⌘ (3) Encode states and outputs into a binary code
 - ☒ – state assignment or state encoding
 - ☒ – output encoding
 - ☒ – possibly input encoding (if under our control)
- ⌘ (4) Realize logic to implement functions for states and outputs
 - ☒ – combinational logic implementation and optimization
 - ☒ – choices made in steps 2 and 3 can have large effect on resulting logic

Finite string pattern recognizer (step 1)

⌘ Finite string pattern recognizer

- ☑ one input (X) and one output (Z)
- ☑ output is asserted whenever the input sequence ...010... has been observed, as long as the sequence 100 has never been seen

⌘ Step 1: understanding the problem statement

- ☑ sample input/output behavior:


X: 0 0 1 0 1 0 1 0 0 1 0 ...
Z: 0 0 0 1 0 1 0 1 0 0 0 ...

X: 1 1 0 1 1 0 1 0 0 1 0 ...
Z: 0 0 0 0 0 0 0 1 0 0 0 ...

Finite string pattern recognizer (step 2)


⌘ Step 2: draw state diagram

 - ☑ for the strings that must be recognized, i.e., 010 and 100
- ☑ a Moore implementation




Finite string pattern recognizer (step 2, cont'd)

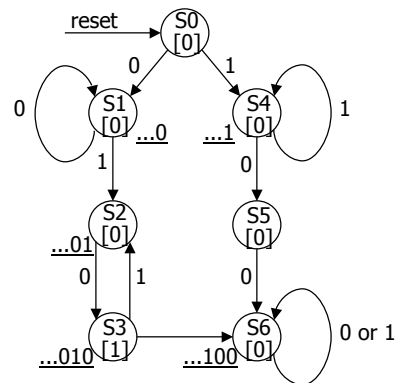- ⌘ Exit conditions from state S3: have recognized ...010
 - ☑ if next input is 0 then have ...0100 = ...100 (state S6)
 - ☑ if next input is 1 then have ...0101 = ...01 (state S2)
- ⌘ Exit conditions from S1: recognizes strings of form ...0 (no 1 seen)
 - ☑ loop back to S1 if input is 0
- ⌘ Exit conditions from S4: recognizes strings of form ...1 (no 0 seen)
 - ☑ loop back to S4 if input is 1



Finite string pattern recognizer (step 2, cont'd)

- ⌘ S2 and S5 still have incomplete transitions
 - ☑ S2 = ...01; If next input is 1, then string could be prefix of (01)1(00) S4 handles just this case
 - ☑ S5 = ...10; If next input is 1, then string could be prefix of (10)1(0) S2 handles just this case
- ⌘ Reuse states as much as possible
 - ☑ look for same meaning
 - ☑ state minimization leads to smaller number of bits to represent states
- ⌘ Once all states have a complete set of transitions we have a final state diagram

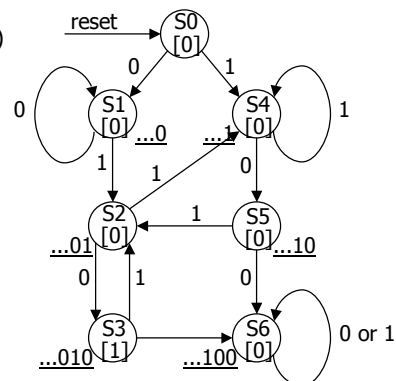

Finite string pattern recognizer (step 3)

⌘ Verilog description including state assignment (or state encoding)

```
module string (clk, X, rst, Q0, Q1, Q2, Z);
input clk, X, rst;
output Q0, Q1, Q2, Z;

reg state[0:2];
`define S0 [0,0,0] //reset state
`define S1 [0,0,1] //strings ending in ...0
`define S2 [0,1,0] //strings ending in ...01
`define S3 [0,1,1] //strings ending in ...010
`define S4 [1,0,0] //strings ending in ...1
`define S5 [1,0,1] //strings ending in ...10
`define S6 [1,1,0] //strings ending in ...100

assign Q0 = state[0];
assign Q1 = state[1];
assign Q2 = state[2];
assign Z = (state == `S3);

always @(posedge clk) begin
if rst state = `S0;
else
case (state)
`S0: if (X) state = `S4 else state = `S1;
`S1: if (X) state = `S2 else state = `S1;
`S2: if (X) state = `S4 else state = `S3;
`S3: if (X) state = `S2 else state = `S6;
`S4: if (X) state = `S4 else state = `S5;
`S5: if (X) state = `S2 else state = `S6;
`S6: state = `S6;
default: begin
$display ("invalid state reached");
state = 3'bxxx;
endcase
end
endmodule
```

Finite string pattern recognizer

⌘ Review of process

- understanding problem
 - write down sample inputs and outputs to understand specification
- derive a state diagram
 - write down sequences of states and transitions for sequences to be recognized
- minimize number of states
 - add missing transitions; reuse states as much as possible
- state assignment or encoding
 - encode states with unique patterns
- simulate realization
 - verify I/O behavior of your state diagram to ensure it matches specification

Complex counter

⌘ A synchronous 3-bit counter has a mode control M

- ☒ when $M = 0$, the counter counts up in the binary sequence
- ☒ when $M = 1$, the counter advances through the Gray code sequence

binary: 000, 001, 010, 011, 100, 101, 110, 111

Gray: 000, 001, 011, 010, 110, 111, 101, 100


⌘ Valid I/O behavior (partial)

Mode Input M	Current State	Next State
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111

Complex counter (state diagram)

⌘ Deriving state diagram

 - ☒ one state for each output combination
- ☒ add appropriate arcs for the mode control



Complex counter (state encoding)

⌘ Verilog description including state encoding

```

module string (clk, M, rst, Z0, Z1, Z2);
input clk, X, rst;
output Z0, Z1, Z2;

reg state[0:2];
`define S0 = [0,0,0];
`define S1 = [0,0,1];
`define S2 = [0,1,0];
`define S3 = [0,1,1];
`define S4 = [1,0,0];
`define S5 = [1,0,1];
`define S6 = [1,1,0];
`define S7 = [1,1,1];

assign Z0 = state[0];
assign Z1 = state[1];
assign Z2 = state[2];


always @(posedge clk) begin
if rst state = `S0;
else
case (state)
`S0: state = `S1;
`S1: if (M) state = `S3 else state = `S2;
`S2: if (M) state = `S6 else state = `S3;
`S3: if (M) state = `S2 else state = `S4;
`S4: if (M) state = `S0 else state = `S5;
`S5: if (M) state = `S4 else state = `S6;
`S6: if (M) state = `S7 else state = `S7;
`S7: if (M) state = `S5 else state = `S0;
endcase
end
endmodule

```

Traffic light controller as two communicating FSMs


⌘ Without separate timer

 - ☒ S0 would require 7 states
- ☒ S1 would require 3 states
- ☒ S2 would require 7 states
- ☒ S3 would require 3 states
- ☒ S1 and S3 have simple transformation
- ☒ S0 and S2 would require many more arcs
 - ☒ C could change in any of seven states



⌘ By factoring out timer

 - ☒ greatly reduce number of states
 - ☒ 4 instead of 20
- ☒ counter only requires seven or eight states
 - ☒ 12 total instead of 20



Traffic light controller FSM

⌘ Specification of inputs, outputs, and state elements

```
module FSM(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
  output HR;
  output HY;
  output HG;
  output FR;
  output FY;
  output FG;
  output ST;
  input TS;
  input TL;
  input C;
  input reset;
  input Clk;

  reg [6:1] state;
  reg ST;

  `define highwaygreen 6'b001100
  `define highwayyellow 6'b010100
  `define farmroadgreen 6'b100001
  `define farmroadyellow 6'b100010

  assign HR = state[6];
  assign HY = state[5];
  assign HG = state[4];
  assign FR = state[3];
  assign FY = state[2];
  assign FG = state[1];
endmodule
```

specify state bits and codes
for each state as well as
connections to outputs

Traffic light controller FSM (cont'd)

```
initial begin state = `highwaygreen; ST = 0; end

always @(posedge Clk)
begin
  if (reset)
    begin state = `highwaygreen; ST = 1; end
  else
    begin
      ST = 0;
      case (state)
        `highwaygreen:
          if (TL & C) begin state = `highwayyellow; ST = 1; end
        `highwayyellow:
          if (TS) begin state = `farmroadgreen; ST = 1; end
        `farmroadgreen:
          if (TL | !C) begin state = `farmroadyellow; ST = 1; end
        `farmroadyellow:
          if (TS) begin state = `highwaygreen; ST = 1; end
      endcase
    end
  end
endmodule
```

case statement
triggered by
clock edge

Timer for traffic light controller

⌘ Another FSM

```
module Timer(TS, TL, ST, Clk);
    output TS;
    output TL;
    input  ST;
    input  Clk;
    integer value;

    assign TS = (value >= 4); // 5 cycles after reset
    assign TL = (value >= 14); // 15 cycles after reset

    always @(posedge ST) value = 0; // async reset

    always @(posedge Clk) value = value + 1;
endmodule
```


Complete traffic light controller

⌘ Tying it all together (FSM + timer)

☒ structural Verilog not supported by DesignWorks (which uses schematic)


```
module main(HR, HY, HG, FR, FY, FG, reset, C, Clk);
    output HR, HY, HG, FR, FY, FG;
    input  reset, C, Clk;

     Timer part1(TS, TL, ST, Clk);
    FSM   part2(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
endmodule
```



Communicating finite state machines

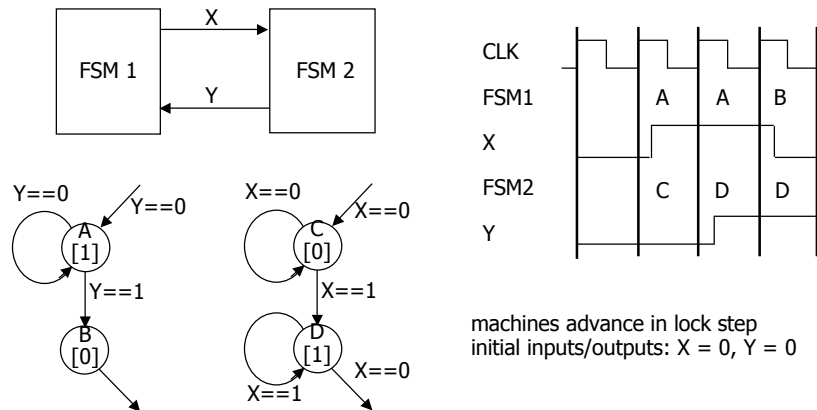
⌘ One machine's output is another machine's input



Data-path and control

⌘ Digital hardware systems = data-path + control

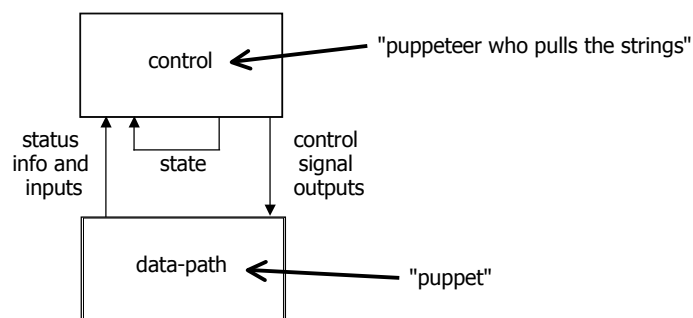- ☒ datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
- ☒ control: FSM generating sequences of control signals that instructs datapath what to do next



Digital combinational lock

⌘ Door combination lock:

- ☒ punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset

- ☒ inputs: sequence of input values, reset
- ☒ outputs: door open/close
- ☒ memory: must remember combination or always have it available

- ☒ open questions: how do you set the internal combination?
 - ☒ stored in registers (how loaded?)
 - ☒ hardwired via switches set by user

Implementation in software

```
integer combination_lock ( ) {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value( ));
    v1 = read_value( );
    if (v1 != c[1]) then error = 1;


    while (!new_value( ));
    v2 = read_value( );
    if (v2 != c[2]) then error = 1;

    while (!new_value( ));
    v3 = read_value( );
    if (v3 != c[3]) then error = 1;

    if (error == 1) then return(0); else return (1);
}
```


Determining details of the specification

 - ⌘ How many bits per input value?
- ⌘ How many values in sequence?
- ⌘ How do we know a new input value is entered?
- ⌘ What are the states and state transitions of the system?



Digital combination lock state diagram

 - ⌘ States: 5 states
 - ☑ represent point in execution of machine
 - ☑ each state has outputs
- ⌘ Transitions: 6 from state to state, 5 self transitions, 1 global
 - ☑ changes of state occur when clock says its ok
 - ☑ based on value of inputs
- ⌘ Inputs: reset, new, results of comparisons
- ⌘ Output: open/closed




Data-path and control structure

⌘ Data-path

- ☒ storage registers for combination values
- ☒ multiplexer
- ☒ comparator

⌘ Control

 - ☒ finite-state machine controller
- ☒ control for data-path (which value to compare)



State table for combination lock

⌘ Finite-state machine


- ☒ refine state diagram to take internal structure into account
- ☒ state table ready for encoding

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open
...						

Encodings for combination lock

⌘ Encode state table

- ☑ state can be: S1, S2, S3, OPEN, or ERR
 - ☑ needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - ☑ and as many as 5: 00001, 00010, 00100, 01000, 10000
 - ☑ choose 4 bits: 0001, 0010, 0100, 1000, 0000
- ☑ output mux can be: C1, C2, or C3
 - ☑ needs 2 to 3 bits to encode
 - ☑ choose 3 bits: 001, 010, 100
- ☑ output open/closed can be: open or closed
 - ☑ needs 1 or 2 bits to encode
 - ☑ choose 1 bit: 1, 0

 



reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...						
0	1	1	0100	1000	-	1

mux is identical to last 3 bits of state
 open/closed is identical to first bit of state
 therefore, we do not even need to implement
 FFs to hold state, just use outputs

Data-path implementation for combination lock

⌘ Multiplexer

 
 
- ☑ easy to implement as combinational logic when few inputs
- ☑ logic can easily get too big for most PLDs



Data-path implementation (cont'd)

⌘ Tri-state logic

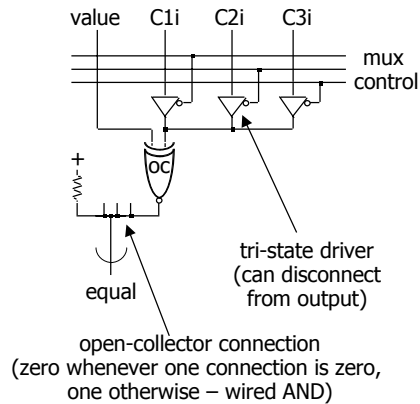 - ☑ utilize a third output state: "no connection" or "float"
- ☑ connect outputs together as long as only one is "enabled"
- ☑ open-collector gates can only output 0, not 1
 - ☑ can be used to implement logical AND with only wires




Tri-state gates

⌘ The third value


- ☑ logic values: "0", "1"
- ☑ don't care: "X" (must be 0 or 1 in real circuit!)
- ☑ third value or state: "Z" — high impedance, infinite R, no connection

⌘ Tri-state gates

 - ☑ additional input – output enable (OE)
- ☑ output values are 0, 1, and Z
- ☑ when OE is high, the gate functions normally
- ☑ when OE is low, the gate is disconnected from wire at output
- ☑ allows more than one gate to be connected to the same output wire
 - ☑ as long as only one has its output enabled at any one time (otherwise, sparks could fly)



	In	OE	Out
non-inverting	X	0	Z
tri-state	0	1	0
buffer	1	1	1

 


Tri-state and multiplexing

⌘ When using tri-state logic

- ☑ (1) make sure never more than one "driver" for a wire at any one time (pulling high and low at the same time can severely damage circuits)
- ☑ (2) make sure to only use value on wire when its being driven (using a floating value may cause failures)

 ⌘ Using tri-state gates to implement an economical multiplexer



when Select is high
Input1 is connected to F

when Select is low
Input0 is connected to F

this is essentially a 2:1 mux


Open-collector gates and wired-AND

⌘ Open collector: another way to connect gate outputs to the same wire

- ☑ gate only has the ability to pull its output low
- ☑ it cannot actively drive the wire high (default – pulled high through resistor)

⌘ Wired-AND can be implemented with open collector logic

 
- ☑ if A and B are "1", output is actively pulled low
- ☑ if C and D are "1", output is actively pulled low
- ☑ if one gate output is low and the other high, then low wins
- ☑ if both gate outputs are "1", the wire value "floats", pulled high by resistor
 - ☑ low to high transition usually slower than it would have been with a gate pulling high
- ☑ hence, the two NAND functions are ANDed together



with outputs wired together
using "wired-AND"
to form $(AB)'(CD)'$

Digital combination lock (new data-path)

 - ⌘ Decrease number of inputs
- ⌘ Remove 3 code digits as inputs
 - ☑ use code registers
 - ☑ make them loadable from value
 - ☑ need 3 load signal inputs (net gain in input $(4*3)-3=9$)
 - ☑ could be done with 2 signals and decoder (ld1, ld2, ld3, load none)



Section summary

- ⌘ FSM design
 - ☑ understanding the problem
 - ☑ generating state diagram
 - ☑ communicating state machines
- ⌘ Four case studies
 - ☑ understand I/O behavior
 - ☑ draw diagrams
 - ☑ enumerate states for the "goal"
 - ☑ expand with error conditions
 - ☑ reuse states whenever possible