


## Computer organization

- Computer design – an application of digital logic design procedures
- Computer = processing unit + memory system
- Processing unit = control + datapath
- Control = finite state machine
  - ▮ inputs = machine instruction, datapath conditions
  - ▮ outputs = register transfer control signals, ALU operation codes
  - ▮ instruction interpretation = instruction fetch, decode, execute
- Datapath = functional units + registers
  - ▮ functional units = ALU, multipliers, dividers, etc.
  - ▮ registers = program counter, shifters, storage registers

CSE 370 - Spring 2000 - Computer Organization - 1

## Structure of a computer


- Block diagram view

 

CSE 370 - Spring 2000 - Computer Organization - 2
 
## Registers

- Selectively loaded – EN or LD input
- Output enable – OE input
- Multiple registers – group 4 or 8 in parallel




OE asserted causes FF state to be connected to output pins; otherwise they are left unconnected (high impedance)

LD asserted during a lo-to-hi clock transition loads new data into FFs


CSE 370 - Spring 2000 - Computer Organization - 3
 
## Register transfer


- Point-to-point connection
  - ▮ dedicated wires
  - ▮ muxes on inputs of each register



 - Common input from multiplexer
  - ▮ load enables for each register
  - ▮ control signals for multiplexer




- Common bus with output enables
  - ▮ output enables and load enables for each register

 

CSE 370 - Spring 2000 - Computer Organization - 4

## Register files


- Collections of registers in one package
  - ▮ two-dimensional array of FFs
  - ▮ address used as index to a particular word
  - ▮ can have separate read and write addresses so can do both at same time
- 4 by 4 register file
  - ▮ 16 D-FFs
  - ▮ organized as four words of four bits each
  - ▮ write-enable (load)
  - ▮ read-enable (output enable)

 

CSE 370 - Spring 2000 - Computer Organization - 5

## Memories

- Larger collections of storage elements
  - ▮ implemented not as FFs but as much more efficient latches
  - ▮ high-density memories use 1 to 5 switches (transistors) per memory bit
- Static RAM – 1024 words each 4 bits wide
  - ▮ once written, memory holds forever (not true for denser dynamic RAM)
  - ▮ address lines to select word (10 lines for 1024 words)
  - ▮ read enable
    - ▮ same as output enable
    - ▮ often called chip select
    - ▮ permits connection of many chips into larger array
  - ▮ write enable (same as load enable)
  - ▮ bi-directional data lines
    - ▮ output when reading, input when writing

 

CSE 370 - Spring 2000 - Computer Organization - 6

### Instruction sequencing

- Example – an instruction to add the contents of two registers (Rx and Ry) and place result in a third register (Rz)
- Step 1: get the ADD instruction from memory into an instruction register
- Step 2: decode instruction
  - ┆ instruction in IR has the code of an ADD instruction
  - ┆ register indices used to generate output enables for registers Rx and Ry
  - ┆ register index used to generate load signal for register Rz
- Step 3: execute instruction
  - ┆ enable Rx and Ry output and direct to ALU
  - ┆ setup ALU to perform ADD operation
  - ┆ direct result to Rz so that it can be loaded into register

### Instruction types


- Data manipulation
  - ┆ add, subtract
  - ┆ increment, decrement
  - ┆ multiply
  - ┆ shift, rotate
  - ┆ immediate operands
- Data staging
  - ┆ load/store data to/from memory
  - ┆ register-to-register move
- Control
  - ┆ conditional/unconditional branches in program flow
  - ┆ subroutine call and return

### Elements of the control unit (aka instruction unit)

- Standard FSM elements
  - ┆ state register
  - ┆ next-state logic
  - ┆ output logic (datapath/control signalling)
  - ┆ Moore or synchronous Mealy machine to avoid loops unbroken by FF
- Plus additional "control" registers
  - ┆ instruction register (IR)
  - ┆ program counter (PC)
- Inputs/outputs
  - ┆ outputs control elements of data path
  - ┆ inputs from data path used to alter flow of program (test if zero)

 
### Instruction execution

- Control state diagram (for each diagram)
  - ┆ reset
  - ┆ fetch instruction
  - ┆ decode
  - ┆ execute
- Instructions partitioned into three classes
  - ┆ branch
  - ┆ load/store
  - ┆ register-to-register
- Different sequence through diagram for each instruction type



 
### Data path (heirarchy)

- Arithmetic circuits constructed in hierarchical and iterative fashion
  - ┆ each bit in datapath is functionally identical
  - ┆ 4-bit, 8-bit, 16-bit, 32-bit datapaths



 
### Data path (ALU)

- ALU block diagram
  - ┆ input: data and operation to perform
  - ┆ output: result of operation and status information



 
### Data path (ALU + registers)

- Accumulator
  - ┆ special register
  - ┆ one of the inputs to ALU
  - ┆ output of ALU stored back in accumulator
- One-address instructions
  - ┆ operation and address of one operand is accumulator register
  - ┆ other operand and destination is accumulator register
  - ┆ AC ← AC op Mem[addr]
  - ┆ "single address instructions" (AC implicit operand)
- Multiple registers
  - ┆ part of instruction used to choose register operands


 
### Data path (bit-slice)

- Bit-slice concept – iterate to build n-bit wide datapaths



### Instruction path


- Program counter
  - ┆ keeps track of program execution
  - ┆ address of next instruction to read from memory
  - ┆ may have auto-increment feature or use ALU
- Instruction register
  - ┆ current instruction
  - ┆ includes ALU operation and address of operand
  - ┆ also holds target of jump instruction
  - ┆ immediate operands
- Relationship to data path
  - ┆ PC may be incremented through ALU
  - ┆ contents of IR may also be required as input to ALU

### Data path (memory interface)

- Memory
  - ┆ separate data and instruction memory (Harvard architecture)
    - ┆ two address buses, two data buses
  - ┆ single combined memory (Princeton architecture)
    - ┆ single address bus, single data bus
- Separate memory
  - ┆ ALU output goes to data memory input
  - ┆ register input from data memory output
  - ┆ data memory address from instruction register
  - ┆ instruction register from instruction memory output
  - ┆ instruction memory address from program counter
- Single memory
  - ┆ address from PC or IR
  - ┆ memory output to instruction and data registers
  - ┆ memory input from ALU output

 
### Block diagram of processor

- Register transfer view of Princeton architecture
  - ┆ which register outputs are connected to which register inputs
  - ┆ arrows represent data-flow, other are control signals from control FSM
  - ┆ MAR may be a simple multiplexer rather than separate register
  - ┆ MBR is split in two (REG and IR)
  - ┆ load control for each register



 
### Block diagram of processor

- Register transfer view of Harvard architecture
  - ┆ which register outputs are connected to which register inputs
  - ┆ arrows represent data-flow, other are control signals from control FSM
  - ┆ two MARs (PC and IR)
  - ┆ two MBRs (REG and IR)
  - ┆ load control for each register



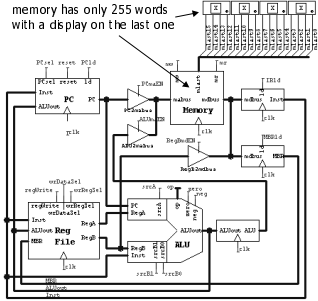
### A simplified processor data-path and memory

- Princeton architecture
- Register file
- Instruction register
- PC incremented through ALU
- Modeled after MIPS r000 (used in 378 textbook by Patterson & Hennessy)
  - really a 32 bit machine
  - we'll do a 16 bit version


 
### Processor control

- Synchronous Mealy machine
- Multiple cycles per instruction



### Processor instructions

- Three principal types (16 bits in each instruction)

type	op	rs	rt	rd	funct
R(register)	3	3	3	3	4
I(Immediate)	3	3	3	7	
J(jump)	3		13		

- Some of the instructions

	op	rs	rt	rd	funct	rd = mem[rs + offset]	
R	add	0	rs	rt	rd	0	rd = rs + rt
	sub	0	rs	rt	rd	1	rd = rs - rt
	and	0	rs	rt	rd	2	rd = rs & rt
	or	0	rs	rt	rd	3	rd = rs   rt
	sll	0	rs	rt	rd	4	rd = (rs < rt)
I	lw	1	rs	rt	offset		rd = mem[rs + offset]
	sw	2	rs	rt	offset		mem[rs + offset] = rt
	beq	3	rs	rt	offset		pc = pc + offset, if (rs == rt)
	addi	4	rs	rt	offset		rt = rs + offset
J	j	5	target address				pc = target address
	halt	7	-				stop execution until reset

### Tracing an instruction's execution

- Instruction: r3 = r1 + r2

R	0	rs=r1	rt=r2	rd=r3	funct=0
---	---	-------	-------	-------	---------

- instruction fetch
  - move instruction address from PC to memory address bus
  - assert memory read
  - move data from memory data bus into IR
  - configure PC to store new value from ALUOut
- instruction decode
  - op-code bits of IR are input to control FSM
  - rest of IR bits encode the operand addresses (rs and rt)
    - these go to register file

### Tracing an instruction's execution (cont'd)


- Instruction: r3 = r1 + r2

R	0	rs=r1	rt=r2	rd=r3	funct=0
---	---	-------	-------	-------	---------

- instruction execute
  - set up ALU inputs
  - configure ALU to perform ADD operation
  - configure register file to store ALU result (rd)


### Tracing an instruction's execution (cont'd)

- Step 1

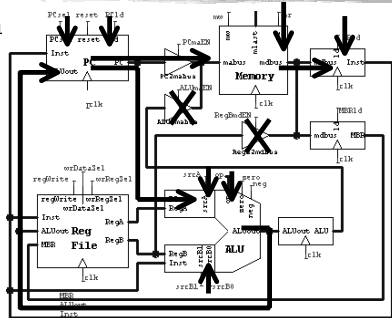


### Tracing an instruction's execution (cont'd)

#### Step 2

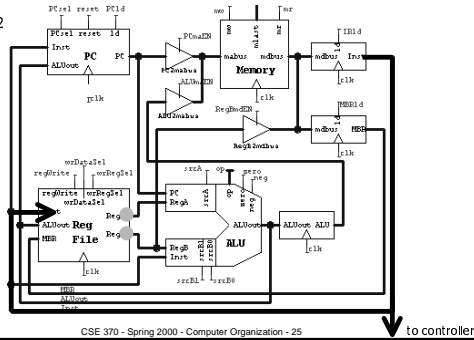

### Tracing an instruction's execution (cont'd)

#### Step 3

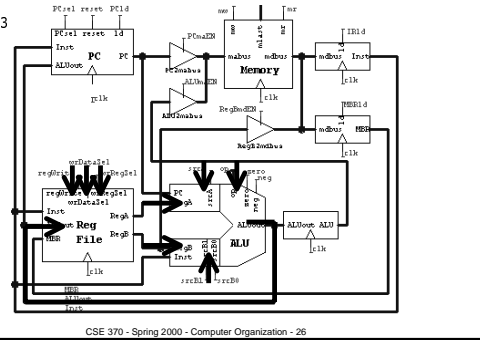

### Register-transfer-level description

- Control
  - transfer data between registers by asserting appropriate control signals
- Register transfer notation - work from register to register
  - instruction fetch:
    - $mabus \leftarrow PC;$  - move PC to memory address bus (PCmaEN, ALUmaEN)
    - memory read; - assert memory read signal (mr, RegBmDEN)
    - $IR \leftarrow memory;$  - load IR from memory data bus (IRld)
    - $op \leftarrow add$  - send PC into A input, 1 into B input, add (srcA, srcB0, srcB1, op)
    - $PC \leftarrow ALUout$  - load result of incrementing in ALU into PC (PCld, PCset)
  - instruction decode:
    - IR to controller
    - values of A and B read from register file (rs, rt)
  - instruction execution:
    - $op \leftarrow add$  - send regA into A input, regB into B input, add (srcA, srcB0, srcB1, op)
    - $rd \leftarrow ALUout$  - store result of add into destination register (regWrite, wrDataSel, wRegSel)


CSE 370 - Spring 2000 - Computer Organization - 27

### Register-transfer-level description (cont'd)

- How many states are needed to accomplish these transfers?
  - data dependencies (where do values that are needed come from?)
  - resource conflicts (ALU, busses, etc.)
- In our case, it takes three cycles
  - one for each step
  - all operation within a cycle occur between rising edges of the clock
- How do we set all of the control signals to be output by the state machine?
  - depends on the type of machine (Mealy, Moore, synchronous Mealy)

CSE 370 - Spring 2000 - Computer Organization - 28


### Review of FSM timing

 

CSE 370 - Spring 2000 - Computer Organization - 29

### FSM controller for CPU (skeletal Moore FSM)

- First pass at deriving the state diagram (Moore machine)
  - these will be further refined into sub-states

 


CSE 370 - Spring 2000 - Computer Organization - 30

### FSM controller for CPU (reset and inst. fetch)

- Assume Moore machine
  - outputs associated with states rather than arcs
- Reset state and instruction fetch sequence
- On reset (go to Fetch state)
  - start fetching instructions
  - PC will set itself to zero


$mabus \leftarrow PC;$   
 $memory\ read;$   
 $IR \leftarrow memory\ data\ bus;$   
 $PC \leftarrow PC + 1;$

 

CSE 370 - Spring 2000 - Computer Organization - 31

### FSM controller for CPU (decode)


- Operation decode state
  - next state branch based on operation code in instruction
  - read two operands out of register file
    - what if the instruction doesn't have two operands?

 

CSE 370 - Spring 2000 - Computer Organization - 32

### FSM controller for CPU (instruction execution)


- For add instruction
  - configure ALU and store result in register
- $rd \leftarrow A + B$
- other instructions may require multiple cycles

 

CSE 370 - Spring 2000 - Computer Organization - 33

### FSM controller for CPU (add instruction)

- Putting it all together and closing the loop
  - the famous instruction fetch decode execute cycle

 

CSE 370 - Spring 2000 - Computer Organization - 34

### FSM controller for CPU

- Now we need to repeat this for all the instructions of our processor
  - fetch and decode states stay the same
  - different execution states for each instruction
    - some may require multiple states if available register transfer paths require sequencing of steps

CSE 370 - Spring 2000 - Computer Organization - 35