CSE370: Introduction to Digital Design

Autumn 2001

## Homework Set 9

For final exam review; not to be turned in

I don't have prepared solutions for these. Feel free to discuss the problems among yourselves; on the mailing list; or with course staff.

Katz 8.7, p.435 (reverse engineering)

Katz 8.21, p.441 (washing machine).

Katz 8.27, p.444 (vending machine).

Referring to the "CSE370 Processor":

How can you tell that this is not a "Harvard" architecture? How would you modify the design to make it so?

Trace through the complete execution of an instruction (other than the one in the notes).

Is it possible for one instruction (take the add, for example), to have the same register used for both inputs and the output?

Suppose the clock frequency is 16MHz. What is the CSU speed, in instructions per second? (not as simple as it seems!)