

Canonical forms

◆ Last lecture

- Logic gates and truth tables
- Implementing logic functions
- CMOS switches

◆ Today's lecture

- deMorgan's theorem
- NAND and NOR
- Canonical forms
 - Sum-of-products (minterms)
 - Product-of-sums (maxterms)

de Morgan's theorem

◆ Replace

- with +, + with •, 0 with 1, and 1 with 0
- All variables with their complements

◆ Example 1: $Z = A'B' + A'C'$

$$\begin{aligned} Z' &= (A'B' + A'C')' \\ &= (A'B')' \cdot (A'C')' \\ &= (A+B) \cdot (A+C) \end{aligned}$$

◆ Example 2: $Z = A'B'C + A'BC + AB'C + ABC'$

$$\begin{aligned} Z' &= (A'B'C + A'BC + AB'C + ABC')' \\ &= (A'B'C)' \cdot (A'BC)' \cdot (AB'C)' \cdot (ABC')' \\ &= (A+B+C) \cdot (A+B'+C) \cdot (A'+B+C) \cdot (A'+B'+C) \end{aligned}$$

NAND and NOR

$(X + Y)' = X' \cdot Y'$
NOR is equivalent to AND
with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0


NAND, NOR, and de Morgan's theorem

◆ de Morgan's

- Standard form: $A'B' = (A + B)'$ $A' + B' = (AB)'$
- Inverted: $A + B = (A'B)'$ $(AB) = (A' + B')$

- AND with complemented inputs \equiv NOR
- OR with complemented inputs \equiv NAND
- OR \equiv NAND with complemented inputs
- AND \equiv NOR with complemented inputs

**pushing
the
bubble**

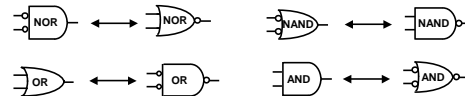

Converting between forms


◆ Introduce inversions ("bubbles")

- Introduce bubbles in pairs
 - Conserve inversions
 - Do not alter logic function

◆ Example

- AND/OR to NAND/NAND

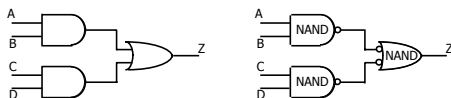
$$\begin{aligned} Z &= AB + CD \\ &= (A'+B')' + (C'+D')' \\ &= [(A'+B')(C'+D')]'' \\ &= [(AB)(CD)]'' \end{aligned}$$



Converting between forms (con't)


◆ Example: AND/OR network to NOR/NOR
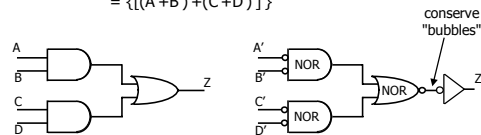
$$\begin{aligned} Z &= AB + CD \\ &= (A'+B')' + (C'+D')' \\ &= [(A'+B')(C'+D')]'' \\ &= \{[(A'+B') + (C'+D')]\}' \end{aligned}$$



Converting between forms (con't)

- ◆ Example: OR/AND to NAND/NAND

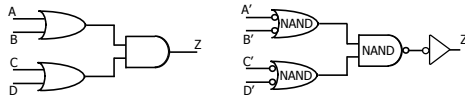


CSE370, Lecture 5

7

Converting between forms (con't)

- ◆ Example: OR/AND to NOR/NOR

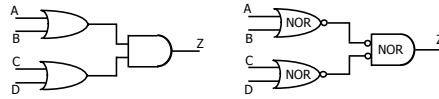


CSE370, Lecture 5

8

Why convert between forms?

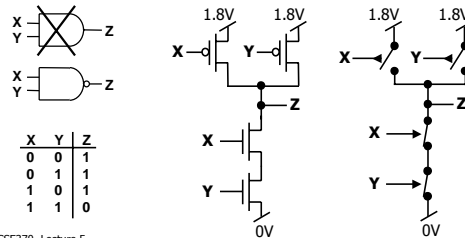- ◆ CMOS logic gates are inverting
 - Get NAND, NOR, NOT
 - Don't get AND, OR, Buffer



CSE370, Lecture 5

9

Canonical forms


- ◆ Canonical forms
 - Standard forms for Boolean expressions
 - Unique algebraic signatures
 - Generally not the simplest forms
 - ✦ Can be minimized
 - Derived from truth table
- ◆ Two canonical forms
 - Sum-of-products (minterms)
 - Product-of-sum (maxterms)

CSE370, Lecture 5

10

Sum-of-products canonical form

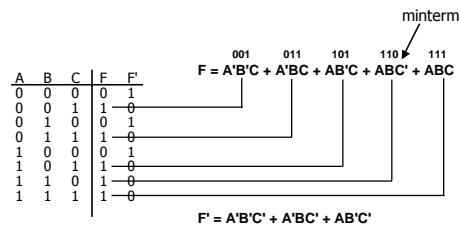- ◆ Also called disjunctive normal form
 - Commonly called a **minterm expansion**



CSE370, Lecture 5

11

Minterms

- ◆ Variables appears exactly once in each minterm
 - In true or inverted form (but not both)

A	B	C	minterms
0	0	0	A'B'C' m0
0	0	1	A'B'C m1
0	1	0	A'BC' m2
0	1	1	A'BC m3
1	0	0	AB'C' m4
1	0	1	AB'C m5
1	1	0	ABC' m6
1	1	1	ABC m7

F in canonical form:
 $F(A,B,C) = \sum m(1,3,5,6,7)$
 $= m1 + m3 + m5 + m6 + m7$
 $= A'B'C + A'BC + AB'C + ABC' + ABC$

canonical form \rightarrow minimal form
 $F(A,B,C) = A'B'C + A'BC + AB'C + ABC + ABC'$
 $= (A'B' + A'B + AB' + AB)C + ABC'$
 $= (A' + A)(B' + B)C + ABC'$
 $= ABC' + C$
 $= AB + C$

short-hand notation

CSE370, Lecture 5

12

Product-of-sums canonical form

- Also called conjunctive normal form
 - Commonly called a **maxterm expansion**

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = (A + B + C)(A + B' + C)(A' + B + C)$

$F' = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C')$

Maxterms

- Variables appears exactly once in each maxterm
 - In true or inverted form (but not both)


A	B	C	maxterms
0	0	0	A+B+C M0
0	0	1	A+B+C' M1
0	1	0	A+B'+C M2
0	1	1	A+B'+C' M3
1	0	0	A'+B+C M4
1	0	1	A'+B+C' M5
1	1	0	A'+B'+C M6
1	1	1	A'+B'+C' M7

F in canonical form:
 $F(A,B,C) = \prod M(0,2,4)$
 $= M0 \cdot M2 \cdot M4$
 $= (A+B+C)(A+B'+C)(A'+B+C)$

canonical form \rightarrow minimal form
 $F(A,B,C) = (A+B+C)(A+B'+C)(A'+B+C)$
 $= (A+B+C)(A+B'+C) \cdot (A+B+C)(A'+B+C)$
 $= (A+C)(B+C)$

short-hand notation

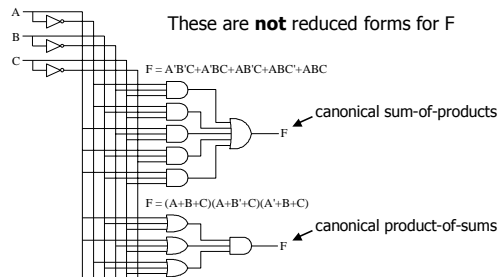Canonical implementations of $F = AB + C$



SOP, POS, and de Morgan's theorem

- Sum-of-products
 - $F' = A'B'C' + A'BC' + AB'C'$
- Apply de Morgan's to get POS
 - $(F)' = (A'B'C' + A'BC' + AB'C')'$
 - $F = (A+B+C)(A+B'+C)(A'+B+C)$
- Product-of-sums
 - $F' = (A+B+C)(A+B'+C)(A'+B+C)(A'+B'+C)$
- Apply de Morgan's to get SOP
 - $(F)' = ((A+B+C)(A+B'+C)(A'+B+C)(A'+B'+C))'$
 - $F = A'B'C' + A'BC' + AB'C' + ABC$

Conversion between canonical forms

- Minterm to maxterm
 - Use maxterms that aren't in minterm expansion
 - $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm
 - Use minterms that aren't in maxterm expansion
 - $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- Minterm of F to minterm of F'
 - Use minterms that don't appear
 - $F(A,B,C) = \sum m(1,3,5,6,7) \quad F'(A,B,C) = \sum m(0,2,4)$
- Maxterm of F to maxterm of F'
 - Use maxterms that don't appear
 - $F(A,B,C) = \prod M(0,2,4) \quad F'(A,B,C) = \prod M(1,3,5,6,7)$