 



## Overview

- ◆ Last lecture
  - Sequential Verilog
- ◆ Today
  - Review of D latches and flip-flops
  - T flip-flops and SR latches
  - State diagrams
  - Asynchronous inputs

## Latches versus flip-flops




## The master-slave D

 


Class example: Draw the timing diagram
 
## How do we make a latch?

- ◆ Two inverters hold a bit
  - As long as power is applied




 - ◆ Storing a new memory
  - Temporarily break the feedback path



 
## How do we make a D F/F?

- ◆ Edge triggering is difficult
  - Label the internal nodes
  - Draw a timing diagram
  - Start with  $Clk=1$


 
## T flip-flop


- ◆ Full name: Toggle flip-flop
- ◆ Output toggles when input is asserted
  - If  $T=1$ , then  $Q \rightarrow Q'$  when  $CLK \uparrow$
  - If  $T=0$ , then  $Q \rightarrow Q$  when  $CLK \uparrow$




Input( $t$ )	$Q(t)$	$Q(t + \Delta t)$
0	0	0
0	1	1
1	0	1
1	1	0
 
## The SR latch

- ◆ Cross-coupled NOR gates
  - Can set ( $S=1, R=0$ ) or reset ( $R=1, S=0$ ) the output



 
- ◆ Cross-coupled NAND gates
  - Can set ( $S=1, R=0$ ) or reset ( $R=1, S=0$ ) the output



## SR latch behavior


- ◆ Truth table and timing

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	disallow

 
 
## SR latch is glitch sensitive

- ◆ Static 0 hazards can set/reset latch
  - Glitch on S input sets latch
  - Glitch on R input resets latch



## Clear and preset in flip-flops


- ◆ Clear and Preset set flip-flop to a known state
  - Used at startup, reset
- ◆ Clear or Reset to a logic 0
  - Synchronous:  $Q=0$  when next clock edge arrives
  - Asynchronous:  $Q=0$  when reset is asserted
    - ☑ Doesn't wait for clock
    - ☑ Quick but dangerous
- ◆ Preset or Set the state to logic 1
  - Synchronous:  $Q=1$  when next clock edge arrives
  - Asynchronous:  $Q=1$  when reset is asserted
    - ☑ Doesn't wait for clock
    - ☑ Quick but dangerous

## State diagrams

- ◆ How do we characterize logic circuits?
  - Combinational circuits: Truth tables
  - Sequential circuits: State diagrams
- ◆ First draw the states
  - States = Unique circuit configurations
- ◆ Second draw the transitions between states
  - Transitions = Changes in state caused by inputs
 
## Example: SR latch



- ◆ Begin by drawing the states
  - States = Unique circuit configurations
  - Possible values for feedback ( $Q, Q'$ )



## Example: SR latch

### ◆ Now draw the state transitions


- Labeling inputs

  

## Observed SR latch behavior
 
### ◆ The 1-1 state is transitory

- Either R or S "gets ahead"
- Latch settles to 0-1 or 1-0 state ambiguously
- Race condition → non-deterministic transition
  - Disallow (R,S) = (1,1)



## System considerations


- Use edge-triggered flip-flops wherever possible
  - Avoid latches
  - Most common: Master-slave D
- Basic rules for correct timing
  - Clock flip-flops synchronously (all at the same time)
    - No flip-flop changes state more than once per clock cycle
    - FF propagation delay > hold time
  - Avoid mixing positive-edge triggered and negative-edge triggered flip-flops in the same circuit

## Asynchronous inputs

- Clocked circuits are synchronous
  - Circuit changes state only at clock edges
  - Signals (voltages) settle in-between clock edges
- Unclocked circuits or signals are asynchronous
  - No master clock
  - Real-world inputs (e.g. a keypress) are asynchronous
- Synchronous circuits have asynchronous inputs
  - Reset signal, memory wait, user input, etc.
  - Inputs "bounce"
  - Inputs can change at any time
    - We must synchronize the input to our clock
    - Inputs will violate flip-flop setup/hold times

 
## Debouncing

- Switch inputs bounce
  - i. e. don't make clean transitions
- Can use SR latch for debouncing
  - Eliminates dynamic hazards
  - "Cleans-up" inputs



 
## Synchronizer failure

- Occurs when FF input changes near clock edge
  - Input is neither 1 or 0 when clock goes high
  - Output may be neither 0 or 1
    - May stay undefined for a long time
  - Undefined state is called metastability


 
## Minimizing synchronizer failures

- ◆ Failure probability can never be 0
  - Can make it small
  - Cascade two (or more) flip-flops
    - ✔ Effectively synchronizes twice
    - ✔ Both would have to fail for system to fail



## Handling asynchronous inputs

- ◆ Never fan-out asynchronous inputs
  - Synchronize at circuit boundary
  - Fan-out synchronized signal

