

Overview

- ◆ Last lecture
 - Introduction to finite state machines
 - ↳ State diagrams
 - Counters as finite state machines
 - ↳ Counter design
- ◆ Today
 - Finish counter design
 - ↳ Our last design example
 - ↳ Self-starting counters

Review: Counter design procedure


1. Draw a state diagram
2. Draw a state-transition table
3. Encode the next-state functions
 - Minimize the logic using k-maps
4. Implement the design

Example: A 5-state counter

Example: A 5-state counter

- ◆ Counter repeats 5 states in sequence
 - Sequence is 000, 010, 011, 101, 110, 000 (not binary)

Step 1: State diagram

 

Step 2: State transition table
Assume D flip-flops

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	-	-	-
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	-	-	-

5-state counter (con't)

Step 3: Encode the next state functions

		C		
C+	A	0	1	X
X	1	X	1	
		B		

C+ = A

		C		
B+	A	1	1	0
X	0	X	X	1
		B		


B+ = B' + A'C'

		C		
A+	A	0	1	0
X	1	X	X	0
		B		

A+ = BC'

5-state counter (con't)


Step 4: Implement the design

 

5-state counter (con't)

- ◆ Is our design robust?
 - What if the counter starts in a 111 state?

 Does our counter get stuck in invalid states???




5-state counter (con't)

- ◆ Back-annotate our design to check it

Fill in state transition table

Draw state diagram

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 

The proper methodology is to **design** your counter to be self-starting

Self-starting counters

- ◆ Invalid states should always transition to valid states
 - Assures startup
 - Assures bit-error tolerance
- ◆ Design your counters to be self-starting
 - Draw all states in the state diagram
 - Fill in the entire state-transition table
 - May limit your ability to exploit don't cares
 - ✦ Choose startup transitions that minimize the logic

Next subject: Finite-state machines

- ◆ Generalize the counter-design methodology
 - State machines have input signals
 - State machines have complex transitions
- ◆ Finite-state machines control digital systems
 - The core of digital design