 


Working with combinational logic

- Simplification
 - two-level simplification
 - exploiting don't cares
 - algorithm for simplification
- Logic realization
 - two-level logic and canonical forms realized with NANDs and NORs
 - multi-level logic, converting between ANDs and ORs
- Time behavior
- Hardware description languages

Design example: 2x2-bit multiplier




block diagram
and
truth table

A2	A1	B2	B1	P8	P4	P2	P1
0	0	0	0	0	0	0	0
		0	1	0	0	0	0
		1	0	0	0	0	0
		1	1	0	0	0	0
0	1	0	0	0	0	0	0
		0	1	0	0	0	1
		1	0	0	0	1	0
		1	1	0	0	1	1
1	0	0	0	0	0	0	0
		0	1	0	0	1	0
		1	0	0	1	0	0
		1	1	0	1	1	0
1	1	0	0	0	0	0	0
		0	1	0	0	1	1
		1	0	0	1	1	0
		1	1	1	0	0	1

4-variable K-map
for each of the 4
output functions


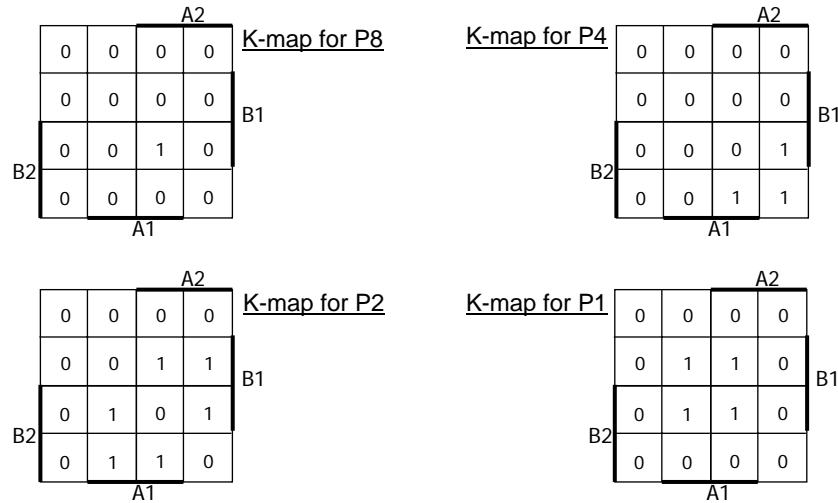
Design example: 2x2-bit multiplier (activity)



Definition of terms for two-level simplification

- **Implicant**
 - single element of ON-set or DC-set or any group of these elements that can be combined to form a subcube
- **Prime implicant**
 - implicant that can't be combined with another to form a larger subcube
- **Essential prime implicant**
 - prime implicant is essential if it alone covers an element of ON-set
 - will participate in ALL possible covers of the ON-set
 - DC-set used to form prime implicants but not to make implicant essential
- **Objective:**
 - grow implicant into prime implicants (minimize literals per term)
 - cover the ON-set with as few prime implicants as possible (minimize number of product terms)


Examples to illustrate terms

  


Algorithm for two-level simplification

- Algorithm: minimum sum-of-products expression from a Karnaugh map
 - Step 1: choose an element of the ON-set
 - Step 2: find "maximal" groupings of 1s and Xs adjacent to that element
 - consider top/bottom row, left/right column, and corner adjacencies
 - this forms prime implicants (number of elements always a power of 2)
 - Repeat Steps 1 and 2 to find all prime implicants
 - Step 3: revisit the 1s in the K-map
 - if covered by single prime implicant, it is essential, and participates in final cover
 - 1s covered by essential prime implicant do not need to be revisited
 - Step 4: if there remain 1s not covered by essential prime implicants
 - select the smallest number of prime implicants that cover the remaining 1s

 
Algorithm for two-level simplification (example)



 
Algorithm for two-level simplification (example)



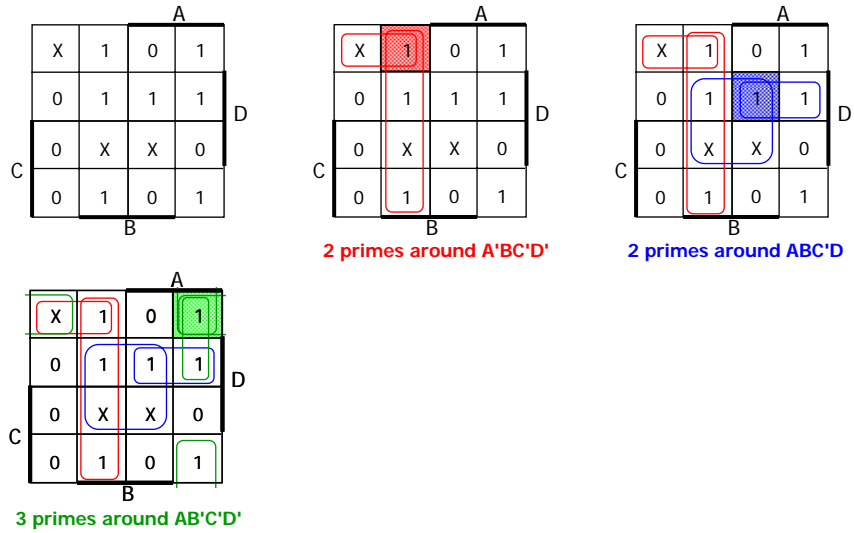
Algorithm for two-level simplification (example)



 Algorithm for two-level simplification (example)



Algorithm for two-level simplification (example)

 


Autumn 2006

CSE370 - III - Working with Combinational Logic

11

Activity

 - List all prime implicants for the following K-map:



- Which are essential prime implicants?
- What is the minimum cover?

Autumn 2006

CSE370 - III - Working with Combinational Logic

12

Activity


- List all prime implicants for the following K-map:




- Which are essential prime implicants? CD' BD AC'D
- What is the minimum cover? CD' BD AC'D

Implementations of two-level logic

 - Sum-of-products
 - AND gates to form product terms (minterms)
 - OR gate to form sum




 - Product-of-sums
 - OR gates to form sum terms (maxterms)
 - AND gates to form product



Why NANDs and NORs

 
- CMOS technology makes it easier to build NANDs and NORs than ANDs and ORs
- MOS transistors have three terminals: drain, gate, and source
 - N-type pass "0" well, P-type pass "1" well



n-channel

open when:
voltage at G is low

 closed when:
 $\text{voltage}(G) > \text{voltage}(S/D) + \epsilon$




p-channel

closed when:
voltage at G is low

open when:
 $\text{voltage}(G) < \text{voltage}(S/D) - \epsilon$

 
A simple MOS transistor network (1-input)



what is the
relationship
between x and y?

X	Z
0 volts	
3 volts	

Two input networks

 

what is the relationship between X, Y and Z1 and Z2?

X	Y	Z1	Z2
0 volts	0 volts		
0 volts	3 volts		
3 volts	0 volts		
3 volts	3 volts		


Two-level logic using NAND and NOR gates

- NAND-NAND and NOR-NOR networks

- de Morgan's law: $(A + B)' = A' \cdot B'$ $(A \cdot B)' = A' + B'$
- written differently: $A + B = (A' \cdot B')'$ $(A \cdot B) = (A' + B')'$


- In other words —

 - OR is the same as NAND with complemented inputs
- AND is the same as NOR with complemented inputs
- NAND is the same as OR with complemented inputs
- NOR is the same as AND with complemented inputs




Two-level logic using NAND gates (cont'd)

 - OR gate with inverted inputs is a NAND gate
 - de Morgan's: $A' + B' = (A \cdot B)'$
- Two-level NAND-NAND network
 - inverted inputs are not counted
 - in a typical circuit, inversion is done once and signal distributed




Two-level logic using NOR gates (cont'd)

 - AND gate with inverted inputs is a NOR gate
 - de Morgan's: $A' \cdot B' = (A + B)'$
- Two-level NOR-NOR network
 - inverted inputs are not counted
 - in a typical circuit, inversion is done once and signal distributed



Conversion between forms (cont'd)

- Example: map AND/OR network to NOR/NOR network

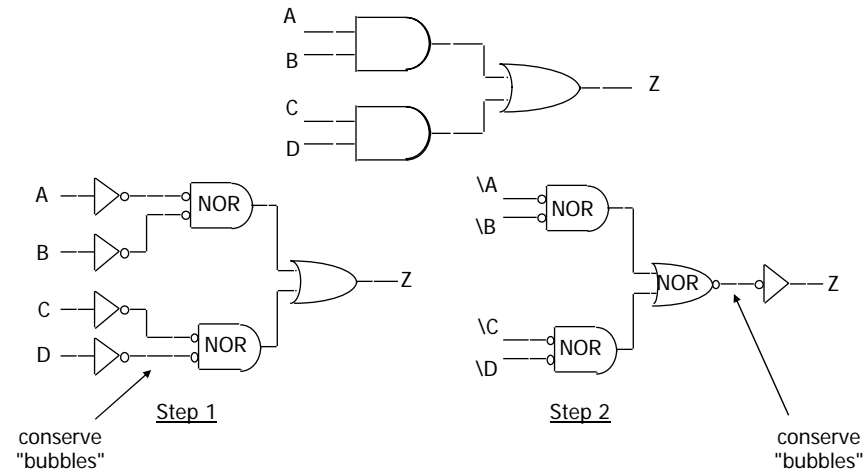


Autumn 2006

CSE370 - III - Working with Combinational Logic

21

Conversion between forms (cont'd)

 - Example: verify equivalence of two forms




$$\begin{aligned}
 Z &= \{ [(A' + B)' + (C' + D)']' \}' \\
 &= \{ (A' + B) \cdot (C' + D) \}' \\
 &= (A' + B)' + (C' + D)' \\
 &= (A \cdot B) + (C \cdot D) \quad \checkmark
 \end{aligned}$$

Autumn 2006

CSE370 - III - Working with Combinational Logic


22

Activity: convert to NAND gates

 


Activity: convert to NAND gates

■ Example

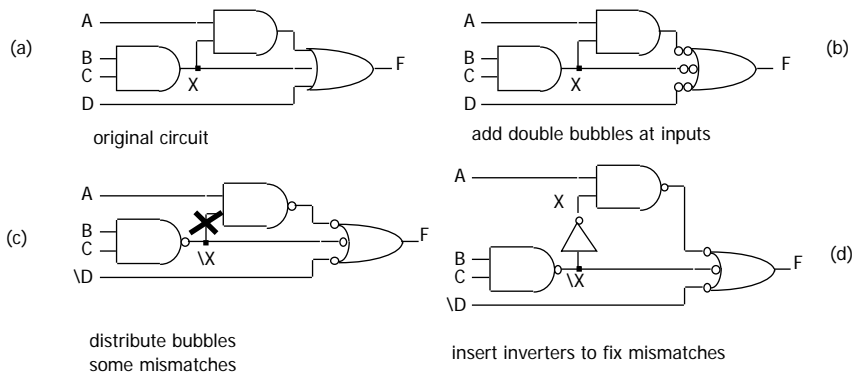


Multi-level logic

- $x = A D F + A E F + B D F + B E F + C D F + C E F + G$
 - reduced sum-of-products form – already simplified
 - 6 x 3-input AND gates + 1 x 7-input OR gate (that may not even exist!)
 - 25 wires (19 literals plus 6 internal wires)
- $x = (A + B + C) (D + E) F + G$
 - factored form – not written as two-level S-o-P
 - 1 x 3-input OR gate, 2 x 2-input OR gates, 1 x 3-input AND gate
 - 10 wires (7 literals plus 3 internal wires)

 


Conversion of multi-level logic to NAND gates

- $F = A (B + C D) + B C'$

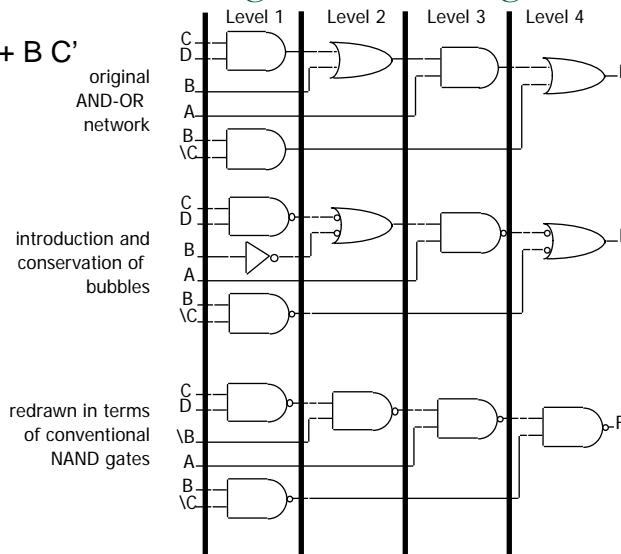

Conversion of multi-level logic to NORs

■ $F = A(B + CD) + BC'$

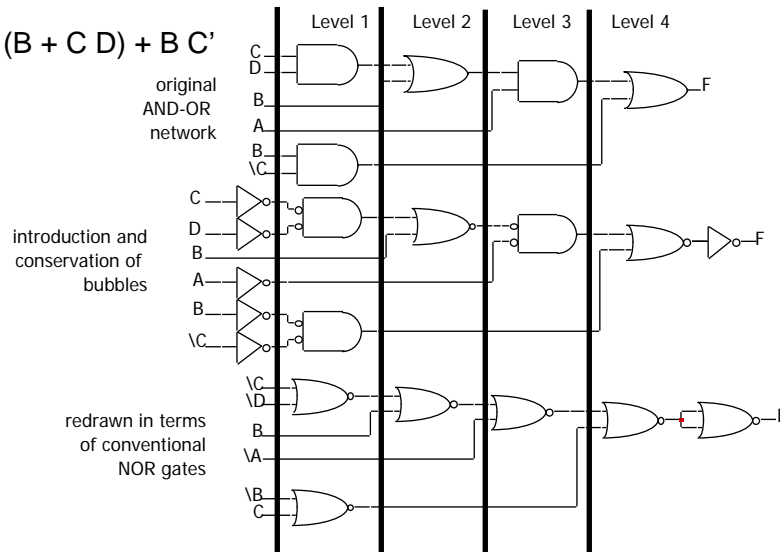

Autumn 2006

CSE370 - III - Working with Combinational Logic

27

Summary for multi-level logic

- Advantages
 - circuits may be smaller
 - gates have smaller fan-in
 - circuits may be faster
- Disadvantages
 - more difficult to design
 - tools for optimization are not as good as for two-level
 - analysis is more complex

Autumn 2006

CSE370 - III - Working with Combinational Logic

28


Time behavior of combinational networks

- Waveforms
 - visualization of values carried on signal wires over time
 - useful in explaining sequences of events (changes in value)
- Simulation tools are used to create these waveforms
 - input to the simulator includes gates and their connections
 - input stimulus, that is, input signal waveforms
- Some terms
 - gate delay — time for change at input to cause change at output
 - min delay – typical/nominal delay – max delay
 - careful designers design for the worst case
 - rise time — time for output to transition from low to high voltage
 - fall time — time for output to transition from high to low voltage
 - pulse width — time that an output stays high or stays low between changes

Momentary changes in outputs


- Can be useful — pulse shaping circuits
- Can be a problem — incorrect circuit operation (glitches/hazards)
- Example: pulse shaping circuit

- $A' \cdot A = 0$
- delays matter

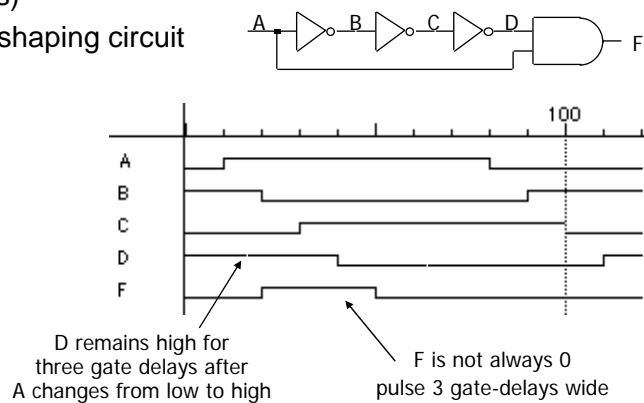

Oscillatory behavior

- Another pulse shaping circuit

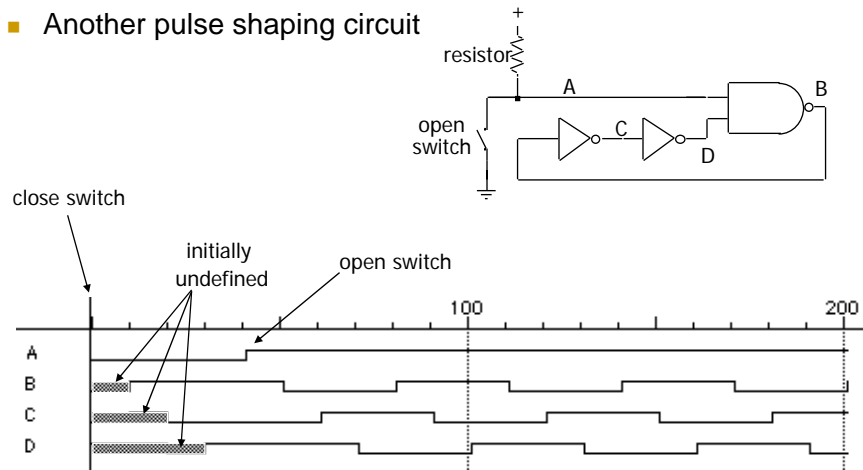

Hardware description languages

- Describe hardware at varying levels of abstraction
- Structural description
 - textual replacement for schematic
 - hierarchical composition of modules from primitives
- Behavioral/functional description
 - describe what module does, not how
 - synthesis generates circuit for module
- Simulation semantics

HDLs

- Abel (circa 1983) - developed by Data-I/O
 - targeted to programmable logic devices
 - not good for much more than state machines
- ISP (circa 1977) - research project at CMU
 - simulation, but no synthesis
- Verilog (circa 1985) - developed by Gateway (absorbed by Cadence)
 - similar to Pascal and C
 - delays is only interaction with simulator
 - fairly efficient and easy to write
 - IEEE standard
- VHDL (circa 1987) - DoD sponsored standard
 - similar to Ada (emphasis on re-use and maintainability)
 - simulation semantics visible
 - very general but verbose
 - IEEE standard

Verilog

- Supports structural and behavioral descriptions
- Structural
 - explicit structure of the circuit
 - e.g., each logic gate instantiated and connected to others
- Behavioral
 - program describes input/output behavior of circuit
 - many structural implementations could have same behavior
 - e.g., different implementation of one Boolean function
- We'll mostly be using behavioral Verilog in Aldec ActiveHDL
 - rely on schematic when we want structural descriptions

Structural model

```
module xor_gate (out, a, b);
  input      a, b;
  output     out;
  wire      abar, bbar, t1, t2;

  inverter invA (abar, a);
  inverter invB (bbar, b);
  and_gate and1 (t1, a, bbar);
  and_gate and2 (t2, b, abar);
  or_gate  or1 (out, t1, t2);

endmodule
```

Simple behavioral model

- Continuous assignment

```
module xor_gate (out, a, b);
  input      a, b;
  output     out;
  reg       out;

  assign #6 out = a ^ b;

endmodule
```

simulation register -
keeps track of
value of signal

delay from input change
to output change

Simple behavioral model

- always block

```
module xor_gate (out, a, b);  
    input        a, b;  
    output       out;  
    reg          out;  
  
    always @(a or b) begin  
        #6 out = a ^ b;  
    end  
  
endmodule
```

specifies when block is executed
ie. triggered by which signals

Driving a simulation through a “testbench”

```
module testbench (x, y);  
    output       x, y;  
    reg [1:0]    cnt;  
  
    initial begin  
        cnt = 0;  
        repeat (4) begin  
            #10 cnt = cnt + 1;  
            $display ("@ time=%d, x=%b, y=%b, cnt=%b",  
                $time, x, y, cnt); end  
            #10 $finish;  
        end  
  
        assign x = cnt[1];  
        assign y = cnt[0];  
    endmodule
```

2-bit vector


initial block executed
only once at start
of simulation

print to a console

directive to stop
simulation

Complete simulation

 - Instantiate stimulus component and device to test in a schematic



Comparator example

```
module Compare1 (Equal, Alarger, Blarger, A, B);
  input  A, B;
  output Equal, Alarger, Blarger;

  assign #5 Equal = (A & B) | (~A & ~B);
  assign #3 Alarger = (A & ~B);
  assign #3 Blarger = (~A & B);
endmodule
```

Hardware description languages vs. programming languages

- Program structure
 - instantiation of multiple components of the same type
 - specify interconnections between modules via schematic
 - hierarchy of modules (only leaves can be HDL in Aldec ActiveHDL)
- Assignment
 - continuous assignment (logic always computes)
 - propagation delay (computation takes time)
 - timing of signals is important (when does computation have its effect)
- Data structures
 - size explicitly spelled out - no dynamic structures
 - no pointers
- Parallelism
 - hardware is naturally parallel (must support multiple threads)
 - assignments can occur in parallel (not just sequentially)

Hardware description languages and combinational logic

- Modules - specification of inputs, outputs, bidirectional, and internal signals
- Continuous assignment - a gate's output is a function of its inputs at all times (doesn't need to wait to be "called")
- Propagation delay- concept of time and delay in input affecting gate output
- Composition - connecting modules together with wires
- Hierarchy - modules encapsulate functional blocks

Working with combinational logic summary

- Design problems
 - filling in truth tables
 - incompletely specified functions
 - simplifying two-level logic
- Realizing two-level logic
 - NAND and NOR networks
 - networks of Boolean functions and their time behavior
- Time behavior
- Hardware description languages
- Later
 - combinational logic technologies
 - more design case studies