
 


Test Slide

 

CSE 370 Spring 2006 Introduction to Digital Design Lecture 5: Canonical Forms



Last Lecture

- Logic Gates
- Different Implementations
- Bubbles

Today

- Canonical Forms
- Sum of Products
- Product of Sums
- Boolean Cubes

Administrivia

- Homework 2 was modified Monday evening. See online for the modification. The two problems that were dropped will appear on the next homework.

Puzzle


Suppose a light has to be lit by switching on simultaneously n switches. We may push any one of the n buttons at any time but we don't know if they are on or off. What is the smallest number of steps necessary to guarantee that we turn the light on starting from any initial configuration of the switches?

Canonical Forms

- Unique forms for Boolean functions
- Unique algebraic signatures:
 - Generically not the simplest
 - Can be simplified
- Two canonical forms
 - Sum of products
 - Product of sums

Sum of Products Canonical Form

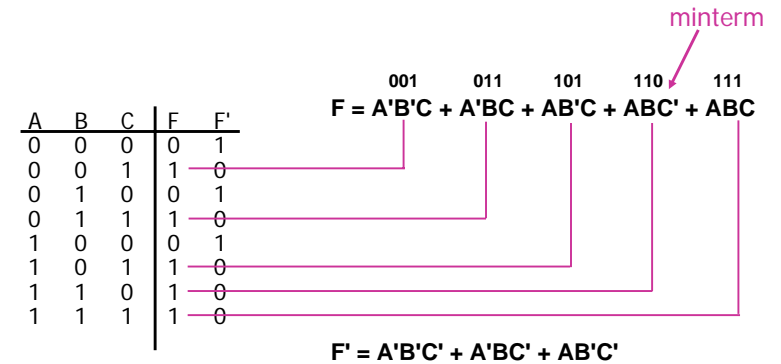- Also called disjunctive normal form (DNF)
 - Commonly called a **minterm expansion**



Minterms

- Variables appears exactly once in each minterm
 - In true or inverted form (but not both)

A	B	C	minterms
0	0	0	A'B'C' m0
0	0	1	A'B'C m1
0	1	0	A'BC' m2
0	1	1	A'BC m3
1	0	0	AB'C' m4
1	0	1	AB'C m5
1	1	0	ABC' m6
1	1	1	ABC m7


short-hand notation

F in canonical form:
 $F(A,B,C) = \Sigma m(1,3,5,6,7)$
 $= m1 + m3 + m5 + m6 + m7$
 $= A'B'C + A'BC + AB'C + ABC' + ABC$

canonical form \rightarrow minimal form
 $F(A,B,C) = A'B'C + A'BC + AB'C + ABC + ABC'$
 $= (A'B' + A'B + AB' + AB)C + ABC'$
 $= ((A' + A)(B' + B))C + ABC'$
 $= ABC' + C$
 $= AB + C$

Product of Sums Canonical Form

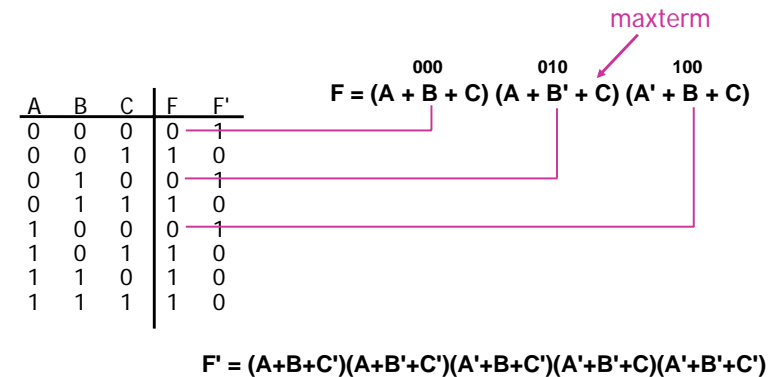- Also called conjunctive normal form (CNF)
 - Commonly called a **maxterm expansion**



Maxterms

- Variables appears exactly once in each maxterm
 - In true or inverted form (but not both)

A	B	C	maxterms	
0	0	0	A+B+C	M0
0	0	1	A+B+C'	M1
0	1	0	A+B'+C	M2
0	1	1	A+B'+C'	M3
1	0	0	A'+B+C	M4
1	0	1	A'+B+C'	M5
1	1	0	A'+B'+C	M6
1	1	1	A'+B'+C'	M7

short-hand notation

F in canonical form:

$$F(A,B,C) = \prod M(0,2,4)$$

$$= M0 \cdot M2 \cdot M4$$

$$= (A+B+C)(A+B'+C)(A'+B+C)$$


canonical form → minimal form

$$F(A,B,C) = (A+B+C)(A+B'+C)(A'+B+C)$$

$$= (A+B+C)(A+B'+C) \cdot (A+B+C)(A'+B+C)$$

$$= (A+C)(B+C)$$

Canonical Decompositions of $F=AB+C$

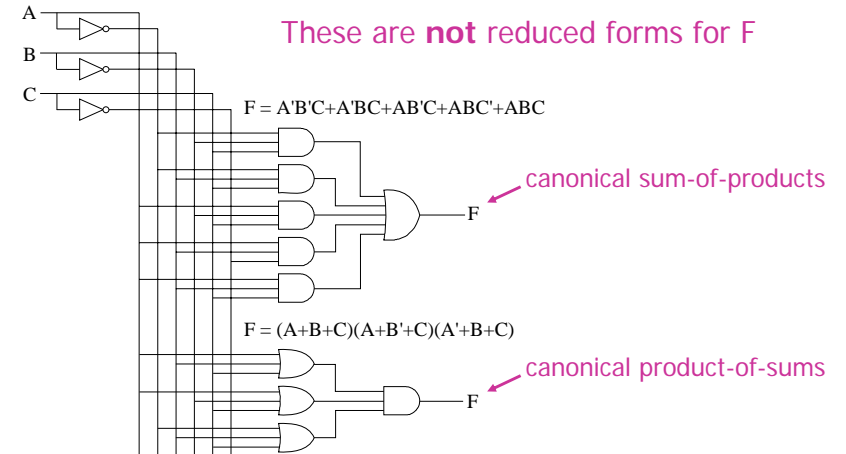

Exercise

Express the following binary function in canonical sum of products and product of sum form:

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


POS, SOP, and DeMorgan

- Sum-of-products
 - $F' = A'B'C' + A'BC' + AB'C'$
- Apply de Morgan's to get POS
 - $(F)' = (A'B'C' + A'BC' + AB'C')$
 - $F = (A+B+C)(A+B'+C)(A'+B+C)$
- Product-of-sums
 - $F' = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C)$
- Apply de Morgan's to get SOP
 - $(F)' = ((A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C))'$
 - $F = A'B'C + A'BC + AB'C + ABC' + ABC$

Conversions Between Canonical Forms


- Minterm to maxterm
 - Use maxterms that aren't in minterm expansion
 - $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm
 - Use minterms that aren't in maxterm expansion
 - $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- Minterm of F to minterm of F'
 - Use minterms that don't appear
 - $F(A,B,C) = \sum m(1,3,5,6,7) \quad F'(A,B,C) = \sum m(0,2,4)$
- Maxterm of F to maxterm of F'
 - Use maxterms that don't appear
 - $F(A,B,C) = \prod M(0,2,4) \quad F'(A,B,C) = \prod M(1,3,5,6,7)$

Alternative Implementations of $F=AB+C$

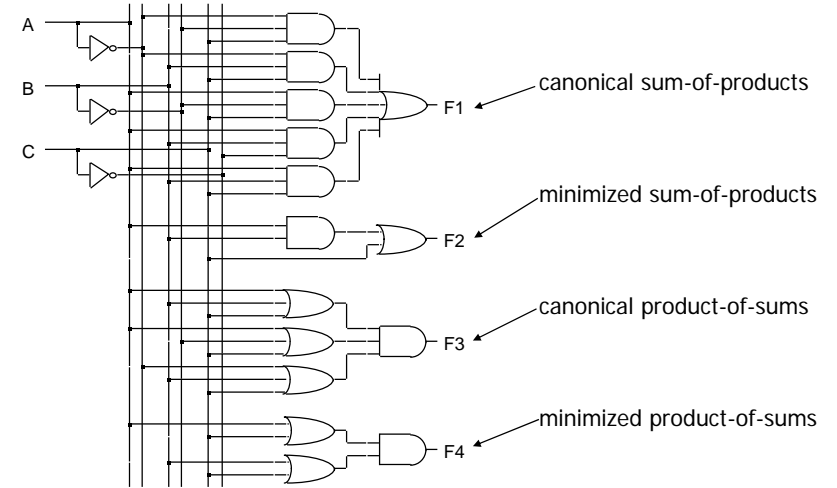

Waveforms of Four Alternatives

 - Waveforms are essentially identical
 - except for timing hazards (glitches)
 - delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)



Incompletely Specified Functions

- Example: binary coded decimal increment by 1
 - BCD digits encode the decimal digits 0 – 9 in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Annotations:

- off-set of W (rows 1-4)
- on-set of W (rows 5-8)
- don't care (DC) set of W (rows 9-16)
- these inputs patterns should never be encountered in practice – "don't care" about associated output values, can be exploited in minimization

Incompletely Specified Functions: Notation

- Don't cares and canonical forms
 - so far, only represented on-set
 - also represent don't-care-set
 - need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
 - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - $Z = \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
 - $Z = \Pi [M(1,3,5,7,9) \cdot D(10,11,12,13,14,15)]$


Simplification of Two Level Logic

- Find a minimal sum of products or product of sums realization
 - exploit don't care information in the process
- Algebraic simplification
 - not an algorithmic/systematic procedure
 - how do you know when the minimum realization has been found?
- Computer-aided design tools
 - precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
 - to understand automatic tools and their strengths and weaknesses
 - ability to check results (on small examples)

Uniting Theorem


- Key tool to simplification: $A(B' + B) = A$
- Essence of simplification of two-level logic
 - find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$

 

Boolean Cubes

 
- Visual technique for identifying when the uniting theorem can be applied
- n input variables = n-dimensional "cube"



Truth Tables To Boolean Cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- Example:

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

 


ON-set = solid nodes
 OFF-set = empty nodes
 DC-set = 'x'd nodes

Three Variable Example

- Binary full-adder carry-out logic


A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

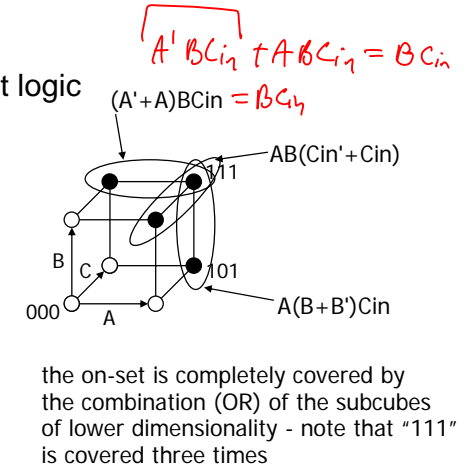

$$\text{Cout} = \text{BCin} + \text{AB} + \text{ACin}$$

Three Variable Example

- Sub-cubes of higher dimension than 2

 

$$F(A,B,C) = \Sigma m(4,5,6,7)$$

on-set forms a square
 i.e., a cube of dimension 2

represents an expression in one variable
 i.e., 3 dimensions - 2 dimensions

A is asserted (true) and unchanged
 B and C vary

This subcube represents the literal A


m-dimensional cubes in a n-dimensional Boolean space

- In a 3-cube (three variables):
 - a 0-cube, i.e., a single node, yields a term in 3 literals
 - a 1-cube, i.e., a line of two nodes, yields a term in 2 literals
 - a 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
 - a 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
 - an m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals

Gray Codes


- A listing of the vertices of the Boolean cube in which we only move along the edges.

Example:

 

0	00
1	01
2	11
3	10


Example:

 

0	000
1	001
2	011
3	010
4	110
5	111
6	101
7	100

Gray Codes

- Binary reflected Gray codes

 

Gray code on n bits \Rightarrow Gray code on n+1 bits

Append 0 to Gray code of n bits, followed by appending 1 to the reverse-ordered Gray code of n bits

Gray Code Uses

- Use Gray codes to help visualize higher dimensional Boolean cubes.

- Avoid spurious intermediate states

We want $001 \Rightarrow 110$

We get $001 \Rightarrow 000 \Rightarrow 010 \Rightarrow 110$

Gray codes help avoid synchronizing errors

- Example: measuring angles



Puzzle

Suppose a light has to be lit by switching on simultaneously n switches. We may push any one of the n buttons at any time but we don't know if they are on or off. What is the smallest number of steps necessary to guarantee that we turn the light on starting from any initial configuration of the switches?