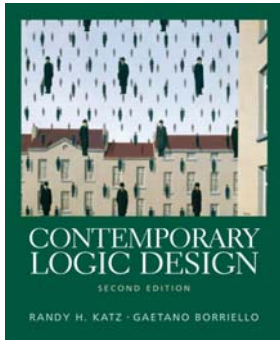


CSE 370 Spring 2006

Introduction to Digital Design

Lecture 7: Karnaugh and Beyond



Last Lecture

- Quiz
- Karnaugh Maps
- K-maps & Minimization

Today

- Design Examples & K-maps
- Minimization Algorithm

Administrivia

- Pick up Quiz 1
Average: 9.2/10, Median 10/10
- Lab 3 this week (Verilog!)
- Homework 3 on the web

Quiz Review

Problem 1: -5_{10} as a four bit expression using

a) sign and magnitude

$$-5 = 1101_2$$

↑
neg

b) ones-complement

$$-5 = 1010_2$$

c) twos-complement

$$\begin{array}{r} 1010_2 \\ + 0001 \\ \hline 1011_2 \end{array}$$

ones comp + 1

$$5 = 4 + 1 = 101_2$$

$$\downarrow$$

$$010_2$$

Quiz Review

$$f = AB + B'C + AC'$$

a) Truth table

	A	B	C	AB	$\overline{B}C$	$A\overline{C}$	F
0	0	0	0	0	0	0	0
1	0	0	1	0	1	0	1
2	0	1	0	0	0	0	0
3	0	1	1	0	0	0	0
4	1	0	0	0	0	1	1
5	1	0	1	0	0	0	1
6	1	1	0	1	0	0	1
7	1	1	1	1	0	0	1

b) Sum of products

$$f = \overline{A}\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C + A\overline{B}\overline{C} + ABC$$

$$= \sum m(1, 4, 5, 6, 7)$$

↑
minterms

Quiz Review


$$f = AB + B'C + AC'$$

b) Product of Sums

$$F = (A+B+C)(A+\bar{B}+C)(A+\bar{B}+\bar{C})$$


$$f = \prod M(0, 2, 3)$$

c) Circuit using AND, OR, NOT

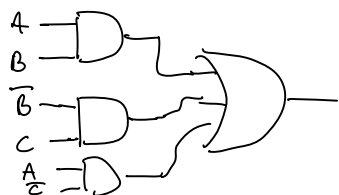

Karnaugh Maps

■ Last Time 4 literal K-map

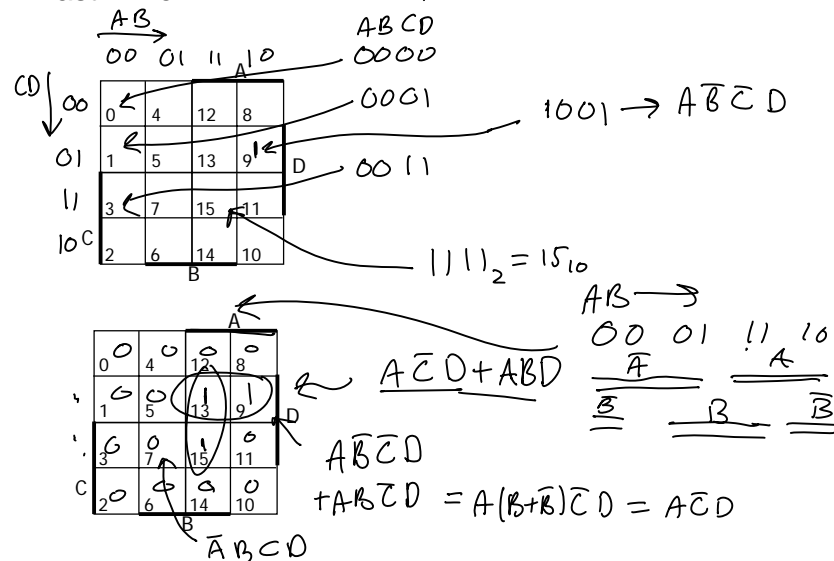


Karnaugh Map Don't Cares

$x = \text{do not care}$

■ $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$

■ without don't cares just covered 1's $X = 0$ s

■ $f = A'D + B'C'D$

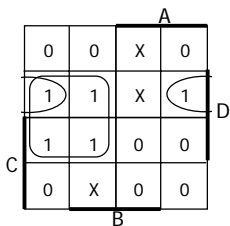

Karnaugh Map Don't Cares


■ $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$

■ $f = A'D + B'C'D$

■ $f = A'D + C'D$

without don't cares

with don't cares

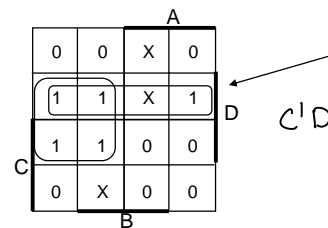


by using don't care as a "1" a 2-cube can be formed rather than a 1-cube to cover this node

don't cares can be treated as 1s or 0s

depending on which is more advantageous

Design example: two-bit comparator

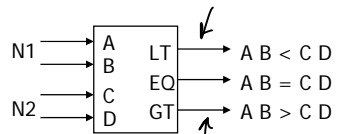


block diagram and truth table

A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
		0	1	1	0	0
		1	0	1	0	0
		1	1	1	0	0
0	1	0	0	0	0	1
		0	1	0	1	0
		1	0	1	0	0
		1	1	1	0	0
1	0	0	0	0	0	1
		0	1	0	0	1
		1	0	0	1	0
		1	1	1	0	0
1	1	0	0	0	0	1
		0	1	0	0	1
		1	0	0	0	1
		1	1	0	1	0

we'll need a 4-variable Karnaugh map for each of the 3 output functions

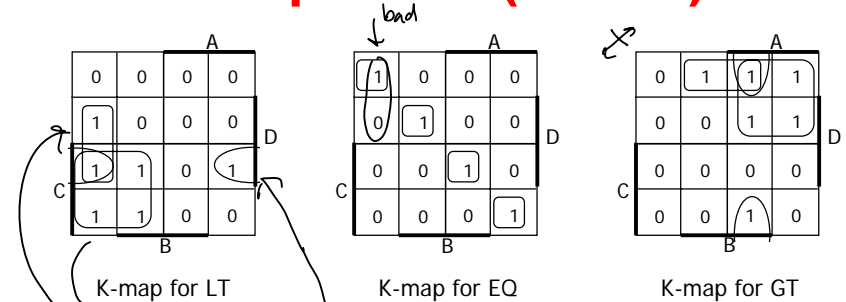Design example: two-bit comparator (cont'd)




$$LT = A'B'D + A'C + B'CD$$

$$EQ = A'B'C'D' + A'B'CD + ABCD + AB'CD' = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$$

$$GT = BC'D' + AC' + ABD'$$

LT and GT are similar (flip A/C and B/D)

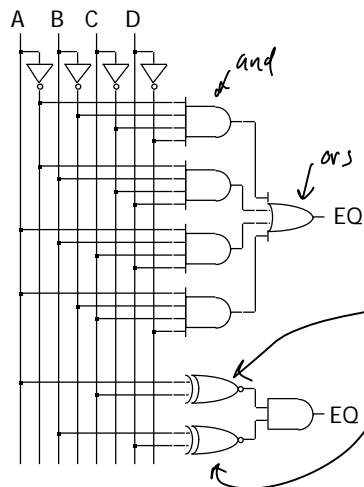
Design example: two-bit comparator (cont'd)



two alternative implementations of EQ with and without XOR

XNOR is implemented with at least 3 simple gates

Design example: 2x2-bit multiplier

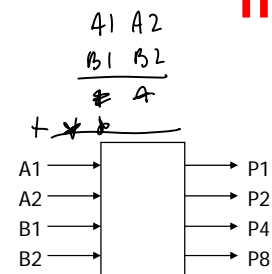


block diagram and truth table


A2	A1	B2	B1	P8	P4	P2	P1
0	0	0	0	0	0	0	0
		0	1	0	0	0	0
		1	0	0	0	0	0
		1	1	0	0	0	0
0	1	0	0	0	0	0	0
		0	1	0	0	0	1
		1	0	0	0	1	0
		1	1	0	0	1	1
1	0	0	0	0	0	0	0
		0	1	0	0	1	0
		1	0	0	1	0	0
		1	1	0	1	1	0
1	1	0	0	0	0	0	0
		0	1	0	0	1	1
		1	0	0	1	1	0
		1	1	1	0	0	1

4-variable K-map for each of the 4 output functions

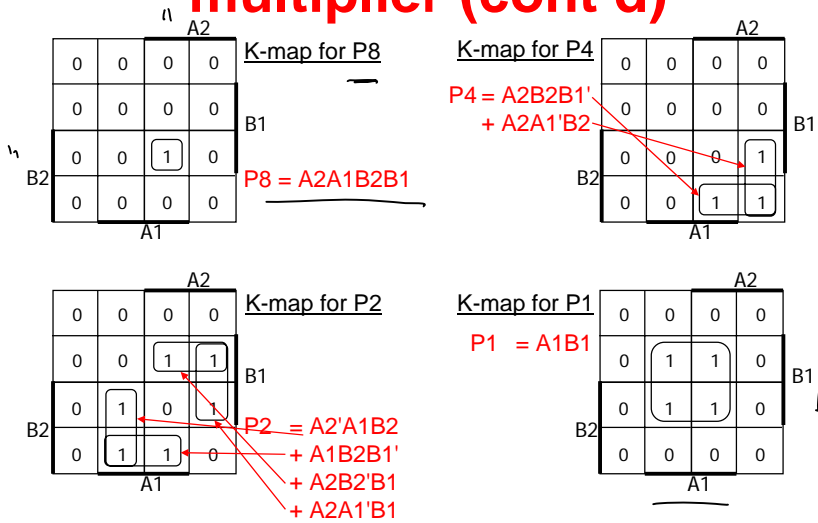
Design example: 2x2-bit multiplier (cont'd)



Design example: BCD increment by 1

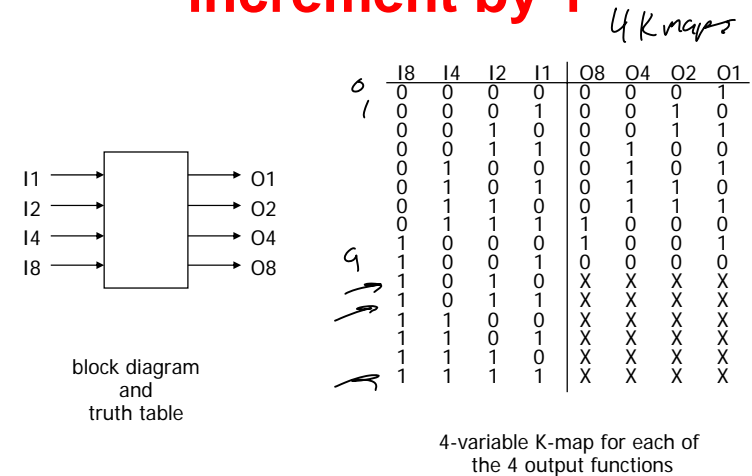

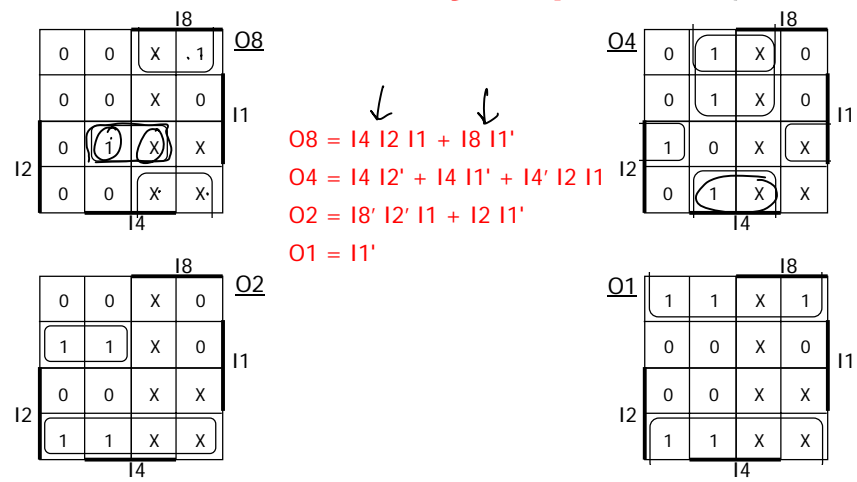
Design example: BCD increment by 1 (cont'd)



Definition of terms for two-level simplification

- Implicant
 - single element of ON-set or DC-set or any group of these elements that can be combined to form a subcube
- Prime implicant
 - implicant that can't be combined with another to form a larger subcube
- Essential prime implicant
 - prime implicant is essential if it alone covers an element of ON-set
 - will participate in ALL possible covers of the ON-set
 - DC-set used to form prime implicants but not to make implicant essential
- Objective:
 - grow implicant into prime implicants (minimize literals per term)
 - cover the ON-set with as few prime implicants as possible (minimize number of product terms)


Examples to illustrate terms

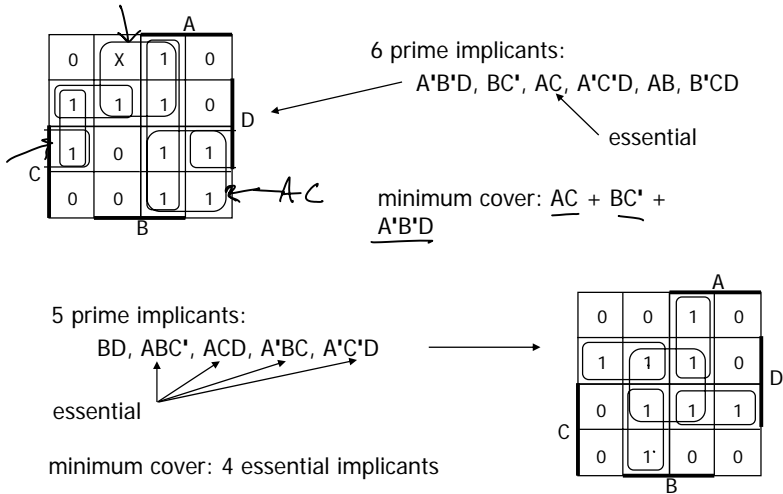

Algorithm for two-level simplification


- Algorithm: minimum sum-of-products expression from a Karnaugh map
- Step 1: choose an element of the ON-set
- Step 2: find "maximal" groupings of 1s and Xs adjacent to that element
 - consider top/bottom row, left/right column, and corner adjacencies
 - this forms prime implicants (number of elements always a power of 2)
- Repeat Steps 1 and 2 to find all prime implicants
- Step 3: revisit the 1s in the K-map
 - if covered by single prime implicant, it is essential, and participates in final cover
 - 1s covered by essential prime implicant do not need to be revisited
- Step 4: if there remain 1s not covered by essential prime implicants
 - select the smallest number of prime implicants that cover the remaining 1s

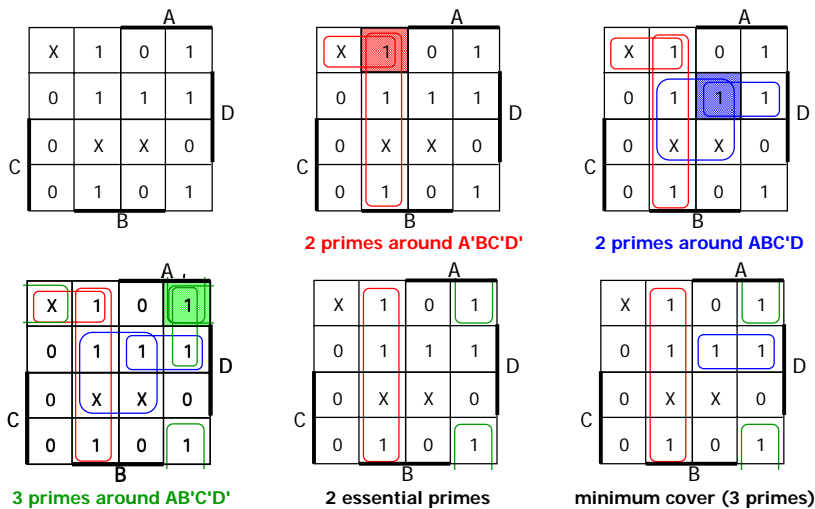Algorithm for two-level simplification (example)



Activity

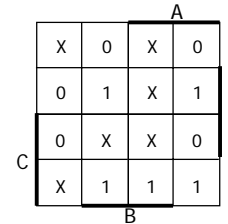- List all prime implicants for the following K-map:



- Which are essential prime implicants?
- What is the minimum cover?

Loose end: POS minimization using k-maps

- Using k-maps for POS minimization
 - Encircle the zeros in the map
 - Interpret indices complementary to SOP form

		AB		A	
		00	01	11	10
CD	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1
		B		D	

$$F = (B'+C+D)(B+C+D')(A'+B'+C)$$

Check using de Morgan's on SOP

$$F' = BC'D' + B'C'D + ABC'$$


$$(F')' = (BC'D' + B'C'D + ABC')'$$

$$(F')' = (BC'D')' + (B'C'D)' + (ABC')'$$

$$F = (B'+C+D)(B+C+D')(A'+B'+C)$$

Implementations of two-level logic

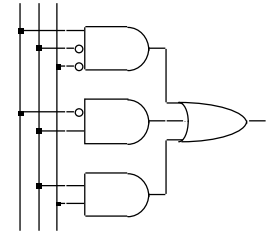- Sum-of-products
 - AND gates to form product terms (minterms)
 - OR gate to form sum



- Product-of-sums
 - OR gates to form sum terms (maxterms)
 - AND gates to form product

