 


# CSE 370 Spring 2006 Introduction to Digital Design

## Lecture 13: Introduction to Sequential Logic



### Last Lecture

- Adders


### Today

- Sequential Logic

## Administrivia

- Quiz #2

## Sequential versus combinational

 

Apply fixed inputs A, B  
Wait for clock edge  
Observe C  
Wait for another clock edge  
Observe C again


Combinational: C will stay the same  
Sequential: C may be different

## Sequential logic


- Two types
  - Synchronous = clocked
  - Asynchronous = self-timed
- Has state
  - State = memory
- Employs feedback
- Assumes steady-state signals
  - Signals are valid after they have settled
  - State elements hold their settled output values
 
# Sequential versus combinational (again)

- Combinational systems are **memoryless**
  - Outputs depend only on the present inputs




 - Sequential systems have **memory**
  - Outputs depend on the present **and** the previous inputs



 
# Synchronous sequential systems

- **Memory** holds a system's **state**
  - Changes in state occur at specific times
  - A periodic signal times or **clocks** the state changes
  - The clock period is the time between state changes



 
State changes occur at rising edge of clock




duty cycle = pulsewidth/period (here it is 50%)
 
# Steady-state abstraction

- Outputs retain their **settled values**
  - The clock period must be long enough for all voltages to settle to a **steady state** before the next state change



Clock hides transient behavior

 


# Example: A sequential system

- Door combination lock
  - Enter 3 numbers in sequence and the door opens
  - If there is an error the lock must be reset
  - After the door opens the lock must be reset
  - Inputs: Sequence of numbers, reset
  - Outputs: Door open/close
  - Memory: Must remember the combination

 
# Understand the problem

- Consider I/O and unknowns
  - How many bits per input?
  - How many inputs in sequence?
  - How do we know a new input is entered?
  - How do we represent the system states?


 
# Implement using sequential logic


- Behavior
  - Clock tells us when to look at inputs
    - After inputs have settled
  - Sequential: Enter sequence of numbers
  - Sequential: Remember if error occurred
- Need a finite-state diagram
  - Assume synchronous inputs
  - State sequence
    - Enter 3 numbers serially
    - Remember if error occurred
  - All states have outputs
    - Lock open or closed


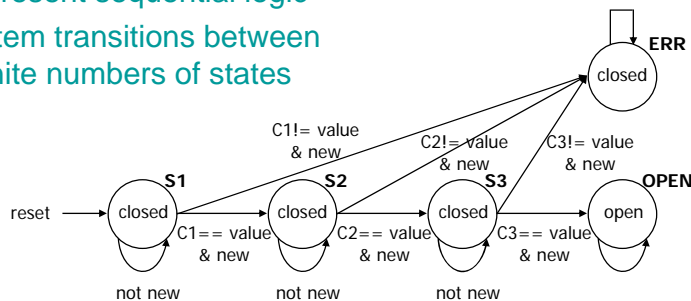
# Finite-state diagram


- States: 5
  - Each state has outputs
- Outputs: open/closed
- Inputs: reset, new, results of comparisons
  - Assume synchronous inputs

We use state diagrams to represent sequential logic  
 System transitions between finite numbers of states



 
# Separate data path and control

- Data path
  - Stores combination
  - Compares inputs with combination
- Control
  - Finite state-machine controller
  - Control for data path
  - State changes clocked


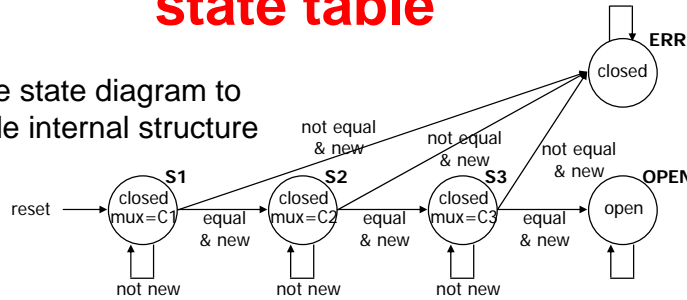
# Refine diagram; generate state table

- Refine state diagram to include internal structure



- Generate state table

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open
...						

# Encode state table

- State can be: S1, S2, S3, OPEN, or ERR
  - Need at least 3 bits to encode: 000, 001, 010, 011, 100
  - Can use 5 bits: 00001, 00010, 00100, 01000, 10000
  - Choose 4 bits: 0001, 0010, 0100, 1000, 0000
- Output to mux can be: C1, C2, or C3
  - Need 2 or 3 bits to encode
  - Choose 3 bits: 001, 010, 100
- Output open/closed can be: Open or closed
  - Need 1 or 2 bits to encode
  - Choose 1 bit: 1, 0


# Encode state table (con't)

- Good encoding choice!
  - Mux control is identical to last 3 state bits
  - Open/closed is identical to first state bit
  - Output encoding  $\Rightarrow$  the outputs and state bits are the same

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...						
0	1	1	0100	1000	-	1
...						


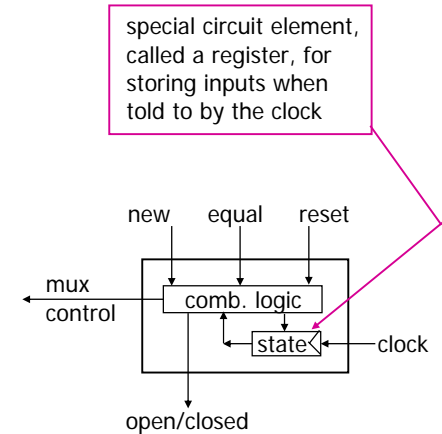
# Implementing the controller

- We will learn how to design the controller given the encoded state-transition table



  
# Designing the datapath

- Four 3:1 multiplexers
  - 2-input ANDs and 3-input OR
- Four single-bit comparators
  - 2-input XNORs
- 4-input AND



 
# Where did we use memory?

- **Memory:** Stored combination, state (errors or successes in past inputs)



 
# Where did we use feedback?

- **Feedback:** Comparator output ("equal" signal)


 
# Where did we use clock?

- **Clock** synchronizes the inputs
  - Accept inputs when **clock** goes high
- Controller is clocked
  - Mux-control and open/closed signals change on the **clock** edge



## Then next 5 weeks...

- We learn the details
  - Latches, flip-flops, registers
  - Shift registers, counters
  - State machines
  - Timing and timing diagrams
  - Synchronous and asynchronous inputs
    - Metastability
  - Clock skew
  - Moore and Mealy machines
  - One-hot encoding
  - More...