 


CSE 370 Spring 2006

Introduction to Digital Design

Lecture 17: Introduction to Finite State Machines



Last Lecture

- Clock Skew
- Asynchronous Inputs
- Registers

Today

- Finite State Machines

Date	Activity
5/5	Lab 6: Clock Skew, Asynchronous Inputs, Registers
5/6	Reading: Finish Chapter 6, pp. 307-326
5/7	Lab 7: More Finite State Machines
5/8	Reading: Finish Chapter 7, pp. 355-367
5/9	Lab 8: Finite State Machine Examples
5/10	Lab 9: State Encoding
5/11	Lab 9: No Class: Holiday!
5/12	Lab 9: Field Programmable Gate Arrays
5/13	Final Exam 8:30-10:20 a.m.

Administrivia


- Homework 6 due Friday

Finite State Machines

- Sequential circuits
 - primitive sequential elements
 - combinational logic
- Models for representing sequential circuits
 - finite-state machines (Moore and Mealy)
- Basic sequential circuits revisited
 - shift registers
 - counters
- Design procedure
 - state diagrams
 - state transition table
 - next state functions
- Hardware description languages


Abstraction of state elements

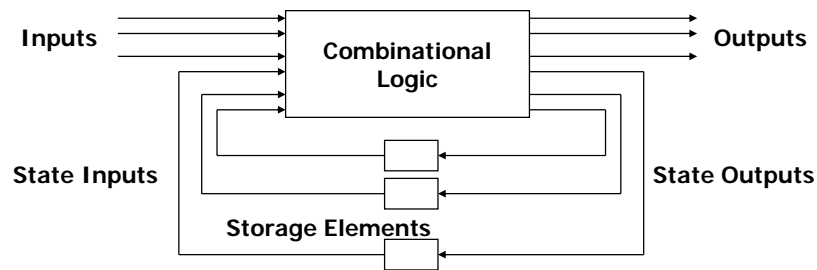- Divide circuit into combinational logic and state
- Localize the feedback loops and make it easy to break cycles
- Implementation of storage elements leads to various forms of sequential logic




Forms of sequential logic

 - Asynchronous sequential logic – state changes occur whenever state inputs change (elements may be simple wires or delay elements)
- Synchronous sequential logic – state changes occur in lock step across all storage elements (using a periodic waveform - the clock)




Finite state machine representations

 - States: determined by possible values in sequential storage elements
- Transitions: change of state
- Clock: controls when state can change by controlling storage elements
- Sequential logic
 - sequences through a series of states
 - based on sequence of values on input signals
 - clock period defines elements of sequence



 Example finite state machine diagram


- Combination lock from earlier
 - 5 states
 - 5 self-transitions
 - 6 other transitions between states
 - 1 reset transition (from all states) to state S1



Can any sequential system be represented with a state diagram?

Shift register

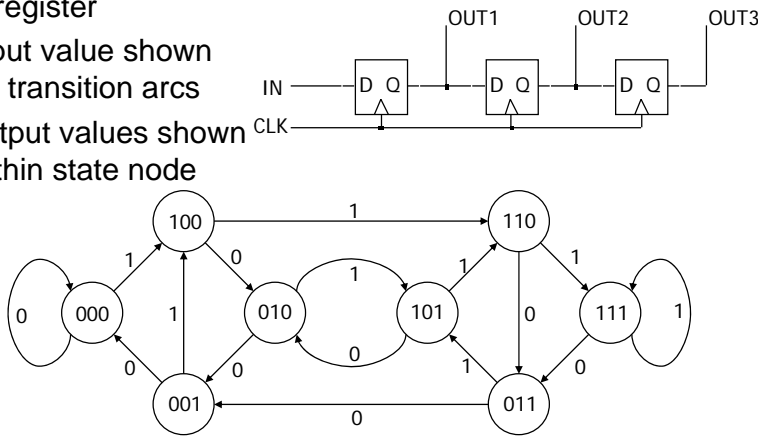
- input value shown on transition arcs
- output values shown within state node



Counters are simple finite state machines

Counters

 
- proceed through well-defined sequence of states in response to enable
- Many types of counters: binary, BCD, Gray-code
 - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
 - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...



How do we turn a state diagram into logic?

Counter

 - 3 flip-flops to hold state
- logic to compute next state
- clock signal controls when flip-flop memory can change
 - wait long enough for combinational logic to compute new value
 - don't wait too long as that is low performance




FSM design procedure

- Start with counters
 - simple because output is just state
 - simple because no choice of next state based on input
- State diagram to state transition table
 - tabular form of state diagram
 - like a truth-table
- State encoding
 - decide on representation of states
 - for counters it is simple: just its value
- Implementation
 - flip-flop for each state bit
 - combinational logic based on encoding

FSM design procedure: state diagram to encoded state transition table

 - Tabular form of state diagram
- Like a truth-table (specify output for all input combinations)
- Encoding of states: easy for counters – just use value



	current state	next state
0	000	001
1	001	010
2	010	011
3	011	100
4	100	101
5	101	110
6	110	111
7	111	000


Implementation

- D flip-flop for each state bit
- Combinational logic based on encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Verilog notation to show function represents an input to D-FF

 
$N1 \leq C1'$
 $N2 \leq C1C2' + C1'C2$
 $\leq C1 \text{ xor } C2$
 $N3 \leq C1C2C3' + C1'C3 + C2'C3$
 $\leq (C1C2)C3' + (C1' + C2')C3$
 $\leq (C1C2) \text{ xor } C3$




Back to the shift register

- Input determines next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 


$N1 \leq In$
 $N2 \leq C1$
 $N3 \leq C2$

 

More complex counter example

 - Complex counter
 - repeats 5 states in sequence
 - not a binary number representation
- Step 1: derive the state transition diagram
 - count sequence: 000, 010, 011, 101, 110
- Step 2: derive the state transition table from the state transition diagram




Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	-	-	-
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	-	-	-

note the don't care conditions that arise from the unused state codes

More complex counter example (cont'd)

Step 3: K-maps for next state functions

 


$$C+ \leq A$$

$$B+ \leq B' + A'C'$$


$$A+ \leq BC'$$

Self-starting counters (cont'd)

 Re-deriving state transition table from don't care assignment



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 


Self-starting counters

Start-up states

- at power-up, counter may be in an unused or invalid state
- designer must guarantee that it (eventually) enters a valid state

Self-starting solution

 - design counter so that invalid states eventually transition to a valid state
- may limit exploitation of don't cares



Activity


2-bit up-down counter (2 inputs)

- direction: D = 0 for up, D = 1 for down
- count: C = 0 for hold, C = 1 for count

Activity (cont'd)

Counter/shift-register model

 - Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - next state
 - function of current state and inputs
 - outputs
 - values of flip-flops



General state machine model

- Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - next state
 - function of current state and inputs
 - outputs
 - function of current state and inputs (Mealy machine)
 - function of current state only (Moore machine)

