 


CSE 370 Spring 2006

Introduction to Digital Design

Lecture 19: More Moore and Mealy Machines



Last Lecture

- Moore and Mealy Machines

Today

- Moore and Mealy Machines

Administrivia


- HW 7 Out
- Lab 7 this week
- Quiz 3 graded, pick up (Average 8.74, Median 9.9)

Quiz Review

1. In this problem we want to design a three bit Grey code counter. This counter will cycle through the following states
000,001,011,010,110,111,101,100,000,etc.
in the order listed above. Further the counter should provide a reset input (call it R) which if it is set will return the counter to the state 000.
 - a) Draw a state transition diagram for this counter. Each state should be labeled by the three bits listed above. You should label the transitions between these states with arrows labeled by the value R takes.
 - b) Create and fill out a state transition table for this counter. It should have four inputs and three outputs.


Quiz Review

 - c) Draw a circuit which implements the counter and changes state at the positive edge of the clock. Your circuit should have as input R and as output the bits of the counter, S1, S2, and S3. You are allowed to use any fan in AND and OR gates, inverters as well as




Comparison of Mealy and Moore machines (cont'd)


■ Moore

 

■ Mealy

 

■ Synchronous Mealy

 

FSM design


■ FSM-design procedure

1. State diagram and state-transition table
2. State minimization
3. State assignment (or state encoding)
4. Minimize next-state logic
5. Implement the design

Example: Sequence detector

- Design a circuit to detect 3 or more 1's in a bit string
 - Assume Moore machine
 - Assume D flip-flops
 - Assume flip-flops have a reset

 
1. State diagram and state-transition table



| reset | current state | input | next state | current output |
|-------|---------------|-------|------------|----------------|
| 1 | - | - | A | 0 |
| 0 | A | 0 | A | 0 |
| 0 | A | 1 | B | 0 |
| 0 | B | 0 | A | 0 |
| 0 | B | 1 | C | 0 |
| 0 | C | 0 | A | 0 |
| 0 | C | 1 | D | 0 |
| 0 | D | 0 | A | 1 |
| 0 | D | 1 | D | 1 |

 
2. State minimization & 3. State encoding

- State diagram is already minimized
- Try a binary encoding



| reset | current state | input | next state | current output |
|-------|---------------|-------|------------|----------------|
| 1 | — | — | 00 | 0 |
| 0 | 00 | 0 | 00 | 0 |
| 0 | 00 | 1 | 01 | 0 |
| 0 | 01 | 0 | 00 | 0 |
| 0 | 01 | 1 | 10 | 0 |
| 0 | 10 | 0 | 00 | 0 |
| 0 | 10 | 1 | 11 | 0 |
| 0 | 11 | 0 | 00 | 1 |
| 0 | 11 | 1 | 11 | 1 |

4. Minimize next-state logic

 


$$\text{MSB+} = L\text{In} + M\text{In}$$

$$\text{LSB+} = L'\text{In} + M\text{In}$$

$$\text{Out+} = ML$$


Notation
 M := MSB
 L := LSB
 In := Input

5. Implement the design

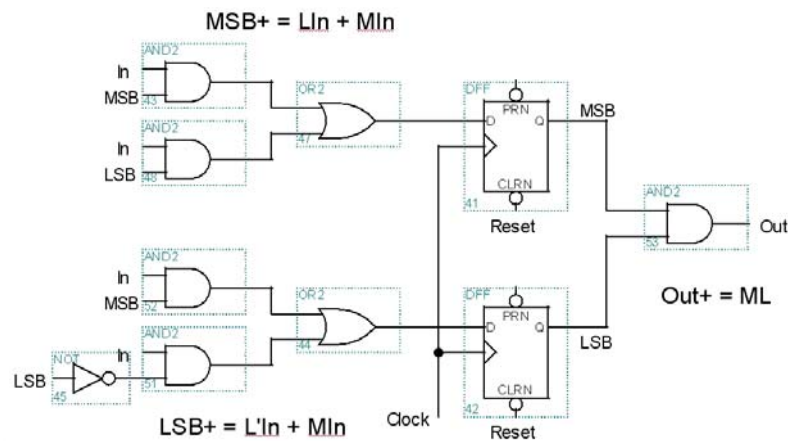

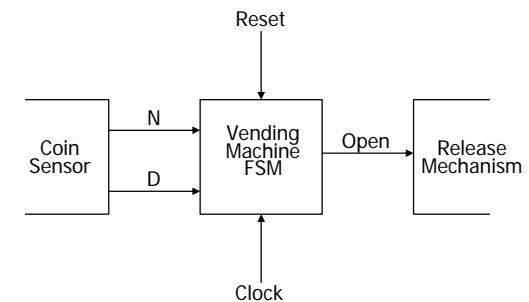
Example: vending machine

- Release item after 15 cents are deposited
- Single coin slot for dimes, nickels
- No change



 
Example: vending machine (cont'd)

- Suitable abstract representation
 - tabulate typical input sequences:
 - 3 nickels
 - nickel, dime
 - dime, nickel
 - two dimes
 - draw state diagram:
 - inputs: N, D, reset
 - output: open chute
 - assumptions:
 - assume N and D asserted for one cycle
 - each state has a self loop for N = D = 0 (no coin)



 Example: vending machine (cont'd)

- Minimize number of states - reuse states whenever possible



| present state | inputs | | next state | output open |
|---------------|--------|---|------------|-------------|
| | D | N | | |
| 0¢ | 0 | 0 | 0¢ | 0 |
| | 0 | 1 | 5¢ | 0 |
| | 1 | 0 | 10¢ | 0 |
| 5¢ | 1 | 1 | - | - |
| | 0 | 0 | 5¢ | 0 |
| | 0 | 1 | 10¢ | 0 |
| 10¢ | 1 | 1 | - | - |
| | 0 | 0 | 10¢ | 0 |
| | 0 | 1 | 15¢ | 0 |
| 15¢ | 1 | 0 | 15¢ | 0 |
| | 1 | 1 | - | - |
| | - | - | 15¢ | 1 |

symbolic state table



Example: vending machine (cont'd)

- Uniquely encode states

| present state | inputs | | next state | output open |
|---------------|--------|-----|------------|-------------|
| | Q1 Q0 | D N | | |
| 0 0 | 0 0 | 0 0 | 0 0 | 0 |
| | | 0 1 | 0 1 | 0 |
| | | 1 0 | 1 0 | 0 |
| | | 1 1 | - - | - |
| 0 1 | 0 0 | 0 0 | 0 1 | 0 |
| | | 0 1 | 1 0 | 0 |
| | | 1 0 | 1 1 | 0 |
| | | 1 1 | - - | - |
| 1 0 | 0 0 | 0 0 | 1 0 | 0 |
| | | 0 1 | 1 1 | 0 |
| | | 1 0 | 1 1 | 0 |
| | | 1 1 | - - | - |
| 1 1 | - - | - - | 1 1 | 1 |

Example: Moore implementation

- Mapping to logic

  

$$D1 = Q1 + D + Q0 N$$

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$

Example: vending machine (cont'd)

One-hot encoding

| present state | | | | inputs | | next state output | | | | |
|---------------|----|----|----|--------|---|-------------------|----|----|----|------|
| Q3 | Q2 | Q1 | Q0 | D | N | D3 | D2 | D1 | D0 | open |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| | | | | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| | | | | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| | | | | 1 | 1 | - | - | - | - | - |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| | | | | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| | | | | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| | | | | 1 | 1 | - | - | - | - | - |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| | | | | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| | | | | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| | | | | 1 | 1 | - | - | - | - | - |
| 1 | 0 | 0 | 0 | - | - | 1 | 0 | 0 | 0 | 1 |

$$D0 = Q0 D' N'$$

$$D1 = Q0 N + Q1 D' N'$$

$$D2 = Q0 D + Q1 N + Q2 D' N'$$


$$D3 = Q1 D + Q2 D + Q2 N + Q3$$

$$OPEN = Q3$$

Equivalent Mealy and Moore state diagrams


Moore machine

■ outputs associated with state

 


Mealy machine

■ outputs associated with transitions

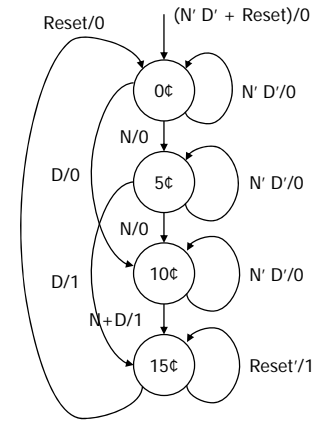

Example: Mealy implementation

 

| present state | | inputs | | next state | | output |
|---------------|----|--------|---|------------|----|--------|
| Q1 | Q0 | D | N | D1 | D0 | open |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| | | 0 | 1 | 0 | 1 | 0 |
| | | 1 | 0 | 1 | 0 | 0 |
| | | 1 | 1 | - | - | - |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| | | 0 | 1 | 1 | 0 | 0 |
| | | 1 | 0 | 1 | 1 | 1 |
| | | 1 | 1 | - | - | - |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| | | 0 | 1 | 1 | 1 | 1 |
| | | 1 | 0 | 1 | 1 | 1 |
| | | 1 | 1 | - | - | - |
| 1 | 1 | - | - | 1 | 1 | 1 |

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


Example: Mealy implementation

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$


$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$

 make sure OPEN is 0 when reset
- by adding AND gate




Vending machine: Moore to synch. Mealy

- OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$
- Implementation now looks like a synchronous Mealy machine
 - it is common for programmable devices to have FF at end of logic

 




Vending machine: Mealy to synch. Mealy

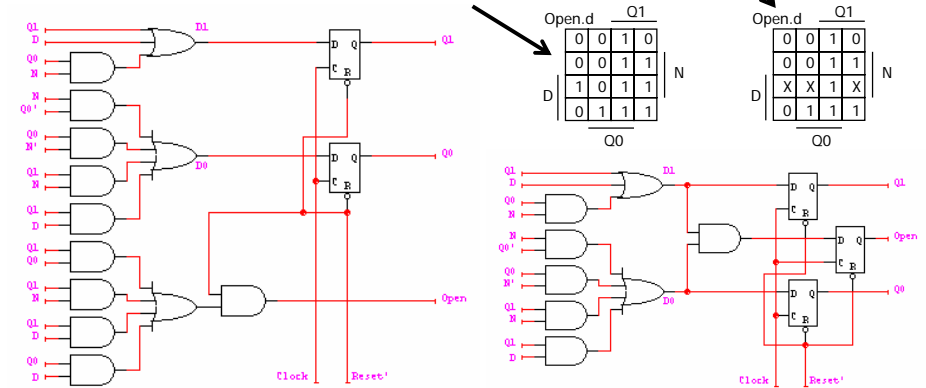- $OPEN.d = Q1Q0 + Q1N + Q1D + Q0D$
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$





Mealy and Moore examples

- Recognize A,B = 0,1
- Mealy or Moore?

   

Mealy and Moore examples (cont'd)

  - Recognize A,B = 1,0 then 0,1
- Mealy or Moore?




HDLs and Sequential Logic

- Flip-flops
 - representation of clocks - timing of state changes
 - asynchronous vs. synchronous
- FSMs
 - structural view (FFs separate from combinational logic)
 - behavioral view (synthesis of sequencers – not in this course)
- Data-paths = data computation (e.g., ALUs, comparators) + registers
 - use of arithmetic/logical operators
 - control of storage elements

 Example: reduce-1-string-by-1

- Remove one 1 from every string of 1s on the input



Verilog FSM - Reduce 1s example

- Moore machine

```


module reduce (clk, reset, in, out);
    input clk, reset, in;
    output out;

    parameter zero = 2'b00;
    parameter one1 = 2'b01;
    parameter twols = 2'b10;

    reg out;
    reg [2:1] state; // state variables
    reg [2:1] next_state;

    always @(posedge clk)
        if (reset) state = zero;
        else state = next_state;
    
```

 state assignment
(easy to change,
if in one place)



Moore Verilog FSM (cont'd)

```

always @(in or state)
    case (state)
        zero:
            // last input was a zero
            begin
                if (in) next_state = one1;
                else next_state = zero;
            end
        one1:
            // we've seen one 1
            begin
                if (in) next_state = twols;
                else next_state = zero;
            end
        twols:
            // we've seen at least 2 ones
            begin
                if (in) next_state = twols;
                else next_state = zero;
            end
    endcase
endmodule
    
```

crucial to include
all signals that are
input to state determination

note that output
depends only on state

```


always @(state)
    case (state)
        zero: out = 0;
        one1: out = 0;
        twols: out = 1;
    endcase
    
```

Mealy Verilog FSM

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables
  reg next_state;

  always @(posedge clk)
    if (reset) state = zero;
    else state = next_state;

   always @(in or state)
    case (state)
      zero: // last input was a zero
        begin
          out = 0;
          if (in) next_state = one;
          else next_state = zero;
        end
      one: // we've seen one 1
        if (in) begin
          next_state = one; out = 1;
        end else begin
          next_state = zero; out = 0;
        end
    endcase
endmodule
```



Synchronous Mealy Machine

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables

  always @(posedge clk)
    if (reset) state = zero;
    else
      case (state)
        zero: // last input was a zero
          begin
            out = 0;
            if (in) state = one;
            else state = zero;
          end
        one: // we've seen one 1
          if (in) begin
            state = one; out = 1;
          end else begin
            state = zero; out = 0;
          end
      endcase
    end
endmodule
```

Finite state machines summary

- Models for representing sequential circuits
 - abstraction of sequential elements
 - finite state machines and their state diagrams
 - inputs/outputs
 - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
 - deriving state diagram
 - deriving state transition table
 - determining next state and output functions
 - implementing combinational logic
- Hardware description languages