 


CSE 370 Spring 2006

Introduction to Digital Design

Lecture 24: Design Examples



Last Lecture

- Factoring FSMs
- Output encoding
- Communicating FSMs
- Design Example

Today

- Design Examples

Administrivia

- Hand in HW #8

- Quiz #4

Combine ^{AM} (5, 5, 5, 1) and any (,), x, +, -, or ÷
to get 24.
 $(5 - (1 \div 5)) \times 5 = 24$

Sequential logic examples

- Basic design approach: a 4-step design process
- Implementation examples and case studies
 - finite-string pattern recognizer
 - complex counter
 - door combination lock

General FSM design procedure

- (1) Determine inputs and outputs
- (2) Determine possible states of machine
 - state minimization
- (3) Encode states and outputs into a binary code
 - state assignment or state encoding
 - output encoding
 - possibly input encoding (if under our control)
- (4) Realize logic to implement functions for states and outputs
 - combinational logic implementation and optimization
 - choices in steps 2 and 3 can have large effect on resulting logic

Complex counter

- A synchronous 3-bit counter has a mode control M
 - when M = 0, the counter counts up in the binary sequence
 - when M = 1, the counter advances through the Gray code sequence

binary: 000, 001, 010, 011, 100, 101, 110, 111


Gray: 000, 001, 011, 010, 110, 111, 101, 100

- Valid I/O behavior (partial)

Mode Input M	Current State	Next State
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111

Complex counter (state diagram)

 - Deriving state diagram
 - one state for each output combination
 - add appropriate arcs for the mode control



Complex counter (state encoding)

- Verilog description including state encoding

```

module string (clk, M, rst, Z0, Z1, Z2);
    input clk, X, rst;
    output Z0, Z1, Z2;

    parameter S0 = [0,0,0];
    parameter S1 = [0,0,1];
    parameter S2 = [0,1,0];
    parameter S3 = [0,1,1];
    parameter S4 = [1,0,0];
    parameter S5 = [1,0,1];
    parameter S6 = [1,1,0];
    parameter S7 = [1,1,1];


    reg state[0:2];

    always @(posedge clk) begin
        if rst state = S0;
        else
            case (state)
                S0: state = S1;
                S1: if (M) state = S3 else state = S2;
                S2: if (M) state = S6 else state = S3;
                S3: if (M) state = S2 else state = S4;
                S4: if (M) state = S0 else state = S5;
                S5: if (M) state = S4 else state = S6;
                S6: if (M) state = S7 else state = S7;
                S7: if (M) state = S5 else state = S0;
            endcase
        end
    end

    assign Z0 = state[0];
    assign Z1 = state[1];
    assign Z2 = state[2];
endmodule
    
```

Data-path and control

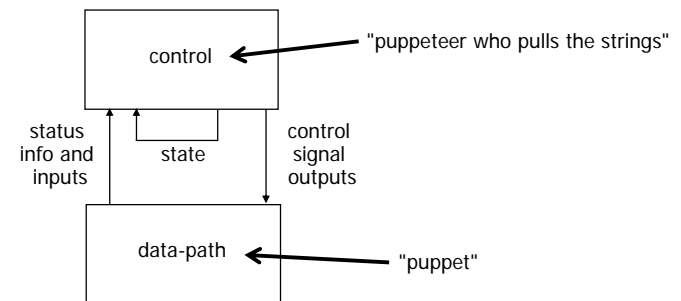- Digital hardware systems = data-path + control
 - datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
 - control: FSM generating sequences of control signals that instructs datapath what to do next



Digital combinational lock

- Door combination lock:
 - punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
- inputs: sequence of input values, reset
- outputs: door open/close
- memory: must remember combination or always have it available
- open questions: how do you set the internal combination?
 - stored in registers (how loaded?)
 - hardwired via switches set by user

Implementation in software

```
integer combination_lock ( ) {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value( ));
    v1 = read_value( );
    if (v1 != c[1]) then error = 1;


    while (!new_value( ));
    v2 = read_value( );
    if (v2 != c[2]) then error = 1;

    while (!new_value( ));
    v3 = read_value( );
    if (v2 != c[3]) then error = 1;

    if (error == 1) then return(0); else return (1);
}
```


Determining details of the specification

 - How many bits per input value?
- How many values in sequence?
- How do we know a new input value is entered?
- What are the states and state transitions of the system?




Digital combination lock state diagram

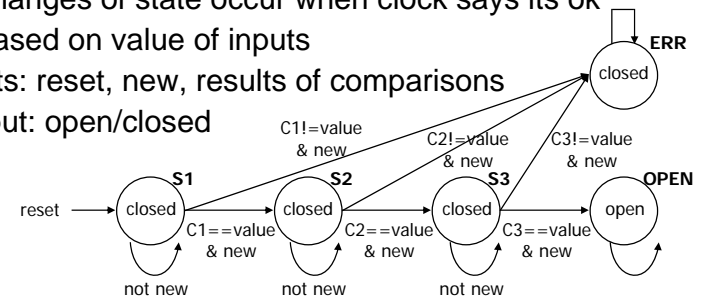- States: 5 states
 - represent point in execution of machine
 - each state has outputs
- Transitions: 6 from state to state, 5 self transitions, 1 global
 - changes of state occur when clock says its ok
 - based on value of inputs
- Inputs: reset, new, results of comparisons
- Output: open/closed



Data-path and control structure

 - Data-path
 - storage registers for combination values
 - multiplexer
 - comparator
- Control
 - finite-state machine controller
 - control for data-path (which value to compare)




State table for combination lock

- Finite-state machine
 - refine state diagram to take internal structure into account
 - state table ready for encoding

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open
...						

Encodings for combination lock

- Encode state table
 - state can be: S1, S2, S3, OPEN, or ERR
 - needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - and as many as 5: 00001, 00010, 00100, 01000, 10000
 - choose 4 bits: 0001, 0010, 0100, 1000, 0000
 - output mux can be: C1, C2, or C3
 - needs 2 to 3 bits to encode
 - choose 3 bits: 001, 010, 100
 - output open/closed can be: open or closed
 - needs 1 or 2 bits to encode
 - choose 1 bit: 1, 0

 


reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...						
0	1	1	0100	1000	-	1
...						

mux is identical to last 3 bits of state
open/closed is identical to first bit of state
therefore, we do not even need to implement FFs to hold state, just use outputs

Data-path implementation for combination lock


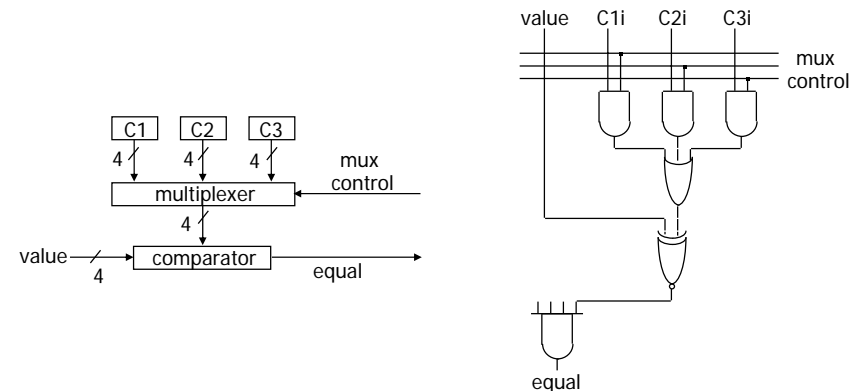
- Multiplexer
 - easy to implement as combinational logic when few inputs
 - logic can easily get too big for most PLDs



Data-path implementation (cont'd)


Tri-state logic

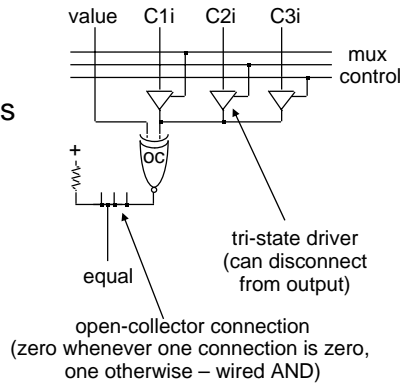 - utilize a third output state: "no connection" or "float"
- connect outputs together as long as only one is "enabled"
- open-collector gates can only output 0, not 1
 - can be used to implement logical AND with only wires




Tri-state gates

- The third value
 - logic values: "0", "1"
 - don't care: "X" (must be 0 or 1 in real circuit!)
 - third value or state: "Z" — high impedance, infinite R, no connection
- Tri-state gates
 - additional input – output enable (OE)
 - output values are 0, 1, and Z
 - when OE is high, the gate functions normally
 - when OE is low, the gate is disconnected from wire at output
 - allows more than one gate to be connected to the same output wire
 - as long as only one has its output enabled at any one time (otherwise, sparks could fly)

 


	In	OE	Out
non-inverting tri-state buffer	X	0	Z
	0	1	0
	1	1	1

 

Tri-state and multiplexing

 - When using tri-state logic
 - (1) make sure never more than one "driver" for a wire at any one time (pulling high and low at the same time can severely damage circuits)
 - (2) make sure to only use value on wire when its being driven (using a floating value may cause failures)
- Using tri-state gates to implement an economical multiplexer




when Select is high
Input1 is connected to F

when Select is low
Input0 is connected to F

this is essentially a 2:1 mux


Open-collector gates and wired-AND

- Open collector: another way to connect gate outputs to the same wire
 - gate only has the ability to pull its output low
 - it cannot actively drive the wire high (default – pulled high through resistor)
- Wired-AND can be implemented with open collector logic
 - if A and B are "1", output is actively pulled low
 - if C and D are "1", output is actively pulled low
 - if one gate output is low and the other high, then low wins
 - if both gate outputs are "1", the wire value "floats", pulled high by resistor
 - low to high transition usually slower than it would have been with a gate pulling high
 - hence, the two NAND functions are ANDed together

 

Digital combination lock (new data-path)

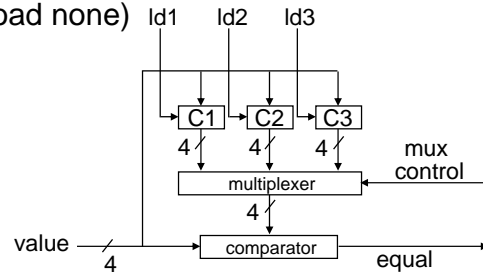- Decrease number of inputs
- Remove 3 code digits as inputs
 - use code registers
 - make them loadable from value
 - need 3 load signal inputs (net gain in input $(4*3)-3=9$)
 - could be done with 2 signals and decoder (ld1, ld2, ld3, load none)



Section summary

- FSM design
 - understanding the problem
 - generating state diagram
 - communicating state machines
- Four case studies
 - understand I/O behavior
 - draw diagrams
 - enumerate states for the "goal"
 - expand with error conditions
 - reuse states whenever possible