

Lecture 8: Combinational Verilog

CSE 370, Autumn 2007
Benjamin Ylvisaker

Where We Are

- Last lecture: Minimization with K-maps
- This lecture: Combinational Verilog
- Next lecture: ROMs, PLAs and PALs, oh my!
- Homework 3 ongoing
- Lab 2 done; lab 3 next week

Specifying Circuits

- Schematics
 - Structural description
 - Build more complex circuits using hierarchy
 - Large circuits are unreadable
- HDLs (Hardware description languages)
 - Not conventional programming languages
 - Very restricted parallel languages
 - Synthesize code to produce a circuit

Quick History Lesson


- Abel (-1983)
 - Developed by Data-I/O
 - Targeted to PLDs
- Verilog (-1985)
 - Developed by Gateway (now part of Cadence)
 - **Syntax** similar to C
 - Moved to public domain in 1990
- VHDL (-1987)
 - DoD sponsored
 - **Syntax** similar to Ada

Verilog and VHDL Dominant

- Both “IEEE standard” languages
- Most tools support both
- Verilog is “simpler”
 - Less, more concise syntax
- VHDL is more structured
 - More sophisticated type system
 - Better modularity features

Simulation and Synthesis

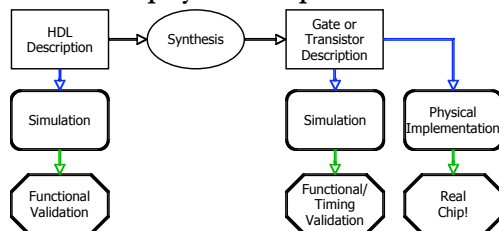- Simulation
 - “Execute” a design with some test data
- Synthesis
 - Generate a physical implementation




Simulation and Synthesis (cont'd)

- Simulation
 - Model circuit behavior
 - Can include timing estimates
 - Allows for easier design exploration
- Synthesis
 - Converts HDL code to “netlists”
 - Can still simulate the generated netlists
- Simulation and synthesis in the CSE curriculum
 - 370: Learn simulation
 - 467: Learn something about synthesis


Simulation

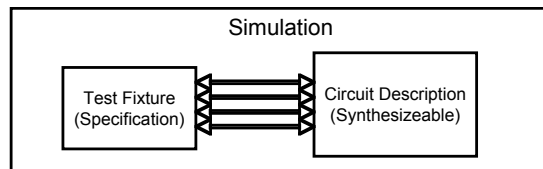- You provide an environment
 - Use non-circuit constructs (Active-HDL waveforms, random number generators, etc)
 - Can write arbitrary Verilog code



Specifying Circuits in Verilog

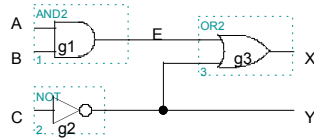- There are three major styles
 - Instances 'n wires
 - Continuous assignments
 - “always” blocks



“Structural”

```
wire E;
and g1(E,A,B);
not g2(Y,C);
or g3(X,E,Y);
```

“Behavioral”

```
wire E;
assign E = A & B;
assign Y = ~ C;
assign X = E | Y;
```

```
reg E, X, Y;
always @ (A or B or C)
begin
    E = A & B;
    Y = ~C;
    X = E | Y;
end
```

Data Types

- Values on a wire
 - 0, 1, x (unknown or conflict), z (unconnected)
- Vectors
 - A[3:0] vector of 4 bits: A[3], A[2], A[1], A[0]
 - Interpreted as an unsigned binary number
 - Indices must be constants
 - Concatenation
 - B = {A[3], A[3], A[3], A[3], A[3:0]};
 - B = {4{A[3]}, A[3:0]};
 - Style: good to use unnecessary size specs sometimes
 - a[7:0] = b[7:0] + c[7:0];
 - Built-in reductions: C = &A[5:7];

Data Types That Do Not Exist

- structures (records)
- Pointers
- Objects
- Recursive types
- (Remember, Verilog is not C or Java or Lisp or ...)

Numbers

- Format: <sign><size><base format><number>
- I4
 - Decimal
- -4'b11
 - 4-bit 2's complement of 0011
- 12'b0000_0100_0110
 - 12 bit binary number ('_'s ignored)
- 12'h4Ab
 - 12 bit hexadecimal number

Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ & ~& ~ ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{}	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

> >= < <=	greater than greater than or equal to less than less than or equal to	Relational Relational Relational Relational
== !=	logical equality logical inequality	Equality Equality
=== !==	case equality case inequality	Equality Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional


Similar to C operators

Two Abstraction Mechanisms

- Modules
 - More structural
 - Heavily used in 370 and “real” Verilog code
- Functions
 - More behavioral
 - Used to some extent in “real” Verilog, but not much in 370

Basic Building Blocks: Modules

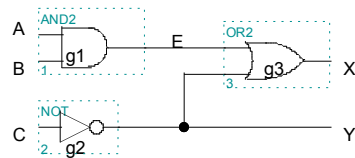
- Instantiated, not called
- Illegal to nest module defs
- Instances “execute” in parallel
- Wires are used for connections
- and, or, not built-in primitive modules
 - List output first
 - Arbitrary number of inputs next
- Names are case sensitive
 - Cannot begin with number
- // for comments



```
// first simple example
module smpl (X, Y, A, B, C);
  input A, B, C;
  output X, Y;
  wire E;
  and g1 (E, B, B);
  not g2 (Y, C);
  or g3 (X, E, Y);
endmodule
```

Module Ports

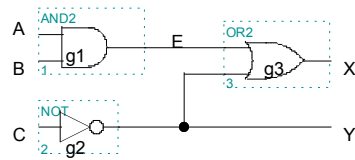- Modules interact with the rest of a design through ports
 - input
 - output
 - inout
- Same example with continuous assignments:



```
// first simple example
module smpl (X, Y, A, B, C);
  input A, B, C;
  output X, Y;
  assign X = (A&B) | ~C;
  assign Y = ~C;
endmodule
```

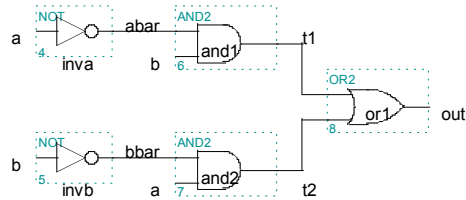

Bigger Structural Example

```

• module xor_gate (out,a,b);
  input  a,b;
  output out;
  wire  abar, bbar, t1, t2;
  not   inva (abar,a);
  not   invb (bbar,b);
  and   and1 (t1,abar,b);
  and   and2 (t2,bbar,a);
  or    or1 (out,t1,t2);
endmodule

```

8 built-in gates:
 and, or, nand, nor,
 buf, not, xor, xnor



Behavioral Full Adder



```

• module full_addr (Sum,Cout,A,B,Cin);
  input  A, B, Cin;
  output Sum, Cout;
  assign {Cout, Sum} = A + B + Cin;
endmodule

```

{Cout, Sum} is a concatenation

Behavioral 4-bit Adder

```
• module add4 (SUM, OVER, A, B);  
  input [3:0] A;  
  input [3:0] B;  
  output [3:0] SUM;  
  output OVER;  
  assign {OVER, SUM[3:0]} = A[3:0] + B[3:0];  
endmodule
```

Continuous Assignment

- Continuously evaluated
 - Think of them as collections of logic gates
 - Evaluated in parallel

```
assign A = X | (Y & ~Z);
```

```
assign B[3:0] = 4'b01XX;
```

```
assign C[15:0] = 4'h00ff;
```

```
assign #3 {Cout, Sum[3:0]} = A[3:0] + B[3:0] + Cin;
```

Hierarchy Example: Comparator

- ```
module Compare1 (Equal, Alarger, Blarger, A, B);
 input A, B;
 output Equal, Alarger, Blarger;
 assign Equal = (A & B) | (~A & ~B);
 assign Alarger = (A & ~B);
 assign Blarger = (~A & B);
endmodule
```

## 4-bit Comparator

- ```
// Make a 4-bit comparator from 4 1-bit comparators
module Compare4(Equal, Alarger, Blarger, A4, B4);
  input [3:0] A4, B4;
  output Equal, Alarger, Blarger;
  wire e0, e1, e2, e3, A10, A11, A12, A13, B10, B11, B12, B13;

  Compare1 cp0(e0, A10, B10, A4[0], B4[0]);
  Compare1 cp1(e1, A11, B11, A4[1], B4[1]);
  Compare1 cp2(e2, A12, B12, A4[2], B4[2]);
  Compare1 cp3(e3, A13, B13, A4[3], B4[3]);

  assign Equal = (e0 & e1 & e2 & e3);
  assign Alarger = (A13 | (A12 & e3) |
                  (A11 & e3 & e2) |
                  (A10 & e3 & e2 & e1));
  assign Blarger = (~Alarger & ~Equal);
endmodule
```

Sequential assigns don't make any sense

- `assign A = X | (Y & ~Z);`

```
assign B = W | A;
```

```
assign A = Y & Z;
```

- You can't reassign a variable with continuous assignments

Always Blocks

- `reg A, B, C;`

Variables that appear on the left hand side in an always block must be declared as "reg"s

```
always @ (W or X or Y or Z)
```

Sensitivity list

```
begin
```

```
  A = X | (Y & ~Z);
```

```
  B = W | A;
```

```
  A = Y & Z;
```

Statements in an always block are executed in sequence

```
  if (A & B) begin
```

```
    B = Z;
```

```
    C = W | Y;
```

```
  end
```

```
end
```

All variables must be assigned on every control path!!! (otherwise you get the dreaded "inferred latch")

Functions

- Functions can be used for combinational logic that you want to reuse

```
• module and_gate (out, in1, in2);  
  input    in1, in2;  
  output   out;  
  
  assign out = myfunction(in1, in2);  
  
  function myfunction;  
  input in1, in2;  
  begin  
    myfunction = in1 & in2;  
  end  
endfunction  
endmodule
```

Verilog Tips

- **Do not** write C-code
 - Think hardware, not algorithms
 - Verilog is **inherently parallel**
 - Compilers don't map algorithms to circuits well
- Do describe hardware circuits
 - First draw a dataflow diagram
 - Then start coding
- References
 - Tutorial and reference manual are found in ActiveHDL help
 - And in today's reading assignment
 - "Starter's Guide to Verilog 2001" by Michael Ciletti
 - copies for borrowing in hardware lab

Thank You for Your Attention

Thank You for Your Attention

- Read lab 2
- Continue homework 2
- Continue reading the book