

Overview

- ◆ Last lecture
 - Ant-brain FSM
- ◆ Today
 - Sequential Logic Examples

Finite string pattern recognizer (step 1)

- ◆ Finite string pattern recognizer
 - one input (X) and one output (Z)
 - output is asserted whenever the input sequence ...010... has been observed, as long as the sequence 100 has never been seen

- ◆ Step 1: understanding the problem statement
 - sample input/output behavior:

X: 0 0 1 0 1 0 1 0 0 1 0 ...
Z: 0 0 0 1 0 1 0 1 0 0 0 ...


X: 1 1 0 1 1 0 1 0 0 1 0 ...
Z: 0 0 0 0 0 0 0 1 0 0 0 ...

Sequential logic examples

- ◆ Basic design approach: a 4-step design process
- ◆ Hardware description languages and finite state machines
- ◆ Implementation examples and case studies
 - finite-string pattern recognizer
 - complex counter
 - traffic light controller
 - door combination lock

Finite string pattern recognizer (step 2)

 - ◆ Step 2: draw state diagram
 - for the strings that must be recognized, i.e., 010 and 100
 - a Moore implementation



General FSM design procedure


- ◆ (1) Determine inputs and outputs
- ◆ (2) Determine possible states of machine
 - - state minimization
- ◆ (3) Encode states and outputs into a binary code
 - - state assignment or state encoding
 - - output encoding
 - - possibly input encoding (if under our control)
- ◆ (4) Realize logic to implement functions for states and outputs
 - - combinational logic implementation and optimization
 - - choices made in steps 2 and 3 can have large effect on resulting logic

Finite string pattern recognizer (step 2, cont'd)

- ◆ Exit conditions from state S3: have recognized ...010
 - if next input is 0 then have ...0100 = ...100 (state S6)
 - if next input is 1 then have ...0101 = ...01 (state S2)

- ◆ Exit conditions from S1: recognizes strings of form ...0 (no 1 seen)
 - loop back to S1 if input is 0

 - ◆ Exit conditions from S4: recognizes strings of form ...1 (no 0 seen)
 - loop back to S4 if input is 1



Finite string pattern recognizer (step 2, cont'd)


- ◆ S2 and S5 still have incomplete transitions

- S2 = ...01; If next input is 1, then string could be prefix of (01)1(00) S4 handles just this case
- S5 = ...10; If next input is 1, then string could be prefix of (10)1(0) S2 handles just this case

- ◆ Reuse states as much as possible

- look for same meaning
- state minimization leads to smaller number of bits to represent states

 - ◆ Once all states have a complete set of transitions we have a final state diagram



CSE370, Lecture 23

Complex counter

- ◆ A synchronous 3-bit counter has a mode control M

- when M = 0, the counter counts up in the binary sequence
- when M = 1, the counter advances through the Gray code sequence

binary: 000, 001, 010, 011, 100, 101, 110, 111
 Gray: 000, 001, 011, 010, 110, 111, 101, 100

- ◆ Valid I/O behavior (partial)

Mode Input M	Current State	Next State
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111

CSE370, Lecture 23

10

Finite string pattern recognizer (step 3)

- ◆ Verilog description including state assignment (or state encoding)

```

module string (clk, X, rst, Q0, Q1, Q2, Z);
input clk, X, rst;
output Q0, Q1, Q2, Z;

reg state[0:2];
`define S0 [0,0,0] //reset state
`define S1 [0,0,1] //strings ending in ...0
`define S2 [0,1,0] //strings ending in ...01
`define S3 [0,1,1] //strings ending in ...010
`define S4 [1,0,0] //strings ending in ...1
`define S5 [1,0,1] //strings ending in ...10
`define S6 [1,1,0] //strings ending in ...100

assign Q0 = state[0];
assign Q1 = state[1];
assign Q2 = state[2];
assign Z = (state == 'S3);

always @(posedge clk) begin
    if rst state = 'S0;
    else
        case (state)
            'S0: if (X) state = 'S4 else state = 'S1;
            'S1: if (X) state = 'S2 else state = 'S1;
            'S2: if (X) state = 'S4 else state = 'S3;
            'S3: if (X) state = 'S2 else state = 'S6;
            'S4: if (X) state = 'S4 else state = 'S5;
            'S5: if (X) state = 'S2 else state = 'S6;
            'S6: state = 'S6;
        default: begin
            $display ("invalid state reached");
            state = 3'bxxx;
        endcase
    end
end
endmodule
    
```


CSE370, Lecture 23

8

Complex counter (state diagram)

- ◆ Deriving state diagram

 - one state for each output combination
- add appropriate arcs for the mode control



CSE370, Lecture 23

11

Finite string pattern recognizer

- ◆ Review of process

- understanding problem
 - ↳ write down sample inputs and outputs to understand specification
- derive a state diagram
 - ↳ write down sequences of states and transitions for sequences to be recognized
- minimize number of states
 - ↳ add missing transitions; reuse states as much as possible
- state assignment or encoding
 - ↳ encode states with unique patterns
- simulate realization
 - ↳ verify I/O behavior of your state diagram to ensure it matches specification

CSE370, Lecture 23

9

Complex counter (state encoding)

- ◆ Verilog description including state encoding

```

module string (clk, M, rst, Z0, Z1, Z2);
input clk, X, rst;
output Z0, Z1, Z2;

reg state[0:2];
`define S0 = [0,0,0];
`define S1 = [0,0,1];
`define S2 = [0,1,0];
`define S3 = [0,1,1];
`define S4 = [1,0,0];
`define S5 = [1,0,1];
`define S6 = [1,1,0];
`define S7 = [1,1,1];

assign Z0 = state[0];
assign Z1 = state[1];
assign Z2 = state[2];

always @(posedge clk) begin
    if rst state = 'S0;
    else
        case (state)
            'S0: state = 'S1;
            'S1: if (M) state = 'S3 else state = 'S2;
            'S2: if (M) state = 'S6 else state = 'S3;
            'S3: if (M) state = 'S2 else state = 'S4;
            'S4: if (M) state = 'S0 else state = 'S5;
            'S5: if (M) state = 'S4 else state = 'S6;
            'S6: if (M) state = 'S7 else state = 'S7;
            'S7: if (M) state = 'S5 else state = 'S0;
        endcase
    end
end
endmodule
    
```


CSE370, Lecture 23

12

Traffic light controller as two communicating FSMs


Without separate timer

 - S0 would require 7 states
- S1 would require 3 states
- S2 would require 7 states
- S3 would require 3 states
- S1 and S3 have simple transformation
- S0 and S2 would require many more arcs
 - C could change in any of seven states



By factoring out timer

 - greatly reduce number of states
 - 4 instead of 20
- counter only requires seven or eight states
 - 12 total instead of 20



Timer for traffic light controller

Another FSM

```

module Timer(TS, TL, ST, Clk);
    output TS;
    output TL;
    input  ST;
    input  Clk;
    integer value;

    assign TS = (value >= 4); // 5 cycles after reset
    assign TL = (value >= 14); // 15 cycles after reset

    always @(posedge ST) value = 0; // async reset

    always @(posedge Clk) value = value + 1;
endmodule
    
```

Traffic light controller FSM

Specification of inputs, outputs, and state elements

```

module FSM(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
    output HR;
    output HY;
    output HG;
    output FR;
    output FY;
    output FG;
    output ST;
    input  TS;
    input  TL;
    input  C;
    input  reset;
    input  Clk;

    reg [6:1] state;
    reg      ST;

    `define highwaygreen 6'b001100
    `define highwayyellow 6'b010100
    `define farmroadgreen 6'b100001
    `define farmroadyellow 6'b100010

    assign HR = state[6];
    assign HY = state[5];
    assign HG = state[4];
    assign FR = state[3];
    assign FY = state[2];
    assign FG = state[1];
    
```

specify state bits and codes for each state as well as connections to outputs


Complete traffic light controller

Tying it all together (FSM + timer)

```

module main(HR, HY, HG, FR, FY, FG, reset, C, Clk);
    output HR, HY, HG, FR, FY, FG;
    input  reset, C, Clk;

     Timer part1(TS, TL, ST, Clk);
    FSM part2(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
endmodule
    
```



Traffic light controller FSM (cont'd)

```


initial begin state = `highwaygreen; ST = 0; end

always @(posedge Clk)
begin
    if (reset)
        begin state = `highwaygreen; ST = 1; end
    else
        begin
            ST = 0;
            case (state)
                `highwaygreen:
                    if (TL & C) begin state = `highwayyellow; ST = 1; end
                `highwayyellow:
                    if (TS) begin state = `farmroadgreen; ST = 1; end
                `farmroadgreen:
                    if (TL | !C) begin state = `farmroadyellow; ST = 1; end
                `farmroadyellow:
                    if (TS) begin state = `highwaygreen; ST = 1; end
            endcase
        end
    end
endmodule
    
```

case statement triggered by clock edge


Communicating finite state machines

 One machine's output is another machine's input



Data-path and control

 - ◆ Digital hardware systems = data-path + control
 - datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
 - control: FSM generating sequences of control signals that instructs datapath what to do next




CSE370, Lecture 23

19

Determining details of the specification

 - ◆ How many bits per input value?
- ◆ How many values in sequence?
- ◆ How do we know a new input value is entered?
- ◆ What are the states and state transitions of the system?



CSE370, Lecture 23

22

Digital combinational lock


- ◆ Door combination lock:
 - punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
 - inputs: sequence of input values, reset
 - outputs: door open/close
 - memory: must remember combination or always have it available
 - open questions: how do you set the internal combination?
 - ✘ stored in registers (how loaded?)
 - ✘ hardwired via switches set by user

CSE370, Lecture 23

20

Digital combination lock state diagram

 - ◆ States: 5 states
 - represent point in execution of machine
 - each state has outputs
- ◆ Transitions: 6 from state to state, 5 self transitions, 1 global
 - changes of state occur when clock says its ok
 - based on value of inputs
- ◆ Inputs: reset, new, results of comparisons
- ◆ Output: open/closed



CSE370, Lecture 23

23

Implementation in software

```
integer combination_lock () {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value());
    v1 = read_value();
    if (v1 != c[1]) then error = 1;

    while (!new_value());
    v2 = read_value();
    if (v2 != c[2]) then error = 1;

    while (!new_value());
    v3 = read_value();
    if (v2 != c[3]) then error = 1;


    if (error == 1) then return(0); else return (1);
}
```

CSE370, Lecture 23

21

Data-path and control structure

 - ◆ Data-path
 - storage registers for combination values
 - multiplexer
 - comparator
- ◆ Control
 - finite-state machine controller
 - control for data-path (which value to compare)



CSE370, Lecture 23

24

State table for combination lock

◆ Finite-state machine

- refine state diagram to take internal structure into account
- state table ready for encoding

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...
0	1	1	S3	OPEN	-	open
...


CSE370, Lecture 23

25

Data-path implementation (cont'd)

◆ Tri-state logic

 - utilize a third output state: "no connection" or "float"
- connect outputs together as long as only one is "enabled"
- open-collector gates can only output 0, not 1
 - can be used to implement logical AND with only wires




CSE370, Lecture 23

28

Encodings for combination lock

◆ Encode state table

 - state can be: S1, S2, S3, OPEN, or ERR
 - needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - and as many as 5: 00001, 00010, 00100, 01000, 10000
 - choose 4 bits: 0001, 0010, 0100, 1000, 0000
- output mux can be: C1, C2, or C3
 - needs 2 to 3 bits to encode
 - choose 3 bits: 001, 010, 100
- output open/closed can be: open or closed
 - needs 1 or 2 bits to encode
 - choose 1 bit: 1, 0



reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...
0	1	1	0100	1000	-	1

mux is identical to last 3 bits of state
open/closed is identical to first bit of state
therefore, we do not even need to implement FFs to hold state, just use outputs

...CSE370, Lecture 23

26


Tri-state gates

◆ The third value


- logic values: "0", "1"
- don't care: "X" (must be 0 or 1 in real circuit!)
- third value or state: "Z" — high impedance, infinite R, no connection

◆ Tri-state gates

 - additional input — output enable (OE)
- output values are 0, 1, and Z
- when OE is high, the gate functions normally
- when OE is low, the gate is disconnected from wire at output
- allows more than one gate to be connected to the same output wire
 - as long as only one has its output enabled at any one time (otherwise, sparks could fly)



	In	OE	Out
non-inverting	X	0	Z
tri-state	0	1	0
buffer	1	1	1

 


CSE370, Lecture 23

29

Data-path implementation for combination lock

◆ Multiplexer

 - easy to implement as combinational logic when few inputs
- logic can easily get too big for most PLDs



CSE370, Lecture 23


27

Tri-state and multiplexing

◆ When using tri-state logic

- make sure never more than one "driver" for a wire at any one time (pulling high and low at the same time can severely damage circuits)
- make sure to only use value on wire when its being driven (using a floating value may cause failures)

 ◆ Using tri-state gates to implement an economical multiplexer



when Select is high
Input1 is connected to F

when Select is low
Input0 is connected to F


this is essentially a 2:1 mux

CSE370, Lecture 23

30

Open-collector gates and wired-AND

- ◆ Open collector: another way to connect gate outputs to the same wire
 - gate only has the ability to pull its output low
 - it cannot actively drive the wire high (default – pulled high through resistor)
- ◆ Wired-AND can be implemented with open collector logic
 - if A and B are "1", output is actively pulled low
 - if C and D are "1", output is actively pulled low
 - if one gate output is low and the other high, then low wins
 - if both gate outputs are "1", the wire value "floats", pulled high by resistor
 - ✦ low to high transition usually slower than it would have been with a gate pulling high
 - hence, the two NAND functions are ANDed together

 


CSE370, Lecture 23

31

Digital combination lock (new data-path)

 - ◆ Decrease number of inputs
- ◆ Remove 3 code digits as inputs
 - use code registers
 - make them loadable from value
 - need 3 load signal inputs (net gain in input $(4*3)-3=9$)
 - ✦ could be done with 2 signals and decoder (ld1, ld2, ld3, load none)



CSE370, Lecture 23

32