

Lecture 5

◆ Logistics

- HW2 posted on Wed, due 10/8
- Lab1 done
- Final exam schedule confirmed: 12/8 8:30am here Gowen 201

◆ Last lecture

- Logic gates and truth tables
- Implementing logic functions

◆ Today's lecture

- Example using de Morgan's theorem
- Canonical forms
- Converting to use NAND and NOR

The "WHY" slide

◆ More de Morgan's theorem?

- De Morgan's theorem is extremely useful and is used all the time for design implementation. But it is initially not an easy thing to do, so practicing it over and over is critical.

◆ Canonical forms

- There are many forms to expression one Boolean function. It is good to have one standard way. Canonical form is the standard form for Boolean expressions. It has a nice property that allows you to go back and forth between truth table/expressions/gates easily.

◆ Converting to use NAND and NOR

- NAND and NOR are more efficient gates than AND or OR (and therefore more common). Your computer is built almost exclusively on NAND and NOR gates. It is good to knowhow to convert any logic circuits to a NAND/NOR circuit.

de Morgan's theorem

◆ Replace

- \cdot with $+$, $+$ with \cdot , 0 with 1, and 1 with 0
- All variables with their complements

◆ Example 1: $Z = A'B' + A'C'$

$$Z' = (A'B' + A'C)'$$

$$= (A+B) \cdot (A+C)$$

◆ Example 2: $Z = A'B'C + A'BC + AB'C + ABC'$

$$Z' = (A'B'C + A'BC + AB'C + ABC)'$$

$$= (A+B+C) \cdot (A+B'+C) \cdot (A'+B+C) \cdot (A'+B'+C)$$

Canonical forms

◆ Canonical forms

- Standard forms for Boolean expressions
- Generally not the simplest forms
 - ✦ Can be minimized
- Derived from truth table

◆ Two canonical forms

- Sum-of-products (minterms)
- Product-of-sum (maxterms)

Sum-of-products canonical form (SOP)

- ◆ Also called disjunctive normal form (DNF)
 - Commonly called a **minterm expansion**

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

001 011 101 110 111

F = A'B'C + A'BC + AB'C + ABC' + ABC

minterm

F' = A'B'C' + A'BC' + AB'C'

Minterms

- ◆ Variables appears exactly once in each minterm
 - In true or inverted form (but not both)

A	B	C	minterms
0	0	0	A'B'C' m0
0	0	1	A'B'C m1
0	1	0	A'BC' m2
0	1	1	A'BC m3
1	0	0	AB'C' m4
1	0	1	AB'C m5
1	1	0	ABC' m6
1	1	1	ABC m7

short-hand notation

F in canonical form:

$$\begin{aligned}
 F(A,B,C) &= \sum m(1,3,5,6,7) \\
 &= m1 + m3 + m5 + m6 + m7 \\
 &= A'B'C + A'BC + AB'C + ABC' + ABC
 \end{aligned}$$

canonical form → minimal form

$$\begin{aligned}
 F(A,B,C) &= A'B'C + A'BC + AB'C + ABC' + ABC \\
 &= AB + C
 \end{aligned}$$

Product-of-sums canonical form (POS)

- ◆ Also called conjunctive normal form (CNF)
 - Commonly called a **maxterm expansion**

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = (A + B + C) (A + B' + C) (A' + B + C)$

$F' = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C)(A'+B'+C')$

maxterm

Maxterms

- ◆ Variables appears exactly once in each maxterm
 - In true or inverted form (but not both)

A	B	C	maxterms
0	0	0	A+B+C M0
0	0	1	A+B+C' M1
0	1	0	A+B'+C M2
0	1	1	A+B'+C' M3
1	0	0	A'+B+C M4
1	0	1	A'+B+C' M5
1	1	0	A'+B'+C M6
1	1	1	A'+B'+C' M7

F in canonical form:


$$\begin{aligned}
 F(A,B,C) &= \prod M(0,2,4) \\
 &= M_0 \cdot M_2 \cdot M_4 \\
 &= (A+B+C)(A+B'+C)(A'+B+C)
 \end{aligned}$$

canonical form \rightarrow minimal form

$$\begin{aligned}
 F(A,B,C) &= (A+B+C)(A+B'+C)(A'+B+C) \\
 &= AB + C
 \end{aligned}$$

short-hand notation

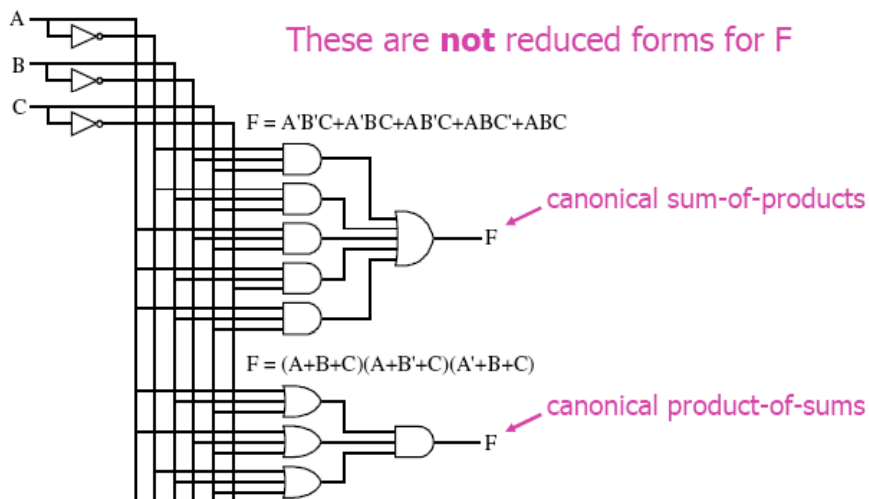Canonical implementations of $F = AB + C$



CSE370, Lecture 5

9

Conversion between canonical forms

- ◆ Minterm to maxterm
 - Use maxterms that aren't in minterm expansion
 - $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- ◆ Maxterm to minterm
 - Use minterms that aren't in maxterm expansion
 - $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- ◆ Minterm of F to minterm of F'
 - Use minterms that don't appear
 - $F(A,B,C) = \sum m(1,3,5,6,7) \quad F'(A,B,C) = \sum m(0,2,4)$
- ◆ Maxterm of F to maxterm of F'
 - Use maxterms that don't appear
 - $F(A,B,C) = \prod M(0,2,4) \quad F'(A,B,C) = \prod M(1,3,5,6,7)$

CSE370, Lecture 5


10

SOP, POS, and de Morgan's theorem

- ◆ Sum-of-products
 - $F' = A'B'C' + A'BC' + AB'C'$
- ◆ Apply de Morgan's to get POS
 - $(F')' = (A'B'C' + A'BC' + AB'C')'$
 - $F = (A+B+C)(A+B'+C)(A'+B+C)$
- ◆ Product-of-sums
 - $F' = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C)(A'+B'+C')$
- ◆ Apply de Morgan's to get SOP
 - $(F')' = ((A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C)(A'+B'+C'))'$
 - $F = A'B'C + A'BC + AB'C + ABC' + ABC$

NAND/NOR more common/efficient

 - ◆ CMOS logic gates are more common and efficient in the inverted forms
 - NAND, NOR, NOT
 - Even though Canonical forms discussed so far used AND/OR, NAND/NOR preferred for real hardware implementation



X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

NAND and NOR (truth table)

$(X + Y)' = X' \cdot Y'$
 NOR is equivalent to AND
 with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
 NAND is equivalent to OR
 with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0


NAND and NOR (logic gates)

◆ de Morgan's

- Standard form: $A'B' = (A + B)'$ $A' + B' = (AB)'$
- Inverted: $A + B = (A'B)'$ $(AB) = (A' + B')$

- AND with complemented inputs \equiv NOR
- OR with complemented inputs \equiv NAND
- OR \equiv NAND with complemented inputs
- AND \equiv NOR with complemented inputs

pushing
the
bubble

 

Converting to use NAND/NOR



- ◆ Introduce inversions ("bubbles")

- Introduce bubbles in pairs
 - ☛ Conserve inversions
 - ☛ Do not alter logic function

- ◆ Example

- AND/OR to NAND/NAND

 
 
$$\begin{aligned}
 Z &= AB + CD \\
 &= (A'+B')'+(C'+D)' \\
 &= [(A'+B')(C'+D)]' \\
 &= [(AB)'(CD)']
 \end{aligned}$$



Converting to use NAND/NOR (con't)


- ◆ Example: AND/OR network to NOR/NOR
  
$$\begin{aligned}
 Z &= AB+CD \\
 &= (A'+B')'+(C'+D)' \\
 &= [(A'+B')+(C'+D)]' \\
 &= \{[(A'+B')+(C'+D)]'\}'
 \end{aligned}$$



Converting to use NAND/NOR (con't)

- ◆ Example: OR/AND to NAND/NAND

 

Converting to use NAND/NOR(con't)

- ◆ Example: OR/AND to NOR/NOR

