

## Lecture 17

---

### ◆ Logistics

- HW6 due today, HW7 out last Monday --- due on Monday
- Midterm review Tuesday 4:15pm Room TBA

### ◆ Last lecture

- Introduction to finite state machines
- Counters as finite state machines

### ◆ Today

- Finish counter design
- More complex finite-state machines
- Introduction of Moore and Mealy machines

## Review: Counter design procedure

---


1. Draw a state diagram
2. Draw a state-transition table
3. Encode the next-state functions
  - Minimize the logic using k-maps
4. Implement the design

*Example: A 5-state counter*

## Example: A 5-state counter

- ◆ Counter repeats 5 states in sequence
  - Sequence is 000, 010, 011, 101, 110, 000 (not binary)

Step 1: State diagram

 

Step 2: State transition table  
Assume D flip-flops

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	-	-	-
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	-	-	-

## 5-state counter (con't)

Step 3: Encode the next state functions

<u>C+</u>	<u>C</u>										
<table border="1" style="border-collapse: collapse; text-align: center;"> <tr> <td style="border: none;"></td> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td style="border: none; text-align: right;">A</td> <td>X</td> <td>1</td> <td>X</td> <td>1</td> </tr> </table>		0	0	0	X	A	X	1	X	1	
	0	0	0	X							
A	X	1	X	1							
$C+ = A$											


<u>B+</u>	<u>C</u>										
<table border="1" style="border-collapse: collapse; text-align: center;"> <tr> <td style="border: none;"></td> <td>1</td> <td>1</td> <td>0</td> <td>X</td> </tr> <tr> <td style="border: none; text-align: right;">A</td> <td>X</td> <td>0</td> <td>X</td> <td>1</td> </tr> </table>		1	1	0	X	A	X	0	X	1	
	1	1	0	X							
A	X	0	X	1							
$B+ = B' + A'C'$											

<u>A+</u>	<u>C</u>										
<table border="1" style="border-collapse: collapse; text-align: center;"> <tr> <td style="border: none;"></td> <td>0</td> <td>1</td> <td>0</td> <td>X</td> </tr> <tr> <td style="border: none; text-align: right;">A</td> <td>X</td> <td>1</td> <td>X</td> <td>0</td> </tr> </table>		0	1	0	X	A	X	1	X	0	
	0	1	0	X							
A	X	1	X	0							
$A+ = BC'$											

## 5-state counter (con't)

---

### Step 4: Implement the design

 


## 5-state counter (con't)

---
 
### ◆ Is our design robust?

- What if the counter starts in a 111 state?

Does our counter get stuck in invalid states???



## 5-state counter (con't)

- ◆ Back-annotate our design to check it

[Fill in state transition table](#)


[Draw state diagram](#)

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

$$A+ = BC'$$

$$B+ = B' + A'C'$$

$$C+ = A$$

 

## Self-starting counters

- ◆ Invalid states should **always** transition to valid states
  - Assures startup
  - Assures bit-error tolerance
- ◆ Design your counters to be self-starting
  - Draw **all** states in the state diagram
  - Fill in the **entire** state-transition table
  - May limit your ability to exploit don't cares
    - ☛ Choose startup transitions that minimize the logic

## Finite state machines: more than counters

---

- ◆ FSM: A system that visits a **finite** number of logically distinct states
- ◆ Counters are simple FSMs
  - Outputs and states are identical
  - Visit states in a fixed sequence
- ◆ FSMs are typically more complex than counters
  - Outputs can depend on current state and on inputs
  - State sequencing depends on current state and on inputs

## FSM design

---


- Counter-design procedure
  1. State diagram
  2. State-transition table
  3. Next-state logic minimization
  4. Implement the design
- FSM-design procedure
  1. State diagram
  2. state-transition table
  3. State minimization
  4. State encoding
  5. Next-state logic minimization
  6. Implement the design

## Example: A vending machine


- ◆ 15 cents for a cup of coffee
- ◆ Doesn't take pennies or quarters
- ◆ Doesn't provide any change

- **FSM-design procedure**

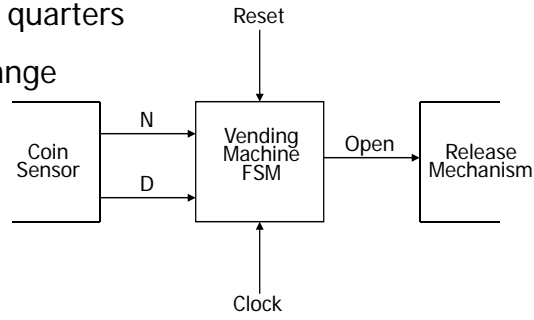1. State diagram
2. state-transition table
3. State minimization
4. State encoding
5. Next-state logic minimization
6. Implement the design



## A vending machine: state diagram

 


## A vending machine: State transition table

present state	inputs		next state	output open
	D	N		
S0	0	0	S0	0
	0	1	S1	0
	1	0	S2	0
	1	1	--	--
S1	0	0	S1	0
	0	1	S3	0
	1	0	S4	1
	1	1	--	--
S2	0	0	S2	0
	0	1	S5	1
	1	0	S6	1
	1	1	--	--
S3	0	0	S3	0
	0	1	S7	1
	1	0	S8	1
	1	1	--	--
S4	--	--	S4	1
S5	--	--	S5	1
S6	--	--	S6	1
S7	--	--	S7	1
S8	--	--	S8	1

CSE370, Lecture 17

13

## A vending machine: State minimization

 

present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	--	--
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	--	--
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	--	--
15¢	--	--	15¢	1

symbolic state table


CSE370, Lecture 17

14

## A vending machine: State encoding

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
1	1	1	1	-	-	-
		-	-	1	1	1

## A vending machine: Logic minimization

 


$$D1 = Q1 + D + Q0 N$$

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$



## A vending machine: Implementation

 


CSE370, Lecture 17

17
 
## Generalized FSM model

- ◆ State variables (state vector) holds circuit state
  - Stored in registers
- ◆ Combinational logic computes next state and outputs
  - Next state is a function of current state and inputs
  - Outputs are functions of
    - ✦ Current state (Moore machine)
    - ✦ Current state and inputs (Mealy machine)



CSE370, Lecture 17

18