

## Lecture 19

---

### ◆ Logistics

- HW7 due now
- A few days off before HW8 kicks in
- Midterm review session tomorrow 4:15 EEB125
- Midterm 2 in class (45min long, starts at 10:35am)

### ◆ Last lecture

- Moore and Mealy machines

### ◆ Today


- A bigger example: Hungry Robot Ant in Maze

## Robotic ant in a maze

---

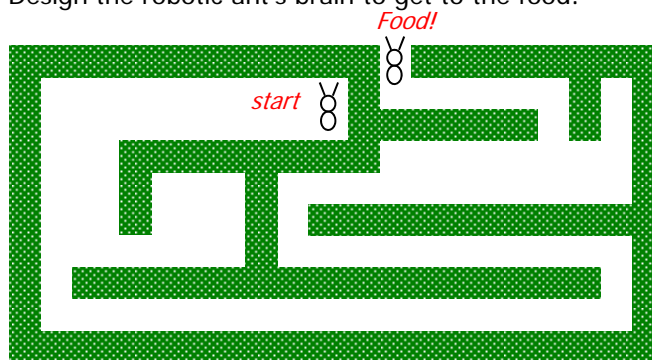
### ◆ Robot ant, physical maze

- Maze has no islands
- Corridors are wider than ant
- Design the robotic ant's brain to get to the food!


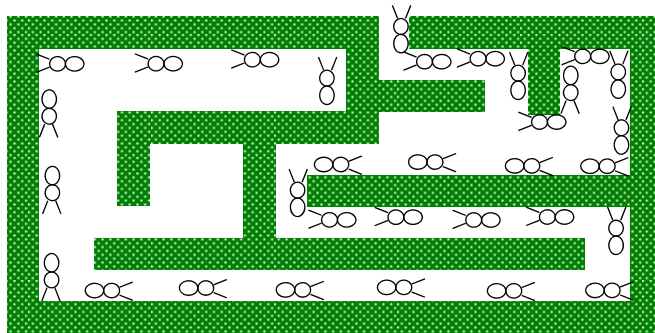
## Robot ant specifics

- ◆ Sensors: L and R antennae, 1 if touching wall
- ◆ Actuators: F - forward step, TL/TR - turn left/right
- ◆ Goal: find way out of maze to get to food.
- ◆ Strategy: keep the wall on the right




CSE370, Lecture 19

3

## Example: ant brain (special case 1)

- ◆ Left (L) Antenna touching the wall

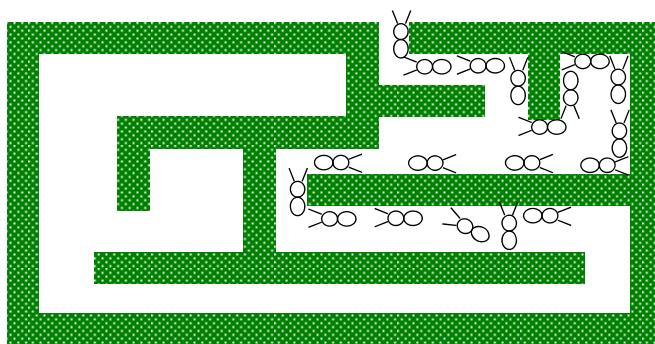


CSE370, Lecture 19

4

## Example: ant brain (special case 2)

---

### ◆ Ant Lost

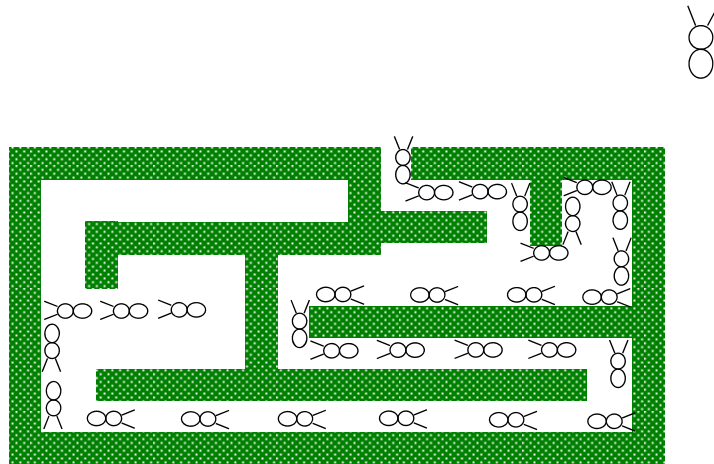


CSE370, Lecture 19

5

## Example: ant brain (special case 2)

---


### ◆ Ant Lost (another example)

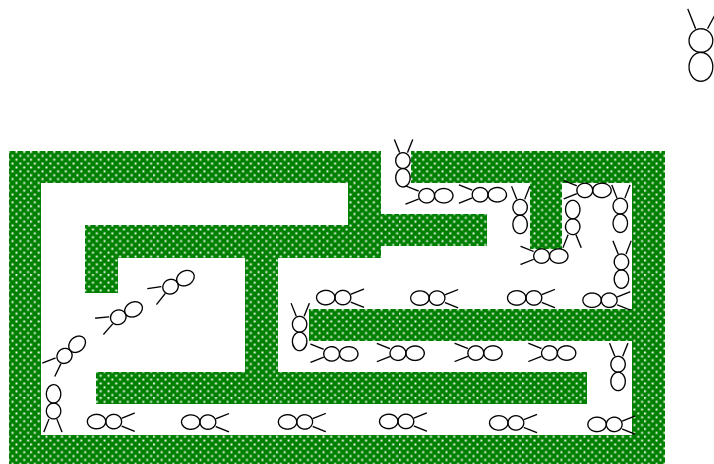

CSE370, Lecture 19

6

## Robot Ant behavior

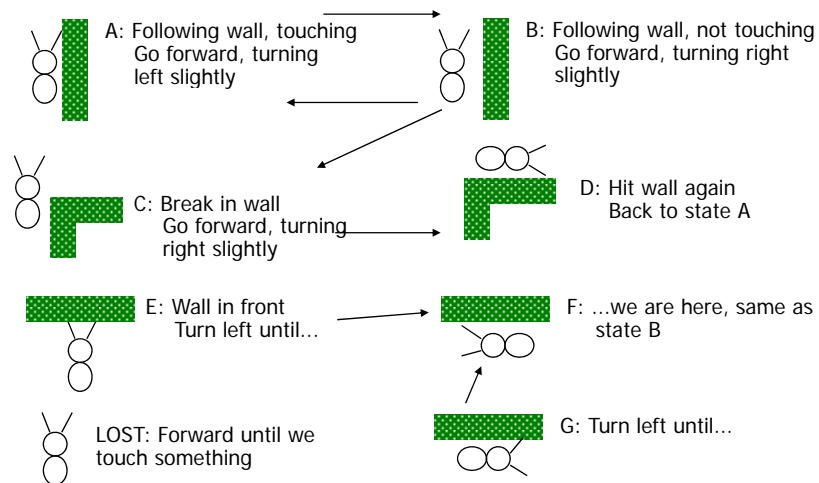

CSE370, Lecture 19

7

## Notes & strategy

### ◆ Notes

- Maze has no islands
- Corridors are wider than ant
- Don't worry about startup
- Assume a Moore machine
- Assume D flip-flops

### ◆ Strategy

- Keep the wall on the right

CSE370, Lecture 19

8


## Design the ant-brain FSM

---

1. State diagram
2. State-transition table
3. State minimization
4. State encoding
5. Next-state logic minimization
6. Implement the design

## Robot Ant behavior

---

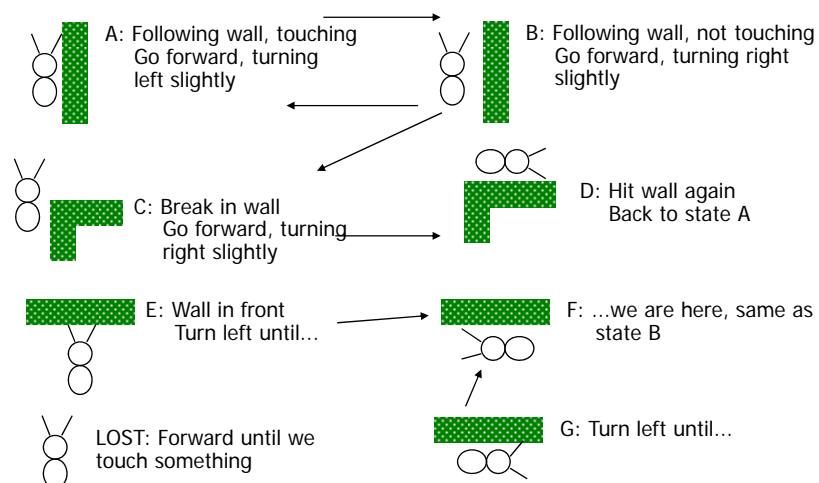

## Notations

---

### ◆ Sensors on L and R antennae


- Sensor = "1" if touching wall; "0" if not touching wall
  - ☒ L'R' ≡ no wall
  - ☒ L'R ≡ wall on right
  - ☒ LR' ≡ wall on left
  - ☒ LR ≡ wall in front

### ◆ Movement

- F ≡ forward one step
- TL ≡ turn left slightly
- TR ≡ turn right slightly

## 1. State Diagram


---

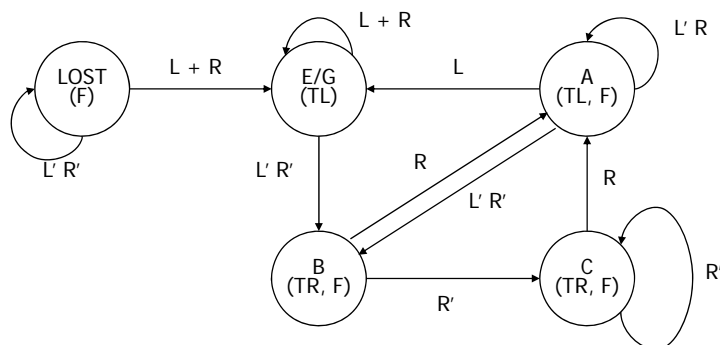

## 2. State Transition Table


◆ Using symbolic states and outputs

state	L	R	next state	outputs
LOST	0	0	LOST	F
LOST	-	1	E/G	F
LOST	1	-	E/G	F
E/G	0	0	B	TL
E/G	-	1	E/G	TL
E/G	1	-	E/G	TL
B	-	0	C	TR, F
B	-	1	A	TR, F
A	0	0	B	TL, F
A	0	1	A	TL, F
A	1	-	E/G	TL, F
C	-	0	C	TR, F
C	-	1	A	TR, F

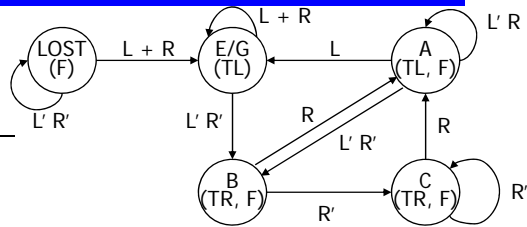


## 3. State minimization

◆ Any equivalent states?

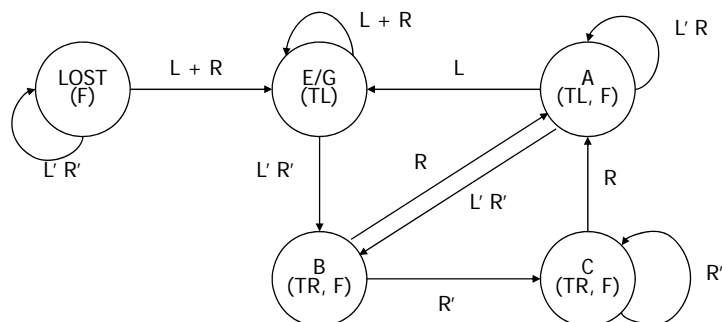

Sure! Now you can represent states with 2 bits

---

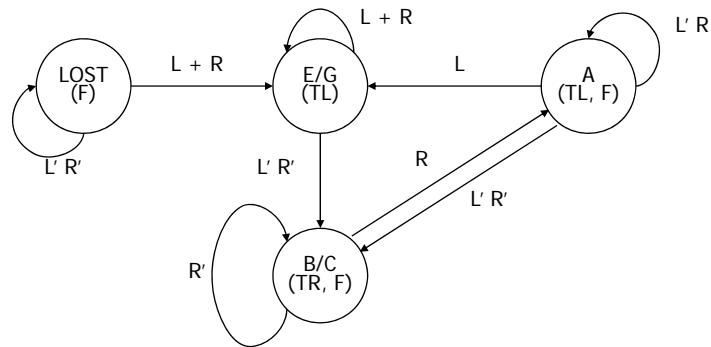

## 4. State encoding

---

state	L	R	next state	outputs	state X,Y	inputs L,R	next state X+,Y+	F	TR	TL
LOST	0	0	LOST	F	00	00	00	1	0	0
LOST	-	1	E/G	F	00	-1	01	1	0	0
LOST	1	-	E/G	F	00	1-	01	1	0	0
E/G	0	0	B/C	TL	01	00	11	0	0	1
E/G	0	1	E/G	TL	01	01	01	0	0	1
E/G	1	-	E/G	TL	01	1-	01	0	0	1
A	0	0	B	TL, F	10	00	11	1	0	1
A	-	1	A	TL, F	10	-1	10	1	0	1
A	1	-	E/G	TL, F	10	1-	01	1	0	1
B/C	-	0	B/C	TR, F	11	-0	11	1	1	0
B/C	-	1	A	TR, F	11	-1	10	1	1	0



## 5. Next state logic minimization

state X,Y	inputs		next state		outputs		
	L	R	X',Y'	F	TR	TL	
00	0	0	00	1	0	0	
00	-	1	01	1	0	0	
00	1	-	01	1	0	0	
01	0	0	11	0	0	1	
01	0	1	01	0	0	1	
01	1	-	01	0	0	1	
10	0	0	11	1	0	1	
10	-	1	10	1	0	1	
10	1	-	01	1	0	1	
11	-	0	11	1	1	0	
11	-	1	10	1	1	0	

X+

0	1	1	1
0	0	1	1
0	0	1	0
0	0	1	0

Y

Y+

0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	1

Y

F

1	0	1	1
1	0	1	1
1	0	1	1
1	0	1	1

Y

TR

0	0	1	0
0	0	1	0
0	0	1	0
0	0	1	0

Y


TL

0	1	0	1
0	1	0	1
0	1	0	1
0	1	0	1

Y
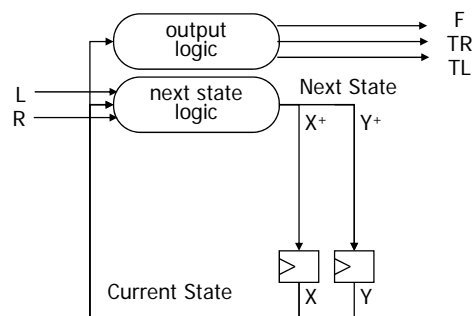
## 6. Circuit Implementation


- ◆ Outputs are a function of the current state only - Moore machine


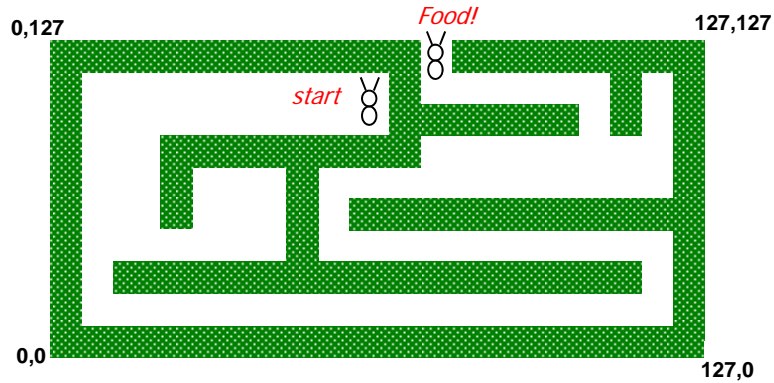
## Extra credit (worth 15pts equivalent in a midterm)

Design the robotic ant's brain with virtual maze representation

- Due last day in class, Friday, June 6; printouts only
- Graded on clarity and completeness of explanation
- No questions will be answered



CSE370, Lecture 19

19

## The maze

### ◆ Virtual maze

- $128 \times 128$  grid
  - ↳ Stored in memory
  - ↳ 16384 8-bit words
- $YX$  is maze addresses
  - ↳  $X$  is the ant's horizontal position (7 bits)
  - ↳  $Y$  is the ant's vertical position (7 bits)
- Each memory location says
  - ↳ 00000001  $\equiv$  No wall
  - ↳ 00000010  $\equiv$  North wall
  - ↳ 00000100  $\equiv$  West wall
  - ↳ 00001000  $\equiv$  South wall
  - ↳ 00010000  $\equiv$  East wall
  - ↳ 00100000  $\equiv$  Exit

Can have multiple walls  
Example: 00001100  
 $\Rightarrow$  Walls on South and East


CSE370, Lecture 19

20


## Design of different components

---

Predesigned:

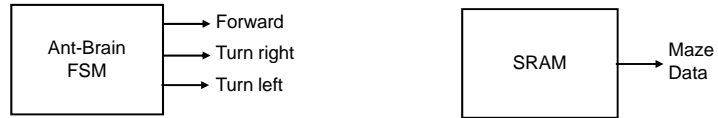

Submit the designs for:

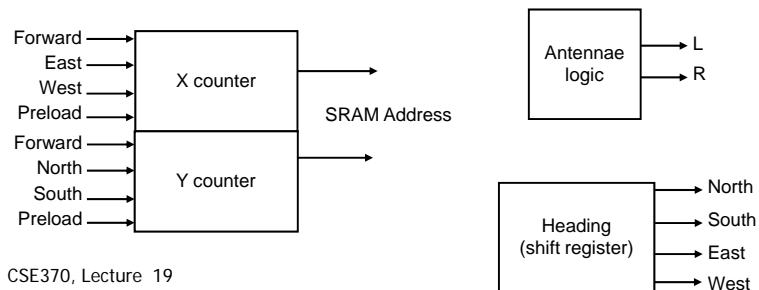

CSE370, Lecture 19

21

## Recommendations

---

- ◆ Memory controller
  - Move horizontally: Increment or decrement  $X$
  - Move vertically: Increment or decrement  $Y$
- ◆ Shift register for heading
  - N: 0001
  - W: 0010
  - S: 0100
  - E: 1000
  - Rotate right when ant turns right
  - Rotate left when ant turns left
- ◆ Combinational logic for antennae logic

CSE370, Lecture 19

22