

Lecture 4

- Logic gates and truth tables
- Implementing logic functions
- Canonical forms
 - Sum-of-products
 - Product-of-sums

1

Logic gates and truth tables

■ AND	$X \cdot Y$	XY	<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	X	Y	Z	0	0	0	0	1	0	1	0	0	1	1	1
X	Y	Z																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
■ OR	$X + Y$		<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	X	Y	Z	0	0	0	0	1	1	1	0	1	1	1	1
X	Y	Z																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
■ NOT	X'	\bar{X}	<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>X</th><th>Y</th></tr> </thead> <tbody> <tr> <td>0</td><td>1</td></tr> <tr> <td>1</td><td>0</td></tr> </tbody> </table>	X	Y	0	1	1	0									
X	Y																	
0	1																	
1	0																	

2

Logic gates and truth tables

■ NAND	$\overline{X \cdot Y}$	\overline{XY}	<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	X	Y	Z	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	Z																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
■ NOR	$\overline{X + Y}$		<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>X</th><th>Y</th><th>Z</th> </tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>1</td> </tr> <tr> <td>0</td><td>1</td><td>0</td> </tr> <tr> <td>1</td><td>0</td><td>0</td> </tr> <tr> <td>1</td><td>1</td><td>0</td> </tr> </tbody> </table>	X	Y	Z	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	Z																
0	0	1																
0	1	0																
1	0	0																
1	1	0																


3

Logic gates and truth tables

■ XOR	$X \oplus Y$	<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	X	Y	Z	0	0	0	0	1	1	1	0	1	1	1	0
X	Y	Z															
0	0	0															
0	1	1															
1	0	1															
1	1	0															
■ XNOR	$\overline{X \oplus Y}$	<table border="1" style="display: inline-table; vertical-align: middle;"> <thead> <tr> <th>X</th> <th>Y</th> <th>Z</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	X	Y	Z	0	0	1	0	1	0	1	0	0	1	1	1
X	Y	Z															
0	0	1															
0	1	0															
1	0	0															
1	1	1															

4

Realizing Boolean formulas

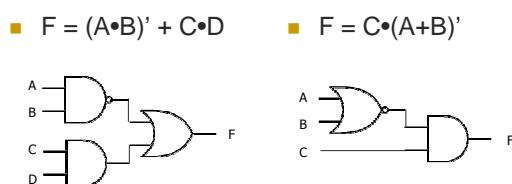

5

Realizing truth tables


- Given a truth table
 1. Write the Boolean expression
 2. Minimize the Boolean expression
 3. Draw as gates

6

Example

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1
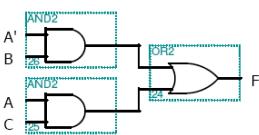
$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$



7

Example: Binary full adder

- 1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned} \text{Sum} &= A'B'Cin + A'BCin' + AB'Cin' + ABCin \\ \text{Cout} &= A'BCin + AB'Cin + ABCin' + ABCin \end{aligned}$$


Both Sum and Cout can be minimized.

8

Full adder: Sum

Before Boolean minimization
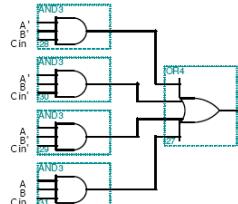
$$\begin{aligned} \text{Sum} &= A'B'Cin + A'BCin' \\ &\quad + AB'Cin' + ABCin \end{aligned}$$



After Boolean minimization

$$\text{Sum} = (A \oplus B) \oplus Cin$$




9

Full adder: Carry-out


Before Boolean minimization
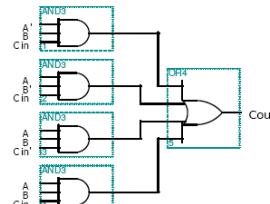
$$\begin{aligned} \text{Cout} &= A'BCin + AB'Cin \\ &\quad + ABCin' + ABCin \end{aligned}$$




After Boolean minimization

$$\text{Cout} = BCin + ACin + AB$$

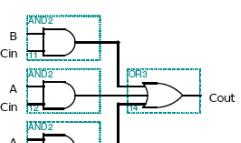

10

Preview: 2-bit ripple-carry adder

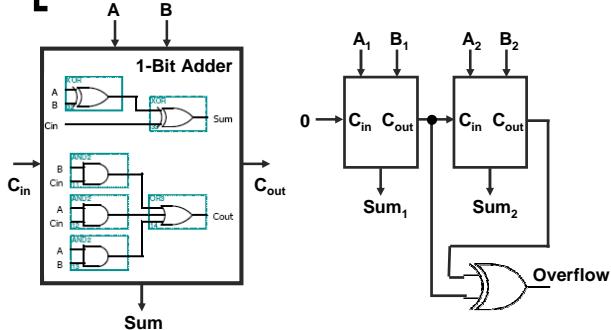


11

Many possible mappings

- Many ways to map expressions to gates

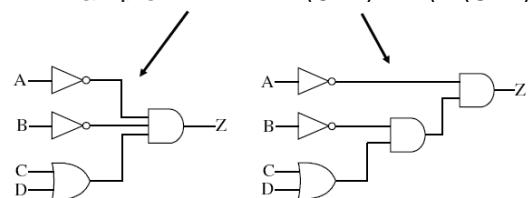- Example: $Z = \bar{A} \cdot \bar{B} \cdot (C + D) = \bar{A} \cdot (\bar{B} \cdot (C + D))$



?

What is the optimal realization?

- We use the axioms and theorems of Boolean algebra to “optimize” our designs
- Design goals vary
 - Reduce the number of gates?
 - Reduce the number of gate inputs?
 - Reduce the number of cascaded levels of gates?

13

What is the optimal realization?

- How do we explore the tradeoffs?
 - Logic minimization: Reduce number of gates and complexity
 - Logic optimization: Maximize speed and/or minimize power
 - CAD tools

14

Canonical forms

- Canonical forms
 - Standard forms for Boolean expressions
 - Derived from truth table
 - Generally not the simplest forms (can be minimized)
- Two canonical forms
 - Sum-of-products (minterms)
 - Product-of-sums (maxterms)

15

Sum-of-products (SOP)

- Also called *disjunctive normal form* (DNF) or *minterm expansion*

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = A'B'C + A'BC + AB'C + ABC' + ABC$
 $F' = A'B'C' + A'BC' + AB'C'$

16

Minterms

- Variables appear exactly once in each minterm in true or inverted form (but not both)

A	B	C	minterms
0	0	0	$A'B'C$ m0
0	0	1	$A'B'C$ m1
0	1	0	$A'BC$ m2
0	1	1	$A'BC$ m3
1	0	0	$AB'C$ m4
1	0	1	$AB'C$ m5
1	1	0	ABC' m6
1	1	1	ABC m7

short-hand notation

17

Product-of-sums (POS)

- Also called *conjunctive normal form* (CNF) or *maxterm expansion*

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = (A + B + C)(A + B' + C)(A' + B + C)$
 $F' = (A + B + C')(A + B' + C')(A' + B + C)(A' + B' + C')$

18

Maxterms

- Variables appear exactly once in each maxterm in true or inverted form (but not both)


A	B	C	maxterms
0	0	0	$A+B+C$ M0
0	0	1	$A+B+C'$ M1
0	1	0	$A+B'+C$ M2
0	1	1	$A+B'+C'$ M3
1	0	0	$A'+B+C$ M4
1	0	1	$A'+B+C'$ M5
1	1	0	$A'+B'+C$ M6
1	1	1	$A'+B'+C'$ M7

short-hand notation

$$\begin{aligned} F \text{ in canonical form:} \\ F(A,B,C) &= \prod M(0,2,4) \\ &= M0 \cdot M2 \cdot M4 \\ &= (A+B+C)(A+B'+C)(A'+B+C) \end{aligned}$$

19

Example: $F = AB+C$

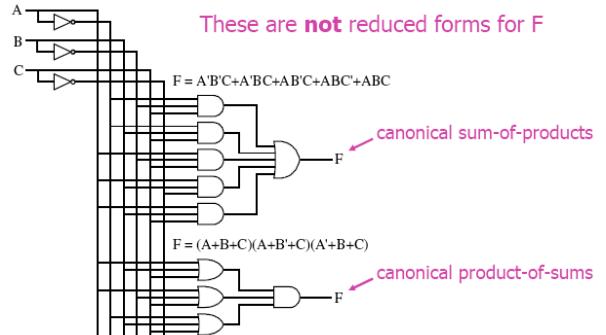

From SOP to POS and back

- Minterm to maxterm
 - Use maxterms that aren't in minterm expansion
 - $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm
 - Use minterms that aren't in maxterm expansion
 - $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$

21

From SOP to POS and back

- Minterm of F to minterm of F'
 - Use minterms that don't appear
 - $F(A,B,C) = \sum m(1,3,5,6,7) \quad F' = \sum m(0,2,4)$
- Maxterm of F to maxterm of F'
 - Use maxterms that don't appear
 - $F(A,B,C) = \prod M(0,2,4) \quad F' = \prod M(1,3,5,6,7)$

22

SOP, POS, and DeMorgan's

- Sum-of-products
 - $F' = A'B'C' + A'BC' + AB'C'$
- Apply DeMorgan's to get POS
 - $(F')' = ((A'B'C') + (A'BC') + (AB'C'))'$
 - $F = (A+B+C)(A+B'+C)(A'+B+C)$

23

SOP, POS, and DeMorgan's

- Product-of-sums
 - $F' = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C')$
- Apply DeMorgan's to get SOP
 - $(F')' = ((A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C'))'$
 - $F = A'B'C + A'BC + AB'C + ABC$

24