


Lecture 12

- Time/space trade offs
- Adders

1

Time vs. speed: Linear chain


- 8-input OR function with 2-input gates

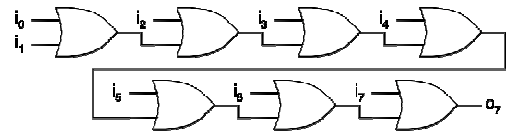

Gates: 7
Max delay: 7

2

Time vs. speed: Tree

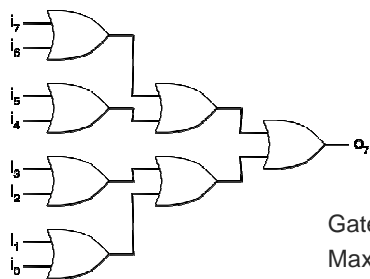


Gates: 7
Max delay: 3

3

Modified circuit

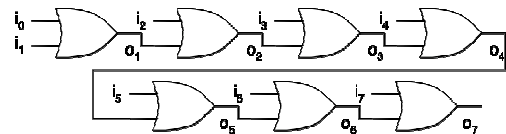
- Calculate the OR of the first 2 inputs, the OR of the first 3, and so on, up to the OR of all 8



Gates: 7
Max delay: 7

4

Parallel version

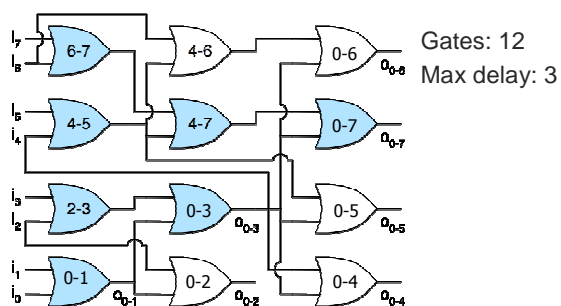

Gates: 12
Max delay: 3

5

Binary half adder

- 1-bit half adder
 - Computes sum, carry-out
 - No carry-in
 - Sum = $A'B + AB' = A \text{ xor } B$
 - Cout = AB

A	B	S	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



6

Binary full adder

1-bit full adder

- Computes sum, carry-out
 - Carry-in allows cascaded adders
- Sum = Cin xor A xor B
- Cout = ACin + BCin + AB

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



Full adder: Using 2 half adders


Multilevel logic

- Slower
- Fewer gates: 5 vs. 6
 - 2 XORs, 2 ANDs, 1 OR


A	B	C _{in}	S	C _{out}	C _{out}
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1

$$\begin{aligned} \text{Sum} &= (A \oplus B) \oplus \text{Cin} \\ \text{Cout} &= \text{ACin} + \text{BCin} + \text{AB} \\ &= (A \oplus B)\text{Cin} + \text{AB} \end{aligned} \quad \left. \vphantom{\begin{aligned} \text{Sum} \\ \text{Cout} \end{aligned}} \right\} \text{Distributive law?}$$

Full adder: Using 2 half adders

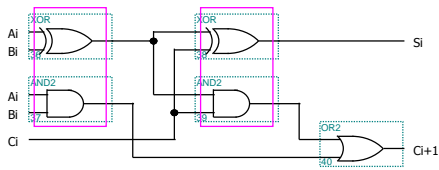


4-bit ripple-carry adder

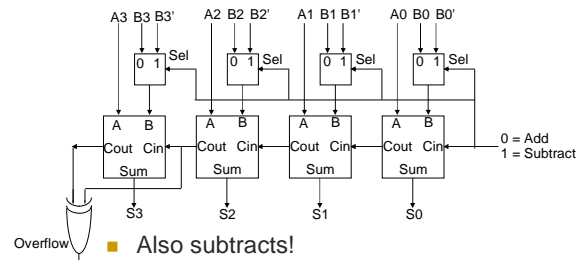

- Also subtracts!
 - Twos complement: $A - B = A + (-B) = A + B' + 1$

Problem: Ripple-carry delay


Carry propagation limits adder speed

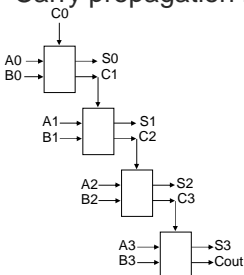

0111
+ 0001

1000


Ripple-carry delay

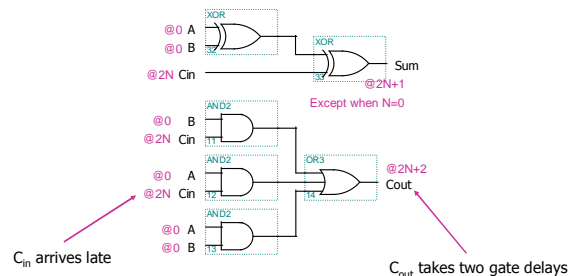

C_{in} arrives late

C_{out} takes two gate delays


Ripple-carry delay

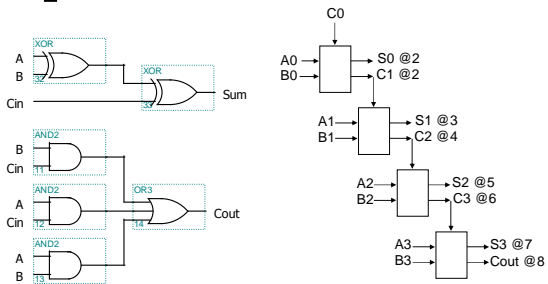

13

Can we be more clever?

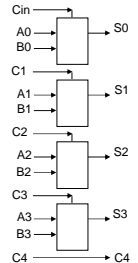- Let's compute all the carries in parallel
 - Derive carries from the data inputs
 - Not from intermediate carries
 - Use two-level logic
 - Compute all sums in parallel
 - How do we do that???



14

Speeding up the adder

- Need to find a way to "predict" Cout for all bits without knowing what Cin is

Cout is always 0

$$\begin{array}{r} 0 \\ + 0 \\ \hline \end{array}$$
 Predict Cout

Cout is always 1

$$\begin{array}{r} 1 \\ + 1 \\ \hline \end{array}$$
 Predict Cout

Call this GENERATE

Cout is 0 if Cin is 0
 Cout is 1 if Cin is 1

$$\begin{array}{r} 0 \\ + 1 \\ \hline \end{array}$$
 Predict Cout

Cout is 0 if Cin is 0
 Cout is 1 if Cin is 1

$$\begin{array}{r} 1 \\ + 0 \\ \hline \end{array}$$
 Predict Cout

Call this PROPAGATE

15


Lookahead logic: Pi and Gi

- Step 1: Getting Pi and Gi
 - Carry generate: $G_i = A_i B_i$
 - Generate carry when $A = B = 1$
 - Carry propagate: $P_i = A_i \text{ xor } B_i$
 - Propagate carry-in to carry-out when $(A \text{ xor } B) = 1$

16

Lookahead logic: Sum and carry

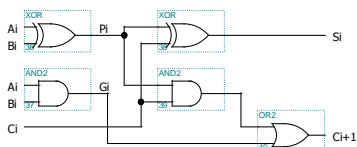- Step 2: Calculate Sum and Cout
 - $S_i = A_i \text{ xor } B_i \text{ xor } C_i = P_i \text{ xor } C_i$
 - $C_{i+1} = A_i B_i + C_i(A_i \text{ xor } B_i) = G_i + C_i P_i$



17


Lookahead logic: Carries

- Step 3: Express all carries in terms of C0, G, and P
 - Derive intermediate results directly from inputs rather than from carries
 - Allows "sum" computations to proceed in parallel

$$\begin{aligned} C_1 &= G_0 + P_0 C_0 \\ C_2 &= G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0 \\ C_3 &= G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \\ C_4 &= G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$


18

Lookahead logic: Carries

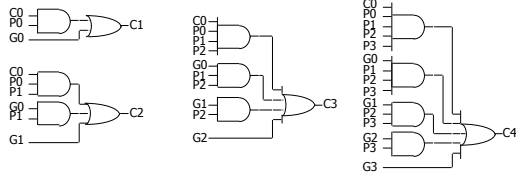


Logic complexity increases with adder size

Lookahead logic: Sum

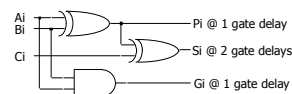

Lookahead logic timing

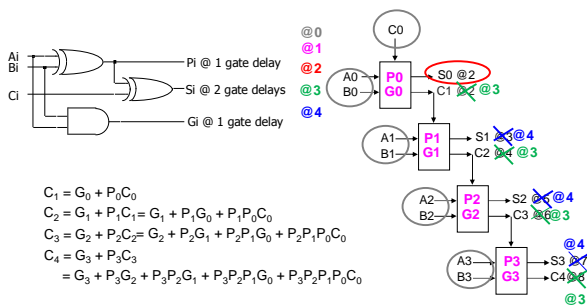

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

$$C_4 = G_3 + P_3C_3 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0$$

Summary: Lookahead logic

- Compute all the carries in parallel
 - Derive carries from data inputs not from intermediate carries
 - Compute all sums in parallel using two-level logic
- Cascade simple adders to make large adders
- Speed improvement
- Complex combinational logic

