

Lecture 9

- ◆ Logistics
 - HW3 due Wednesday
 - Lab4 going on this week
 - Midterm 1 Friday, Review Session Thursday 4:30, place TBA
 - material up to end of last lecture

- ◆ Last lecture
 - K-map design examples
 - Multiplexers

- ◆ Today
 - Demultiplexers
 - Programmable Logic Devices
 - PLAs
 - PALs

CSE370, Lecture 9

1

The "WHY" slide

- Demultiplexers
 - Natural complement to multiplexers

- Programmable Logic Devices (PLDs)
 - Often you want to have a look up table of functions stored away somewhere in your device. Rather than having specific circuits build every time, it would be nice to have a "general-purpose" structure that could be "programmed" for a specific usage. PLDs have a generic structure that allows any function to be expressed and stored.

- And it is nice if it is reprogrammable. Some PLDs are reprogrammable (like your memory sticks).

CSE370, Lecture 9

2


Switching-network logic blocks

- ◆ Multiplexer (MUX)

- Routes one of many inputs to a single output
- Also called a *selector*

- ◆ Demultiplexer (DEMUX)

 - Routes a single input to one of many outputs
- Also called a *decoder*




We construct these devices from:
 • logic gates
 • networks of transistor switches

CSE370, Lecture 9

3

Logic sharing with MUX/DEMUX

 

CSE370, Lecture 9


4

Multiplexers

- ◆ 2:1 mux: $Z = S_0'In_0 + S_0In_1$

- ◆ 4:1 mux: $Z = S_1'S_0'In_0 + S_1'S_0In_1 + S_1S_0'In_2 + S_1S_0In_3$

 - ◆ 8:1 mux: $Z = S_2'S_1'S_0'In_0 + S_2'S_1S_0In_1 + \dots$



CSE370, Lecture 9

5


Multiplexers as general-purpose logic

- ◆ Implementing a $2^{n-1}:1$ mux as a function of n variables

- ($n-1$) mux control variables $S_0 - S_{n-2}$
- One data variable S_{n-1}
- Four possible values for each data input: 0, 1, S_{n-1} , S_{n-1}'
- Example: $F(A,B,C,D)$ implemented using an 8:1 mux

A	B	AB	00	01	11	10
C	D		00	01	11	10
00	00	00	1	0	1	1
01	01	01	1	0	0	0
11	11	11	0	1	0	1
10	10	10	0	1	1	0

 Choose A,B,C as control variables
 Choose D as a data variable



CSE370, Lecture 9

6

Demultiplexers (DEMUX)

Basic concept

- Single data input; n control inputs ("selects"); 2^n outputs
- Single input connects to one of 2^n outputs
- "Selects" decide which output is connected to the input
- When used as a decoder, the input is called an "enable" (G)

1:2 Decoder:
 $Out_0 = G \cdot S'$
 $Out_1 = G \cdot S$

2:4 Decoder:
 $Out_0 = G \cdot S_1 \cdot S_0'$
 $Out_1 = G \cdot S_1 \cdot S_0$
 $Out_2 = G \cdot S_1 \cdot S_0'$
 $Out_3 = G \cdot S_1 \cdot S_0$


3:8 Decoder:
 $Out_0 = G \cdot S_2' \cdot S_1' \cdot S_0'$
 $Out_1 = G \cdot S_2' \cdot S_1' \cdot S_0$
 $Out_2 = G \cdot S_2' \cdot S_1 \cdot S_0'$
 $Out_3 = G \cdot S_2' \cdot S_1 \cdot S_0$
 $Out_4 = G \cdot S_2 \cdot S_1' \cdot S_0'$
 $Out_5 = G \cdot S_2 \cdot S_1' \cdot S_0$
 $Out_6 = G \cdot S_2 \cdot S_1 \cdot S_0'$
 $Out_7 = G \cdot S_2 \cdot S_1 \cdot S_0$

CSE370, Lecture 9


7

Logic-gate implementation of demultiplexers

1:2 demux

 

2:4 demux

 


CSE370, Lecture 9

8

Demultiplexers as general-purpose logic

A $n:2^n$ demux can implement any function of n variables

 - DEMUX as logic building block
- Use variables as select inputs
- Tie enable input to logic 1
- Sum the appropriate minterms (extra OR gate)



demultiplexer "decodes"
appropriate minterms
from the control signals

CSE370, Lecture 9

9


Demultiplexers as general-purpose logic

Example

$$F1 = A'BCD + A'B'CD + ABCD$$

$$F2 = ABC'D' + ABC$$

$$F3 = (A'+B'+C'+D')$$

 


CSE370, Lecture 9

10

Cascading demultiplexers

5:32 demux

 


CSE370, Lecture 9

11

Programmable logic (PLAs & PALs)

Concept: Large array of uncommitted AND/OR gates

 - Actually NAND/NOR gates
- You program the array by making or breaking connections
- Programmable block for sum-of-products logic




CSE370, Lecture 9

12

All two-level logic functions are available

- You "program" the wire connections

 


CSE370, Lecture 9

13

Programming the wire connections

 - Fuse: Comes connected; break unwanted connections
- Anti-fuse: Comes disconnected; make wanted connections




CSE370, Lecture 9

14

Short-hand notation


- Draw multiple wires as a single wire or bus
- \times signifies a connection

Before Programming

 

CSE370, Lecture 9

After Programming

 


15

PLA example

$$\begin{aligned} F_1 &= ABC \\ F_2 &= A + B + C \\ F_3 &= A'B'C \\ F_4 &= A' + B' + C' \\ F_5 &= A \oplus B \oplus C \\ F_6 &= A \oplus B \oplus C \end{aligned}$$

A	B	C	F1	F2	F3	F4	F5	F6
0	0	0	0	0	1	1	0	0
0	0	1	0	0	0	1	1	0
0	1	0	0	1	0	1	1	1
0	1	1	0	1	0	1	0	0
1	0	0	1	0	1	0	1	1
1	0	1	1	0	1	1	0	0
1	1	0	1	1	0	1	0	0
1	1	1	1	1	0	1	1	1


CSE370, Lecture 9

 

16

PLAs versus PALs

 
- We've been looking at PLAs
 - Fully programmable AND / OR arrays
- Programmable array logic (PAL)
 - Programmable AND array
 - OR array is prewired
 - Cheaper and faster than PLAs



CSE370, Lecture 9

17

Example: BCD to Gray code converter

 

CSE370, Lecture 9

18

Example: BCD to Gray --- Wire a PLA


Minimized functions:

$$W = A + BC + BD$$

$$X = BC'$$

$$Y = B + C$$

$$Z = A'B'C'D + BCD + AD' + B'CD'$$

 

CSE370, Lecture 9

19

Example: Wire a PAL

Minimized functions:

$$W = A + BC + BD$$


$$X = BC'$$

$$Y = B + C$$

$$Z = A'B'C'D + BCD + AD' + B'CD'$$

Fine example for the use of PAL
(because no shared AND terms)

 Many AND gates wasted, but
still faster and cheaper than PLA



20

Compare implementations for this example

- PLA:
 - No shared logic terms in this example
 - 10 decoded functions (10 AND gates)
- PAL:
 - Z requires 4 product terms
 - Need a PAL that handles 4 product terms for each output
 - 16 decoded functions (16 AND gates)
 - 6 unused AND gates
- This decoder is a good candidate for PALS
 - 10 of 16 possible inputs are decoded
 - No sharing among AND terms
- Next time an alternative
 - Read-only memory (ROM)

CSE370, Lecture 9

21

Midterm 1 Topics Covered

- ◆ Combinational logic basics
 - Binary/hex/decimal numbers
 - Ones and twos complement arithmetic
 - Truth tables
 - Boolean algebra
 - Basic logic gates
 - Schematic diagrams
 - de Morgan's theorem
 - AND/OR to NAND/NOR logic conversion
 - K-maps (up to 4 variables), logic minimization, don't cares
 - SOP, POS
 - Minterm and maxterm expansions (canonical, minimized)

CSE370, Lecture 9

22

Midterm 1 Topics Covered (continued)

- ◆ Combinational logic applications
 - Combinational design
 - Input/output encoding
 - Truth table
 - K-map
 - Boolean equations
 - Schematics
 - Multiplexers

CSE370, Lecture 9

23