

## Lecture 20

- ◆ Logistics
  - Graded HW back today
  - HW7 Due next Wednesday
  - Lab 9 starts next week (2 week lab)
- ◆ Last lecture
  - Intro to Moore and Mealy machines
- ◆ Today
  - More Moore and Mealy machines
  - A bigger FSM example: Hungry Robot Ant in Maze


## The "WHY" slide

- ◆ Bigger FSM example
  - Many things in the world are finite state machines (are we humans?) and most of them are far bigger and more complex than the examples we had so far. It is good to be able to understand and solve for a project-level FSM problem that's a lot more realistic to FSMs that you may design in industry or in grad school.


## Example: A vending machine

- ◆ 15 cents for a cup of coffee
- ◆ Doesn't take pennies or quarters
- ◆ Doesn't provide any change


Previously we had mix of Moore and Mealy

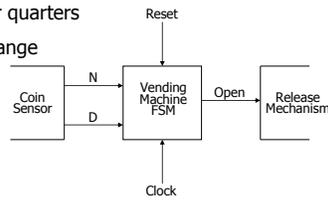

## A vending machine: Moore machine

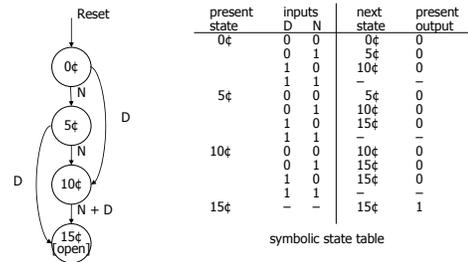

## A vending machine: Mealy machine

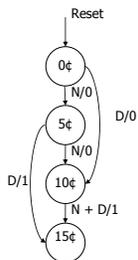


present state	inputs D N	next state	present output
0¢	0 0	0¢	0
	0 1	5¢	0
	1 0	10¢	0
5¢	0 0	5¢	0
	0 1	10¢	0
	1 0	15¢	1
10¢	0 0	10¢	0
	0 1	15¢	1
	1 0	15¢	1
15¢	- -	15¢	1

symbolic state table


## A vending machine: State encoding

Moore				Mealy			
present state	inputs D N	next state	present output	present state	inputs D N	next state	present output
Q1 Q0	D N	D1 D0		Q1 Q0	D N	D1 D0	
0 0	0 0	0 0	0	0 0	0 0	0 0	0
0 0	0 1	0 1	0	0 1	0 0	0 1	0
0 0	1 0	1 0	0	1 0	1 0	1 0	0
0 1	0 0	0 1	0	0 1	0 0	0 1	0
0 1	0 1	1 0	0	0 1	0 1	1 0	0
0 1	1 0	1 1	0	1 0	1 0	1 1	1
0 1	1 1	- -	-	1 1	1 1	- -	-
1 0	0 0	1 0	0	1 0	0 0	1 0	0
1 0	0 1	1 1	0	0 1	1 1	1 1	1
1 0	1 0	1 1	0	1 0	1 0	1 1	1
1 0	1 1	- -	-	1 1	1 1	- -	-
1 1	- -	1 1	1	1 1	- -	1 1	1

## A vending machine: Logic minimization

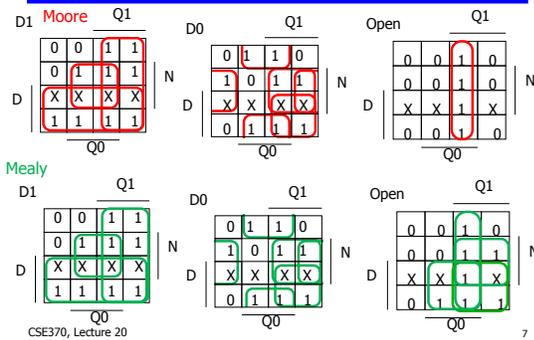


## A vending machine: Implementation

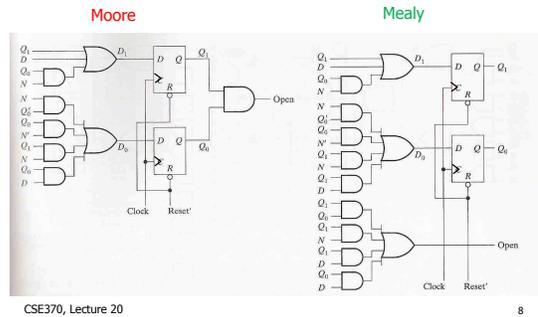
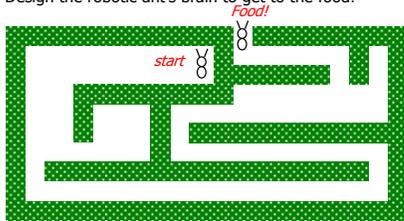
## Robotic ant in a maze

- Robot ant, physical maze
  - Maze has no islands
  - Corridors are wider than ant
  - Design the robotic ant's brain to get to the food!




CSE370, Lecture 20

9
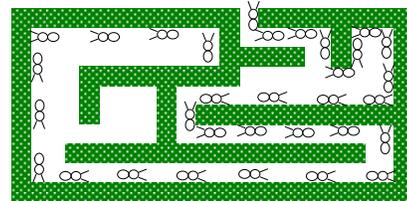
## Robot ant specifics

- Sensors: L and R antennae, 1 if touching wall
- Actuators: F - forward step, TL/TR - turn left/right
- Goal: find way out of maze to get to food.
- Strategy: keep the wall on the right




CSE370, Lecture 20

10

## Example: ant brain (special case 1)

- Left (L) Antenna touching the wall

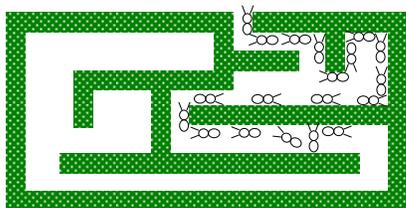


CSE370, Lecture 20

11

## Example: ant brain (special case 2)

- Ant Lost

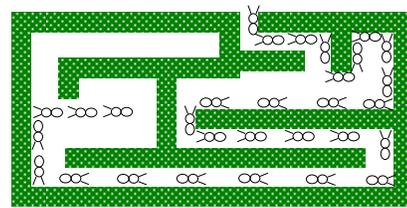


CSE370, Lecture 20

12

## Example: ant brain (special case 2)


### ◆ Ant Lost (another example)

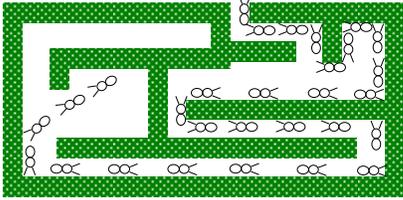

CSE370, Lecture 20

13

## Robot Ant behavior

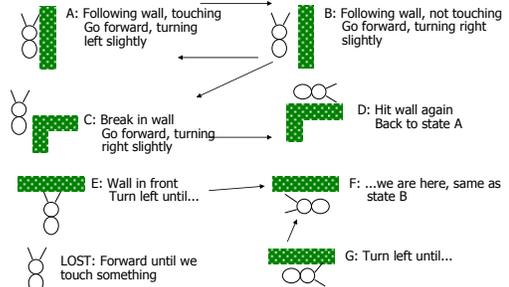

CSE370, Lecture 20

14

## Notes & strategy

### ◆ Notes

- Maze has no islands
- Corridors are wider than ant
- Don't worry about startup
- Assume a Moore machine
- Assume D flip-flops

### ◆ Strategy

- Keep the wall on the right

CSE370, Lecture 20

15

## Design the ant-brain FSM

1. State diagram
2. State-transition table
3. State minimization
4. State encoding
5. Next-state logic minimization
6. Implement the design

CSE370, Lecture 20

16

## Notations

### ◆ Sensors on L and R antennae

- Sensor = "1" if touching wall; "0" if not touching wall
  - ⇒ L'R' = no wall
  - ⇒ L'R = wall on right
  - ⇒ LR' = wall on left
  - ⇒ LR = wall in front

### ◆ Movement

- F = forward one step
- TL = turn left slightly
- TR = turn right slightly

CSE370, Lecture 20

17

## 1. State Diagram

CSE370, Lecture 20


18

## State Minimization, Encoding, and Circuit

- ◆ Next class
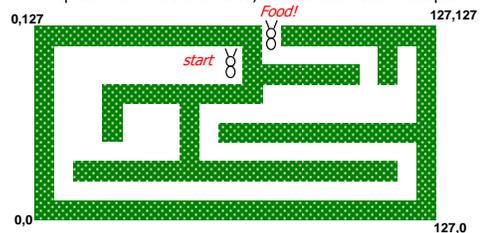
## Extra credit (worth 10pts equivalent in a midterm)

- Design the robotic ant's brain with virtual maze representation
  - Due last day in class, Friday, March 13; printouts only
  - Graded on clarity and completeness of explanation
  - No questions will be answered, no late submission accepted



## The maze

- ◆ Virtual maze
  - 128 × 128 grid
    - ↳ Stored in memory
    - ↳ 16384 8-bit words
  - $XY$  is maze addresses
    - ↳  $X$  is the ant's horizontal position (7 bits)
    - ↳  $Y$  is the ant's vertical position (7 bits)
  - Each memory location says
    - ↳ 00000001 ≡ No wall
    - ↳ 00000010 ≡ North wall
    - ↳ 00000100 ≡ West wall
    - ↳ 00001000 ≡ South wall
    - ↳ 00010000 ≡ East wall
    - ↳ 00100000 ≡ Exit


Can have multiple walls  
Example: 00001100  
⇒ Walls on South and East

## Design of different components

Predesigned:



Submit the designs for:

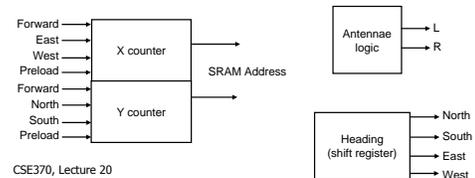

## Recommendations

- ◆ Memory controller
  - Move horizontally: Increment or decrement  $X$
  - Move vertically: Increment or decrement  $Y$
- ◆ Shift register for heading
  - N: 0001
  - W: 0010
  - S: 0100
  - E: 1000
  - Rotate right when ant turns right
  - Rotate left when ant turns left
- ◆ Combinational logic for antennae logic