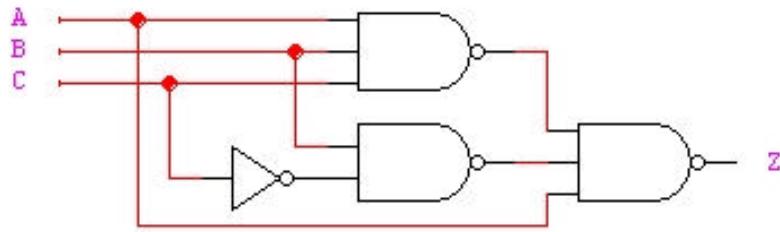


Reverse Engineering Example

Write down the Boolean expression for the following circuit:



$$F(A, B, C) =$$

Simplify the function using Boolean algebra:

Write the truth table, canonical SOP form, and minimize again using the K-map.

		AB		A	
		00	01	11	10
C	0				
	1				

B

Draw the re-implementation of the better design.

Minimize the following 5-input function using the K-maps below

$$f(A, B, C, D, E) = \sum m(0, 1, 4, 8, 9, 10, 12, 17, 18, 22, 24, 25)$$

