

Levels in Processor Design

- **Circuit design**
 - Keywords: transistors, wires etc. Results in gates, flip-flops etc.
- **Logical design**
 - Putting gates (AND, NAND, ...) and flip-flops together to build basic blocks such as registers, ALU's etc (cf. CSE 370)
- **Register transfer**
 - Describes execution of instructions by showing data flow between the basic blocks
- **Processor description (the ISA)**
- **System description**
 - Includes memory hierarchy, I/O, multiprocessing etc

10/20/2004

CSE378 Single cycle implementation.

1

Register transfer level

- Two types of components (cf. CSE 370)
 - *Combinational*: the output is a function of the input (e.g., adder)
 - *Sequential*: state is remembered (e.g., register)


10/20/2004

CSE378 Single cycle implementation.

2

Synchronous design

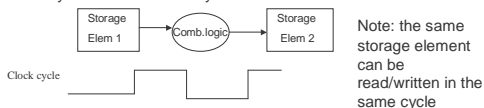
- Use of a periodic clock
 - *edge-triggered* clocking determines when signals can be read and when the output of circuits is stable
 - Values in storage elements can be updated only at clock edges
 - Clock tells when events can occur, e.g., when signals sent by control unit are obeyed in the ALU



10/20/2004

CSE378 Single cycle implementation.

3

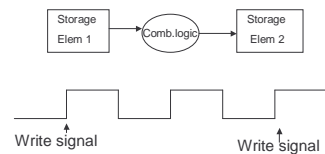


10/20/2004

CSE378 Single cycle implementation.

4

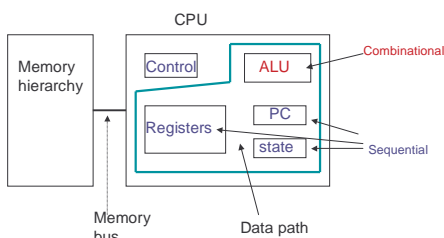Processor design: data path and control unit



10/20/2004

CSE378 Single cycle implementation.

5

Processor design

- **Data path**
 - How does data flow between various basic blocks
 - What operations can be performed when data flows
 - What can be done in one clock cycle
- **Control unit**
 - Sends signals to data path elements
 - Tells what data to move, where to move it, what operations are to be performed
- **Memory hierarchy**
 - Holds program and data


10/20/2004

CSE378 Single cycle implementation.

6

Data path basic building blocks. Storage elements

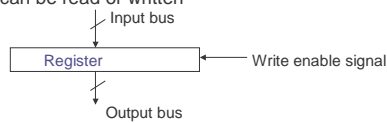- Basic building block (at the RT level) is a register
- In our mini-MIPS implementation registers will be 32-bits
- A register can be read or written




10/20/2004

CSE378 Single cycle implementation.

7

Register file

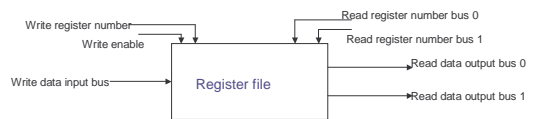- Array of registers (32 for the integer registers in MIPS)
- ISA tells us that we should be able to:
 - read 2 registers, write one register in a given instruction (at this point we want one instruction per cycle)
 - Register file needs to know which registers to read/write




10/20/2004

CSE378 Single cycle implementation.

8

Memory

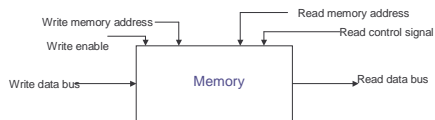- Conceptually, like register file but much larger
- Can only read one location or write to one location per cycle




10/20/2004

CSE378 Single cycle implementation.


9

Combinational elements

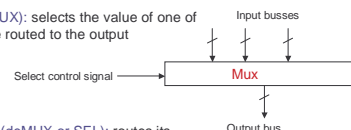Multiplexor (MUX): selects the value of one of its inputs to be routed to the output



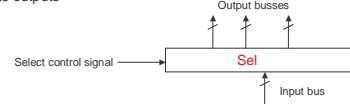Demultiplexor (deMUX or SEL): routes its input to one of its outputs




10/20/2004

CSE378 Single cycle implementation.

10

Arithmetic and Logic Unit (ALU - combinational)

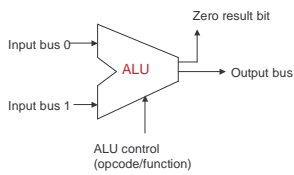- Computes (arithmetic or logical operation) output from its two inputs




10/20/2004

CSE378 Single cycle implementation.

11

 Putting basic blocks together (skeleton of data path for arith/logical operations)



10/20/2004

CSE378 Single cycle implementation.

12

