

Pipelining: Some definitions

- ◆ Latency: Time to perform a computation
 - ⇒ Data in to data out
- ◆ Throughput: Input or output data rate
 - ⇒ Typically the clock rate
- ◆ Combinational delays drive performance
 - ⇒ Define $d \equiv$ delay through slowest combinational stage
 - $n \equiv$ number of stages from input to output
 - ◆ Latency $n \cdot d$ (in sec)
 - ◆ Throughput $1/d$ (in Hz)


Pipelining: What and why

◆ What?

- ⇒ Subdivide combinational logic
- ⇒ Add registers between logic blocks

◆ Why?

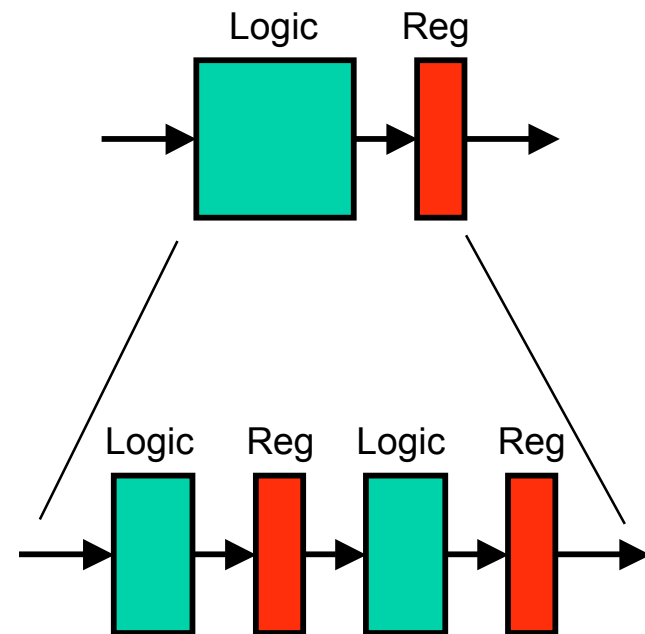- ⇒ Increase clock speed
 - ◆ Reduce logic delays
 - ◆ But...takes a few cycles to fill the pipe
- ⇒ Trade latency for throughput
 - ◆ Latency worse
 - ◆ Throughput better
- ⇒ Increase circuit utilization
 - ◆ Simultaneous computations




Pipelining: When and where

◆ When?



- ⇒ Throughput more important than latency
 - ◆ Signal processing
- ⇒ Logic delays \gg flip-flop setup/hold times
- ⇒ No acyclic logic

◆ Where?

 - ⇒ At natural breaks in the combinational logic
- ⇒ Adding registers makes sense



Pipelining example

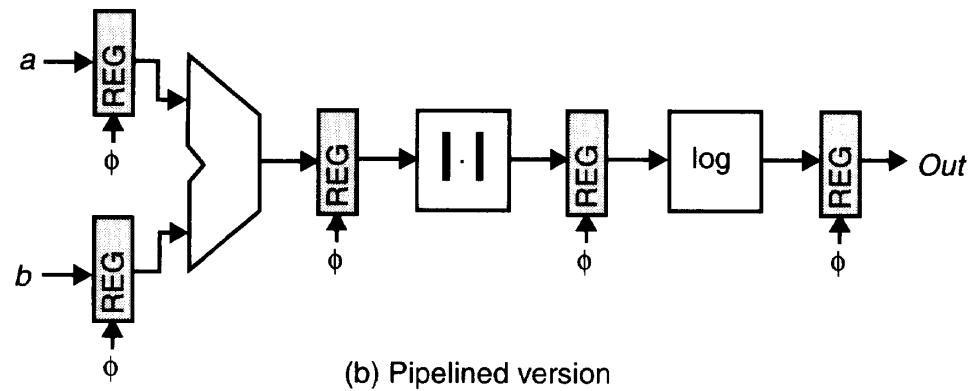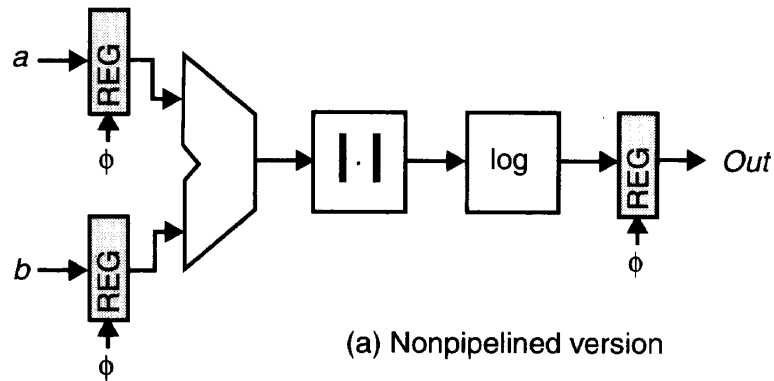


Datapath for the computation of $\log(|a + b|)$

Retiming

- ◆ Retiming: Rearrange storage elements
 - ⇒ To optimize performance
 - ◆ Minimize critical path
 - ◆ Optimize logic across register boundaries
 - ◆ Reduce register count
 - ⇒ Without altering functionality
- ◆ Pipelining adds registers
 - ⇒ To increase the clock speed
- ◆ Retiming moves registers around
 - ⇒ Reschedules computations

Retiming in a nutshell

 - ◆ Change position of FFs
 - ⇒ To optimize an FSM after assignment/optimization
 - ◆ For speed
 - ◆ To suit implementation target
- ◆ Retiming modifies state assignment
 - ⇒ Moving registers alters state codes
 - ⇒ Preserves FSM functionality



Retiming rules


- ◆ Fast optimal algorithm

 - ⇒ See Leiserson & Saxe, 1983

- ◆ Rules:



 - ⇒ Remove one register from each input and add one to each output

  - ⇒ Remove one register from each output and add one to each input





Retiming examples

- ◆ Reduce register count

  


- ◆ Create simplification opportunities

  


Retiming examples (con't)

- ◆ Move logic to suit implementation target

Original Design

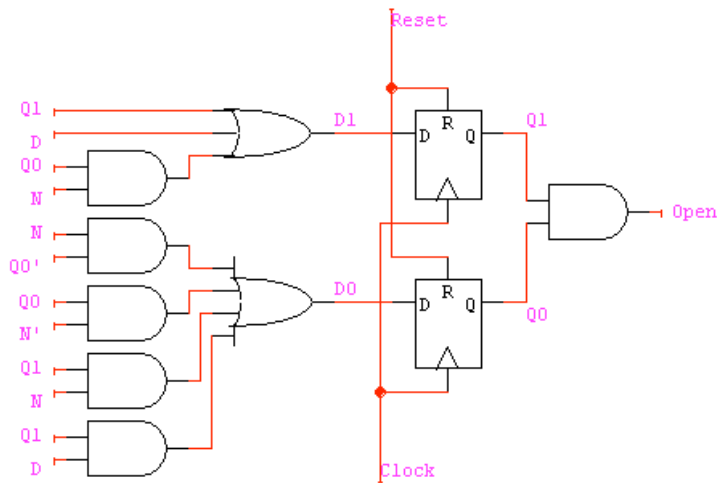


Retimed Design

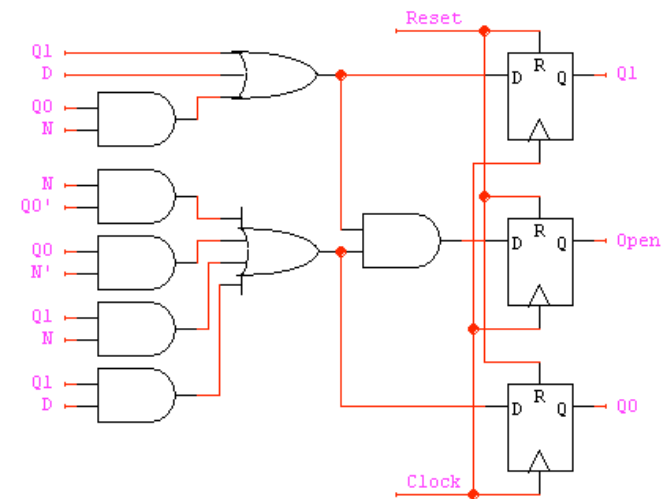

Optimal pipelining


- ◆ Add registers

  - ⇒ Use retiming to find optimal location




 
Example: Digital correlator

- ◆ $y_t = \square(x_t, a_0) + \square(x_{t-1}, a_1) + \square(x_{t-2}, a_2) + \square(x_{t-3}, a_3)$
 - $\square(x, a) = 1$ if $x = a$; 0 otherwise
 - □ passes x to the right (unchanged)




Example: Digital correlator (cont'd)



- ◆ Delays: Comparator = 3; adder = 7

  


Retiming: Step-by-step

 

Retiming: step-by-step (cont'd)

  

and after a few more . . .

 

Formal algorithm for retiming

- ◆ Represent circuit as a directed graph
 - ⇒ Vertices v : Logic gates
 - ⇒ Edges e : Connections between logic (0 or more registers)
 - ⇒ Delay d : Delay of vertex v
 - ⇒ Weight w : Number of registers on edge e
- ◆ Problem statement
 - ⇒ Given cycle time t and the circuit graph
 - ⇒ Adjust weights w (number of registers) so that all path delays $d < t$
 - ◆ Preserving logic functionality
- ◆ Approach
 - ⇒ Generate matrices for w and d
 - ⇒ Iterate to minimize t (use linear programming)

For you to think about...

- ◆ Registers **slow** the data path
 - ⇒ To synchronize delays
- ◆ Hard: Use latches instead of registers
 - ⇒ Permits faster circuits
 - ⇒ Fast data slows down; slow data passes through transparent latch
- ◆ Harder: Self-timed datapath
 - ⇒ Handshaking decides when data passes
- ◆ Hardest: Wave-pipelining
 - ⇒ Delete the registers
 - ◆ Waves of data flow through circuit
 - ◆ Requires equal-delay circuit paths