

Sequential logic implementation


- Sequential circuits
 - primitive sequential elements
 - combinational logic
- Models for representing sequential circuits
 - finite-state machines (Moore and Mealy)
 - representation of memory (states)
 - changes in state (transitions)
- Basic sequential circuits
 - shift registers
 - counters
- Design procedure
 - state diagrams
 - state transition table
 - next state functions

FSMs

1

Any sequential system can be represented with a state diagram

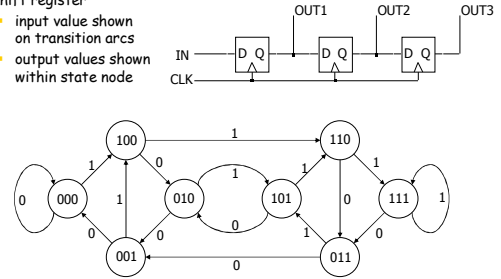- Shift register
 - input value shown on transition arcs
 - output values shown within state node




FSMs

2

State machine model

 - Values stored in registers are the state of the circuit
- Combinational logic computes:
 - next state
 - outputs
 - function of current state and inputs (Mealy machine)
 - function of current state only (Moore machine)




FSMs

3

State Machine Model

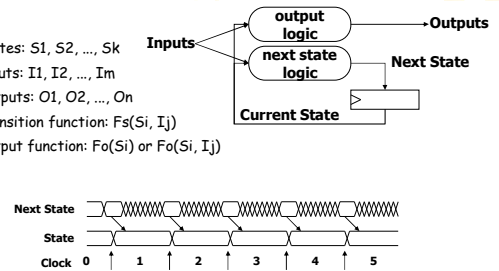- States: S_1, S_2, \dots, S_k
- Inputs: I_1, I_2, \dots, I_m
- Outputs: O_1, O_2, \dots, O_n
- Transition function: $F_s(S_i, I_j)$
- Output function: $F_o(S_i)$ or $F_o(S_i, I_j)$




FSMs

4

How do we turn a state diagram into logic?

 - e.g. counter
 - flip-flops to hold state
 - logic to compute next state
 - clock signal controls when flip-flop memory can change
 - wait just long enough for combinational logic to compute new value



FSMs

5

FSM design procedure

- Describe FSM behavior, e.g. state diagram
 - Inputs and Outputs
 - States (symbolic)
 - State transitions
- State diagram to state transition table, i.e. truth table
 - Inputs: inputs and current state
 - Outputs: outputs and next state
- State encoding
 - decide on representation of states
 - lots of choices
- Implementation
 - flip-flop for each state bit
 - synthesize combinational logic from encoded state table

FSMs

6

Design Problem – Run-Length Encoder

- 7-bit input stream
- 8-bit output stream
 - high-order bit == 0: Data value
 - high-order bit == 1: Repeat count of previous data value
- Valid bit set when 8-bit output is data or count



FSMs

7

RLE Design


- Split design into datapath and control
- Datapath
 - Registers for data values, count
 - Multiplexors
- Control
 - Keep track of what's happening
 - clear count, increment count, send data value, send count
- Control will be an FSM

FSMs

8

Start with Datapath

- We need to know what to control

 


- FSM inputs
 - eq
- FSM outputs
 - clr, inc, valid, cnt,

FSMs

9

FSM Controller

 


FSMs

10

Verilog For State Machines

 - State machine has two parts
 - State register
 - Combinational Logic
 - Next state function
 - Output function
- Each in a different always block



FSMs

11

RLE Module

- rleFSM is one module
- The datapath is specified as a schematic
 - rleFSM is part of schematic
- Possible to describe datapath in the Verilog
 - Text description of inherently graphical design

```

module rleFSM (clk, reset, eq, clr, inc, valid, cnttag);
  input clk, reset;
  input eq;
  output clr;
  output inc;
  output valid;
  output cnttag;

  // Use parameter to define symbolic states
  parameter START1 = 0, START2 = 1, SENDING = 2, COUNTING = 3;
  reg [1:0] state, // current state
           nextState; // next state
    
```

FSMs

12

Verilog for Registers

- Triggering on "posedge CLK" generates a positive, edge-triggered register
 - The only kind of register we will use

```

reg [7:0] state, // current state
    nextState; // next state

always @(posedge CLK) begin
    if (reset)
        state = START1;
    else
        state = nextState;
end
    
```

FSMs

13

Verilog for FSM Logic

```

always @(state or eq) begin
    // Set defaults
    valid = 0; inc = x; clr = x; cnttag = x;
    case (state)
        START1:
            nextState = START2;
        START2:
            nextState = SENDING;
        SENDING: begin
            valid = 1;
            cnttag = 0;
            if (eq) begin
                nextState = COUNTING;
            end else begin
                nextState = SENDING;
            end
        end
        COUNTING: begin
            if (eq) begin
                clr = 0;
                inc = 1;
                nextState = COUNTING;
            end else begin
                valid = 1;
                cnttag = 1;
                nextState = SENDING;
            end
        end
    end
end
    
```

FSMs

14

Implementing an FSM

- Perform state assignment
 - different assignments may give very different results
 - no really good heuristics
 - using an extra bit or two for state works well
 - FPGAs often use a 1-hot encoding
- Convert state diagram to state table
 - equivalent representation
 - mechanical
- State table gives truth table for next state and output functions
 - synthesize into logic circuit
 - e.g. 2-level logic implementation

FSMs

15

RLE State Table

- reset is implicit - resets state register

eq	state	next state	clr	inc	valid	cnttag
-	START1	START2	x	x	0	x
-	START2	SENDING	x	x	0	x
0	SENDING	SENDING	x	x	1	0
1	SENDING	COUNTING	1	x	1	0
0	COUNTING	SENDING	x	x	1	1
1	COUNTING	COUNTING	0	1	0	x

FSMs

16

RLE State Table

- minimal binary encoding
- there are 6 output functions

eq	state	next state	clr	inc	valid	cnttag
-	00	01	x	x	0	x
-	01	10	x	x	0	x
0	10	10	x	x	1	0
1	10	11	1	x	1	0
0	11	10	x	x	1	1
1	11	11	0	1	0	x

FSMs

17

Logic Synthesis

Q1		state		Q0		state		clr		state			
eq		00	01	11	10	00	01	11	10	00	01	11	10
0		0	1	1	1	1	0	0	0	X	X	X	X
1		0	1	1	1	1	0	1	1	X	X	0	1

inc		state		valid		state		cnttag		state			
eq		00	01	11	10	00	01	11	10	00	01	11	10
0		X	X	X	X	0	0	0	1	X	X	X	0
1		X	X	1	X	1	0	0	0	1	X	1	0

$Q1 = Q1 + Q0$
 $Q0 = Q1' Q0' + eq Q1$
 $clr = Q0'$
 $inc = 1$
 $valid = eq' Q1 + Q1 Q0' = Q1 (eq' + Q0')$
 $cnttag = Q0$

6 gates

FSMs

18

RLE State Table

- 1-hot encoding
- there are 8 output functions

eq	state	next state	clr	inc	valid	cnttag
-	0001	0010	x	x	0	x
-	0010	0100	x	x	0	x
0	0100	0100	x	x	1	0
1	0100	1000	1	x	1	0
0	1000	0100	x	x	1	1
1	1000	1000	0	1	0	x

FSMs

19

1-Hot Logic Functions

- Synthesize directly from table

$Q0 = \text{reset}$
 $Q1 = Q0$
 $Q2 = Q1 + eq' (Q2 + Q3)$
 $Q3 = eq (Q2 + Q3)$
 $inc = 1$
 $clr = Q2$
 $valid = Q2 + eq' Q3$
 $cnttag = Q3$


- Same cost as minimal encoding (6 gates)

FSMs

20

Another Example: Ant Brain

 
- Sensors: L and R antennae, 1 if touching wall
- Actuators: F - forward step, TL/TR - turn left/right slightly
- Goal: find way out of maze
- Strategy: keep the wall on the right



FSMs

21

Ant Behavior - Case Analysis

 


FSMs

22

Designing an Ant Brain

 - State Diagram
- Once we have state diagram, we just "turn the crank"




FSMs

23

State Transition Truth Table

 - Use symbolic states and outputs
- Take advantage of extra freedom



state	L	R	next state	outputs
LOST	0	0	LOST	F
LOST	0	1	E/G	F
...
A	0	0	B	TL, F
A	0	1	A	TL, F
A	1	0	E/G	TL, F
A	1	1	E/G	TL, F
B/C	0	0	C	TR, F
B/C	0	1	A	TR, F
...

FSMs

24

Synthesis

- 5 states : at least 3 state variables required (X, Y, Z)
 - state assignment (in this case, arbitrarily chosen)

LOST - 000
 E/G - 001
 A - 010
 B - 011
 C - 100

state X,Y,Z	L R	next state X', Y', Z'	outputs F TR TL
000	00	000	1 0 0
000	01	001	1 0 0
...
010	00	011	1 0 1
010	01	010	1 0 1
010	10	001	1 0 1
010	11	001	1 0 1
011	00	100	1 1 0
011	01	010	1 1 0
...

It now remains to synthesize these 6 functions

FSMs

25

Synthesis of Next State and Output Functions

state X,Y,Z	L R	next state X',Y',Z'	outputs F TR TL
000	00	000	1 0 0
000	01	001	1 0 0
000	10	001	1 0 0
001	00	011	0 0 1
001	01	010	0 0 1
001	10	010	0 0 1
010	00	011	1 0 1
010	01	010	1 0 1
010	10	001	1 0 1
011	00	100	1 1 0
011	01	010	1 1 0
100	00	100	1 1 0
100	01	010	1 1 0

e.g.

$$TR = X + YZ$$

$$X' = XR' + YZR' = R'TR$$




FSMs

26

Don't cares in FSM synthesis

 - What happens to the "unused" states (101, 110, 111)?
- They were exploited as don't cares to minimize the logic
 - if the states can't happen, then we don't care what the functions do
 - if states do happen, we may be in trouble




FSMs

27

Don't Care Example

 - Implement simple count sequence: 000, 010, 011, 101, 110
- Derive the state transition table from the state transition diagram



Present State	Next State		
	C	B	A
0	0	0	x
0	0	1	x
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	x

note the don't care conditions that arise from the unused state codes

FSMs

28

Don't cares in FSMs (cont'd)

- Synthesize logic for next state functions derive input equations for flip-flops

C ⁺	C			
	X	1	1	0
A	X	1	X	0

B ⁺	C			
	X	0	0	1
A	X	1	X	1

A ⁺	C			
	X	1	0	0
A	X	0	X	1

$$C^+ = B$$

$$B^+ = A + B'C$$

$$A^+ = A'C' + AC$$

FSMs

29

Self-starting FSMs

- Deriving state transition table from don't care assignment

C ⁺	C			
	0	1	1	0
A	0	1	1	0

B ⁺	C			
	1	0	0	1
A	1	1	1	1

A ⁺	C			
	1	1	0	0
A	0	0	1	1


Present State	Next State		
	C	B	A
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

FSMs

30


Self-starting FSMs

 - Start-up states
 - at power-up, FSM may be in an used or invalid state
 - design must guarantee that it (eventually) enters a valid state
- Self-starting solution
 - design FSM so that all the invalid states eventually
 - transition to a valid state may limit exploitation of don't cares




Mealy vs. Moore Machines

 - Moore: outputs depend on current state only
- Mealy: outputs may depend on current state and current inputs
- Our ant brain is a Moore machine
 - output does not react immediately to input change
- We could have specified a Mealy FSM
 - outputs have immediate reaction to inputs (do glitches matter?)
 - as inputs change, so does next_state, but doesn't commit until clock tick




Specifying outputs for a Moore machine

 - Output is only function of state
 - specify in state bubble in state diagram
 - example: sequence detector for 01 or 10




Specifying outputs for a Mealy machine

 - Output is function of state and inputs
 - specify output on transition arc between states
 - example: sequence detector for 01 or 10




Comparison of Mealy and Moore machines

- Mealy machines tend to have fewer states
 - different outputs on arcs ($i*n$) rather than states (n)
- Mealy machines react faster to inputs
 - react in same cycle - don't need to wait for clock
 - delay to output depends on arrival of input
- Moore machines are generally safer to use
 - outputs change at clock edge (always one cycle later)
 - in Mealy machines, input change can cause output change as soon as logic is done - a big problem when two machines are interconnected - asynchronous feedback

 


Isn't Mealy Always Better?

 - Example: serial adder - add bits arriving serially on two input wires



 
- Adding 5 serial numbers on 5 separate lines



- What is the clock period of this circuit?

Moore Implementation - Pipelined

- Example: adding 5 serial numbers

 

- What is the clock period of this circuit?