

More Verilog

- Registers
 - Counters
 - Shift registers
- FSMs
- Delayed assignments
- Test Fixtures

Verilog - 1

8-bit Register with Synchronous Reset

```
module reg8 (reset, CLK, D, Q);
input  reset;
input  CLK;
input  [7:0] D;
output [7:0] Q;
reg    [7:0] Q;

    always @(posedge CLK)
        if (reset)
            Q = 0;
        else
            Q = D;

endmodule // reg8
```

Verilog - 2

N-bit Register with Asynchronous Reset

```
module regN (reset, CLK, D, Q);
input  reset;
input  CLK;
parameter N = 8; // Allow N to be changed
input  [N-1:0] D;
output [N-1:0] Q;
reg    [N-1:0] Q;

    always @(posedge CLK or posedge reset)
        if (reset)
            Q = 0;
        else if (CLK == 1)
            Q = D;

endmodule // regN
```

Verilog - 3

Shift Register Example

```
// 8-bit register can be cleared, loaded, shifted left
// Retains value if no control signal is asserted

module shiftReg (CLK, clr, shift, ld, Din, SI, Dout);
input  shiftReg (CLK, clr, shift, ld, Din, SI, Dout);
input  CLK; // clear register
input  clr; // shift
input  shift; // load register from Din
input  ld; // Data input for load
input  [7:0] Din; // Input bit to shift in
input  SI;
output [7:0] Dout;
reg    [7:0] Dout;

    always @(posedge CLK) begin
        if (clr)      Dout <= 0;
        else if (ld)  Dout <= Din;
        else if (shift) Dout <= { Dout[6:0], SI };
    end

endmodule // shiftReg
```

Verilog - 4

Blocking and Non-Blocking Assignments

- Blocking assignments ($Q = A$)
 - variable is assigned immediately before continuing to next statement
 - new variable value is used by subsequent statements
- Non-blocking assignments ($Q <= A$)
 - variable is assigned only after all statements already scheduled are executed
 - value to be assigned is computed here but saved for later
 - usual use: register assignment
 - registers simultaneously take their new values after the clock tick
- Example: swap

```
always @(posedge CLK)          always @(posedge CLK)
begin                          begin
    temp = B;                  A <= B;
    B = A;                     B <= A;
    A = temp;                  end
end                              end
```

Verilog - 5

Swap (continued)

- The real problem is parallel blocks
 - one of the blocks is executed first
 - previous value of variable is lost
- Use delayed assignment to fix this
 - both blocks are scheduled by `posedge CLK`

```
always @(posedge CLK)          always @(posedge CLK)
begin                          begin
    A <= B;                     B <= A;
end                              end
```

Verilog - 6

Non-Blocking Assignment

- Non-blocking assignment is also known as an RTL assignment
 - if used in an always block triggered by a clock edge
 - mimic register-transfer-level semantics - all flip-flops change together
- My rule: ALWAYS use \leftarrow in sequential (posedge clk) blocks

```
// this implements 3 parallel flip-flops
always @(posedge clk)
begin
    B = A; // this implements a shift register
    C = B; // this implements a shift register
    D = C; // this implements a shift register
end
begin
    begin
        {D, C, B} = {C, B, A};
    end
end
begin
    B <= A;
    C <= B;
    D <= C;
end
```

Verilog - 7

Counter Example

- Simple components with a register and extra computation
 - Customized interface and behavior, e.g.
 - counters
 - shift registers


```
// 8-bit counter with clear and count enable controls
module count8 (CLK, clr, cntEn, Dout);
input CLK;
input clr; // clear counter
input cntEn; // enable count
output [7:0] Dout; // counter value
reg [7:0] Dout;

always @(posedge CLK)
if (clr) Dout <= 0;
else if (cntEn) Dout <= Dout + 1;
endmodule
```

Verilog - 8

Finite State Machines

- Recall FSM model

 


- Recommended FSM implementation style
 - Implement combinational logic using a one always block
 - Implement an explicit state register using a second always block

Verilog - 9

Verilog FSM - Reduce 1s example

 - Change the first 1 to 0 in each string of 1's
 - Example Moore machine implementation



```
// State assignment
parameter zero = 0, one1 = 1, twos = 2;

module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
reg [1:0] state; // state register
reg [1:0] next_state;

// Implement the state register
always @(posedge clk)
if (reset) state = zero;
else state = next_state;
```

Verilog - 10

Moore Verilog FSM (cont'd)

```
always @(in or state)
case (state)
out = 0; // defaults
next_state = zero;
zero: begin // last input was a zero
if (in) next_state = one1;
end

one1: begin // we've seen one 1
if (in) next_state = twos;
end

twos: begin // we've seen at least 2 ones
out = 1;
if (in) next_state = twos;
end
// Don't need case default because of default assignments
endcase
endmodule
```

crucial to include all signals that are input to state and output equations


Verilog - 11

Mealy Verilog FSM for Reduce-1s example

```
module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
reg state; // state register
reg next_state;
parameter zero = 0, one = 1;

always @(posedge clk)
if (reset) state = zero;
else state = next_state;

 always @(in or state)
out = 0;
next_state = zero;
case (state)
zero: begin // last input was a zero
if (in) next_state = one;
end
one: // we've seen one 1
if (in) begin
next_state = one; out = 1;
end
endcase
endmodule
```



Verilog - 12


Restricted FSM Implementation Style

- Mealy machine requires two always blocks
 - register needs posedge CLK block
 - input to output needs combinational block
- Moore machine can be done with one always block
 - e.g. simple counter
 - Not a good idea for general FSMs**
 - Can be very confusing (see example)
- Moore outputs
 - Share with state register, use suitable state encoding

Verilog - 13

Single-always Moore Machine (Not Recommended!)
 
```
module reduce (clk, reset, in, out);
    input clk, reset, in;
    output out;
    reg out;
    reg [1:0] state; // state register
    parameter zero = 0, one1 = 1, twos1 = 2;
```



Verilog - 14

Single-always Moore Machine (Not Recommended!)

```
always @(posedge clk)
case (state)
zero: begin
    out = 0;
    if (in) state = one1;
    else state = zero;
end
one1:
    if (in) begin
        state = twos1;
        out = 1;
    end else begin
        state = zero;
        out = 0;
    end
twos1:
    if (in) begin
        state = twos1;
        out = 1;
    end else begin
        state = zero;
        out = 0;
    end
default: begin
    state = zero;
    out = 0;
end
endcase
endmodule
```

← All outputs are registered

← This is confusing: the output does not change until the next clock cycle

Verilog - 15

Delays

- Delays are used for simulation only
 - Delays are useful for modeling time behavior of circuit
 - Synthesis ignores delay numbers
 - If your simulation *relies* on delays, your synthesized circuit will probably not work
- #10 inserts a delay of 10 time units in the simulation

```
module and_gate (out, in1, in2);
    input in1, in2;
    output out;

    assign #10 out = in1 & in2;

endmodule
```

Verilog - 16

Verilog Propagation Delay

- May write things differently for finer control of delays

```
assign #5 c = a | b;
```

```
assign #4 {Cout, S} = Cin + A + B;
```

```
always @(A or B or Cin)
#4 S = A + B + Cin;
#2 Cout = (A & B) | (B & Cin) | (A & Cin);
```

```
assign #3 zero = (sum == 0) ? 1 : 0;
```

```
always @(sum)
if (sum == 0)
#6 zero = 1;
else
#3 zero = 0;
```

Verilog - 17

Initial Blocks

- Like always blocks
 - execute once at the very beginning of simulation
 - not synthesizable
 - use reset instead

Verilog - 18

Tri-State Buffers

- 'Z' value is the tri-stated value
- This example implements tri-state drivers driving BusOut

```

module tstate (EnA, EnB, BusA, BusB, BusOut);
  input EnA, EnB;
  input [7:0] BusA, BusB;
  output [7:0] BusOut;


  assign BusOut = EnA ? BusA : 8'bZ;
  assign BusOut = EnB ? BusB : 8'bZ;
endmodule

```

Verilog - 19

Test Fixtures

 - Provides clock
- Provides test vectors/checks results
 - test vectors and results are precomputed
 - usually read vectors from file
- Models system environment
 - Complex program that simulates external environment
- Test fixture can all the language features
 - initial, delays, read/write files, etc.



Verilog - 20

Verilog Clocks

- ClockGenerator

```

module clockGenerator (CLK);
  parameter period = 10;
  parameter howlong = 100;
  output CLK;
  reg CLK;

  initial begin
    CLK = 0;
    #period/2;
    repeat (howlong) begin
      CLK = 1;
      #period-period/2;
      CLK = 0;
      #period/2;
    end
    $finish;
  end
endmodule // clockGenerator

```

Values assigned in blocks have to be declared "reg"

Stops the simulation

Verilog - 21

Verilog Clocks

- Another clock generator

```

module clock_gen (masterclk);
  `define PERIOD = 10;
  output masterclk;
  reg masterclk;

  initial masterclk = 0;
  always begin
    #PERIOD/2
    masterclk = ~masterclk;
  end
endmodule

```

use `define to make constants easier to find and change

use of initial and always blocks

Verilog - 22

Example Test Fixture

```

module stimulus (a, b, c);
  parameter delay = 10;
  output a, b, c;
  reg [2:0] cnt;

  initial begin
    cnt = 0;
    repeat (8) begin
      #delay cnt=cnt+1;
    end
    #delay $finish;
  end

  assign {c, a, b} = cnt;
endmodule

module full_add1 (A, B, Cin, S, Cout);
  input A, B, Cin;
  output S, Cout;

  assign {Cout, S} = A + B + Cin;
endmodule

module driver; // Structural Verilog connects test-fixture to full adder
  wire a, b, cin, sum, cout;
  stimulus stim (a, b, cin);
  full_add1 fal (a, b, cin, sum, cout);

  initial begin
    $monitor ("%time$td cin=%b, a=%b, b=%b, cout=%d, sum=%d",
              $time, cin, a, b, cout, sum);
  end
endmodule

```

Verilog - 23

Simulation Driver

```

module stimulus (a, b);
  parameter delay = 10;
  output a, b;
  reg [1:0] cnt;

  initial begin
    cnt = 0;
    repeat (4) begin
      #delay cnt = cnt + 1;
    end
    #delay $finish;
  end

  assign {a, b} = cnt;
endmodule

```

2-bit vector

initial block executed only once at start of simulation

directive to stop simulation

bundles two signals into a vector

Verilog - 24

Test Vectors

```
module testData(clk, reset, data);
  input clk;
  output reset, data;
  reg [1:0] testVector [100:0];
  reg reset, data;
  integer count;

  initial begin
    $readmemb("data.b", testVector);
    count = 0;
    { reset, data } = testVector[0];
  end

  always @(posedge clk) begin
    count = count + 1;
    #1 { reset, data } = testVector[count];
  end
endmodule
```

Verilog - 25

Verilog Simulation

- Interpreted vs. compiled simulation
 - performance of the simulation
- Level of simulation
 - accuracy of the model
- Relationship to synthesis
 - can all that can be simulated be synthesized?

Verilog - 26

Interpreted vs. Compiled Simulation

- Interpreted
 - data structures constructed from input file
 - simulator walks data structures and decided when something occurs
 - basic algorithm:
 - take an event from queue, evaluate all modules sensitive to that event, place new events on queue, repeat
- Compiled
 - input file is translated into code that is compiled/linked with kernel
 - basic algorithm:
 - same as above
 - except that now functions associated with elements are simply executed and directly place events on queue
 - overhead of compilation must be amortized over total simulation time and its harder to make changes - need dynamic linking

Verilog - 27

Simulation Level

- Electrical
 - solve differential equations for all devices simultaneously to determine precise analog shape of waveforms
- Transistor
 - model individual transistors as switches - this can be close to electrical simulation if restricted to digital circuits
- Gate
 - use abstraction of Boolean algebra to view gates as black-boxes if only interested in digital values and delay
- Cycle or register-transfer
 - determine correct values only at clock edges, ignore gate delays if interested only in proper logical behavior of detailed implementation
- Functional (or behavioral) level
 - no interest in internal details of circuit implementation (just a program)

Verilog - 28

Simulation Time and Event Queues

- Event queue
 - changes in signal values are "events" placed on the queue
 - queue is a list of changes to propagate
 - priority queue of pending events based on time of occurrence
 - multiple events on same signal can be on queue
- Time
 - advanced whenever an event is taken off the queue
 - advance to time of event
 - parallel activities are implicitly interleaved
 - what do we do about events with zero delay?

Verilog - 29

Verilog Time

- All computations happen in zero time unless there are explicit delays or waits in the code
 - #delay - blocks execution until that much time has passed
 - event placed on queue to wake up block at that time
 - @ or wait - waits for an event, e.g., @(posedge clk) and wait(x==0)
 - nothing happens until that event is taken off the queue
- When an event is removed from the queue, all the blocks sensitive to it are evaluated in parallel and advance to their next blocking point (delay/wait)
- Time advances as long as there are events to process
 - infinite loops are easy to write
 - use explicit \$finish
 - use specified number of clock periods

Verilog - 30

Inertial and Transport Delays

- Inertial Delay
 - `#3 X = A ;`
 - Wait 3 time units, then assign value of A to X
 - The usual way delay is used in simulation
 - models logic delay reasonably
- Transport Delay
 - `X <= #3 A ;`
 - Current value of A is assigned to X, after 3 time units
 - Better model for transmission lines and high-speed logic

Verilog - 31

A few requirements for CSE467...

- Draw data-flow diagrams
 - Algorithm \Rightarrow dataflow \Rightarrow datapath and control
 - Then instance Verilog modules into Xilinx schematics
- Draw state diagrams
 - And do the state encoding
 - One-hot
 - Simplifies combinational logic (reduces # of inputs)
 - More CLBs for state, but less for logic
 - Output based \Rightarrow use same bits for outputs and state
 - Don't need CLBs to decode output from state
 - Modularize your designs

Verilog - 32