

EVOLUTION OF IMPLEMENTATION TECHNOLOGIES


- Logic gates (1950s-60s)
- Regular structures for two-level logic (1960s-70s)
 - muxes and decoders, PLAs
- Programmable sum-of-products arrays (1970s-80s)
 - PLDs, complex PLDs
- Programmable gate arrays (1980s-90s)
 - densities high enough to permit entirely new class of application, e.g., prototyping, emulation, acceleration



**trend toward
higher levels
of integration**


GATE ARRAY TECHNOLOGY (IBM - 1970s)

 - Simple logic gates
 - combine transistors to implement combinational and sequential logic
- Interconnect
 - wires to connect inputs and outputs to logic blocks
- I/O blocks
 - special blocks at periphery for external connections
- Add wires to make connections
 - done when chip is fabbed
 - "mask-programmable"
 - construct any circuit
- Coming back as "Structured ASICs"



FIELD-PROGRAMMABLE GATE ARRAYS

 - Logic blocks
 - to implement combinational and sequential logic
- Interconnect
 - wires to connect inputs and outputs to logic blocks
- I/O blocks
 - special logic blocks at periphery of device for external connections
- Key questions:
 - how to make logic blocks programmable?
 - how to connect the wires?
 - *after the chip has been fabbed*



ENABLING TECHNOLOGY



- Cheap/fast fuse connections
 - small area (can fit lots of them)
 - low resistance wires (fast even if in multiple segments)
 - very high resistance when not connected
 - small capacitance (wires can be longer)
- Pass transistors (switches)
 - used to connect wires
 - bi-directional
- Multiplexors
 - used to connect one of a set of possible sources to input
 - can be used to implement logic functions

PROGRAMMING TECHNOLOGIES

- Fuse and anti-fuse
 - fuse makes or breaks link between two wires
 - typical connections are 50-300 ohm
 - one-time programmable (testing before programming?)
- EPROM and EEPROM
 - high power consumption
 - typical connections are 2K-4K ohm
 - fairly low density
- RAM-based
 - memory bit controls a switch that connects/disconnects two wires
 - typical connections are .5K-1K ohm
 - can be programmed and re-programmed easily (tested at factory)



TRADEOFFS IN FPGAs




- Logic block - how are functions implemented: fixed functions (manipulate inputs) or programmable?
 - support complex functions, need fewer blocks, but they are bigger so less of them on chip
 - support simple functions, need more blocks, but they are smaller so more of them on chip
- Interconnect
 - how are logic blocks arranged?
 - how many wires will be needed between them?
 - are wires evenly distributed across chip?
 - programmability slows wires down - are some wires specialized to long distances?
 - how many inputs/outputs must be routed to/from each logic block?
 - what utilization are we willing to accept? 50%? 20%? 90%?

ALTERA CYCLONE II (LOW-COST STRATIX-II FPGA)


- LE is basic block
 - LUT + register + configurable routing
- LAB: 16 LEs
 - Internal carry chain
 - Shift register chain
 - Shared control signals:
 - clocks, resets, enables
 - Internal connect
- FPGA: Rows and Columns of LABs
 - With memories and multipliers
 - I/Os and PLLs on periphery

Figure 2-1. Cyclone II EP2C20 Device Block Diagram

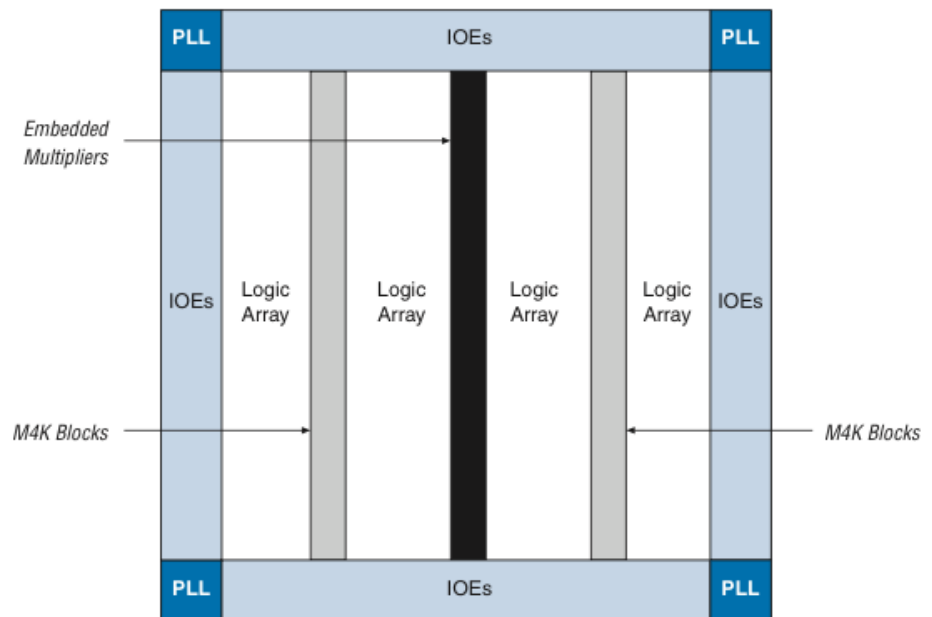


CYCLONE II LE USED FOR LOGIC

Figure 2-3. LE in Normal Mode

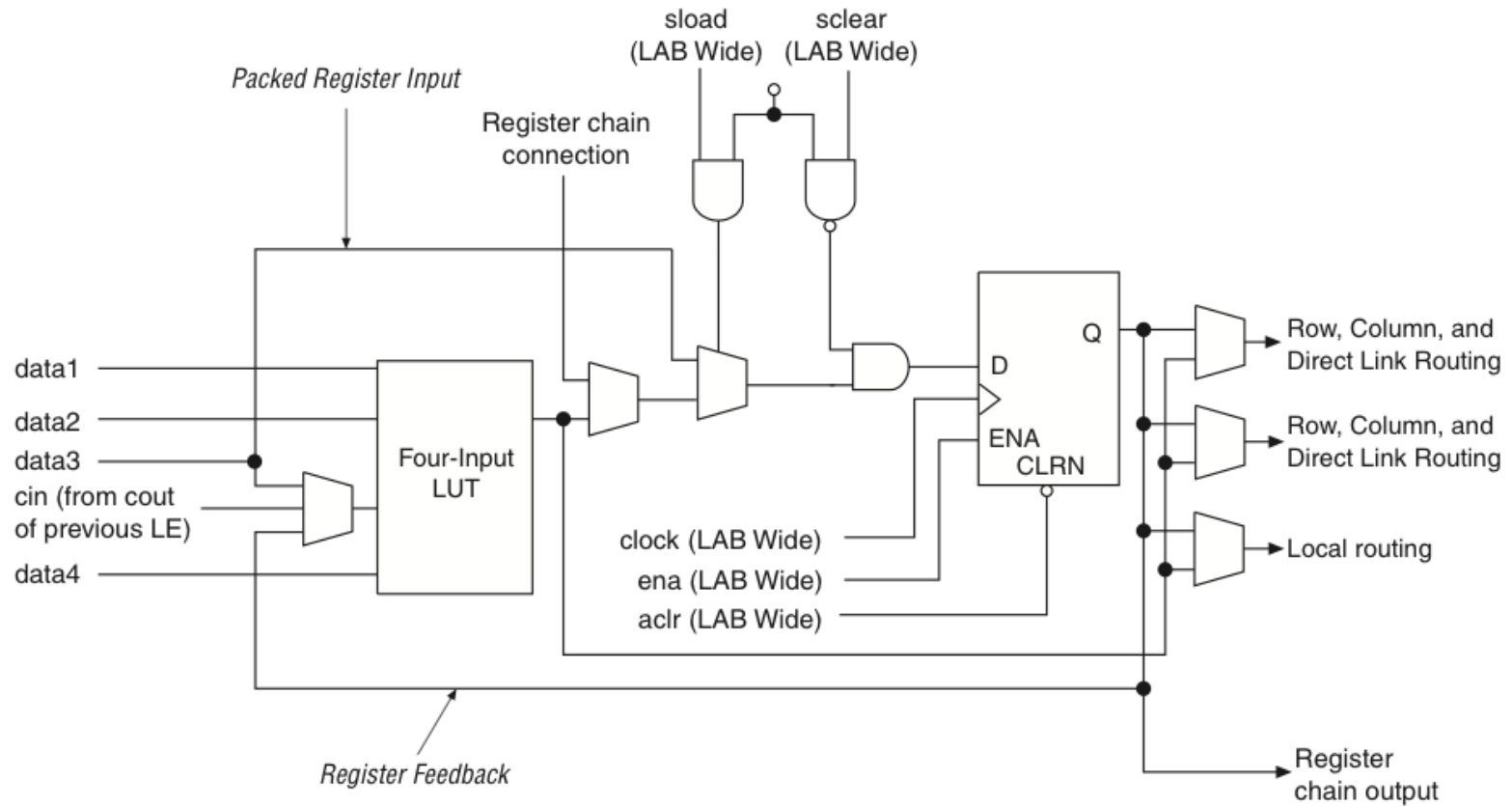


COMBINATIONAL LOGIC

Figure 2-3. LE in Normal Mode

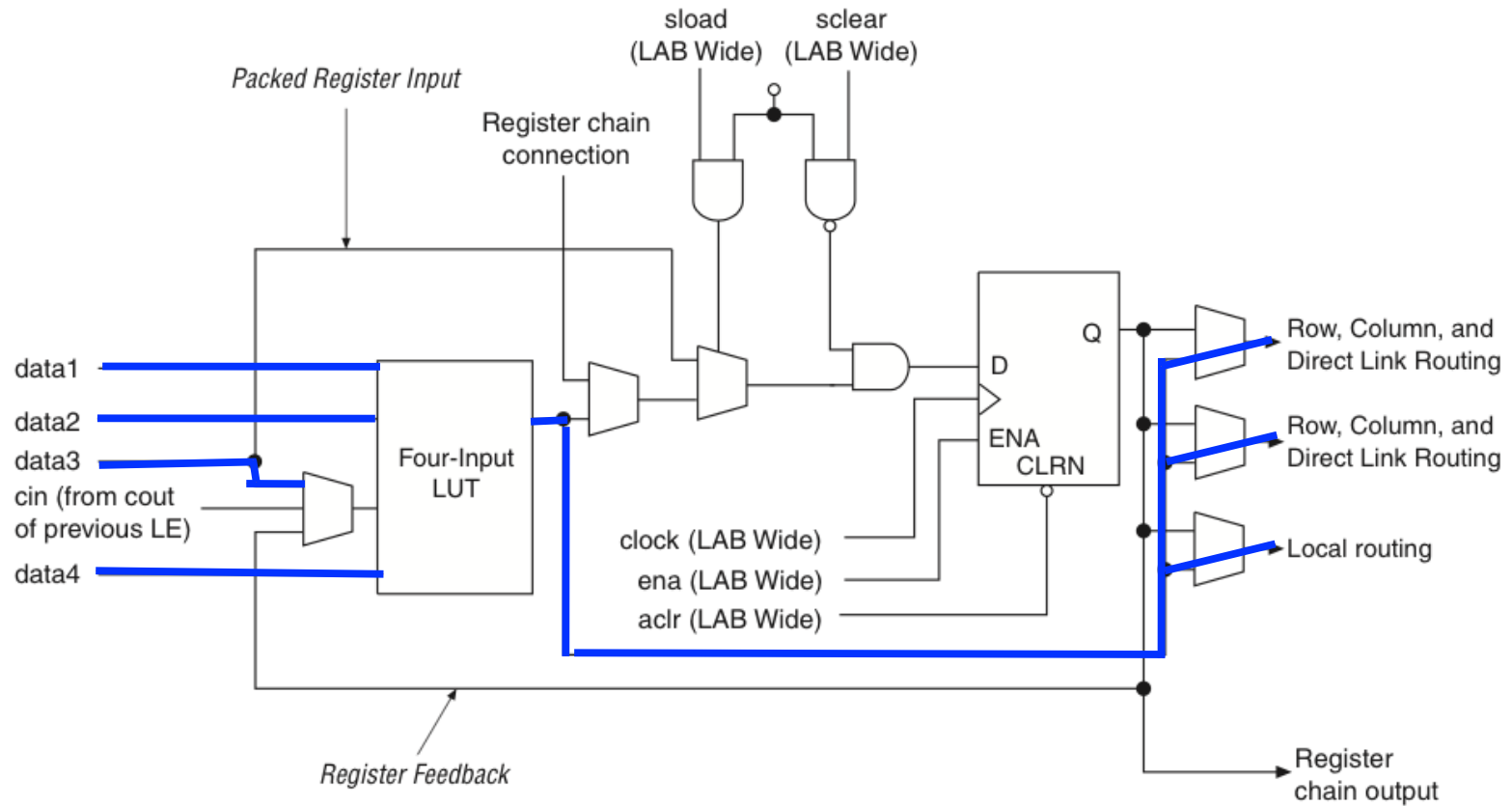


REGISTERED LOGIC

Figure 2-3. LE in Normal Mode

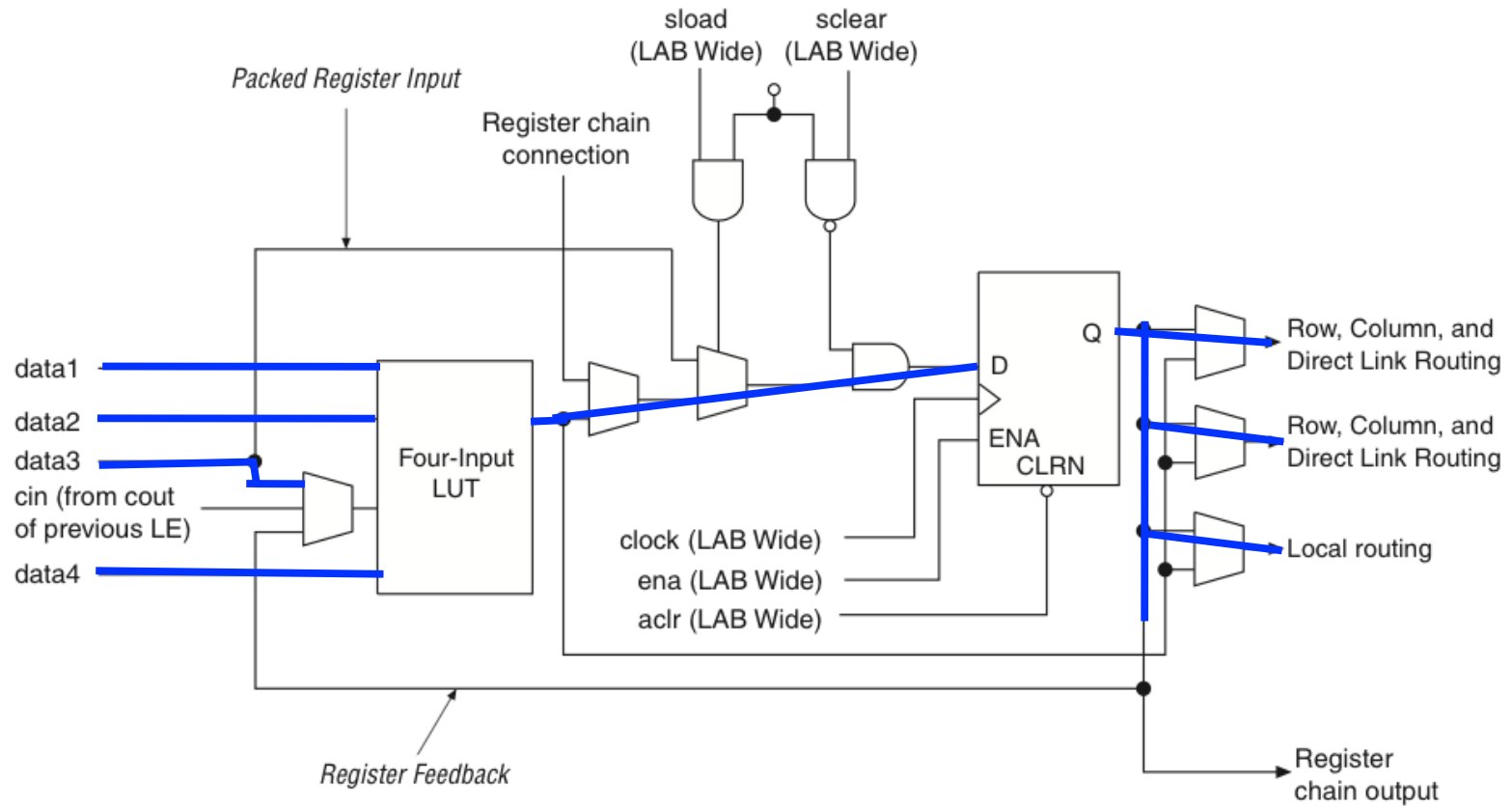


“PACKED” MODE – LUT AND REGISTER

Figure 2-3. LE in Normal Mode

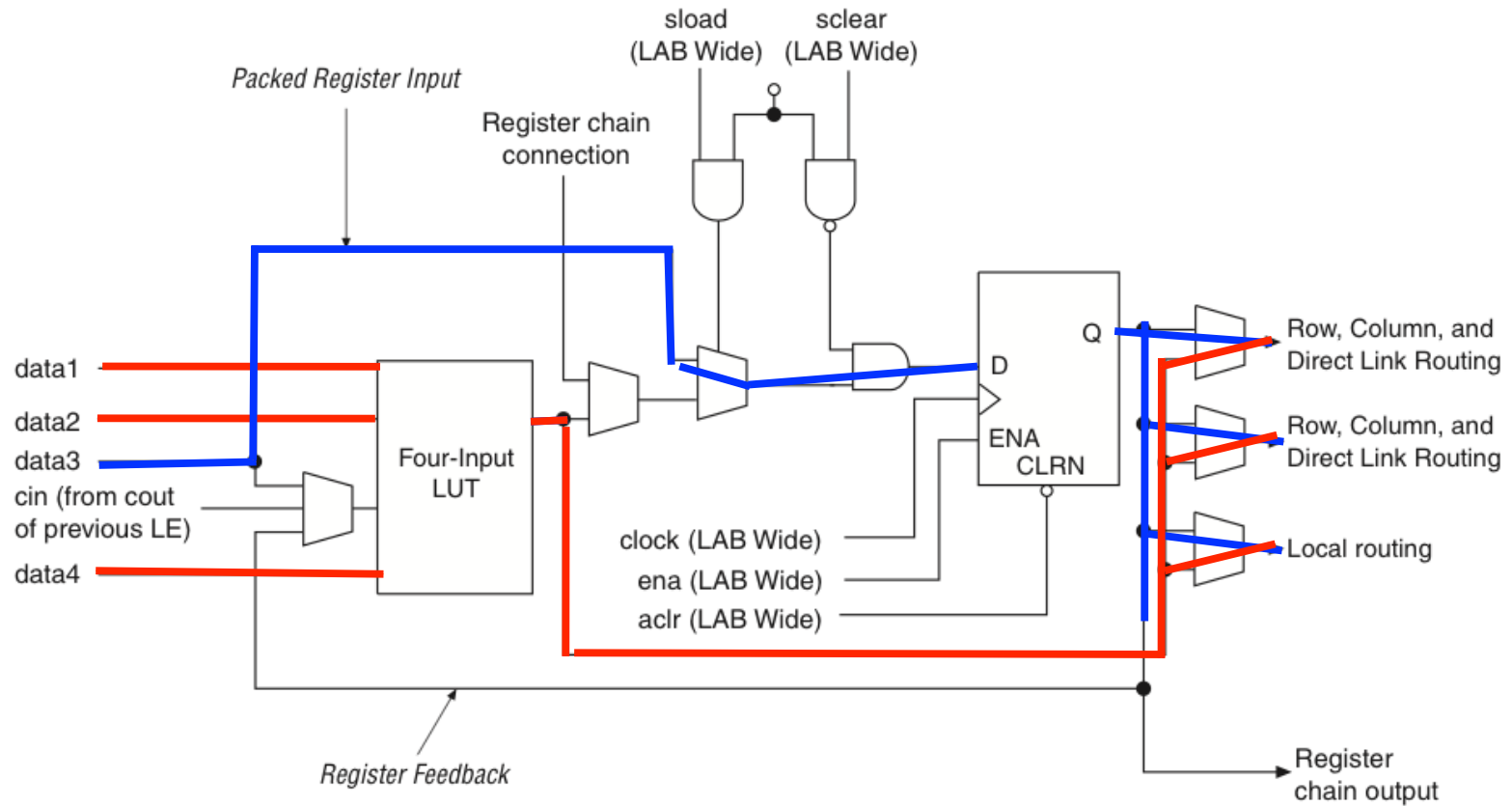


SHIFT REGISTER MODE + LOGIC

Figure 2-3. LE in Normal Mode

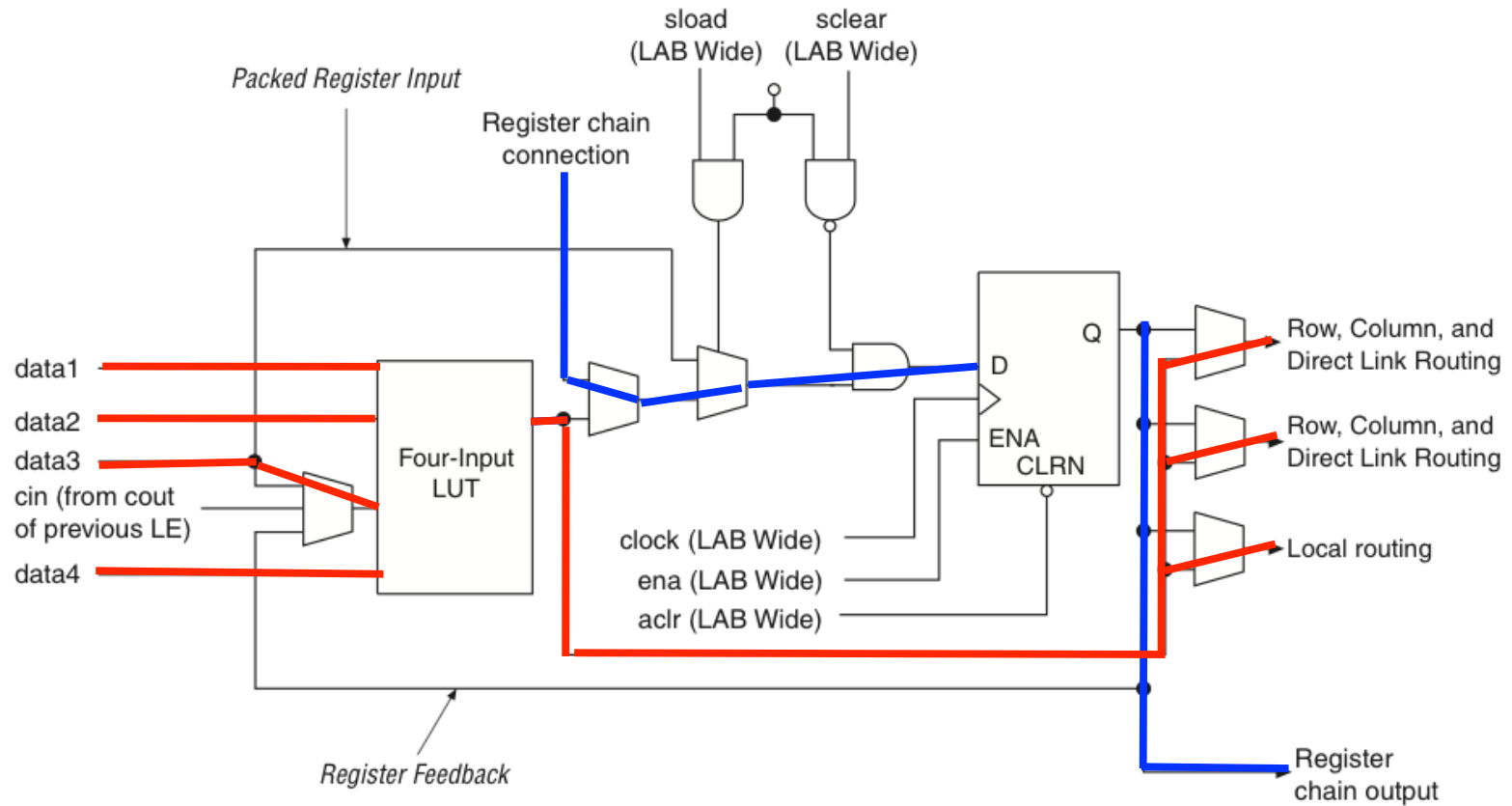


CYCLONE II LE USED FOR ARITHMETIC

Figure 2-4. LE in Arithmetic Mode

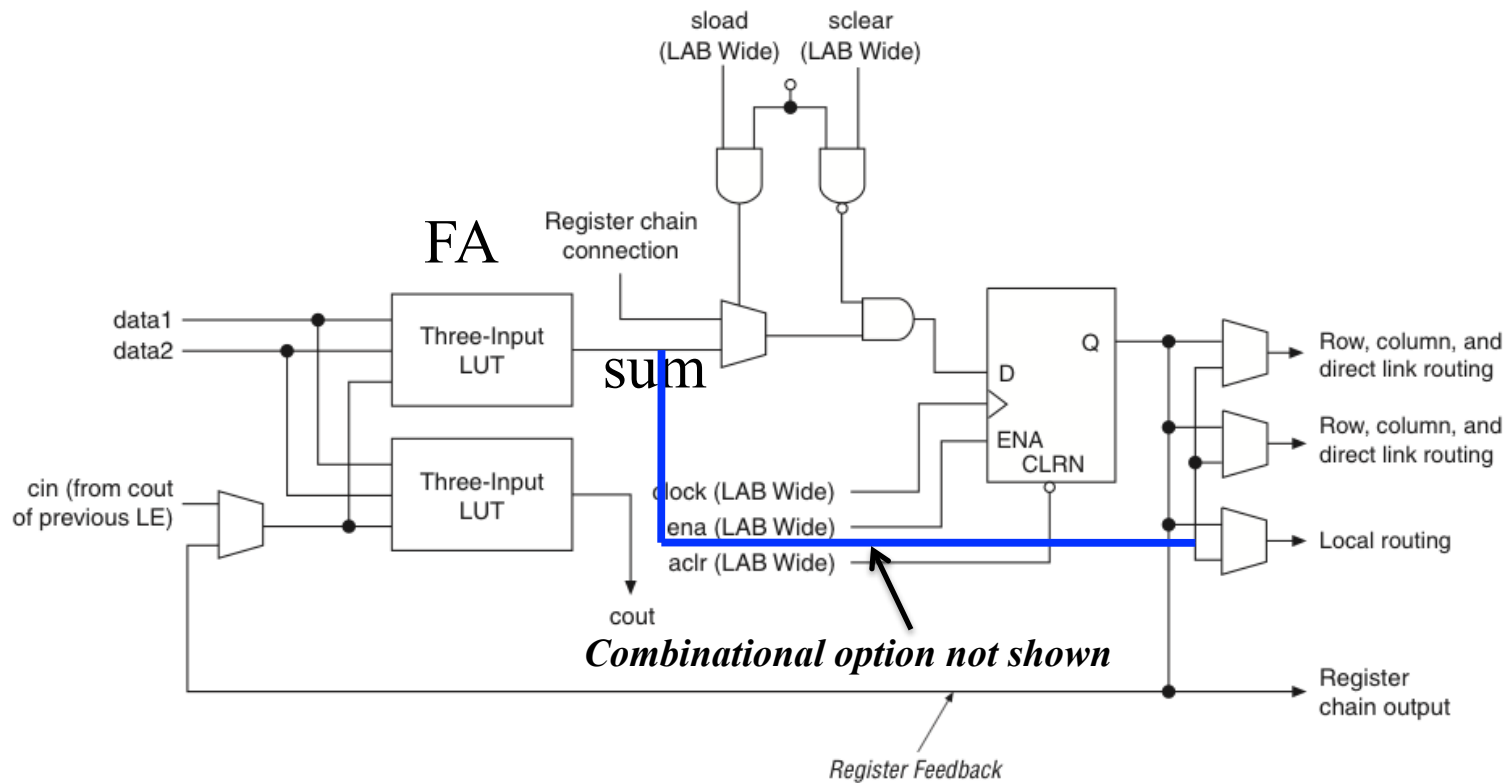


FULL CYCLONE II LE


Figure 2-2. Cyclone II LE

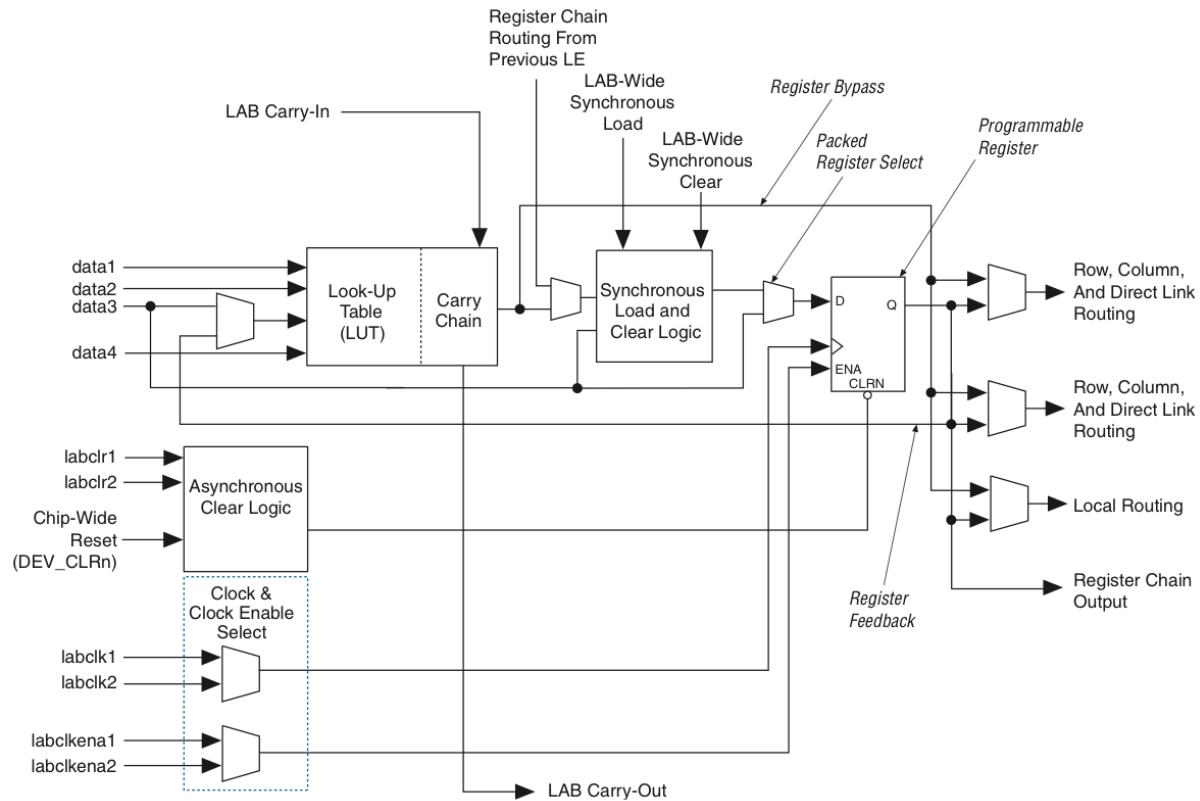

STRATIX II ALM

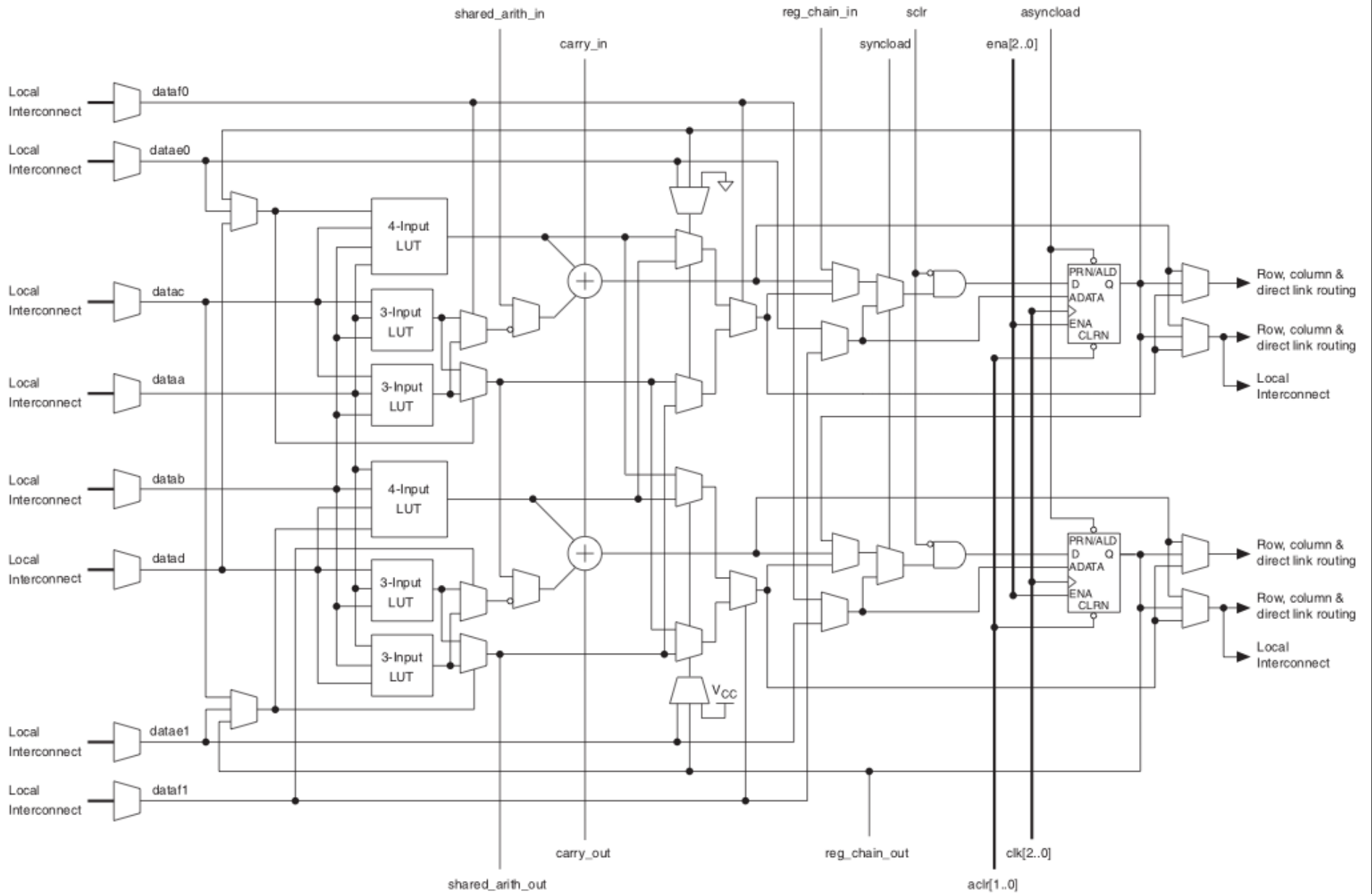


STRITIX III/IV ALM

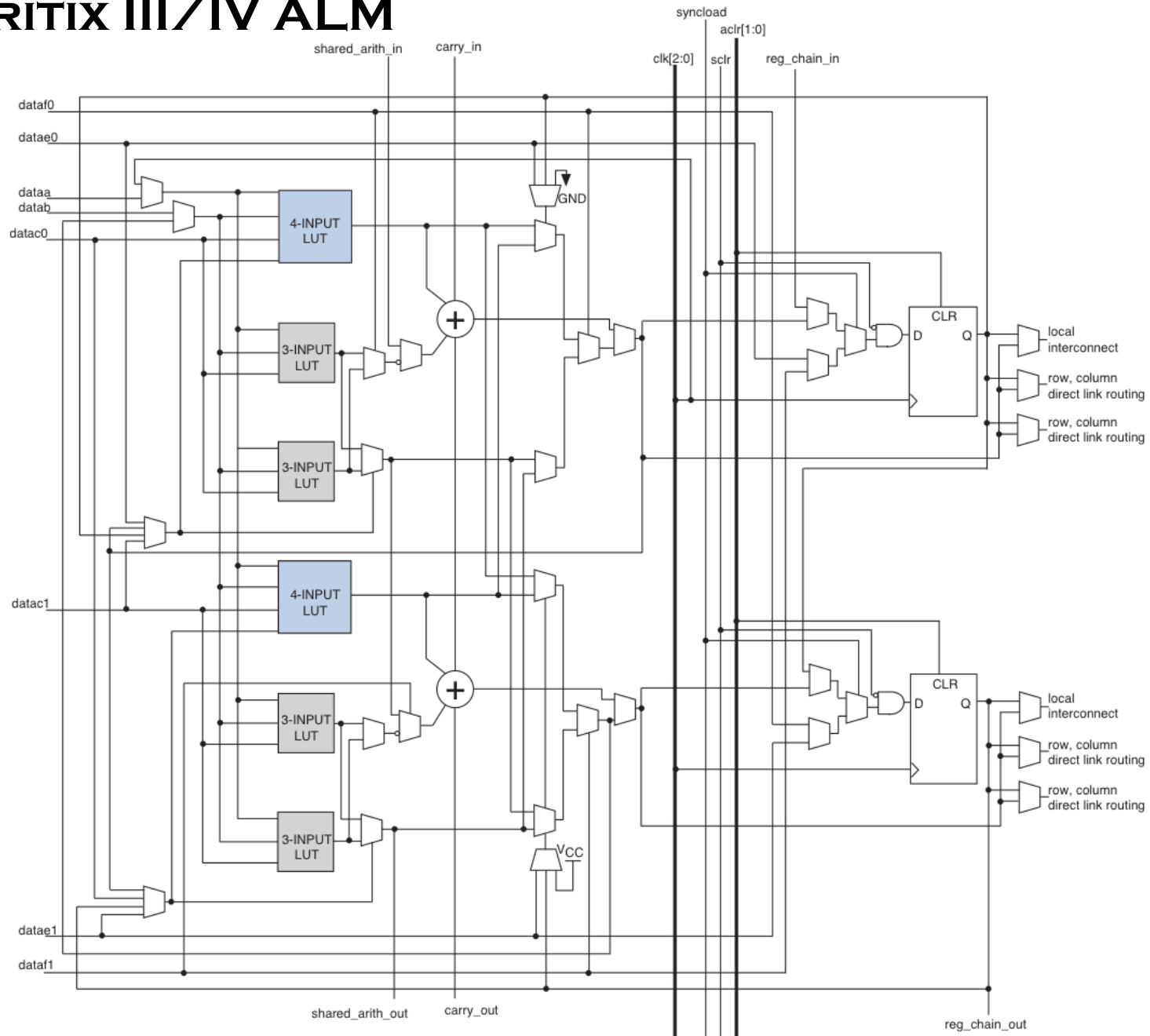


LAB LOCAL INTERCONNECT – LOCAL CONNECTIONS

Figure 2-5. Cyclone II LAB Structure

 


LOCAL INTERCONNECT – CONNECT TO ADJACENT LABS

Figure 2-5. Cyclone II LAB Structure

 

LOCAL INTERCONNECT – CONNECT TO ROW/COLUMN INTERCONNECT


Figure 2-5. Cyclone II LAB Structure

 

LAB CONTROL SIGNALS

- Shared by LEs in LAB
- Constraint on placement


Figure 2-7. LAB-Wide Control Signals

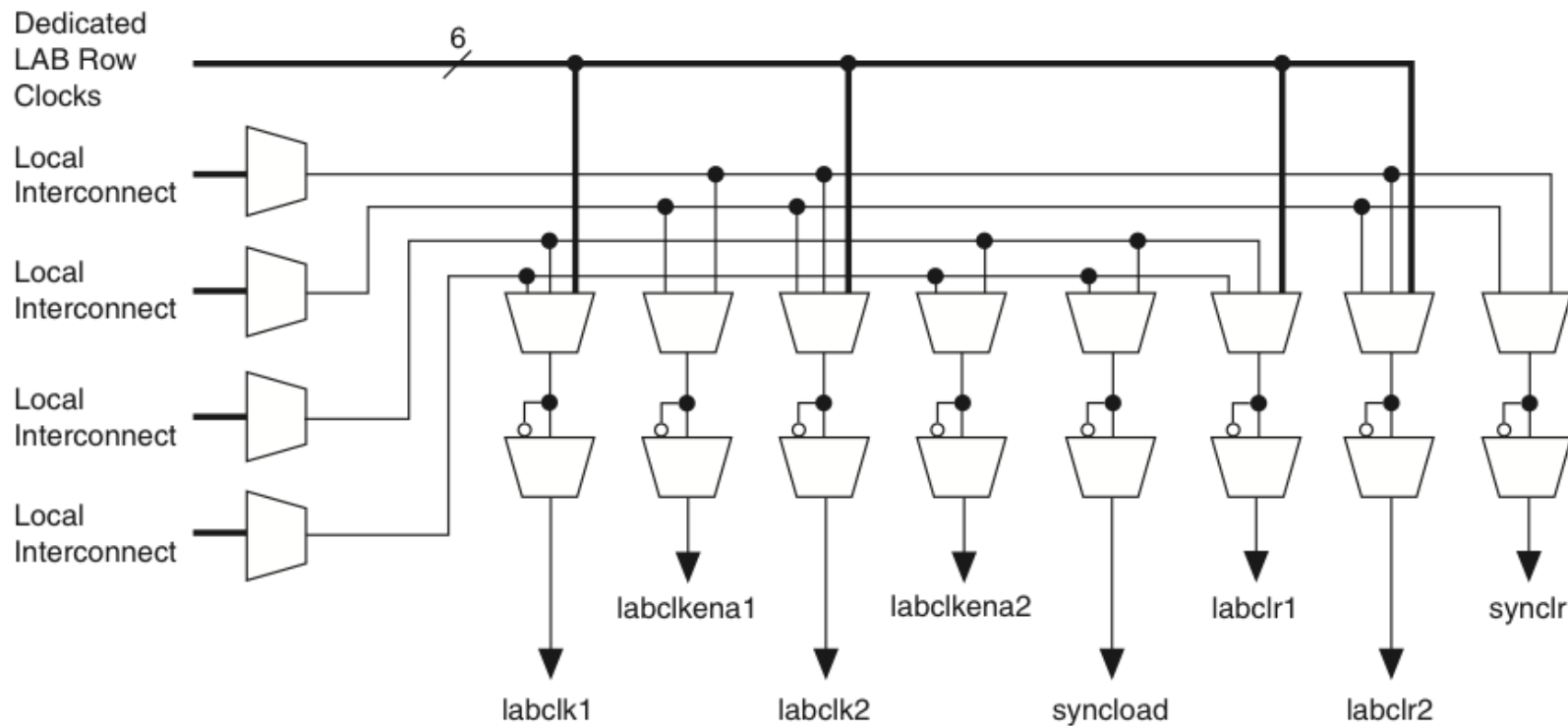

ROW INTERCONNECT

- R4 Interconnects span 4 columns
- R24 Interconnects span width of device
- LABs, memories, multipliers can drive R4s


Figure 2–8. R4 Interconnect Connections

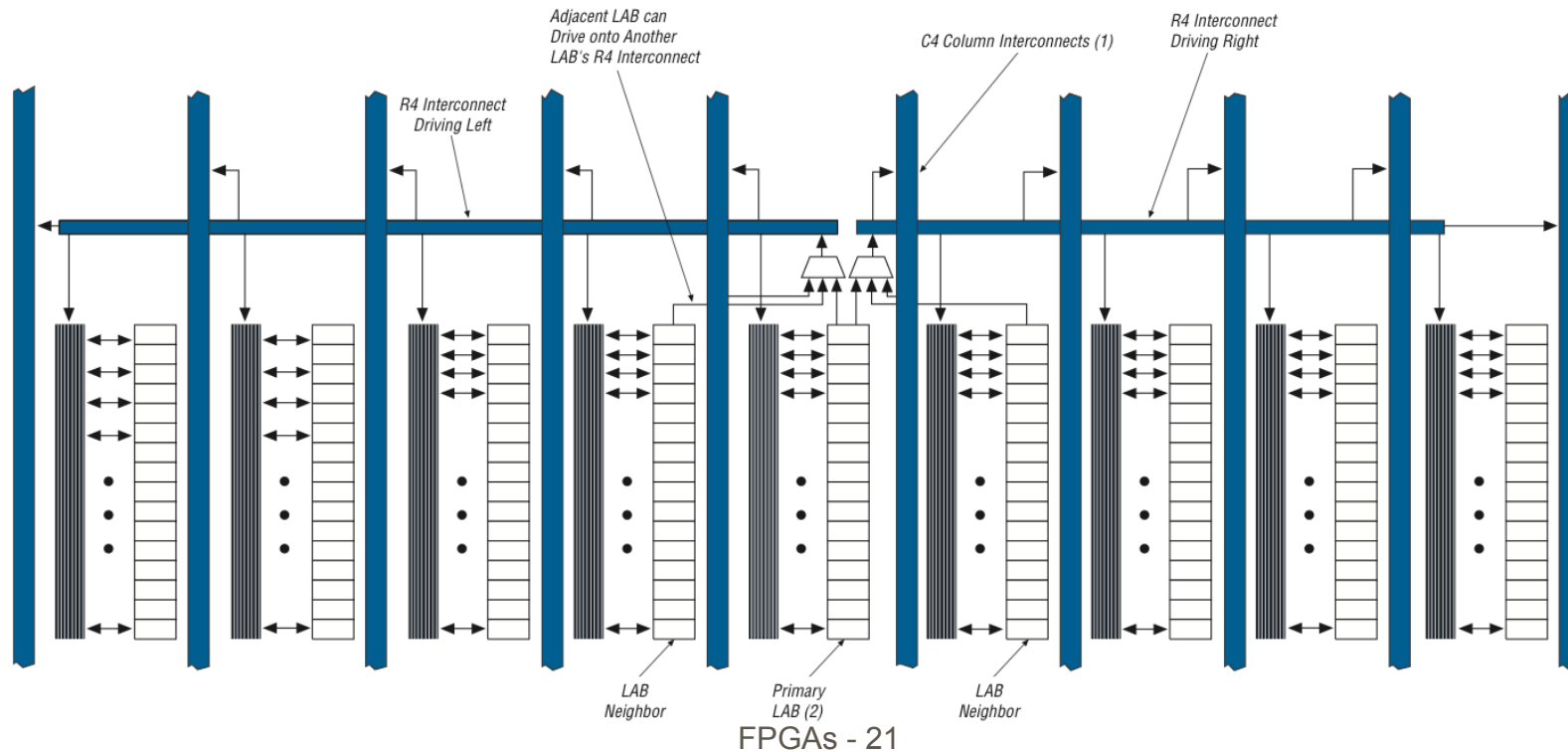

COLUMN INTERCONNECT


- C4 - spans 4 LAB rows
- C16 - spans 16 LAB rows
- LABs directly connected via row interconnect
 - indirectly via column interconnect

Figure 2-10. C4 Interconnect Connections *Note (1)*

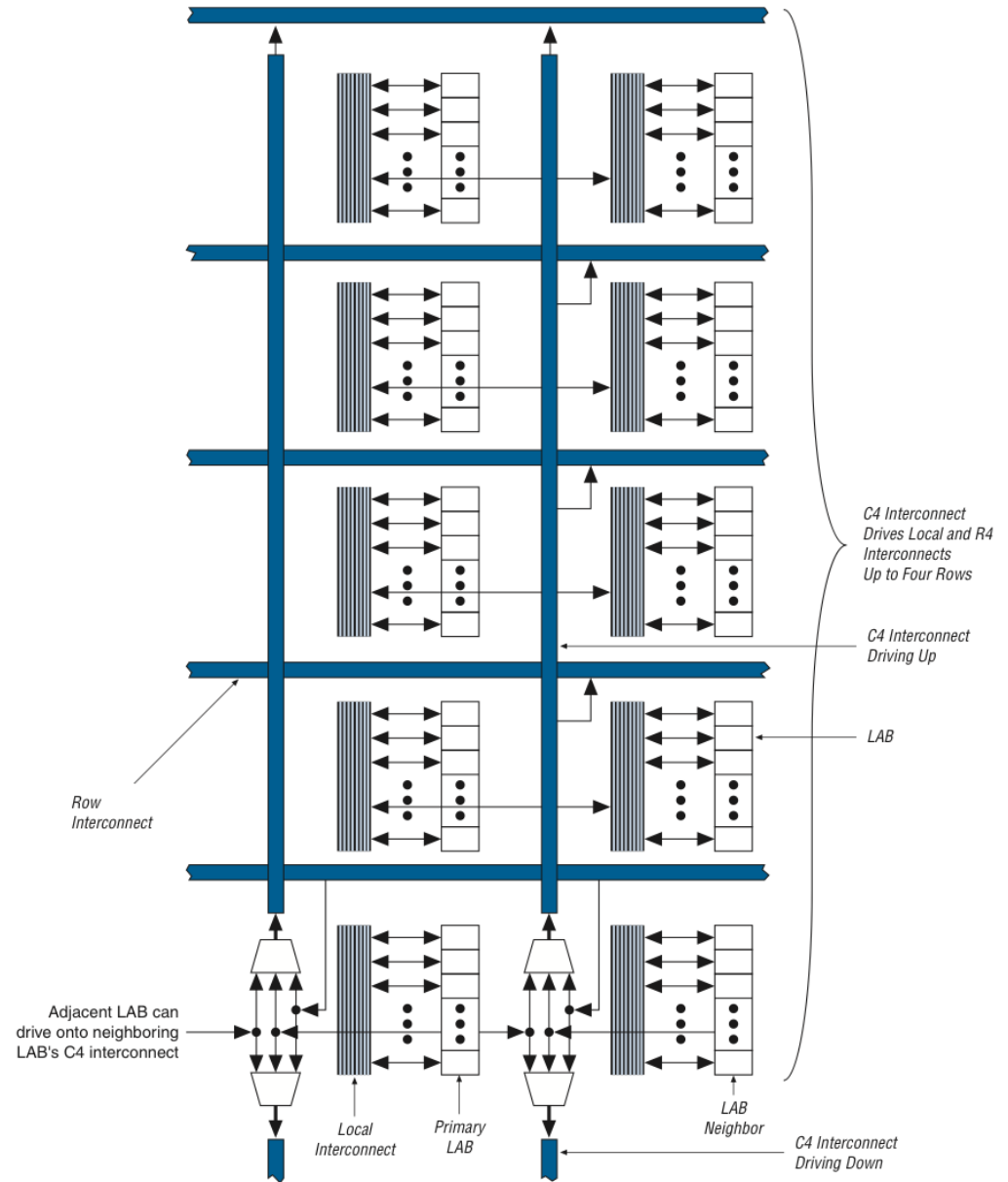

CLOCKS

Figure 2-12. EP2C15 & Larger PLL, CLK[], DPCLK[] & Clock Control Block Locations

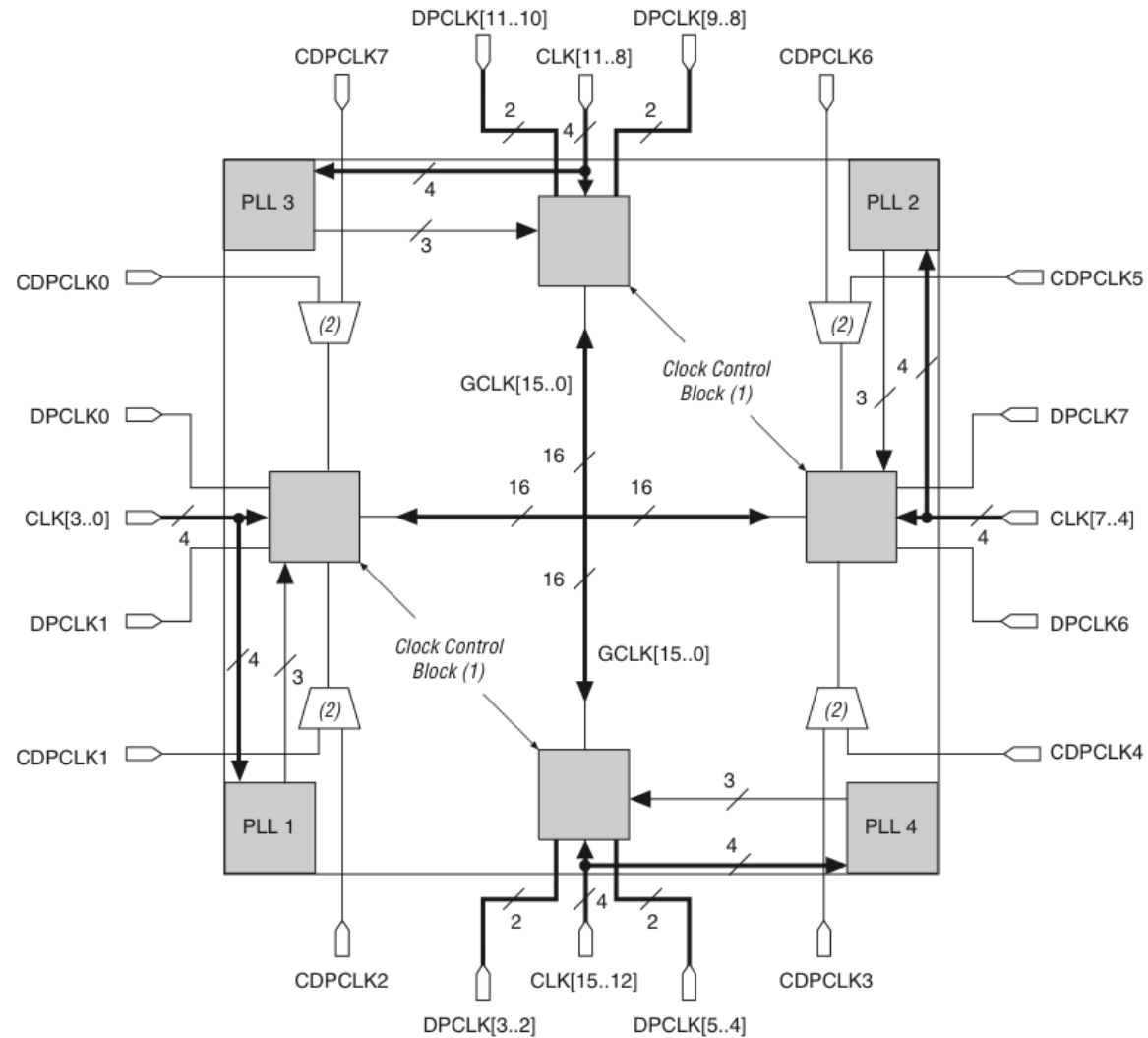

CLOCKS




- Dedicated clock pins
 - low-skew
- Dual-purpose clock pins
 - have programmable delays
 - drive clock control block
- 8 - 16 global clocks
 - Used for all high-fanout control signals
 - clock, reset, enable
 - Driven by clock control block
 - Also locally by logic

CLOCK CONTROL BLOCK


- Selects global clock input
- One per global clock

Figure 2-13. Clock Control Block

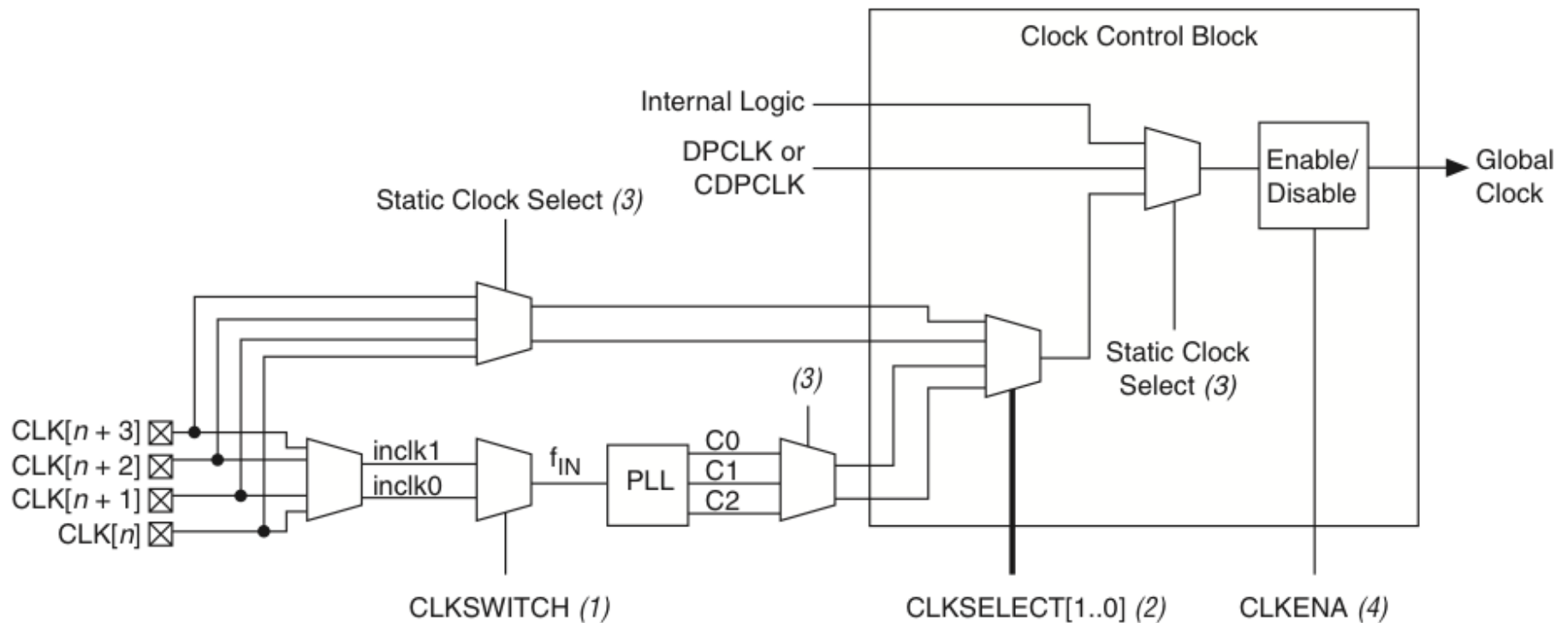

PLL

Figure 2-16. Cyclone II PLL Note (1)

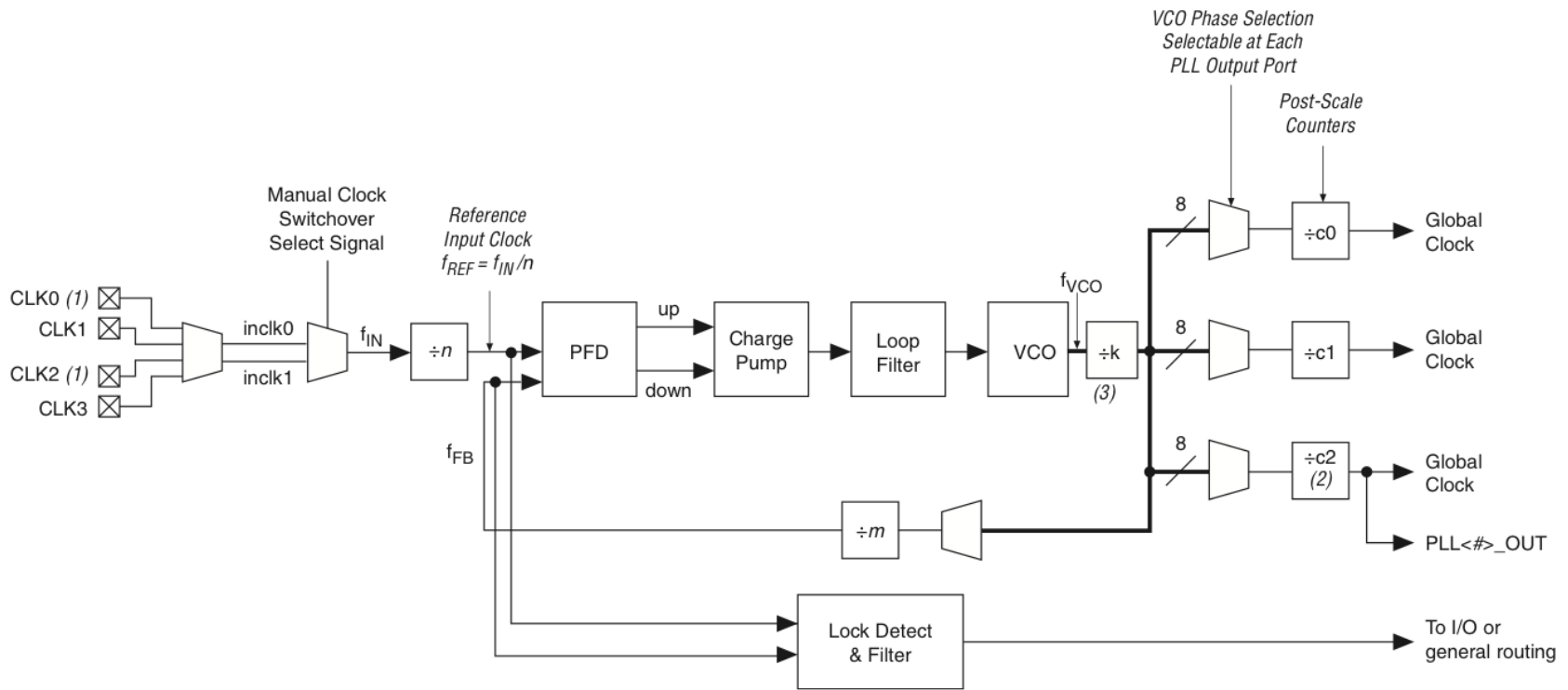

4K MEMORY BLOCK

Feature	Description
Maximum performance (1)	250 MHz
Total RAM bits per M4K block (including parity bits)	4,608
Configurations supported	4K × 1 2K × 2 1K × 4 512 × 8 512 × 9 256 × 16 256 × 18 128 × 32 (not available in true dual-port mode) 128 × 36 (not available in true dual-port mode)
Parity bits	One parity bit for each byte. The parity bit, along with internal user logic, can implement parity checking for error detection to ensure data integrity.
Byte enable	M4K blocks support byte writes when the write port has a data width of 1, 2, 4, 8, 9, 16, 18, 32, or 36 bits. The byte enables allow the input data to be masked so the device can write to specific bytes. The unwritten bytes retain the previous written value.
Packed mode	Two single-port memory blocks can be packed into a single M4K block if each of the two independent block sizes are equal to or less than half of the M4K block size, and each of the single-port memory blocks is configured in single-clock mode.
Address clock enable	M4K blocks support address clock enable, which is used to hold the previous address value for as long as the signal is enabled. This feature is useful in handling misses in cache applications.
Memory initialization file (.mif)	When configured as RAM or ROM, you can use an initialization file to pre-load the memory contents.
Power-up condition	Outputs cleared
Register clears	Output registers only
Same-port read-during-write	New data available at positive clock edge
Mixed-port read-during-write	Old data available at positive clock edge


4K MEMORY

Table 2–7. M4K Memory Modes

Memory Mode	Description
Single-port memory	M4K blocks support single-port mode, used when simultaneous reads and writes are not required. Single-port memory supports non-simultaneous reads and writes.
Simple dual-port memory	Simple dual-port memory supports a simultaneous read and write.
Simple dual-port with mixed width	Simple dual-port memory mode with different read and write port widths.
True dual-port memory	True dual-port mode supports any combination of two-port operations: two reads, two writes, or one read and one write at two different clock frequencies.
True dual-port with mixed width	True dual-port mode with different read and write port widths.
Embedded shift register	M4K memory blocks are used to implement shift registers. Data is written into each address location at the falling edge of the clock and read from the address at the rising edge of the clock.
ROM	The M4K memory blocks support ROM mode. A MIF initializes the ROM contents of these blocks.
FIFO buffers	A single clock or dual clock FIFO may be implemented in the M4K blocks. Simultaneous read and write from an empty FIFO buffer is not supported.


MEMORY CONNECTIONS

Figure 2-17. M4K RAM Block LAB Row Interface

 


MULTIPLIER

Figure 2-18. Multiplier Block Architecture

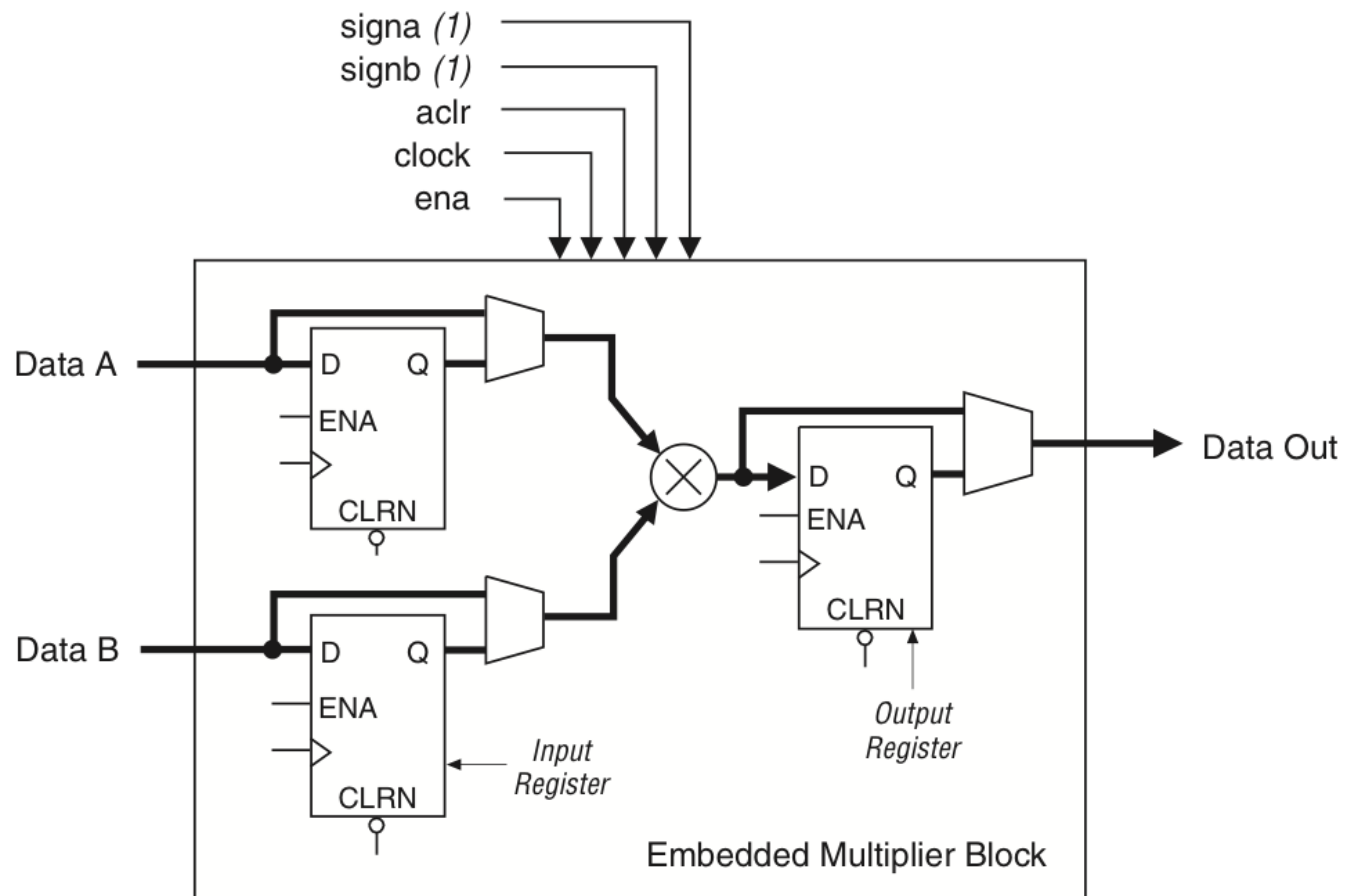

MULTIPLIER CONNECTIONS


Figure 2–19. Embedded Multiplier LAB Row Interface

 


I/O BLOCK

- Output pin
 - Combinational
 - Registered
- Input pin
 - Combinational
 - Registered
- In/Out (tri-state) pin
 - Mix of both

Figure 2-20. Cyclone II IOE Structure

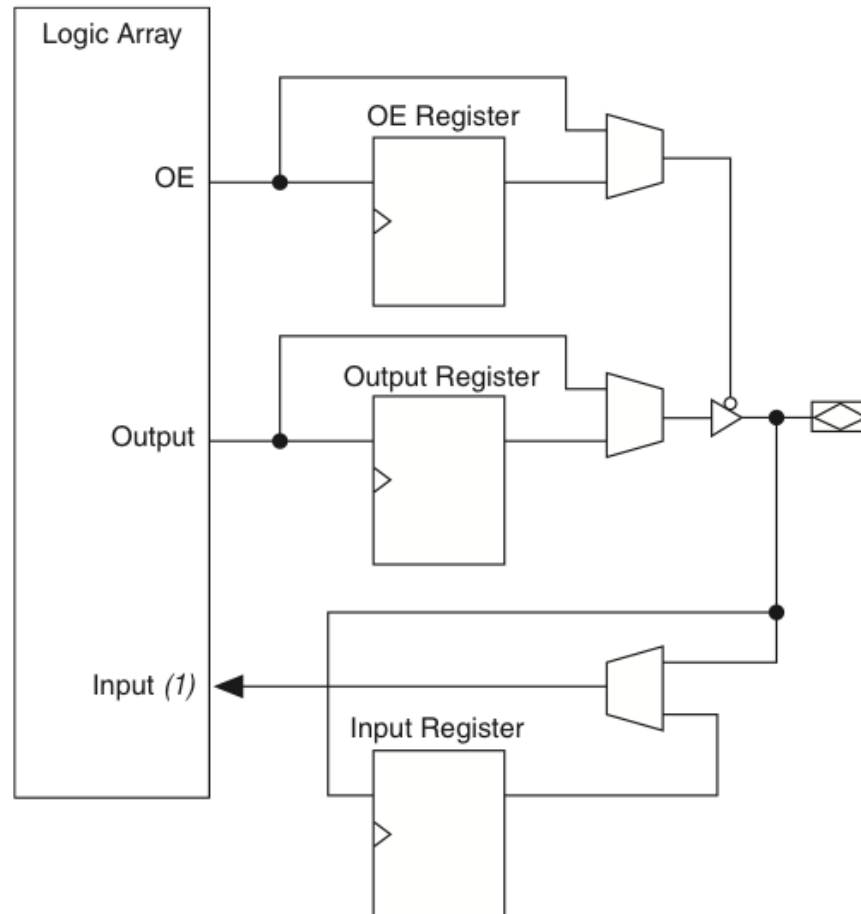


CONNECTIONS TO I/O BLOCK (5 PINS)

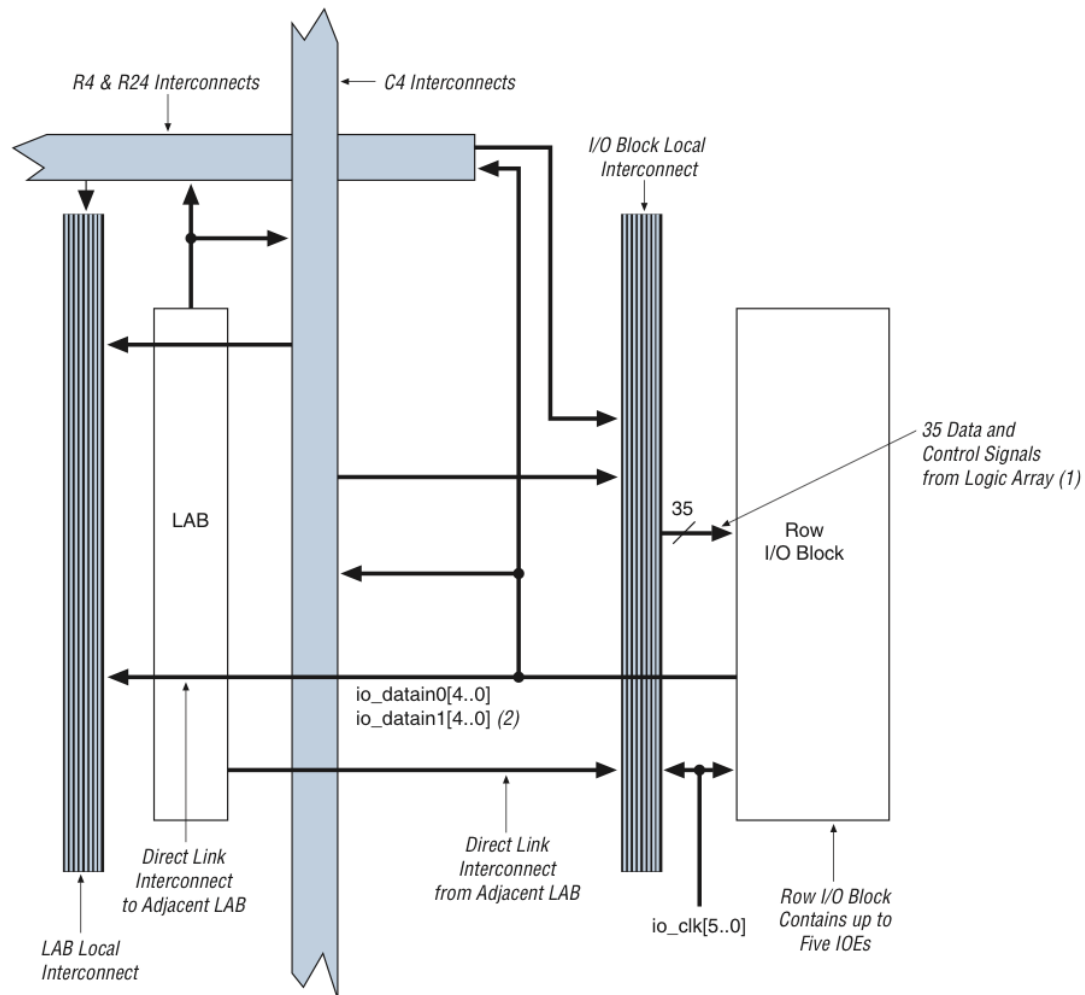

MORE I/O DETAIL

Figure 2–25. Cyclone II IOE in Bidirectional I/O Configuration

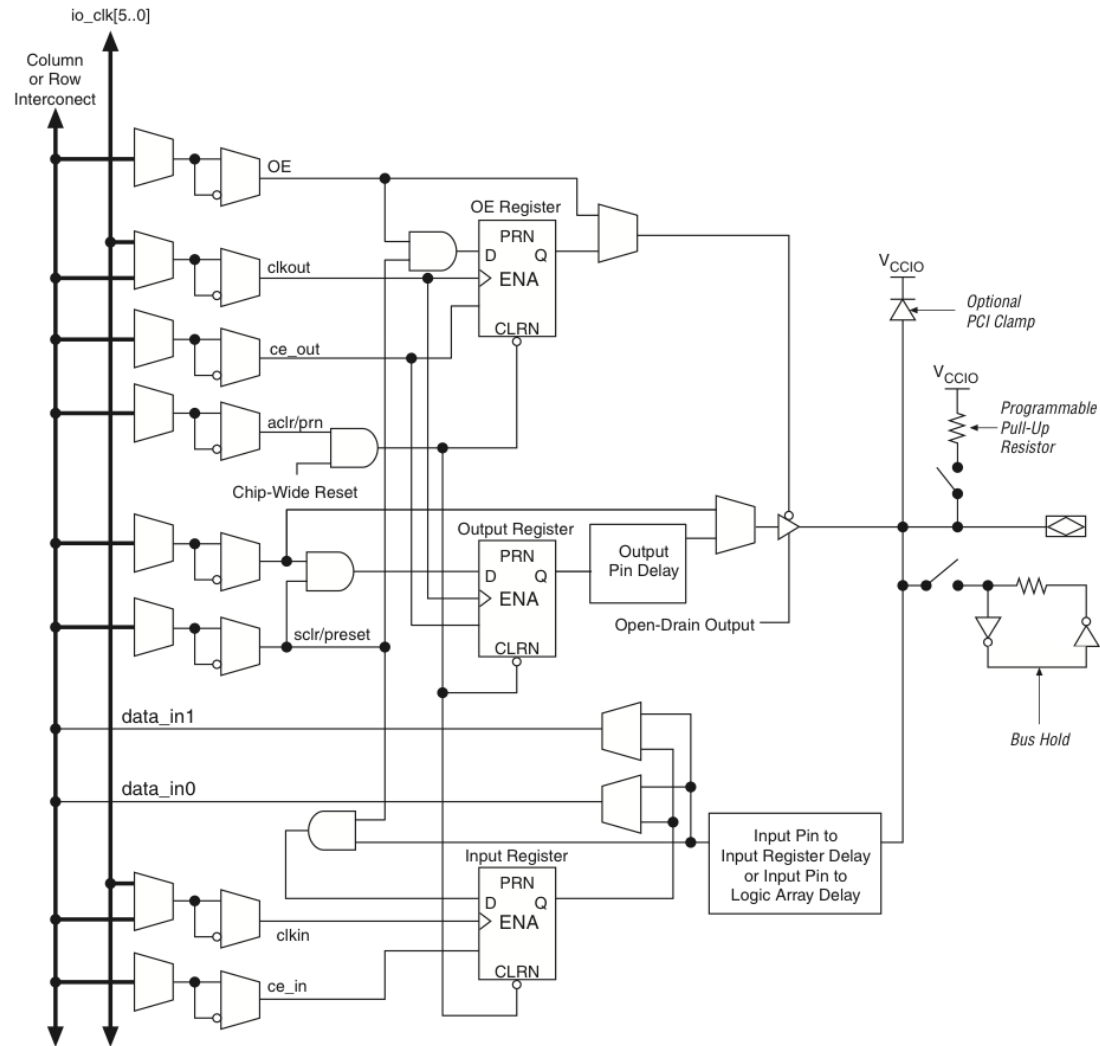

CONFIGURABLE I/Os




- Single-ended and differential
- Voltage and current mode
 - External reference voltage
- Range of voltages: 1.5v, 1.8v, 2.0v, 2.5v, 3.3v
- Range of standards: LVTTL, LVCMOS, SSTL, HSTL, LVDS, LVPECL
- Programmable drive strength: 4 - 20 mA
 - Interface requirement
 - Slew rate control

- I/Os arranged in Banks
 - 4 - 8 per chip
 - Banks each have a different power bus


CYCLONE FLOORPLAN

Figure 2-1. Cyclone II EP2C20 Device Block Diagram

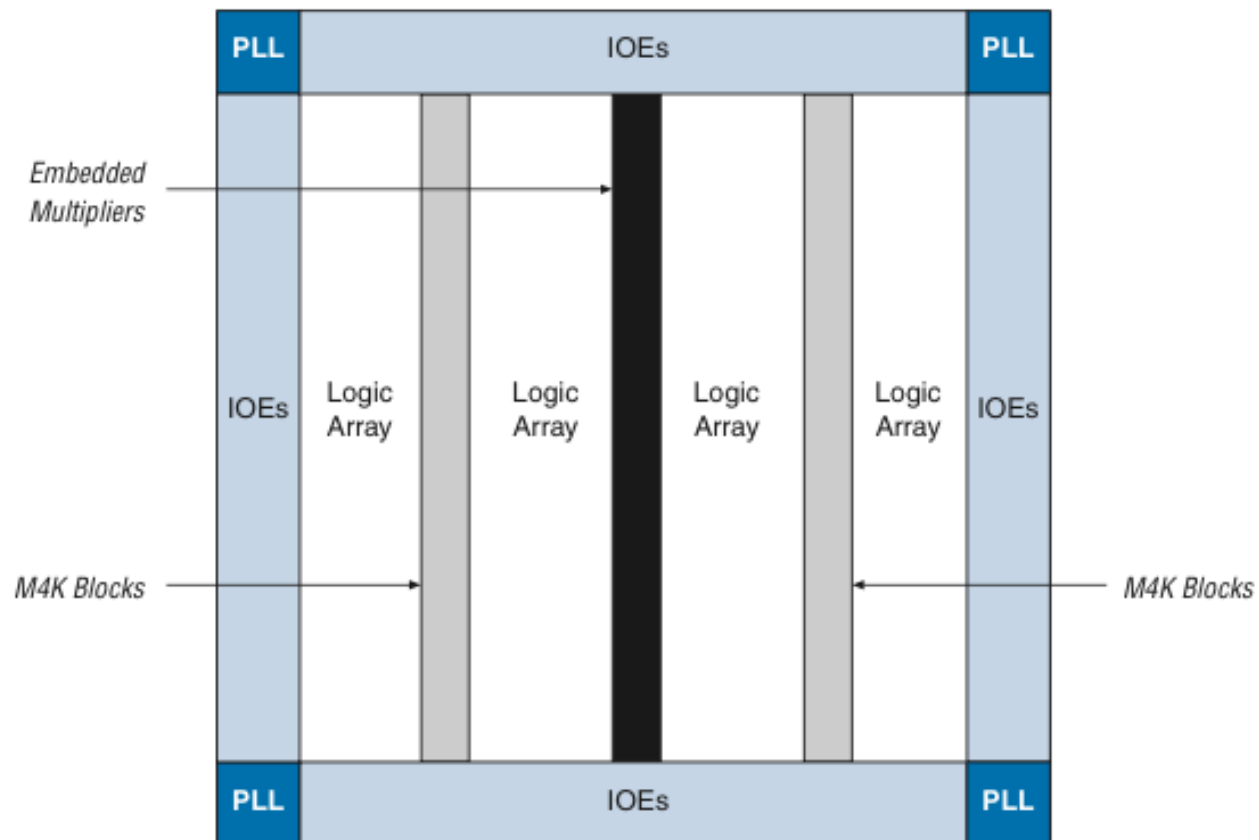


SUPPORT FOR MEMORY INTERFACES

Figure 2-27. DDR SDRAM Interfacing

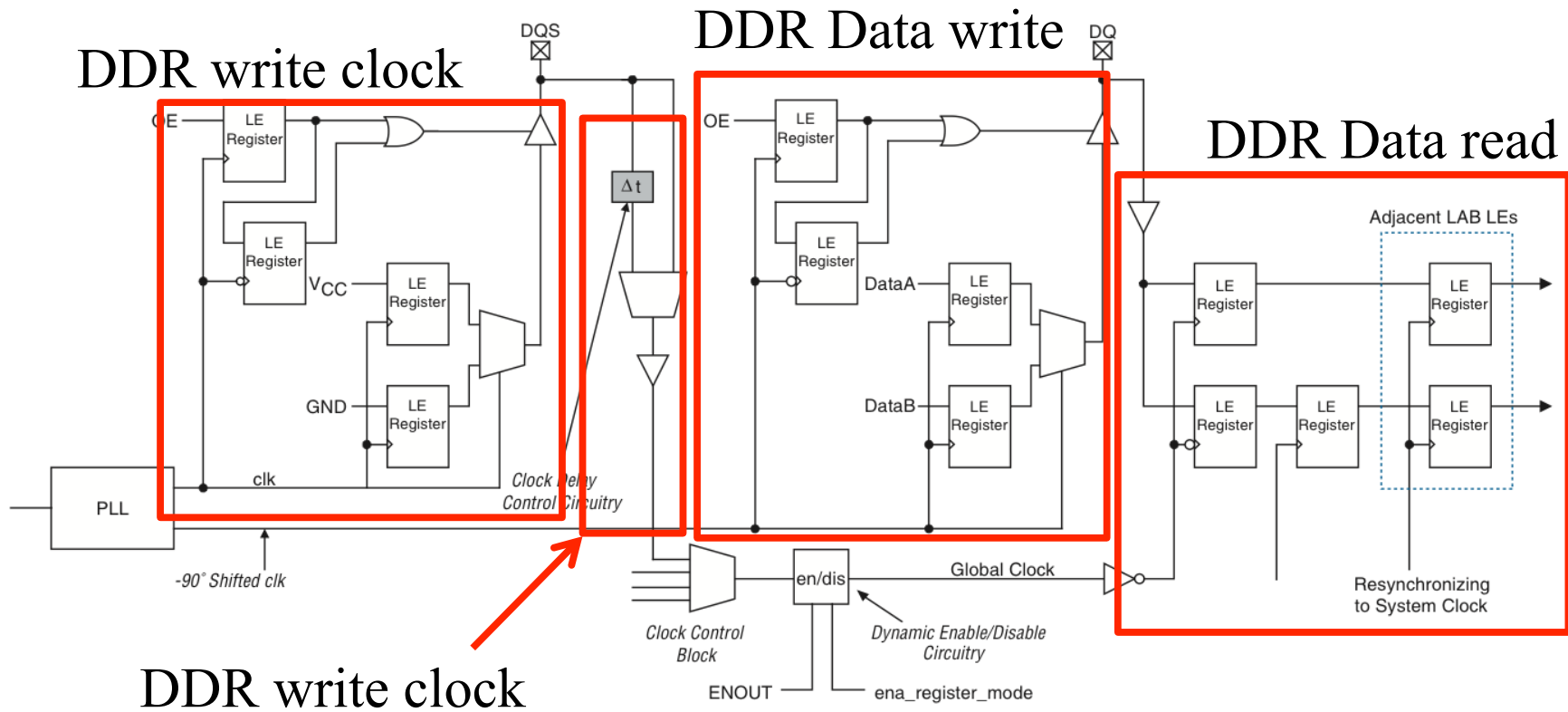


DETAILS OF ONE XILINX VIRTEX SLICE

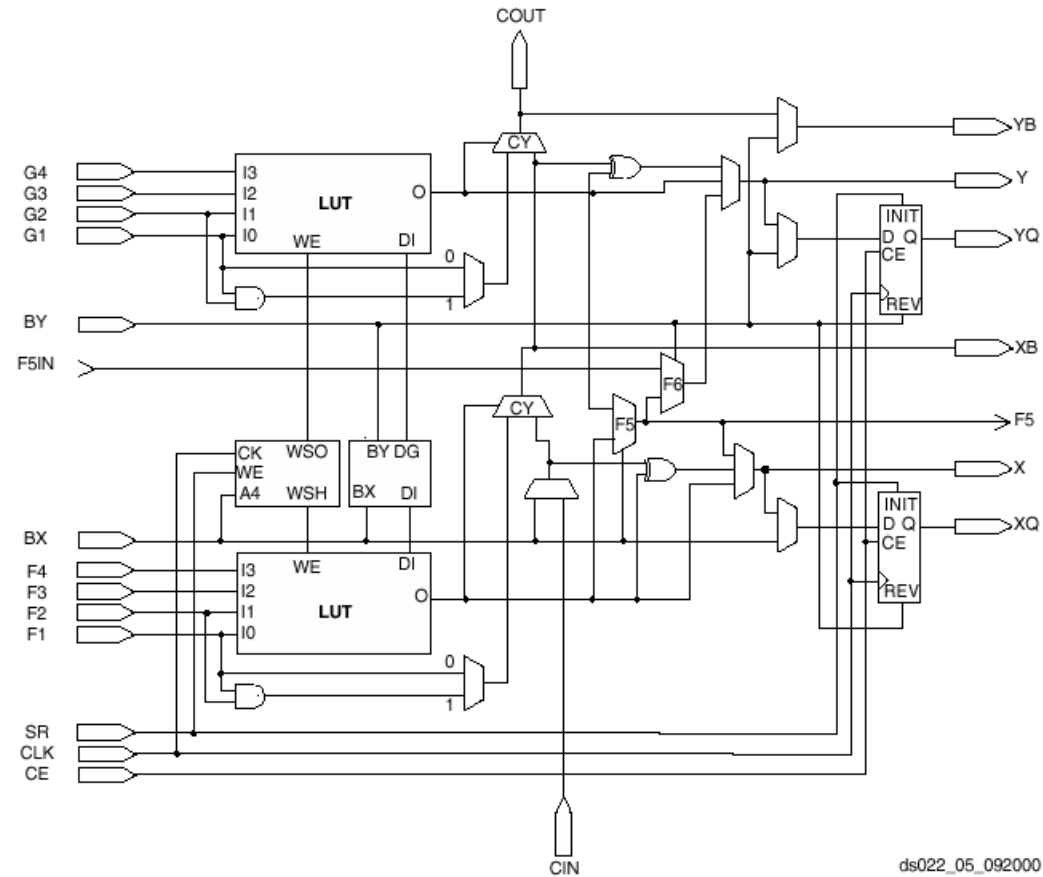

ds022_05_092000

Figure 5: Detailed View of Virtex-E Slice

IMPLEMENTS ANY TWO 4-INPUT FUNCTIONS

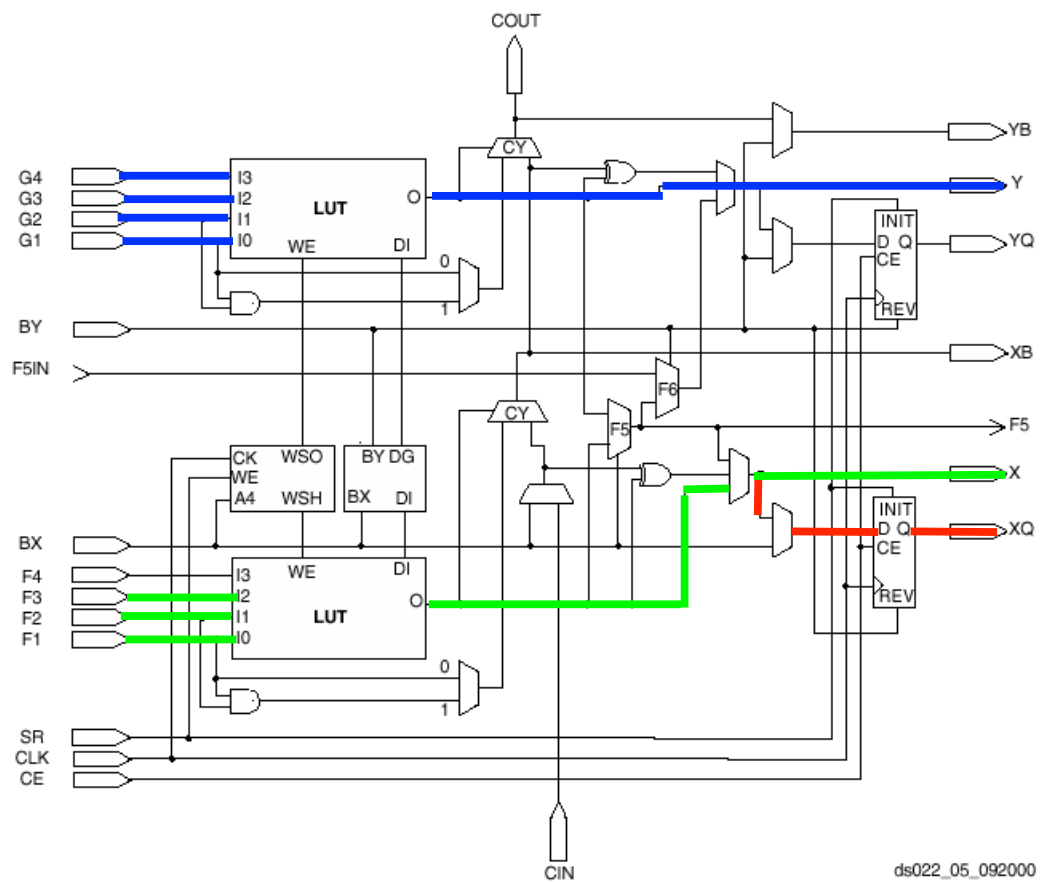


4-input
function

3-input
function;
registered

Figure 5: Detailed View of Virtex-E Slice

IMPLEMENTS ANY 5-INPUT FUNCTION

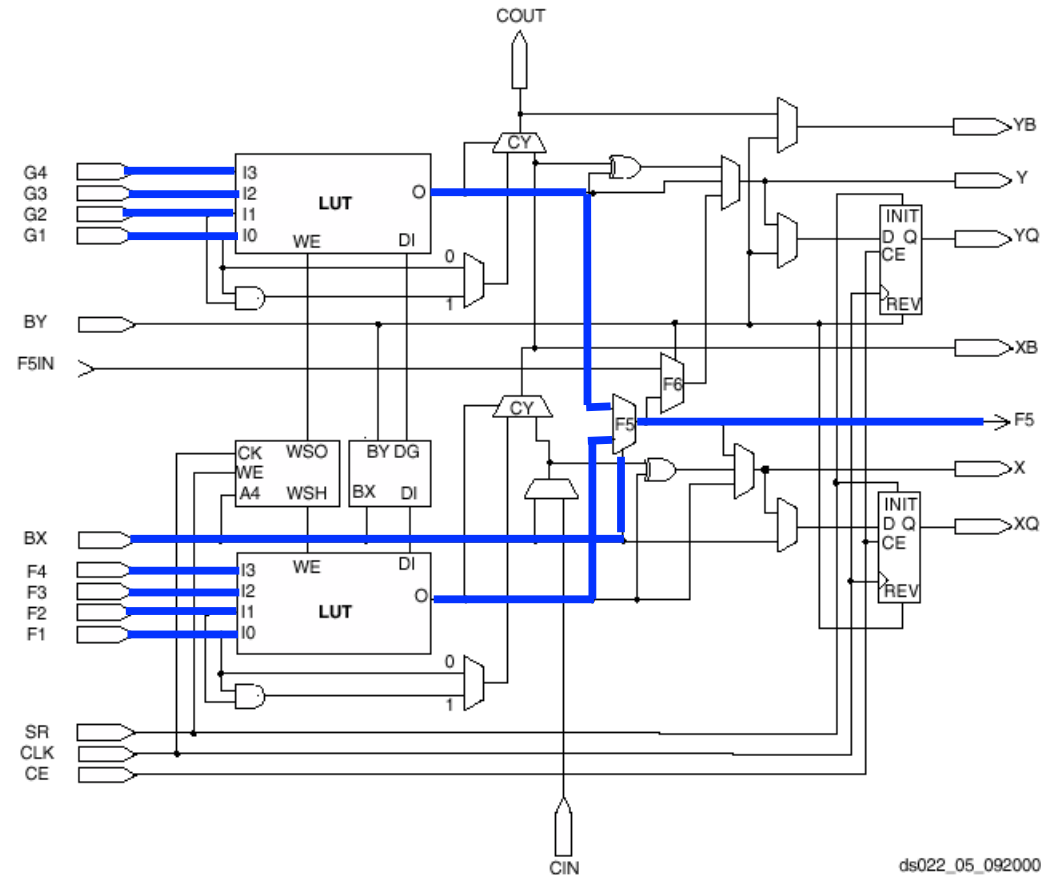


5-input
function

Figure 5: Detailed View of Virtex-E Slice

TWO SLICES: ANY 6-INPUT FUNCTION

from
other
slice

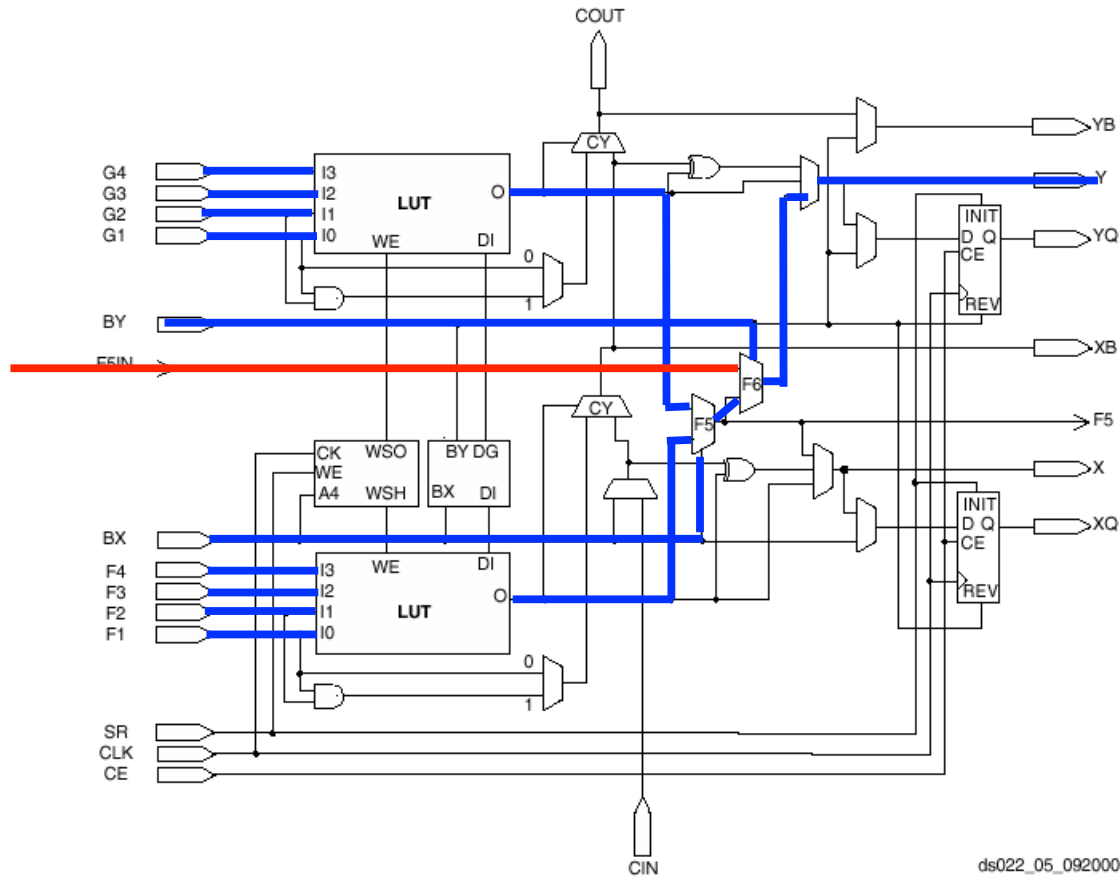

6-input
function

Figure 5: Detailed View of Virtex-E Slice

FAST CARRY CHAIN: ADD TWO BITS PER SLICE

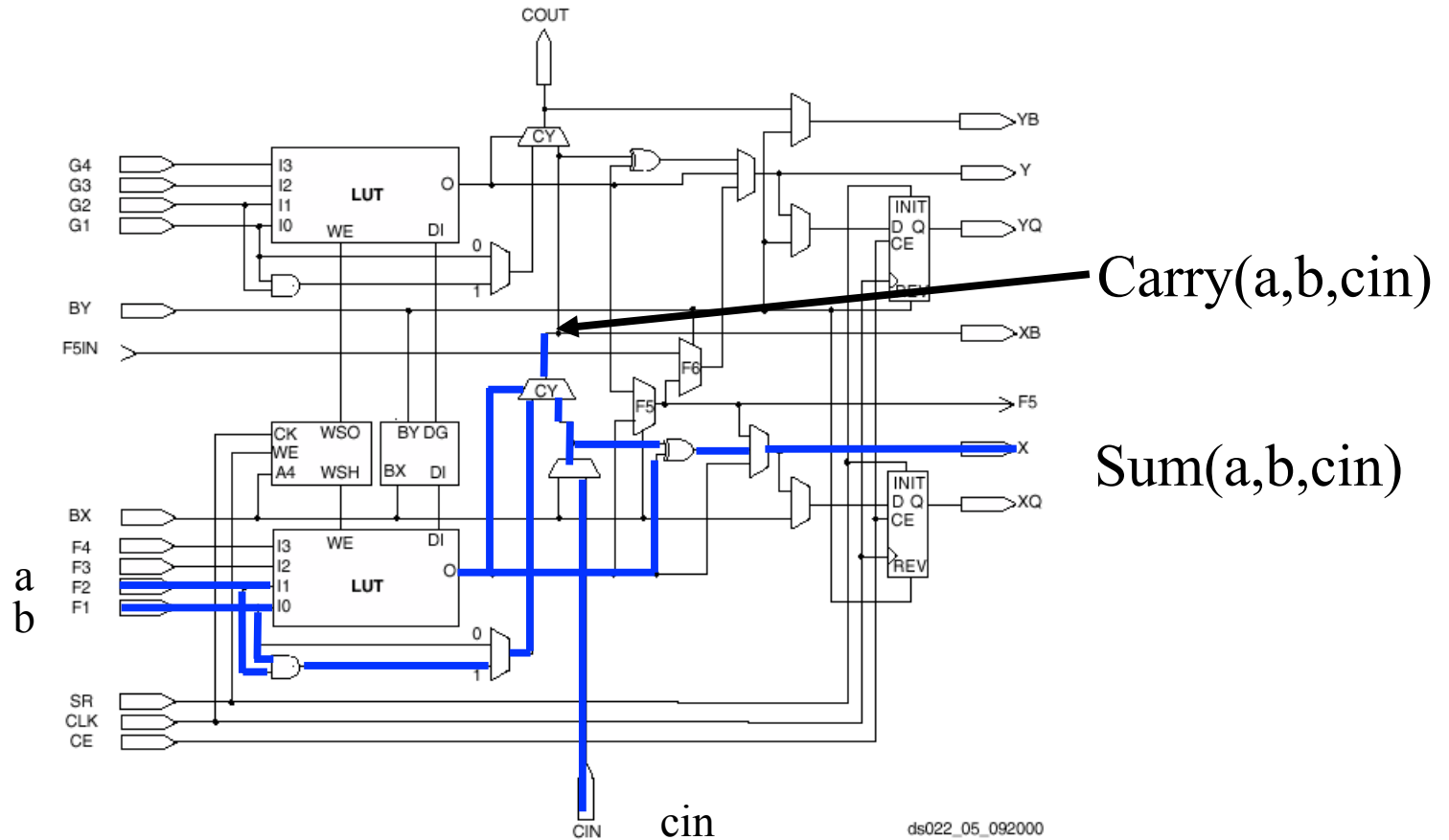


Figure 5: Detailed View of Virtex-E Slice

LOOKUP TABLES USED AS MEMORY (16 x 2) [DISTRIBUTED MEMORY]

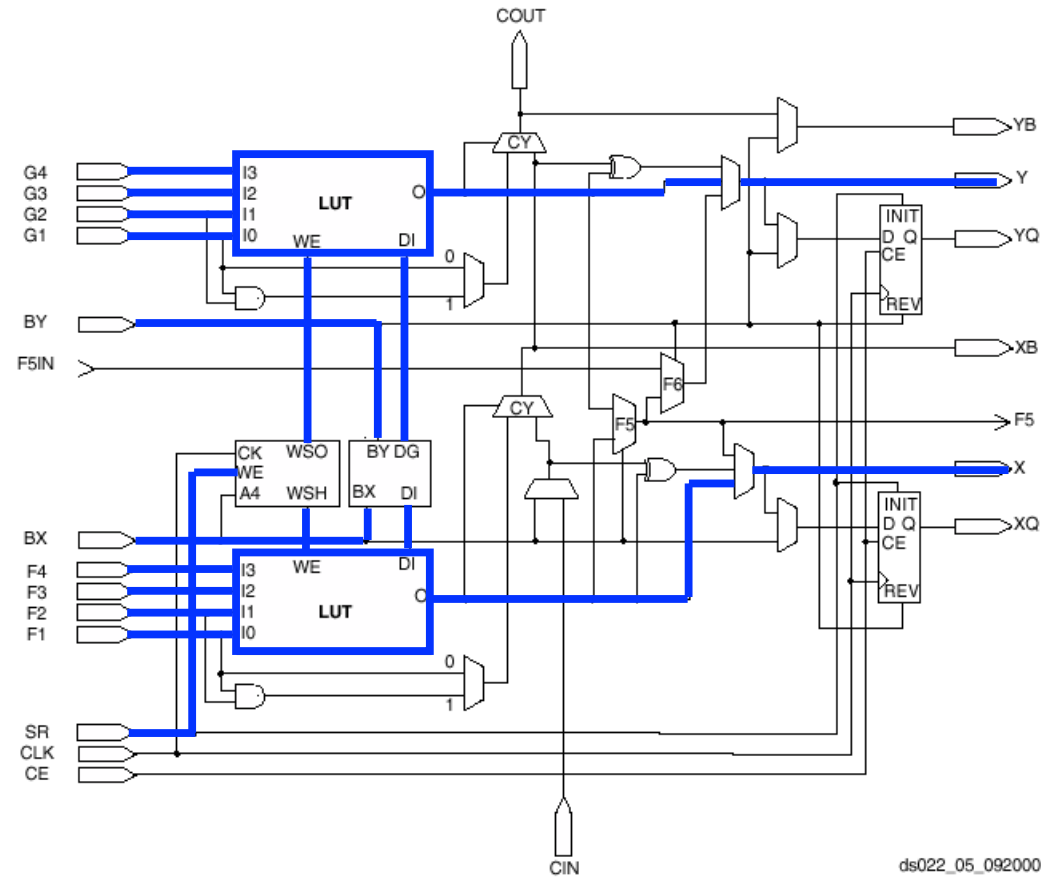


Figure 5: Detailed View of Virtex-E Slice

COMPUTER-AIDED DESIGN



- Can't design FPGAs by hand
 - way too much logic to manage, hard to make changes
- Hardware description languages
 - specify functionality of logic at a high level
- Validation - high-level simulation to catch specification errors
 - verify pin-outs and connections to other system components
 - low-level to verify mapping and check performance
- Logic synthesis
 - process of compiling HDL program into logic gates and flip-flops
- Technology mapping
 - map the logic onto elements available in the implementation technology (LUTs for Xilinx FPGAs)

CAD TOOL PATH (CONT'D)



- Placement and routing
 - assign logic blocks to functions
 - make wiring connections
- Timing analysis - verify paths
 - determine delays as routed
 - look at critical paths and ways to improve
- Partitioning and constraining
 - if design does not fit or is unroutable as placed split into multiple chips
 - if design is too slow prioritize critical paths, fix placement of cells, etc.
 - few tools to help with these tasks exist today
- Generate programming files - bits to be loaded into chip for configuration

CAD TOOLS



- Verilog (or VHDL) use to specify logic at a high-level
 - combine with schematics, library components
- Synthesis: Synopsys/Synplicity/Quartus/ISE/Precision
 - compiles Verilog to logic
 - maps logic to the FPGA cells
 - optimizes logic
- APR - automatic place and route (simulated annealing)
 - provides controllability through constraints
 - handles global signals
- STA - measure delay properties of mapping and aid in iteration

APPLICATIONS OF FPGAs



- Implementation of random logic
 - easier changes at system-level (one device is modified)
 - can eliminate need for full-custom chips
- Prototyping
 - ensemble of gate arrays used to emulate a circuit to be manufactured
 - get more/better/faster debugging done than possible with simulation
- Reconfigurable hardware
 - one hardware block used to implement more than one function
 - functions must be mutually-exclusive in time
 - can greatly reduce cost while enhancing flexibility
 - RAM-based only option
- Special-purpose computation engines
 - hardware dedicated to solving one problem (or class of problems)
 - accelerators attached to general-purpose computers