



Chapter 3 :: Sequential Logic Design

Digital Design and Computer Architecture

David Money Harris and Sarah L. Harris


Bistable Circuit

  - Fundamental building block of other state elements
- Two outputs: Q , \overline{Q}
- No inputs




Bistable Circuit Analysis

 - Consider the two possible cases:
 - $Q = 0$: then $\bar{Q} = 1$ and $Q = 0$ (consistent)



 - $Q = 1$: then $\bar{Q} = 0$ and $Q = 1$ (consistent)




- Bistable circuit stores 1 bit of state in the state variable, Q (or \bar{Q})
- But there are **no inputs to control the state**



SR (Set/Reset) Latch


- SR Latch

 


- Consider the four possible cases:
 - $S = 1, R = 0$
 - $S = 0, R = 1$
 - $S = 0, R = 0$
 - $S = 1, R = 1$

SR Latch Analysis

 – $S = 1, R = 0$: then $Q = 1$ and $\overline{Q} = 0$




 – $S = 0, R = 1$: then $Q = 0$ and $\overline{Q} = 1$




SR Latch Analysis

 – $S = 1, R = 0$: then $Q = 1$ and $\overline{Q} = 0$



 
– $S = 0, R = 1$: then $Q = 0$ and $\overline{Q} = 1$




SR Latch Analysis

– $S = 0, R = 0$: then $Q = Q_{prev}$


$Q_{prev} = 0$

 

$Q_{prev} = 1$

 


 – $S = 1, R = 1$: then $Q = 0$ and $\bar{Q} = 0$




SR Latch Analysis

 - $S = 0, R = 0$: then $Q = Q_{prev}$ and $\bar{Q} = \bar{Q}_{prev}$ (**memory!**)



 
- $S = 1, R = 1$: then $Q = 0$ and $\bar{Q} = 0$ (**invalid state: $\bar{Q} \neq \text{NOT } Q$**)




SR Latch Symbol

- SR stands for Set/Reset Latch
 - Stores one bit of state (Q)
- Control what value is being stored with S , R inputs
 - **Set:** Make the output 1 ($S = 1, R = 0, Q = 1$)
 - **Reset:** Make the output 0 ($S = 0, R = 1, Q = 0$)
- **Must do something to avoid invalid state (when $S = R = 1$)**

SR Latch Symbol

 


D Latch Internal Circuit

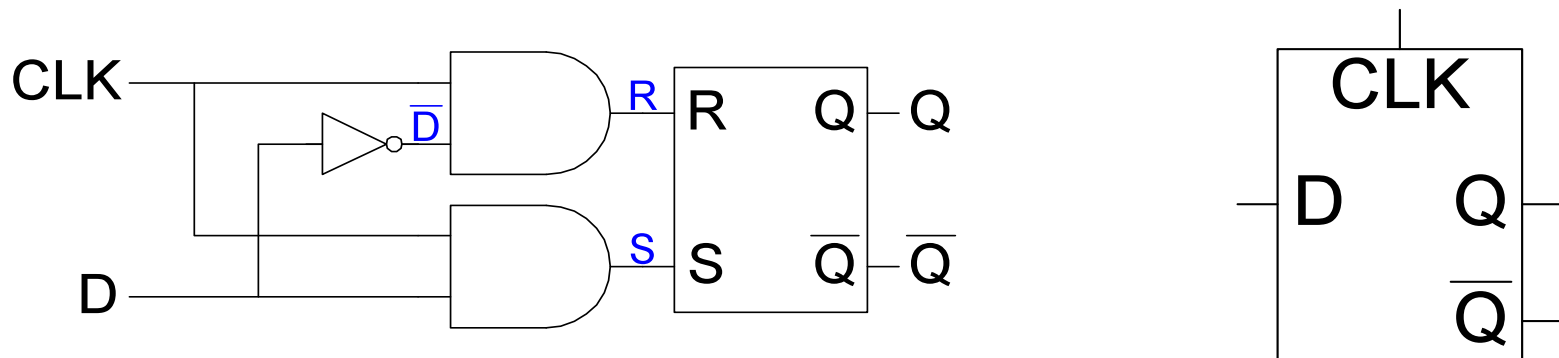

<i>CLK</i>	<i>D</i>	\overline{D}	<i>S</i>	<i>R</i>	<i>Q</i>	\overline{Q}
0	X					
1	0					
1	1					

D Latch Internal Circuit

 


CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X	\overline{X}	0	0	Q_{prev}	\overline{Q}_{prev}
1	0	1	0	1	0	1
1	1	0	1	0	1	0

D Flip-Flop

- Two inputs: CLK , D
- *Function*
 - The flip-flop “samples” D on the rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on the rising edge of CLK
- A flip-flop is called an *edge-triggered* device because it is activated on the clock edge

D Flip-Flop Symbols

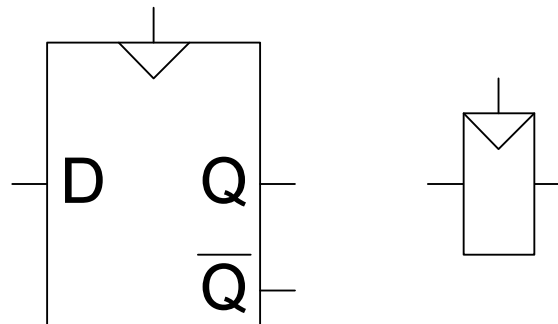

D Flip-Flop Internal Circuit

- Two back-to-back latches (L1 and L2) controlled by complementary clocks


- When $CLK = 0$

- L1 is transparent
- L2 is opaque
- D passes through to N1

- When $CLK = 1$

- L2 is transparent
- L1 is opaque
- N1 passes through to Q

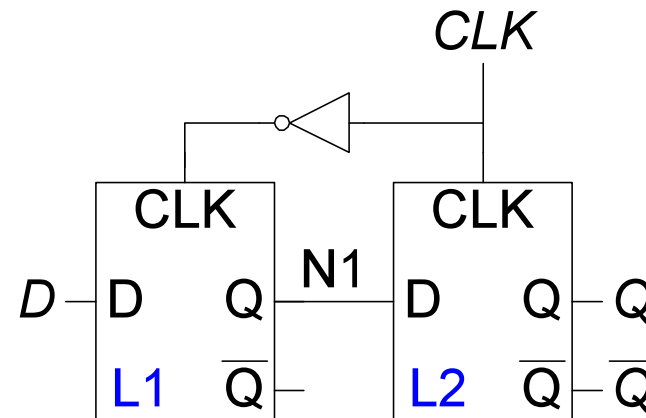- Thus, on the edge of the clock (when CLK rises from $0 \rightarrow 1$)
 - D passes through to Q




Timing

- Flip-flop samples D at clock edge
- D must be stable when it is sampled
- Similar to a photograph, D must be stable around the clock edge
- If D is changing when it is sampled, metastability can occur


Input Timing Constraints

 - Setup time: t_{setup} = time *before* the clock edge that data must be stable (i.e. not changing)
- Hold time: t_{hold} = time *after* the clock edge that data must be stable
- Aperture time: t_a = time around clock edge that data must be stable ($t_a = t_{\text{setup}} + t_{\text{hold}}$)



Output Timing Constraints

 - Propagation delay: t_{pcq} = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- Contamination delay: t_{ccq} = time after clock edge that Q might be unstable (i.e., start changing)




Dynamic Discipline

- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.
- Specifically, the input must be stable
 - at least t_{setup} before the clock edge
 - at least until t_{hold} after the clock edge


Dynamic Discipline

 - The delay between registers has a **minimum** and **maximum** delay, dependent on the delays of the circuit elements



Setup Time Constraint

 
- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.



$$T_c \geq$$

Setup Time Constraint

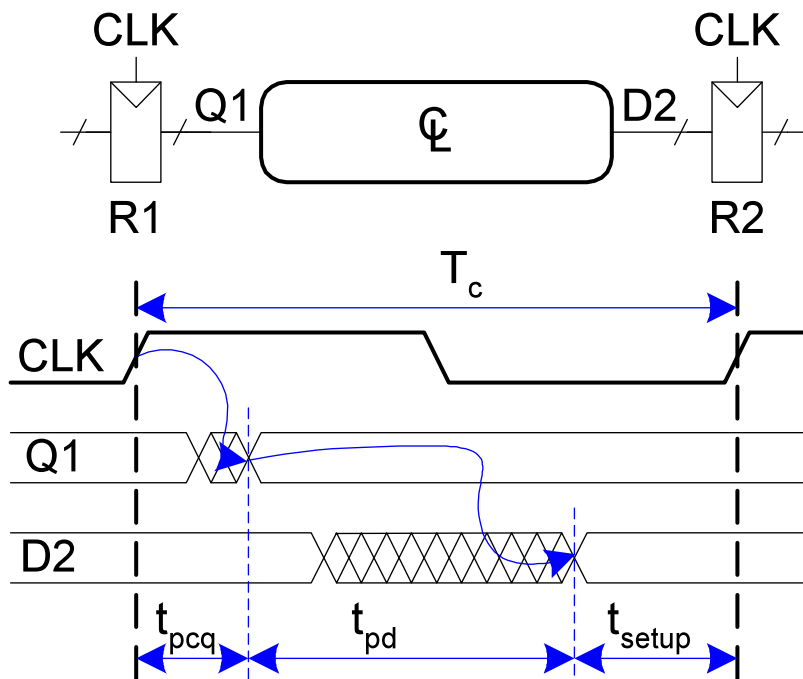
- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq$$

Setup Time Constraint

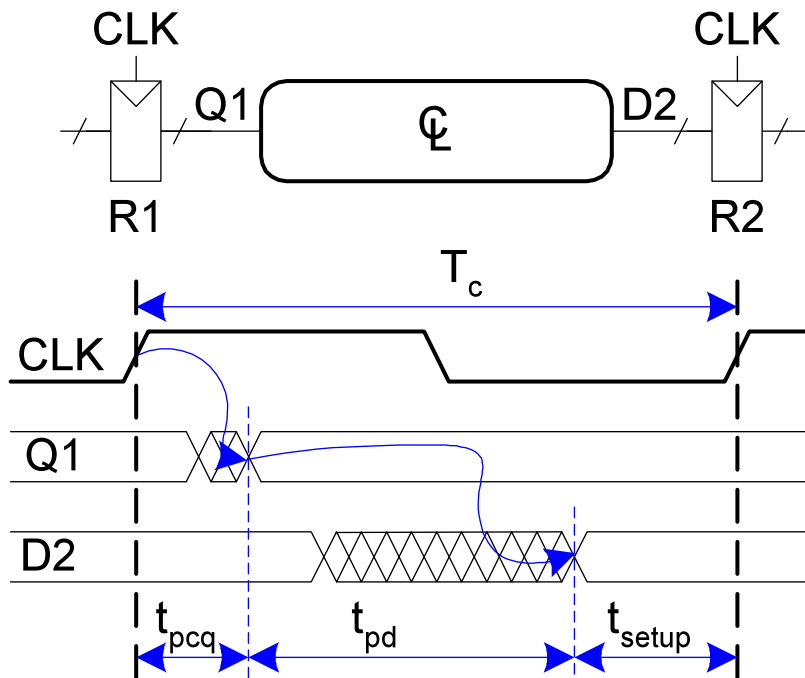
- The setup time constraint depends on the **maximum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least t_{setup} before the clock edge.



$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$

Hold Time Constraint

 
- The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$t_{\text{hold}} <$

Hold Time Constraint

 
- The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$$t_{\text{hold}} < t_{ccq} + t_{cd}$$
$$t_{cd} >$$


Hold Time Constraint

 - The hold time constraint depends on the **minimum** delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least t_{hold} after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

Timing Analysis

 

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$

per gate

$$\left[\begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:


$$T_c \geq$$

$$f_c = 1/T_c =$$

Hold time constraint:

$$t_{ccq} + t_{pd} > t_{hold} ?$$

Timing Analysis

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$

per gate

$$\left[\begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:


$$t_{ccq} + t_{pd} > t_{hold} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ? \text{ No!}$$



Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c =$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$

per gate


$$\left[\begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:

$$t_{ccq} + t_{pd} > t_{hold} ?$$

Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$

per gate

$$\left[\begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$


Hold time constraint:

$$t_{ccq} + t_{pd} > t_{hold} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$


Clock Skew

 - The clock doesn't arrive at all registers at the same time
- Skew is the difference between two clock edges
- Examine the worst case to guarantee that the dynamic discipline is not violated for any register – many registers in a system!



Setup Time Constraint with Clock Skew

 
- In the worst case, the CLK2 is earlier than CLK1



$$T_c \geq$$

Setup Time Constraint with Clock Skew

 - In the worst case, the CLK2 is earlier than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

$$t_{pd} \leq$$

Setup Time Constraint with Clock Skew

 - In the worst case, the CLK2 is earlier than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$

Hold Time Constraint with Clock Skew

 
- In the worst case, CLK2 is later than CLK1



$$t_{ccq} + t_{cd} >$$
$$t_{cd} >$$

Hold Time Constraint with Clock Skew

 
- In the worst case, CLK2 is later than CLK1



$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$
$$t_{cd} >$$

Hold Time Constraint with Clock Skew


 
- In the worst case, CLK2 is later than CLK1



$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$
$$t_{cd} > t_{hold} + t_{skew} - t_{ccq}$$


Violating the Dynamic Discipline

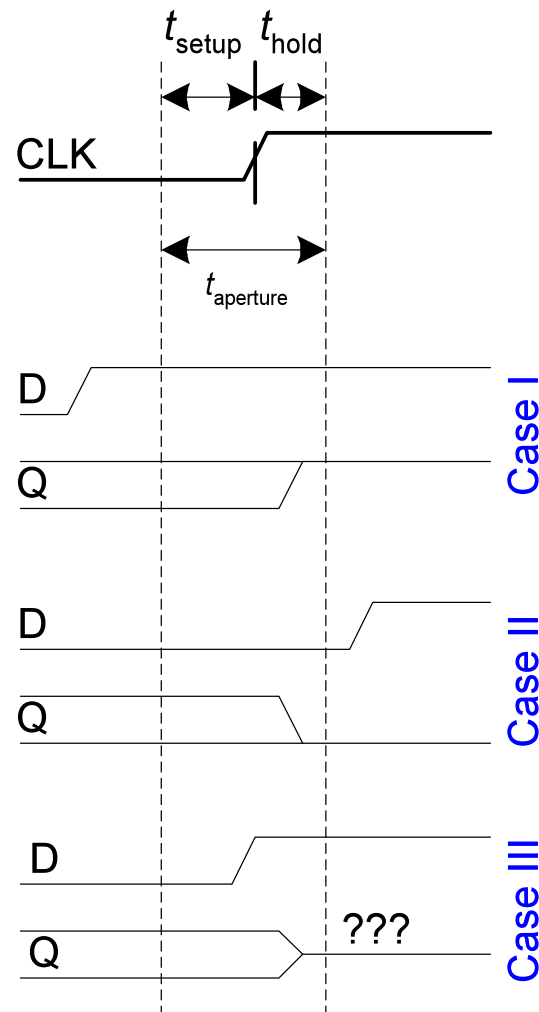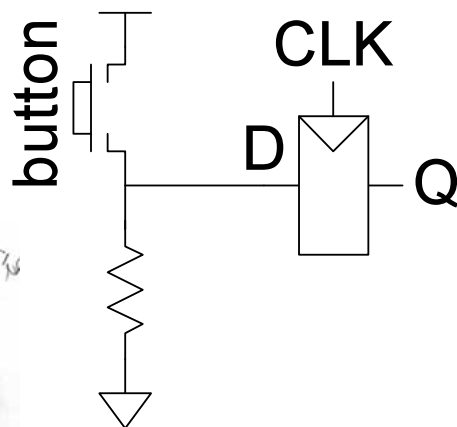- Asynchronous (for example, user) inputs might violate the dynamic discipline




Metastability

 - Any bistable device has two stable states and a metastable state between them
- A flip-flop has two stable states (1 and 0) and one metastable state
- If a flip-flop lands in the metastable state, it could stay there for an undetermined amount of time



Flip-flop Internals

 - Because the flip-flop has feedback, if Q is somewhere between 1 and 0, the cross-coupled gates will eventually drive the output to either rail (1 or 0, depending on which one it is closer to).



- A signal is considered metastable if it hasn't resolved to 1 or 0
- If a flip-flop input changes at a random time, the probability that the output Q is metastable after waiting some time, t , is:

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

t_{res} : time to resolve to 1 or 0

T_0, τ : properties of the circuit

Metastability

- Intuitively:
 - T_0/T_c describes the probability that the input changes at a bad time, i.e., during the aperture time

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$


- τ is a time constant indicating how fast the flip-flop moves away from the metastable state; it is related to the delay through the cross-coupled gates in the flip-flop

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

- In short, if a flip-flop samples a metastable input, if you wait long enough (t), the output will have resolved to 1 or 0 with high probability.


Synchronizers

 - Asynchronous inputs (D) are inevitable (user interfaces, systems with different clocks interacting, etc.).
- The goal of a synchronizer is to make the probability of failure (the output Q still being metastable) low.
- A synchronizer cannot make the probability of failure 0.



Synchronizer Internals

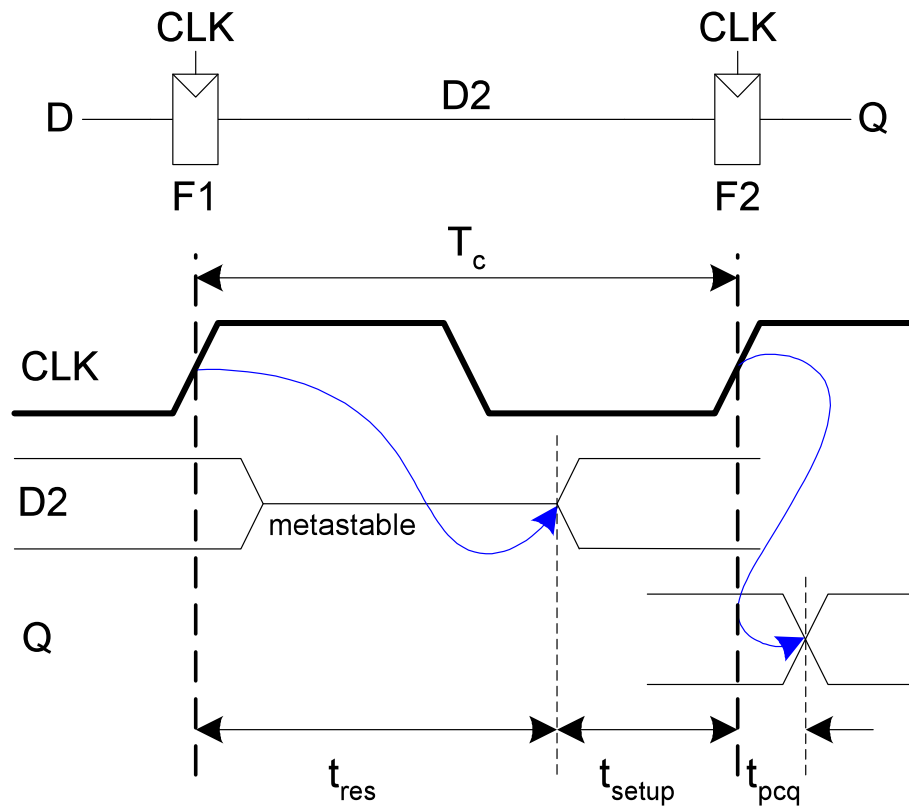
- A synchronizer can be built with two back-to-back flip-flops.
- Suppose the input D is transitioning when it is sampled by flip-flop 1, F1.
- The amount of time the internal signal D2 can resolve to a 1 or 0 is $(T_c - t_{\text{setup}})$.



Synchronizer Probability of Failure

For each sample, the probability of failure of this synchronizer is:
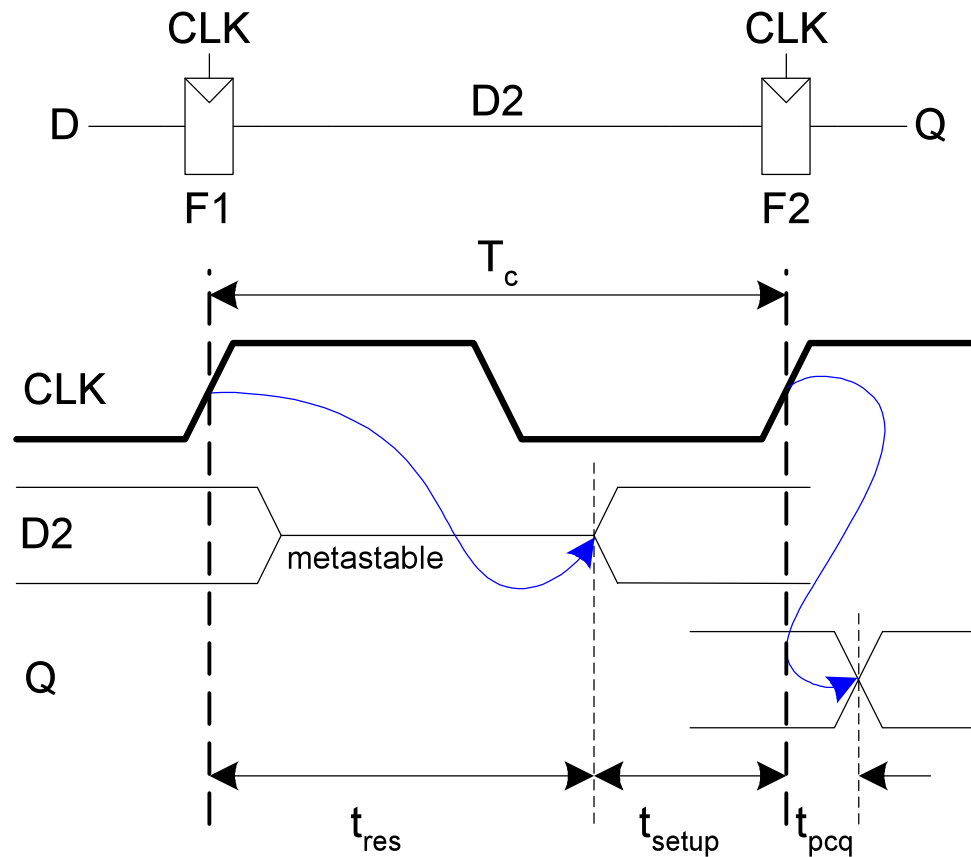
$$P(\text{failure}) = (T_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$



Synchronizer Mean Time Before Failure


- If the asynchronous input changes once per second, the probability of failure per second of the synchronizer is simply $P(\text{failure})$.
- In general, if the input changes N times per second, the probability of failure per second of the synchronizer is:

$$P(\text{failure})/\text{second} = (NT_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$

- Thus, the synchronizer fails, on average, $1/[P(\text{failure})/\text{second}]$
- This is called the *mean time between failures*, MTBF:

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] = (T_c/NT_0) e^{(T_c - t_{\text{setup}})/\tau}$$

Example Synchronizer

 


- Suppose: $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$ $\tau = 200 \text{ ps}$
 $T_0 = 150 \text{ ps}$ $t_{\text{setup}} = 100 \text{ ps}$
 $N = 10 \text{ events per second}$
- What is the probability of failure? MTBF?

$$P(\text{failure}) =$$

$$P(\text{failure})/\text{second} =$$

$$\text{MTBF} =$$

Example Synchronizer

 

- Suppose: $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$ $\tau = 200 \text{ ps}$
 $T_0 = 150 \text{ ps}$ $t_{\text{setup}} = 100 \text{ ps}$
 $N = 10 \text{ events per second}$
- What is the probability of failure? MTBF?

$$P(\text{failure}) = (150 \text{ ps}/2 \text{ ns}) e^{-(1.9 \text{ ns})/200 \text{ ps}}$$

$$= 5.6 \times 10^{-6}$$

$$P(\text{failure})/\text{second} = 10 \times (5.6 \times 10^{-6})$$

$$= 5.6 \times 10^{-5} / \text{second}$$

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] \approx 5 \text{ hours}$$