

```

// decoder : Q 1
module dec8x3(input1, input2, out);

input [1:0] input1 ;
input [5:0] input2 ;
output [2:0] out ;
reg [2:0] out ;

always @(input1 or input2)
begin
case (input1)
    0: out=2;
    1: out=6;
    2:
        case (input2[3:0])
            0 : out=2;
            2 : out=6;
            4 : out=0;
            5 : out=1;
            10: out=7;
            default: out='bx;
        endcase
    endcase
default: out='bx;
endcase
end

endmodule

```

```

// Alu 32 : Q 2
module alu32(a, b, opcode, r, v, z);
input [31:0]a;
input [31:0]b;
input [2:0]opcode;
output [31:0]r;
output v, z;
reg [31:0]r;
reg v, z;

always @ (a or b or opcode)
begin
case(opcode)
    0: begin
        // bitwise AND : no overflow possible
        r=a&b;
        v=1'b0;
    end
    1:begin
        // bitwise OR : no overflow possible
        r=a&b;
        r=a|b;
        v=1'b0;
    end
    2:begin
        // Assuming the inputs to be in 2's complement notation:
        // can just add them irrespective of sign
        // Overflow is detected when a and b have the same sign,
        // and r has the opposite sign of a (or b)
        r=a+b;
        if ((a[31] == b[31])&&(a[31]!=r[31]))
            v=1'b1;
    end
endcase
end

```

```

        else
            v=1'b0;
        end
    3:begin
        // As above : We can subtract normally..
        // Overflow detection : a and b have the OPPOSITE signs,
        // and r has sign OPPOSITE to a (or same as b)
        r=a-b;
        if ((a[31] != b[31])&&(a[31]!=r[31]))
            v=1'b1;
        else
            v=1'b0;
        end
    4:begin
        // Here again we have to check sign. If the sign is the same,
        // then r = (a < b) (NOTE that this works when a and b are positive,
        // as well as when both are negative.
        // But if signs are opposite, then if a is negative, r is 1, else r is 0
        if (a[31]==b[31])
            // a and b are of the same sign
            r = (a < b);
        else
            // a and b are not of the same sign
            r = a[31];
        end
    default:begin
        r='bx;
        v='bx;
    end
endcase
// now handle the setting of z
if (r==32'd0)
    z=1'b1;
else
    z=1'b0;
end
endmodule

```

```

// satc : Q 3
module satc(in, state, clk);
input in, clk;

output [1:0] state ;

reg [1:0] state, nextstate;

// always good to explicitly name states as Parameters
parameter weak_taken=1, strong_taken=0, weak_not_taken=2, strong_not_taken=3;

initial begin
    state = weak_taken;
end

// the stuff that happens at the clock
always @(posedge clk) begin
    state <= nextstate; // NOTE the delayed assignment!
end

```

```
// the "combinatorial" logic
always @(in or state) begin
  //default
  nextstate = state;
// in = 0 means Not taken; 1 means taken
  case (state)
    strong_taken: if (in==0)
      nextstate = weak_taken;
    weak_taken: if (in==1)
      nextstate = strong_taken;
      else nextstate = strong_not_taken;
    weak_not_taken: if (in==1)
      nextstate = strong_taken;
      else nextstate = strong_not_taken;
    strong_not_taken: if (in==1)
      nextstate = weak_not_taken;
  endcase
end

endmodule
```