

Q1: 15 points

First, begin with the truth table.

	A	B	C	Y
$\bar{A}\bar{B}\bar{C}$ ←	0	0	0	1
	0	0	1	0
	0	1	0	0
$\bar{A}BC$ ←	0	1	1	1
	1	0	0	0
$A\bar{B}\bar{C}$ ←	1	0	1	1
ABC ←	1	1	0	1
	1	1	1	0

6 points (truth table and logic)

Write out your logic equation,

$$Y = A\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$$

We could go straight to implementing this into CMOS, but we want to simplify the expression to reduce and optimize our implementation.


Using De Morgan's Law:

$$Y = \overline{(AB + \bar{A}\bar{B}) \cdot \bar{C}} + \overline{(\bar{A}\bar{B} + \bar{A}B) \cdot C} = \overline{((AB + \bar{A}\bar{B}) \cdot \bar{C})} \cdot \overline{((\bar{A}\bar{B} + \bar{A}B) \cdot C)}$$


$$Y = \overline{((\bar{A}B + \bar{A}\bar{B}) + C) \cdot ((\bar{A}\bar{B} + \bar{A}B) + \bar{C})} = \overline{((\bar{A}B) \cdot (\bar{A}\bar{B}) + C) \cdot ((\bar{A}\bar{B} \cdot \bar{A}B) + \bar{C})}$$

$$Y = \overline{(((\bar{A} + B) \cdot (A + B)) + C) \cdot (((\bar{A} + B) \cdot (A + \bar{B})) + \bar{C})}$$

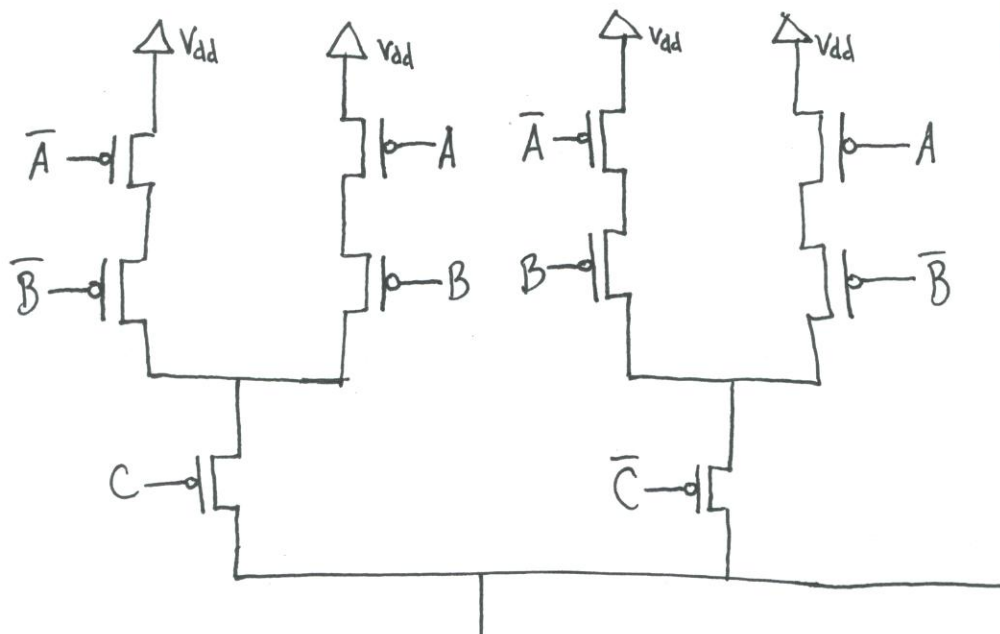Now everything is in terms of two terms and building up the transistor gates follows, replace ANDs with serial connections
ORs with parallel connections.



6 points
drawing out
cmos

 

C code 3 points

```

int xnor3(int A, int B, int C)
{
    return !(A^B^C);
}

```

2)


Delay in combinational circuits:- (5 points)

Delay in combinational circuits is caused by the parasitic capacitance in Mos transistors.


The charging and discharging of capacitances in the internal nodes of the transistor due to the changes in the inputs and outputs is responsible for delay.

The (W/L) values for a transistor are factors in the individual capacitance values along with the oxide capacitance.

A capacitive model for a mosfet:

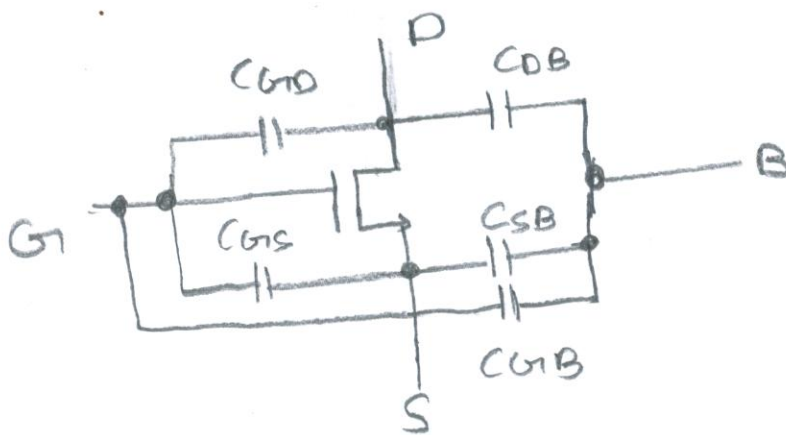

3)

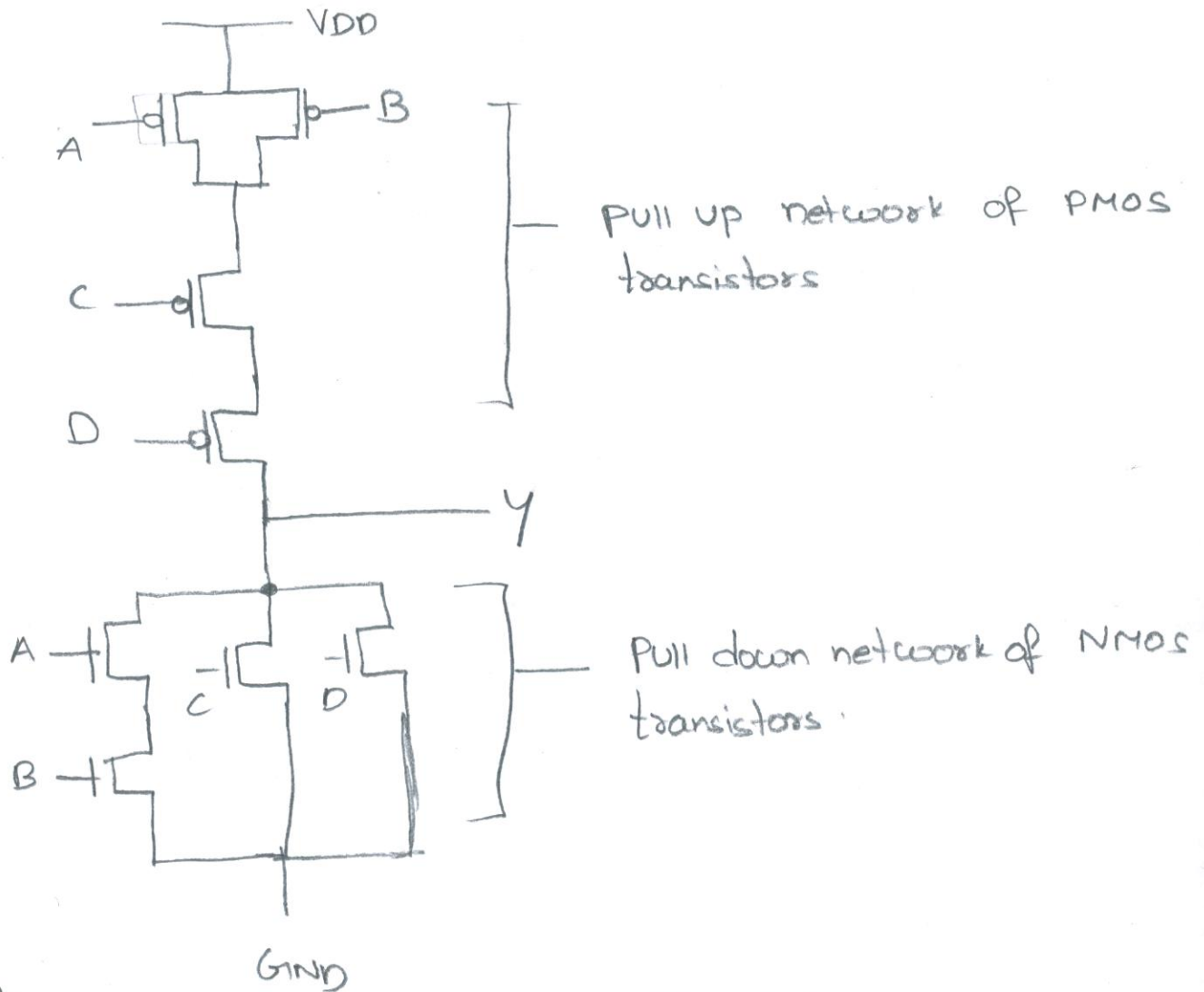

ANSWER:


$$Y = \overline{(A \times B) + C + D}$$

→ 8 points

Pull up network and pull down network complement each other. Analyze pull down network



 Two nmos connected in series (cascade) implements "and" function



Two nmos connected in parallel implements OR A + B

Therefore, the pull down network implements.

$A \wedge B + C + D$. But, CMOS logic is Complementary.

So the final logic function implemented is

$$Y = \overline{(A \wedge B) + C + D}$$

C. Code³ - 2 points
// Assuming A, B, C, D are either 0 or 1.

```
int booleanFunction(int A, int B, int C, int D) {
```

```
    return !(A & B | C | D);
```

```
}
```