

# CSE352 Autumn 2013 Homework #4

Instructor: Mark Oskin

TAs: Vincent Lee, Mark Wyse

Due In Class 11/1/2013

Version 1.1

Please write your name and student ID at the top right corner of each page, and staple or paperclip your work together. We are NOT responsible for losing papers that were not stapled or paperclipped together.

Complete the following questions. Please write legibly and try to draw clean diagrams. Spaghetti wiring in circuit diagrams is difficult to grade. We will not grade work that is too heavily encrypted for us to read (i.e. we can't read it, we can't grade it). Please consider typesetting your work if you think that it may not be legible to the grader. You are encouraged to collaborate with your peers but you must turn in your own work. Justice will be enforced if you are caught cheating.

## **Problem 1** *FPGA and ASIC Cost Analysis (Easy)*

Ben Bitdiddle has established a start up called Herp Derp Incorporated which specializes in making FPGA and ASIC solutions. He is debating whether to use an FPGA or ASIC solution for the launch of his first product. He goes to Alyssa P. Hacker who is now a consultant at L337 Associates who tells him that he should expect to sell 100,000 chips. She also tells him that the NRE costs associated with an ASIC solution and FPGA solution for his design are \$1,000,000 and \$100,000 respectively, and that the cost per unit for an FPGA solution and ASIC solution are \$20 and \$2 respectively. Since Alyssa is doing Ben a favor and not charging him for her time, she doesn't tell him which one he should use. Given the above information, should Ben choose to use an FPGA or ASIC solution? Why?


## **Problem 2** *Finite State Machines (Easy)*

Consider the design of a simple edge detector circuit. The circuit has a one bit input **In** and a one bit output **Out**. **Out** should only be asserted for one cycle when the circuit detects a positive edge in the signal **In** (i.e. a transition from zero to one). The **Out** signal should be asserted the same cycle that the positive edge is detected (i.e. the cycle where the signal is high for the first time). Draw the Mealy style FSM

for this circuit and the corresponding circuit implementation using only registers and simple logic gates. (Make sure to include a reset signal `Reset`).
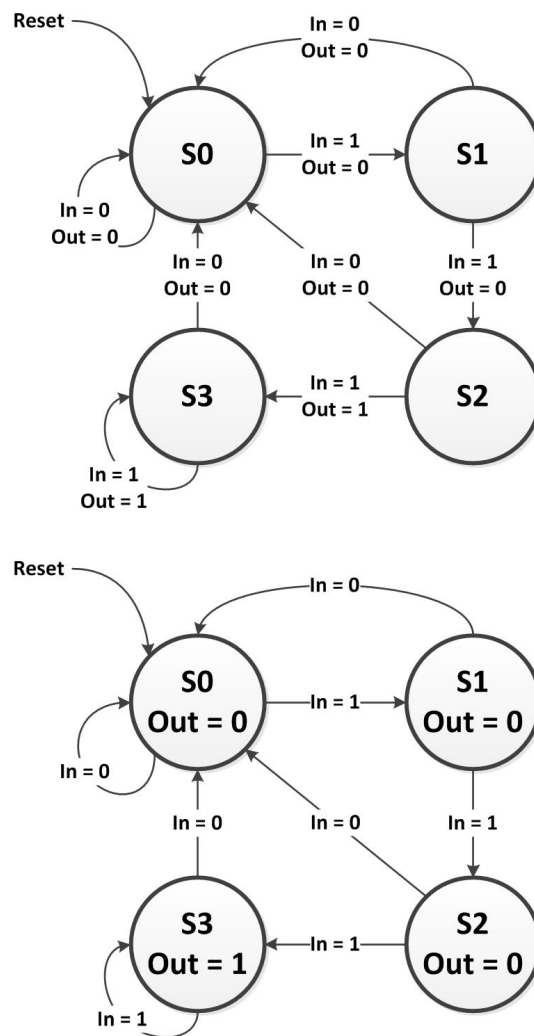
### Problem 3 *Finite State Machines*

Ben Bitdiddle and Alyssa P. Hacker are arguing over whether the following two finite state machines are functionally equivalent. Ben argues that the circuit are functionally equivalent because they will both assert the signal `Out` after the input `In` is asserted for three consecutive cycles. Alyssa disagrees and argues that the FSMs are not functionally equivalent. Who is correct and why?



### Problem 4 *Verilog Practice*

- (a) Write a verilog module that implements the edge detector module `edge_detect` specified in problem 2. Your module should take three inputs: the input signal

**In**, the clock signal **clk**, and the reset signal **Reset**. Your module should produce a single output **Out** which is asserted when a positive edge is detected. If a **Reset** signal is asserted, **Out** should be zero.

- (b) Write a verilog module **odd\_pair** that takes in a serial input **In**, clock signal **clk**, and a reset signal **Rst** and asserts a signal **Odd** if the signal **In** has been asserted for an odd number of cycles and an output signal **Pair** if the value of **In** in the previous cycle is the same as the current cycle. If a **Reset** signal is asserted, **Pair** and **Odd** should be zero.

### **Problem 5** *Blast from the Past (Review)*

Draw the CMOS transistor implementation of the following Boolean expressions. Minimize the number of transistors used:

(a)  $\overline{(A + B)(DC + EC)}$

(b)  $\bar{A}\bar{B} + \bar{C} + \bar{D}$

### **Problem 6** *Finite State Machines (Interview Question)*

Design a Mealy style FSM that takes a one bit input **in** and asserts a one bit signal **out** if the sequence 11011 has been detected. The **out** signal should be asserted the same cycle that the last 1 in the sequence is detected. Sequence can also overlap, for instance if the sequence 11011011 is input, the signal **out** should be asserted on the 5th cycle, and the 8th cycle. Minimize the number of states in your FSM. Make sure to also designate what the initial state of the machine will be on a reset.

### **Problem 7** *Bonus Question: The Logic Gate Pokemon (Optional)*

Make up and draw a new pokemon that we can call the "Logic Gate Pokemon".