

CSE352 Spring 2013 Homework Assignment #7

Due in class Friday June 7th 2013 - NO EXTENSIONS WILL BE GRANTED!

Q1) Modify the single-cycle MIPS processor to implement the following instructions.

Refer to appendix B for a definition of the instructions.

For each instruction, mark up a copy of Figure 7.11 to indicate the changes to the datapath. Name any new control signals.

Mark up a copy of table 7.8 to show the changes to the main decoder. We've left some room for you to add extra signals to your decoder. Describe any other changes that are required.

(a) sliv

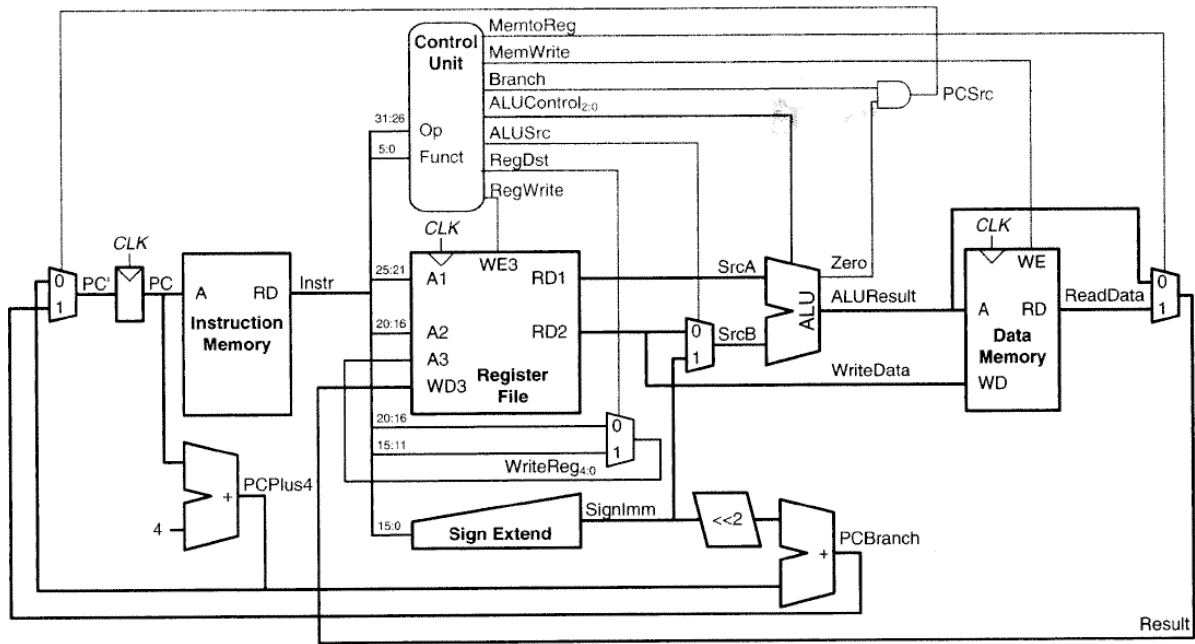


Figure 7.11 Complete single-cycle MIPS processor

(b) sltiu

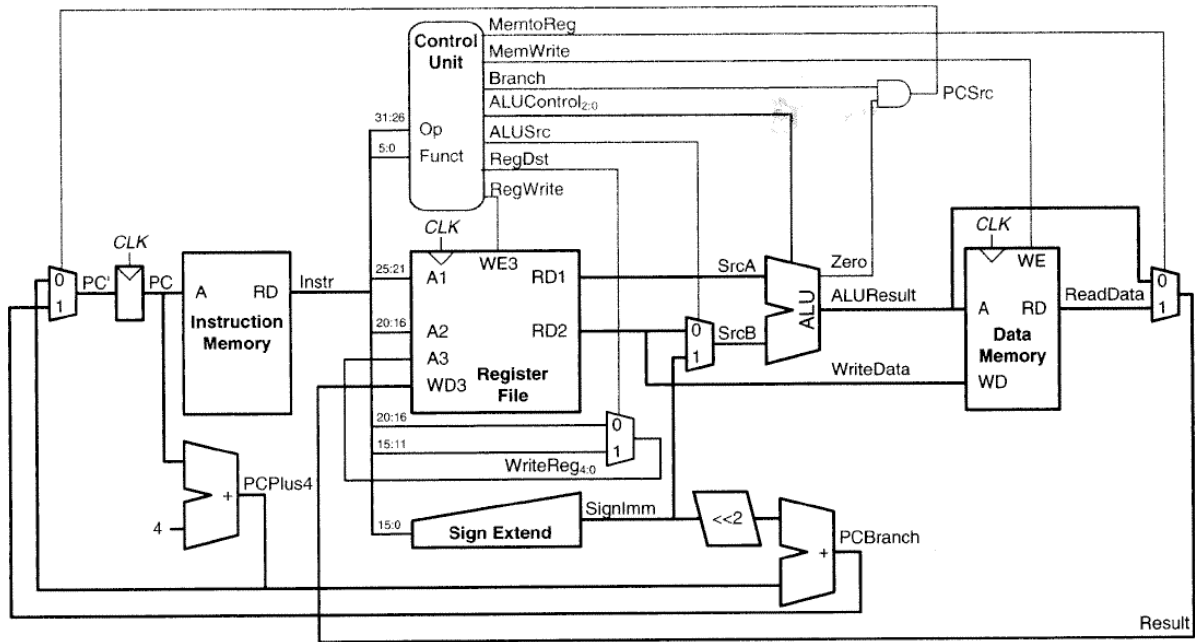


Figure 7.11 Complete single-cycle MIPS processor

(c) bgtz

 


Figure 7.11 Complete single-cycle MIPS processor

(d) Ib

 


Figure 7.11 Complete single-cycle MIPS processor

Instruction	Opcode	Reg Write	Reg Dst	ALU Src	Branch	Mem Write	Memto Reg	ALU Op	Jump			
R-type	000000	1	1	0	0	0	0	10	0			
lw	100011	1	0	1	0	0	1	00	0			
sw	101011	0	X	1	0	1	X	00	0			
beq	000100	0	X	0	1	0	X	01	0			
addi	001000	1	0	1	0	0	0	00	0			
j	000010	0	X	X	X	0	X	XX	1			
slv												
sltiu												
bgtz												
lb												

Table 7.8 Main decoder truth table to mark up with changes

Table B.1 Instructions, sorted by opcode

Opcode	Name	Description	Operation
000000 (0)	R-type	all R-type instructions	see Table B.2
000001 (1) (rt = 0/1)	bltz/bgez	branch less than zero/ branch greater than or equal to zero	if ([rs] < 0) PC = BTA/ if ([rs] ≥ 0) PC = BTA
000010 (2)	j	jump	PC = JTA
000011 (3)	jal	jump and link	\$ra = PC+4, PC = JTA
000100 (4)	beq	branch if equal	if ([rs]==[rt]) PC = BTA
000101 (5)	bne	branch if not equal	if ([rs]!=[rt]) PC = BTA
000110 (6)	blez	branch if less than or equal to zero	if ([rs] ≤ 0) PC = BTA
000111 (7)	bgtz	branch if greater than zero	if ([rs] > 0) PC = BTA
001000 (8)	addi	add immediate	[rt] = [rs] + SignImm
001001 (9)	addiu	add immediate unsigned	[rt] = [rs] + SignImm
001010 (10)	slti	set less than immediate	[rs] < SignImm ? [rt]=1 : [rt]=0
001011 (11)	sltiu	set less than immediate unsigned	[rs] < SignImm ? [rt]=1 : [rt]=0
001100 (12)	andi	and immediate	[rt] = [rs] & ZeroImm
001101 (13)	ori	or immediate	[rt] = [rs] ZeroImm
001110 (14)	xori	xor immediate	[rt] = [rs] ^ ZeroImm
001111 (15)	lui	load upper immediate	[rt] = {Imm, 16'b0}
010000 (16) (rs = 0/4)	mfc0, mtc0	move from/to coprocessor 0	[rt] = [rd]/[rd] = [rt] (rd is in coprocessor 0)
010001 (17)	F-type	fop = 16/17: F-type instructions	see Table B.3
010001 (17) (rt = 0/1)	bclif/bclt	fop = 8: branch if fpcond is FALSE/TRUE	if (fpcond == 0) PC = BTA/ if (fpcond == 1) PC = BTA
100000 (32)	lb	load byte	[rt] = SignExt ([Address] _{7:0})
100001 (33)	lh	load halfword	[rt] = SignExt ([Address] _{15:0})
100011 (35)	lw	load word	[rt] = [Address]
100100 (36)	lbu	load byte unsigned	[rt] = ZeroExt ([Address] _{7:0})
100101 (37)	lhu	load halfword unsigned	[rt] = ZeroExt ([Address] _{15:0})
101000 (40)	sb	store byte	[Address] _{7:0} = [rt] _{7:0}

Table B.1 Instructions, sorted by opcode—Cont'd

Opcode	Name	Description	Operation
101001 (41)	sh	store halfword	[Address] _{15:0} = [rt] _{15:0}
101011 (43)	sw	store word	[Address] = [rt]
110001 (49)	lwc1	load word to FP coprocessor 1	[ft] = [Address]
111001 (56)	swc1	store word to FP coprocessor 1	[Address] = [ft]

Table B.2 R-type instructions, sorted by funct field

Funct	Name	Description	Operation
000000 (0)	sll	shift left logical	[rd] = [rt] << shamt
000010 (2)	srl	shift right logical	[rd] = [rt] >> shamt
000011 (3)	sra	shift right arithmetic	[rd] = [rt] >>> shamt
000100 (4)	sllv	shift left logical variable	[rd] = [rt] << [rs] _{4:0} assembly: sllv rd, rt, rs
000110 (6)	srlv	shift right logical variable	[rd] = [rt] >> [rs] _{4:0} assembly: srlv rd, rt, rs
000111 (7)	srav	shift right arithmetic variable	[rd] = [rt] >>> [rs] _{4:0} assembly: srav rd, rt, rs
001000 (8)	jr	jump register	PC = [rs]
001001 (9)	jalr	jump and link register	\$ra = PC + 4, PC = [rs]
001100 (12)	syscall	system call	system call exception
001101 (13)	break	break	break exception
010000 (16)	mghi	move from hi	[rd] = [hi]
010001 (17)	mthi	move to hi	[hi] = [rs]
010010 (18)	mflo	move from lo	[rd] = [lo]
010011 (19)	mtlo	move to lo	[lo] = [rs]
011000 (24)	mult	multiply	{[hi], [lo]} = [rs] × [rt]
011001 (25)	multu	multiply unsigned	{[hi], [lo]} = [rs] × [rt]
011010 (26)	div	divide	[lo] = [rs]/[rt], [hi] = [rs]%[rt]

(continued)

Table B.2 R-type instructions, sorted by funct field—Cont'd

Funct	Name	Description	Operation
011011 (27)	divu	divide unsigned	[lo] = [rs]/[rt], [hi] = [rs]%[rt]
100000 (32)	add	add	[rd] = [rs] + [rt]
100001 (33)	addu	add unsigned	[rd] = [rs] + [rt]
100010 (34)	sub	subtract	[rd] = [rs] - [rt]
100011 (35)	subu	subtract unsigned	[rd] = [rs] - [rt]
100100 (36)	and	and	[rd] = [rs] & [rt]
100101 (37)	or	or	[rd] = [rs] [rt]
100110 (38)	xor	xor	[rd] = [rs] ^ [rt]
100111 (39)	nor	nor	[rd] = ~([rs] [rt])
101010 (42)	slt	set less than	[rs] < [rt] ? [rd] = 1 : [rd] = 0
101011 (43)	sltu	set less than unsigned	[rs] < [rt] ? [rd] = 1 : [rd] = 0

Table B.3 F-type instructions (fop = 16/17)


Funct	Name	Description	Operation
000000 (0)	add.s/add.d	FP add	[fd] = [fs] + [ft]
000001 (1)	sub.s/sub.d	FP subtract	[fd] = [fs] - [ft]
000010 (2)	mul.s/mul.d	FP multiply	[fd] = [fs] * [ft]
000011 (3)	div.s/div.d	FP divide	[fd] = [fs]/[ft]
000101 (5)	abs.s/abs.d	FP absolute value	[fd] = ([fs] < 0) ? [-fs] : [fs]
000111 (7)	neg.s/neg.d	FP negation	[fd] = [-fs]
111010 (58)	c.seq.s/c.seq.d	FP equality comparison	fpcond = ([fs] == [ft])
111100 (60)	c.lt.s/c.lt.d	FP less than comparison	fpcond = ([fs] < [ft])
111110 (62)	c.le.s/c.le.d	FP less than or equal comparison	fpcond = ([fs] ≤ [ft])

Q2)

In the MIPS 5-stage pipeline we've covered in class/in the textbook, load-store operations require the EX stage to be able to perform address generation (AG) computation and to be followed by the Mem Stage to access the D-cache. So, a better name for the EX stage would be the EX-AG to indicate its double function. With this ordering we saw that:

1. We could avoid RAW dependencies between arithmetic instructions at the cost of forwarding paths between the EX-AG/Mem and Mem/WB pipeline registers and the inputs of the ALU of the EX-AG stage.
2. We could not avoid 1-cycle load latency penalty when the result of a load operation was a source operand for the next instruction.
3. Branch resolution could be performed during the EX-AG stage, resulting in a 2 cycle branch penalty on a taken branch (with a branch-not-taken prediction policy).
4. The Mem stage was not used for arithmetic-logical instructions.

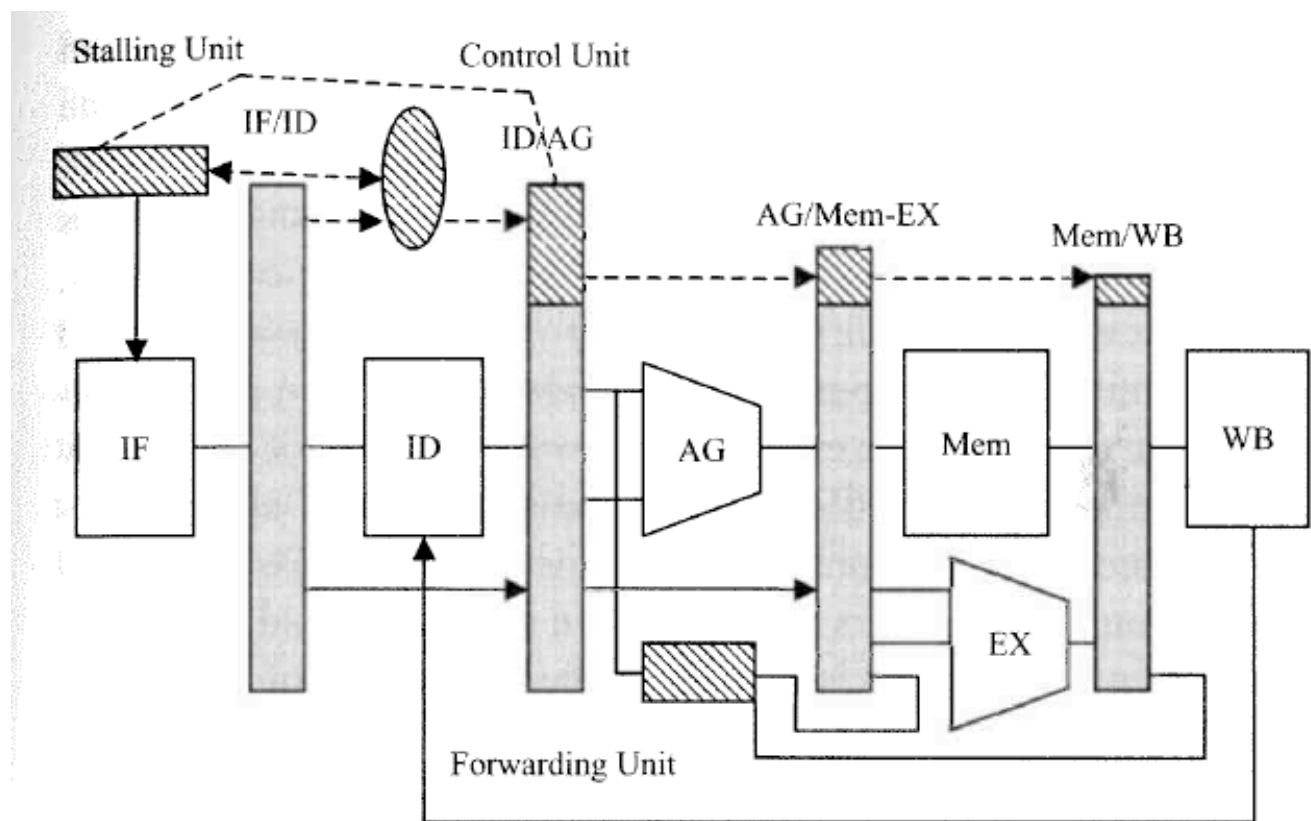(a) Given the alternative five-stage pipeline diagram below, discuss the advantages and disadvantages of this design for each of the 4 points discussed above.



- (b) If the two ALUs in the alternative 5-stage pipeline are used respectively for branch target computation and register comparison, what would be the penalties for branch instructions:
- In the case where stalling occurs as soon as a branch is recognized?
 - In the case where a branch-not-taken prediction policy is used?