

Hardware description languages

- Describe hardware at varying levels of abstraction
- Structural description
 - textual replacement for schematic
 - hierarchical composition of modules from primitives
- Behavioral/functional description
 - describe what module does, not how
 - synthesis generates circuit for module
- Simulation semantics

CSE 370 - Winter 200 - Hardware Description Languages - 1

HDLs

- Abel (circa 1983) - developed by Data-I/O
 - targeted to programmable logic devices
 - not good for much more than state machines
- ISP (circa 1977) - research project at CMU
 - simulation, but no synthesis
- Verilog (circa 1985) - developed by Gateway (now part of Cadence)
 - similar to Pascal and C
 - delays is only interaction with simulator
 - fairly efficient and easy to write
 - IEEE standard
- VHDL (circa 1987) - DoD sponsored standard
 - similar to Ada (emphasis on re-use and maintainability)
 - simulation semantics visible
 - very general but verbose
 - IEEE standard

CSE 370 - Winter 200 - Hardware Description Languages - 2

Verilog

- Supports structural and behavioral descriptions
- Structural
 - explicit structure of the circuit
 - e.g., each logic gate instantiated and connected to others
- Behavioral
 - program describes input/output behavior of circuit
 - many structural implementations could have same behavior
 - e.g., different implementation of one Boolean function
- We'll only be using behavioral Verilog
 - rely on schematic for structural constructs

CSE 370 - Winter 200 - Hardware Description Languages - 3

Structural model

```
module xor_gate (out, a, b);
  input  a, b;
  output out;
  wire  abar, bbar, t1, t2;

  inverter invA (abar, a);
  inverter invB (bbar, b);
  and_gate and1 (t1, a, bbar);
  and_gate and2 (t2, b, abar);
  or_gate  or1 (out, t1, t2);
endmodule
```

CSE 370 - Winter 200 - Hardware Description Languages - 4

Simple behavioral model

- Continuous assignment

```
module and_gate (out, in1, in2);
  input  in1, in2;
  output out;
  reg    out;

  assign #2 out = in1 & in2;
endmodule
```

delay from input change
to output change

CSE 370 - Winter 200 - Hardware Description Languages - 5

Simple behavioral model

- always block

```
module and_gate (out, in1, in2);
  input  in1, in2;
  output out;
  reg    out;

  always @(in1 or in2) begin
    #2 out = in1 & in2;
  end
endmodule
```

simulation register -
keeps track of
value of signal

specifies when block is executed
ie. triggered by which signals

CSE 370 - Winter 200 - Hardware Description Languages - 6

Driving a simulation

```
module stimulus (a, b);
  output      a, b;
  reg [1:0]   cnt;

  initial begin
    cnt = 0;
    repeat (4) begin
      #10 cnt = cnt + 1;
      $display ("@ time=%d, a=%b, b=%b, cnt=%b",
        $time, a, b, cnt);
    end
  end

  assign a = cnt[1];
  assign b = cnt[0];
endmodule
```

2-bit vector

initial block executed only once at start of simulation


print to a console

directive to stop simulation

CSE 370 - Winter 200 - Hardware Description Languages - 7

Complete Simulation

- Instantiate stimulus component and device to test in a schematic

 

CSE 370 - Winter 200 - Hardware Description Languages - 8

Comparator Example

```
module Compare1 (A, B, Equal, Alarger, Blarger);
  input  A, B;
  output Equal, Alarger, Blarger;

  assign #5 Equal = (A & B) | (~A & ~B);
  assign #3 Alarger = (A & ~B);
  assign #3 Blarger = (~A & B);
endmodule
```

CSE 370 - Winter 200 - Hardware Description Languages - 9

More Complex Behavioral Model

```
module life (n0, n1, n2, n3, n4, n5, n6, n7, self, out);
  input  n0, n1, n2, n3, n4, n5, n6, n7, self;
  output out;
  reg   out;
  reg [7:0] neighbors;
  reg [3:0] count;
  reg [3:0] i;

  assign neighbors = {n7, n6, n5, n4, n3, n2, n1, n0};

  always @(neighbors or self) begin
    count = 0;
    for (i = 0; i < 8; i = i+1) count = count + neighbors[i];
    out = (count == 3);
    out = out | ((self == 1) & (count == 2));
  end
endmodule
```

CSE 370 - Winter 200 - Hardware Description Languages - 10

Hardware Description Languages vs. Programming Languages

- Program structure
 - instantiation of multiple components of the same type
 - specify interconnections between modules via schematic
 - hierarchy of modules (only leaves can be HDL in DesignWorks)
- Assignment
 - continuous assignment (logic always computes)
 - propagation delay (computation takes time)
 - timing of signals is important (when does computation have its effect)
- Data structures
 - size explicitly spelled out - no dynamic structures
 - no pointers
- Parallelism
 - hardware is naturally parallel (must support multiple threads)
 - assignments can occur in parallel (not just sequentially)

CSE 370 - Winter 200 - Hardware Description Languages - 11

Hardware Description Languages and Combinational Logic

- Modules - specification of inputs, outputs, bidirectional, and internal signals
- Continuous assignment - a gate's output is a function of its inputs at all times (doesn't need to wait to be "called")
- Propagation delay- concept of time and delay in input affecting gate output
- Composition - connecting modules together with wires
- Hierarchy - modules encapsulate functional blocks
- Specification of don't care conditions

CSE 370 - Winter 200 - Hardware Description Languages - 12

Hardware Description Languages and Sequential Logic

- Flip-flops
 - representation of clocks - timing of state changes
 - asynchronous vs. synchronous
- FSMs
 - structural view (FFs separate from combinational logic)
 - behavioral view (synthesis of sequencers)
- Data-paths = ALUs + registers
 - use of arithmetic/logical operators
 - control of storage elements
- Parallelism
 - multiple state machines running in parallel
- Sequential don't cares

CSE 370 - Winter 200 - Hardware Description Languages - 13

Flip-flop in Verilog

- Use always block's sensitivity list to wait for clock edge

```
module dff (clk, d, q);
    input clk, d;
    output q;
    reg q;

    always @(posedge clk)
        q = d;
endmodule
```

CSE 370 - Winter 200 - Hardware Description Languages - 14

More Flip-flops

- Synchronous/asynchronous reset/set
 - single thread that waits for the clock
 - three parallel threads - only one of which waits for the clock

```
module dff (clk, s, r, d, q);
    input clk, s, r, d;
    output q;
    reg q;

    always @(posedge clk)
        if (reset) q = 'b0;
        else if (set) q = 'b1;
        else q = d;
endmodule

module dff (clk, s, r, d, q);
    input clk, s, r, d;
    output q;
    reg q;

    always @(posedge reset)
        q = 'b0;
    always @(posedge set)
        q = 'b1;
    always @(posedge clk)
        q = d;
endmodule
```

CSE 370 - Winter 200 - Hardware Description Languages - 15

Structural View of an FSM

- Traffic light controller: two always blocks - flip-flops separate from logic

```
module FSM (HL, FL, ST, clk, C, TS, TL);
    output [2:0] HL, FL;    reg [2:0] HL, FL;
    output ST;            reg ST;
    input clk;
    input C, TS, TL;
    reg [1:0] present_state;
    reg [1:0] next_state;

    initial begin HL = 3'b001; FL = 3'b100; present_state = 2'b00; end

    always @(posedge clk) // registers
        present_state = next_state;

    always @(present_state or C or TS or TL)
        // compute next-state and output logic whenever state or inputs change
        // put equations here for next_state[1:0], HL[2:0], FL[2:0], and ST
        // as functions of C, TS, TL, and present_state[1:0]
endmodule
```

CSE 370 - Winter 200 - Hardware Description Languages - 16

Behavioral View of an FSM

- Specification of inputs, outputs, and state elements

```
module FSM(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, clk);
    output HR;
    output HY;
    output HG;
    output FR;
    output FY;
    output FG;
    output ST;
    input TS;
    input TL;
    input C;
    input reset;
    input clk;
    reg [6:1] state;
    reg ST;

    `define highwaygreen 6'b001100
    `define highwayyellow 6'b010100
    `define farmroadgreen 6'b100001
    `define farmroadyellow 6'b100010

    assign HR = state[6];
    assign HY = state[5];
    assign HG = state[4];
    assign FR = state[3];
    assign FY = state[2];
    assign FG = state[1];
endmodule
```

specify state bits and codes for each state as well as connections to outputs

CSE 370 - Winter 200 - Hardware Description Languages - 17

Behavioral View of an FSM (cont'd)

```
initial begin state = 'highwaygreen; ST = 0; end

always @(posedge clk)
begin
    if (reset)
        begin state = 'highwaygreen; ST = 1; end
    else
        begin
            ST = 0;
            case (state)
                'highwaygreen:
                    if (TL & C) begin state = 'highwayyellow; ST = 1; end
                'highwayyellow:
                    if (TS) begin state = 'farmroadgreen; ST = 1; end
                'farmroadgreen:
                    if (TL | !C) begin state = 'farmroadyellow; ST = 1; end
                'farmroadyellow:
                    if (TS) begin state = 'highwaygreen; ST = 1; end
            endcase
        end
    end
endmodule
```

case statement triggered by clock edge

CSE 370 - Winter 200 - Hardware Description Languages - 18

Timer for Traffic Light Controller

Another FSM

```

module Timer(TS, TL, ST, Clk);
output TS;
output TL;
input ST;
input Clk;
integer value;

assign TS = (value >= 4); // 5 cycles after reset
assign TL = (value >= 14); // 15 cycles after reset

always @(posedge ST) value = 0; // async reset

always @(posedge Clk) value = value + 1;

endmodule

```

CSE 370 - Winter 200 - Hardware Description Languages - 19

Complete Traffic Light Controller

Tying it all together (FSM + timer)

```

module main(HR, HY, HG, FR, FY, FG, reset, C, Clk);
output HR, HY, HG, FR, FY, FG;
input reset, C, Clk;

Timer part1(TS, TL, ST, Clk);
FSM part2(HR, HY, HG, FR, FY, FG, ST, TS, TL, C, reset, Clk);
endmodule

```

CSE 370 - Winter 200 - Hardware Description Languages - 20

Verilog FSM - Reduce 1s example

Moore machine


```

`define zero 0
`define one1 1
`define twos 2

module reduce (clk, reset, in, out);
output out;
reg out;
reg [2:1] state; // state variables
reg [2:1] next_state;

always @(posedge clk)
if (reset) state = `zero;
else state = next_state;

```

 

CSE 370 - Winter 200 - Hardware Description Languages - 21

Moore Verilog FSM (cont'd)

```

always @(in or state)
case (state)
`zero:
// last input was a zero
begin
if (in) next_state = `one1;
else next_state = `zero;
end
`one1:
// we've seen one 1
begin
if (in) next_state = `twos;
else next_state = `zero;
end
`twos:
// we've seen at least 2 ones
begin
if (in) next_state = `twos;
else next_state = `zero;
end
endcase

always @(state)
case (state)
`zero: out = 0;
`one1: out = 0;
`twos: out = 1;
endcase
endmodule

```

crucial to include all signals that are input to state and output equations

note that output only depends on state

CSE 370 - Winter 200 - Hardware Description Languages - 22

Mealy Verilog FSM


```

module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
`register state; // state variables
reg next_state;

always @(posedge clk)
if (reset) state = `zero;
else state = next_state;

always @(in or state)
case (state)
`zero: // last input was a zero
begin
out = 0;
if (in) next_state = `one;
else next_state = `zero;
end
`one: // we've seen one 1
if (in) begin
next_state = `one; out = 1;
end else begin
next_state = `zero; out = 0;
end
endcase
endmodule

```

 

CSE 370 - Winter 200 - Hardware Description Languages - 23

Synchronous Mealy Machine

```

module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
reg state; // state variables

always @(posedge clk)
if (reset) state = `zero;
else
case (state)
`zero: // last input was a zero
begin
out = 0;
if (in) state = `one;
else state = `zero;
end
`one: // we've seen one 1
if (in) begin
state = `one; out = 1;
end else begin
state = `zero; out = 0;
end
endcase
endmodule

```

CSE 370 - Winter 200 - Hardware Description Languages - 24