

Sequential logic examples

- Finite state machine concept
 - FSMs are the decision making logic of digital designs
 - partitioning designs into datapath and control elements
 - when inputs are sampled and outputs asserted
- Basic design approach: a 4-step design process
- Implementation examples and case studies
 - finite-string pattern recognizer
 - complex counter
 - traffic light controller
 - door combination lock

CSE 370 - Winter 2000 - Sequential Logic Examples - 1

General FSM design procedure

- (1) Determine inputs and outputs
- (2) Determine possible states of machine
 - - state minimization
- (3) Encode states and outputs into a binary code
 - - state assignment or state encoding
 - - output encoding
 - - possibly input encoding (if under our control)
- (4) Realize logic to implement functions for states and outputs
 - - combinational logic implementation and optimization
 - - choices made in steps 2 and 3 can have large effect on resulting logic

CSE 370 - Winter 2000 - Sequential Logic Examples - 2

Finite string pattern recognizer (step 1)

- Finite string pattern recognizer
 - one input (X) and one output (Z)
 - output is asserted whenever the input sequence ...010... has been observed, as long as the sequence 100 has never been seen
- Step 1: understanding the problem statement
 - sample input/output behavior:


X: 0 0 1 0 1 0 1 0 0 1 0 ...
Z: 0 0 0 1 0 1 0 1 0 0 0 ...

X: 1 1 0 1 1 0 1 0 0 1 0 ...
Z: 0 0 0 0 0 0 0 1 0 0 0 ...

CSE 370 - Winter 2000 - Sequential Logic Examples - 3

Finite string pattern recognizer (step 2)


- Step 2: draw state diagram
 - for the strings that must be recognized, i.e., 010 and 100
 - a Moore implementation

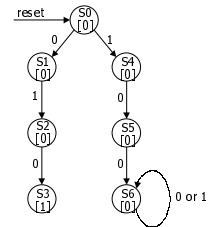

CSE 370 - Winter 2000 - Sequential Logic Examples - 4

Finite string pattern recognizer (step 2, cont'd)


- Exit conditions from state S3: have recognized ...010
 - if next input is 0 then have ...0100 = ...100 (state S6)
 - if next input is 1 then have ...0101 = ...01 (state S2)
- Exit conditions from S1: recognizes strings of form ...0 (no 1 seen)
 - loop back to S1 if input is 0
- Exit conditions from S4: recognizes strings of form ...1 (no 0 seen)
 - loop back to S4 if input is 1

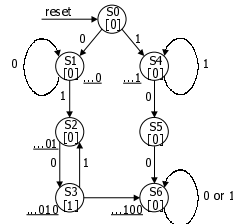

CSE 370 - Winter 2000 - Sequential Logic Examples - 5

Finite string pattern recognizer (step 2, cont'd)

- S2 and S5 still have incomplete transitions
 - S2 = ...01; If next input is 1, then string could be prefix of (01)1(00) S4 handles just this case
 - S5 = ...10; If next input is 1, then string could be prefix of (10)1(0) S2 handles just this case
- Reuse states as much as possible
 - look for same meaning
 - state minimization leads to smaller number of bits to represent states
- Once all states have a complete set of transitions we have a final state diagram

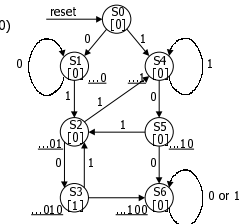

CSE 370 - Winter 2000 - Sequential Logic Examples - 6

Finite string pattern recognizer (step 3)

- Verilog description including state assignment (or state encoding)

```

module string (clk, X, rst, Q0, Q1, Q2, Z);
input clk, X, rst;
output Q0, Q1, Q2, Z;

reg state[0:2];
'define S0 = [0,0,0]; //reset state
'define S1 = [0,0,1]; //strings ending in ...0
'define S2 = [0,1,0]; //strings ending in ...01
'define S3 = [0,1,1]; //strings ending in ...010
'define S4 = [1,0,0]; //strings ending in ...1
'define S5 = [1,0,1]; //strings ending in ...10
'define S6 = [1,1,0]; //strings ending in ...100

always @(posedge clk) begin
    if rst state = 'S0;
    else
        case (state)
            'S0: if (X) state = 'S4 else state = 'S1;
            'S1: if (X) state = 'S2 else state = 'S1;
            'S2: if (X) state = 'S4 else state = 'S3;
            'S3: if (X) state = 'S2 else state = 'S6;
            'S4: if (X) state = 'S4 else state = 'S6;
            'S5: if (X) state = 'S2 else state = 'S6;
            'S6: state = 'S6;
            default: begin
                $display ("invalid state reached");
                state = 3'bxxx;
            endcase
        endcase
end

assign Q0 = state[0];
assign Q1 = state[1];
assign Q2 = state[2];
assign Z = (state == 'S3);
endmodule
    
```

CSE 370 - Winter 2000 - Sequential Logic Examples - 7

Finite string pattern recognizer

- Review of process
 - understanding problem
 - write down sample inputs and outputs to understand specification
 - derive a state diagram
 - write down sequences of states and transitions for sequences to be recognized
 - minimize number of states
 - add missing transitions; reuse states as much as possible
 - state assignment or encoding
 - encode states with unique patterns
 - simulate realization
 - verify I/O behavior of your state diagram to ensure it matches specification

CSE 370 - Winter 2000 - Sequential Logic Examples - 8

Complex counter

- A synchronous 3-bit counter has a mode control M
 - when M = 0, the counter counts up in the binary sequence
 - when M = 1, the counter advances through the Gray code sequence

binary: 000, 001, 010, 011, 100, 101, 110, 111
 Gray: 000, 001, 011, 010, 110, 111, 101, 100


- Valid I/O behavior (partial)

Mode Input M	Current State	Next State
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111

CSE 370 - Winter 2000 - Sequential Logic Examples - 9

Complex counter (state diagram)

- Deriving state diagram
 - one state for each output combination
 - add appropriate arcs for the mode control

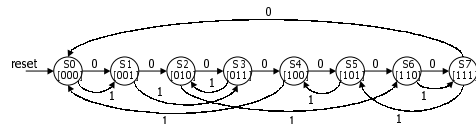

CSE 370 - Winter 2000 - Sequential Logic Examples - 10

Complex counter (state encoding)

- Verilog description including state encoding

```

module string (clk, M, rst, Z0, Z1, Z2);
input clk, X, rst;
output Z0, Z1, Z2;

reg state[0:2];
'define S0 = [0,0,0];
'define S1 = [0,0,1];
'define S2 = [0,1,0];
'define S3 = [0,1,1];
'define S4 = [1,0,0];
'define S5 = [1,0,1];
'define S6 = [1,1,0];
'define S7 = [1,1,1];


always @(posedge clk) begin
    if rst state = 'S0;
    else
        case (state)
            'S0: if (M) state = 'S3 else state = 'S2;
            'S1: if (M) state = 'S3 else state = 'S2;
            'S2: if (M) state = 'S2 else state = 'S4;
            'S3: if (M) state = 'S0 else state = 'S5;
            'S4: if (M) state = 'S0 else state = 'S5;
            'S5: if (M) state = 'S4 else state = 'S6;
            'S6: if (M) state = 'S7 else state = 'S7;
            'S7: if (M) state = 'S5 else state = 'S0;
        endcase
    end
end

assign Z0 = state[0];
assign Z1 = state[1];
assign Z2 = state[2];
endmodule
    
```

CSE 370 - Winter 2000 - Sequential Logic Examples - 11

Traffic light controller as two communicating FSMs


- Without separate timer
 - S0 would require 7 states
 - S1 would require 3 states
 - S2 would require 7 states
 - S3 would require 3 states
 - S1 and S3 have simple transformation
 - S0 and S2 would require many more arcs
 - C could change in any of seven states
- By factoring out timer
 - greatly reduce number of states
 - 4 instead of 20
 - counter only requires seven or eight states
 - 12 total instead of 20

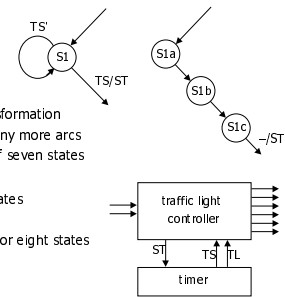

CSE 370 - Winter 2000 - Sequential Logic Examples - 12

Communicating finite state machines


- One machine's output is another machine's input

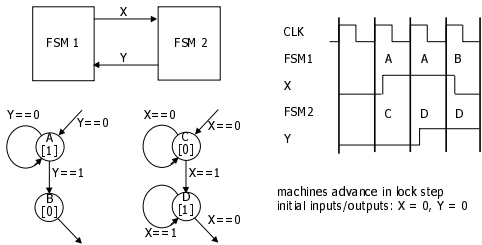

CSE 370 - Winter 2000 - Sequential Logic Examples - 13

Data-path and control

- Digital hardware systems = data-path + control
 - datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
 - control: FSM generating sequences of control signals that instructs datapath what to do next

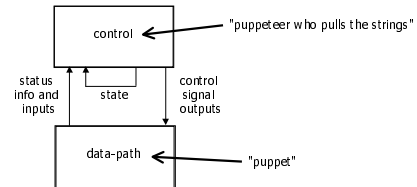

CSE 370 - Winter 2000 - Sequential Logic Examples - 14

Digital combinational lock

- Door combination lock:
 - punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
 - inputs: sequence of input values, reset
 - outputs: door open/close
 - memory: must remember combination or always have it available
- open questions: how do you set the internal combination?
 - stored in registers (how loaded?)
 - hardwired via switches set by user

CSE 370 - Winter 2000 - Sequential Logic Examples - 15

Implementation in software

```
integer combination_lock ( ) {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value ( ));
    v1 = read_value ( );
    if (v1 != c[1]) then error = 1;

    while (!new_value ( ));
    v2 = read_value ( );
    if (v2 != c[2]) then error = 1;


    while (!new_value ( ));
    v3 = read_value ( );
    if (v3 != c[3]) then error = 1;

    if (error == 1) then return(0); else return (1);
}
```

CSE 370 - Winter 2000 - Sequential Logic Examples - 16

Determining details of the specification


- How many bits per input value?
- How many values in sequence?
- How do we know a new input value is entered?
- What are the states and state transitions of the system?

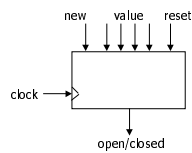

CSE 370 - Winter 2000 - Sequential Logic Examples - 17

Digital combination lock state diagram

- States: 5 states
 - represent point in execution of machine
 - each state has outputs
- Transitions: 6 from state to state, 5 self transitions, 1 global
 - changes of state occur when clock says its ok
 - based on value of inputs
- Inputs: reset, new, results of comparisons
- Output: open/closed

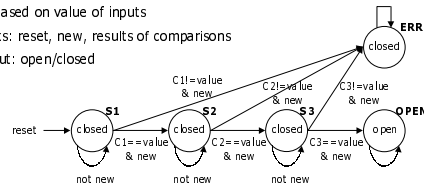

CSE 370 - Winter 2000 - Sequential Logic Examples - 18

Data-path and control structure

- Data-path
 - storage registers for combination values
 - multiplexer
 - comparator
- Control
 - finite-state machine controller
 - control for data-path (which value to compare)

CSE 370 - Winter 2000 - Sequential Logic Examples - 19

State table for combination lock

- Finite-state machine
 - refine state diagram to take internal structure into account
 - state table ready for encoding

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open
...						

CSE 370 - Winter 2000 - Sequential Logic Examples - 20

Encodings for combination lock

- Encode state table
 - state can be: S1, S2, S3, OPEN, or ERR
 - needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - and as many as 5: 00001, 00010, 00100, 01000, 10000
 - choose 4 bits: 0001, 0010, 0100, 1000, 0000
 - output mux can be: C1, C2, or C3
 - needs 2 to 3 bits to encode
 - choose 3 bits: 001, 010, 100
 - output open/closed can be: open or closed
 - needs 1 or 2 bits to encode
 - choose 1 bit: 1, 0

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...						
0	1	1	0100	1000	-	1
...						

CSE 370 - Winter 2000 - Sequential Logic Examples - 21

Data-path implementation for combination lock

- Multiplexer
 - easy to implement as combinational logic when few inputs
 - logic can easily get too big for most PLDs

CSE 370 - Winter 2000 - Sequential Logic Examples - 22

Data-path implementation (cont'd)

- Tri-state logic
 - utilize a third output state: "no connection" or "float"
 - connect outputs together as long as only one is "enabled"
 - open-collector gates can only output 0, not 1
 - can be used to implement logical AND with only wires

CSE 370 - Winter 2000 - Sequential Logic Examples - 23

Tri-state gates


- The third value
 - logic values: "0", "1"
 - don't care: "X" (must be 0 or 1 in real circuit!)
 - third value or state: "Z" — high impedance, infinite R, no connection
- Tri-state gates
 - additional input — output enable (OE)
 - output values are 0, 1, and Z
 - when OE is high, the gate functions normally
 - when OE is low, the gate is disconnected from wire at output
 - allows more than one gate to be connected to the same output wire
 - as long as only one has its output enabled at any one time (otherwise, sparks could fly)

	In	OE	Out
non-inverting	X	0	Z
tri-state	0	1	0
buffer	1	1	1

CSE 370 - Winter 2000 - Sequential Logic Examples - 24


Tri-state and multiplexing

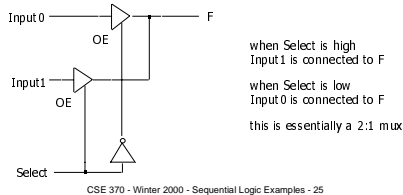- When using tri-state logic
 - (1) make sure never more than one "driver" for a wire at any one time (pulling high and low at the same time can severely damage circuits)
 - (2) make sure to only use value on wire when its being driven (using a floating value may cause failures)
- Using tri-state gates to implement an economical multiplexer




Open-collector gates and wired-AND

- Open collector: a nother way to connect gate outputs to the same wire
 - gate only has the ability to pull its out put low
 - it cannot actively drive the wire high (default – pulled high through resistor)
- Wired-AND can be implemented with open collector logic
 - if A and B are "1", output is actively pulled low
 - if C and D are "1", output is actively pulled low
 - if one gate output is low and the other high, then low wins
 - if both gate outputs are "1", the wire value "floats", pulled high by resistor
 - low to high transition usually slower than it would have been with a gate pulling high
- hence, the two NAND functions are ANDed together

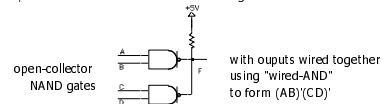

Digital combination lock (new data-path)

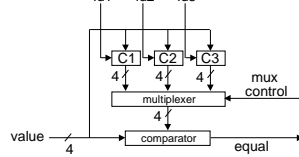- Decrease number of inputs
- Remove 3 code digits as inputs
 - use code registers
 - make them loadable from value
 - need 3 load signal inputs (net gain in input $(4*3)-3=9$)
 - could be done with 2 signals and decoder (ld1, ld2, ld3, load none)



Section summary

- FSM design
 - understanding the problem
 - generating state diagram
 - implementation using synthesis tools
 - iteration on design/specification to improve qualities of mapping
 - communicating state machines
- Four case studies
 - understand I/O behavior
 - draw diagrams
 - enumerate states for the "goal"
 - expand with error conditions
 - reuse states whenever possible