


BCD to 7-segment display controller

⌘ Understanding the problem

input is a 4 bit bcd digit (A, B, C, D)

output is the control signals for the display (7 outputs C0 – C6)

⌘ Block diagram

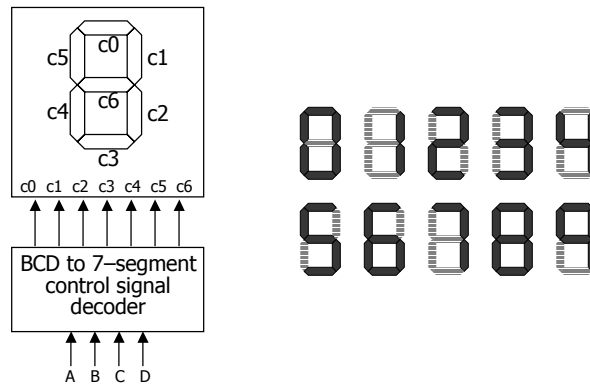

5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 1

Formalize the problem

⌘ Truth table

show don't cares

⌘ Choose implementation target

if ROM, we are done

don't cares imply PAL/PLA may be attractive

⌘ Follow implementation procedure

minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	-	-	-	-	-	-	-	-
1	1	-	-	-	-	-	-	-	-	-

5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 2

Implementation as minimized sum-of-products

⌘ 15 unique product terms when minimized individually

$C0 = A + B D + C + B' D'$
 $C1 = C' D' + C D + B'$
 $C2 = B + C' + D$
 $C3 = B' D' + C D' + B C' D + B' C$
 $C4 = B' D' + C D'$
 $C5 = A + C' D' + B D' + B C'$
 $C6 = A + C D' + B C' + B' C$

5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 3

Implementation as minimized S-o-P (cont'd)

⌘ Can do better

- ☑ 9 unique product terms (instead of 15)
- ☑ share terms among outputs
- ☑ each output not necessarily in minimized form


$C0 = A + B D + C + B' D'$
 $C1 = C' D' + C D + B'$
 $C2 = B + C' + D$
 $C3 = B' D' + C D' + B C' D + B' C$
 $C4 = B' D' + C D'$
 $C5 = A + C' D' + B D' + B C'$
 $C6 = A + C D' + B C' + B' C$

$C0 = B C' D + C D + B' D' + B C D' + A$
 $C1 = B' D + C' D' + C D + B' D'$
 $C2 = B' D + B C' D + C' D' + C D + B C D'$
 $C3 = B C' D + B' D + B' D' + B C D'$
 $C4 = B' D' + B C D'$
 $C5 = B C' D + C' D' + A + B C D'$
 $C6 = B' C + B C' + B C D' + A$

5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 4

PLA implementation

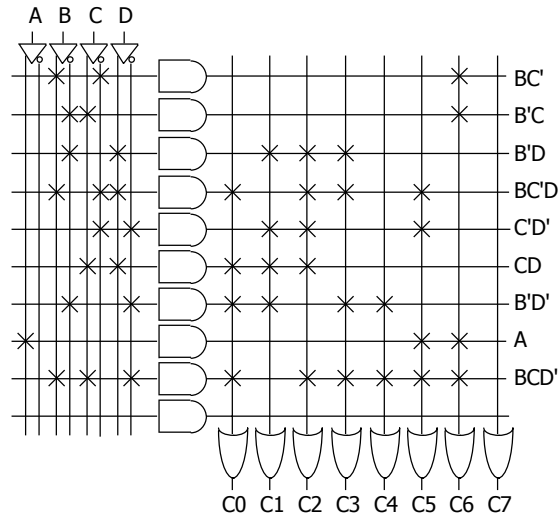

5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 5

PAL implementation

⌘ Limit of 4 product terms per output

☒ decomposition of functions with larger number of terms

☒ do not share terms in PAL anyway

(although there are some with some shared terms)

$$C2 = B + C' + D$$

$$C2 = B'D + B'C'D + C'D' + CD + BCD'$$

$$C2 = B'D + B'C'D + C'D' + W \quad \leftarrow \text{need another input and another output}$$

$$W = CD + BCD'$$

☒ decompose into multi-level logic (hopefully with CAD support)

☒ find common sub-expressions among functions

$$C0 = C3 + A'BX' + ADY$$

$$C1 = Y + A'C5' + C'D'C6$$

$$C2 = C5 + A'B'D + A'CD$$

$$C3 = C4 + BDC5 + A'B'X'$$

$$C4 = D'Y + A'CD'$$

$$C5 = C'C4 + AY + A'BX$$

$$C6 = AC4 + CC5 + C4'C5 + A'B'C$$

$$X = C' + D'$$

$$Y = B'C'$$

5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 6

Production line control


- ⌘ Rods of varying length ($\pm 10\%$) travel on conveyor belt
 - ☑ mechanical arm pushes rods within spec ($\pm 5\%$) to one side
 - ☑ second arm pushes rods too long to other side
 - ☑ rods that are too short stay on belt
 - ☑ 3 light barriers (light source + photocell) as sensors
 - ☑ design combinational logic to activate the arms
- ⌘ Understanding the problem
 - ☑ inputs are three sensors
 - ☑ outputs are two arm control signals
 - ☑ assume sensor reads "1" when tripped, "0" otherwise
 - ☑ call sensors A, B, C

5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 7

Sketch of problem

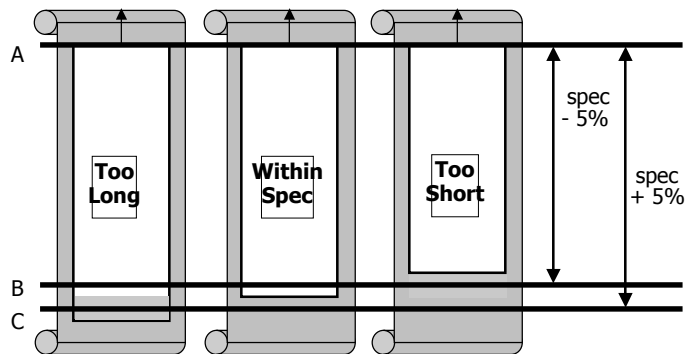- ⌘ Position of sensors
 - ☑ A to B distance = specification - 5%
 - ☑ A to C distance = specification + 5%



5/2/2001

CSE 370 - Spring 2001 - Combinational Implementation - 8

Formalize the problem

⌘ Truth table

show don't cares

A	B	C	Function
0	0	0	do nothing
0	0	1	do nothing
0	1	0	do nothing
0	1	1	do nothing
1	0	0	too short
1	0	1	don't care
1	1	0	in spec
1	1	1	too long

logic implementation now straightforward
just use three 3-input AND gates

"too short" = $AB'C$
(only first sensor tripped)

"in spec" = $A B C'$
(first two sensors tripped)

"too long" = $A B C$
(all three sensors tripped)