
 

 
## Tri-state gates

- ⌘ The third value
  - ☑ logic values: "0", "1"
  - ☑ don't care: "X" (must be 0 or 1 in real circuit!)
  - ☑ third value or state: "Z" — high impedance, infinite R, no connection
- ⌘ Tri-state gates
  - ☑ additional input – output enable (OE)
  - ☑ output values are 0, 1, and Z
  - ☑ when OE is high, the gate functions normally
  - ☑ when OE is low, the gate is disconnected from wire at output
  - ☑ allows more than one gate to be connected to the same output wire
    - ☑ as long as only one has its output enabled at any one time (otherwise, sparks could fly)




	In	OE	Out
non-inverting	X	0	Z
tri-state	0	1	0
buffer	1	1	1



CSE 370 – Spring 2001 - Sequential Logic - 1
 
## Tri-state and multiplexing

- ⌘ When using tri-state logic
  - ☑ (1) make sure never more than one "driver" for a wire at any one time (pulling high and low at the same time can severely damage circuits)
  - ☑ (2) make sure to only use value on wire when its being driven (using a floating value may cause failures)
- ⌘ Using tri-state gates to implement an economical multiplexer



when Select is high  
Input1 is connected to F


when Select is low  
Input0 is connected to F

this is essentially a 2:1 mux

CSE 370 – Spring 2001 - Sequential Logic - 2
 
## More complex counter example

- ⌘ Complex counter
  - ☒ repeats 5 states in sequence
  - ☒ not a binary number representation
- ⌘ Step 1: derive the state transition diagram
  - ☒ count sequence: 000, 010, 011, 101, 110
- ⌘ Step 2: derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	-	-	-
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	-	-	-

note the don't care conditions that arise from the unused state codes

## More complex counter example (cont'd)

- ⌘ Step 3: K-maps for next state functions

	C			
C+	0	0	0	X
A	X	1	X	1
	B			

	C			
B+	1	1	0	X
A	X	0	X	1
	B			

	C			
A+	0	1	0	X
A	X	1	X	0
	B			

$$C+ := A$$

$$B+ := B' + A'C'$$

$$A+ := BC'$$

## Comparison

- ⌘ T FF: 5 gates, 10 literals, 15 wires
- ⌘ RS FF: 3, 5, 12
- ⌘ JK FF: 2, 4, 9
- ⌘ D FF: 3, 5, 9

Summary :

- ⌘ JK FF are most gate and literal efficient
- ⌘ T FF are good mainly for straight forward counters
- ⌘ D FF: Donot need the next state mapping stage. And **less wiring complexity**
- ⌘ JK is **always** better than RS