

Problem 1 – Design a Verilog 16-bit adder module

```
module adder (A, B, sum);  
    input [15:0] A, B;  
    output [15:0] sum;  
  
    assign sum = A + B;  
endmodule
```

Problem 1 – Design a Verilog 16-bit adder module

```
module adder (A, B, sum);  
    input [15:0] A, B;  
    output [15:0] sum;  
    reg    [15:0] sum;  
  
    always @(A or B) begin  
        sum = A + B;  
    end  
endmodule
```

Problem 2 – Design a Verilog 16-bit ALU

```
module alu (A, B, op, result);  
    input [15:0] A, B;    input [2:0] op;  
    output [15:0] result; reg [15:0] result;  


---

  
    always @(A or B or op) begin  
        case (op)  
            0: result = A + B;  
            . . .  
            6: result = B - A;  
            default: result = 16'bX;  
        end  
    end  
endmodule
```

Problem 2 – Design a Verilog 16-bit ALU

```
module alu (A, B, op, result);
```

```
  input [15:0] A, B;    input [2:0] op;
```

```
  output [15:0] result;
```

```
  assign result = (op==0)?(A+B):
```

```
    . . .
```

```
    (op==6)?(B-A): 16'bX;
```

```
endmodule
```

Problem 3 – Design a Verilog Register File (write)

```
module rfile (clk, reset AddrA, AddrB, AddrW, A, B, Din, write);  
    reg [15:0] R0, R1, R2, R3;
```

```
    always @(posedge clk) begin  
        case (AddrW)  
            0: R0 <= Din;  
            1: R1 <= Din;  
            2: R2 <= Din;  
            3: R3 <= Din;  
        endcase  
    endmodule
```

Problem 3 – Design a Verilog Register File (read)

```
module rfile (clk, reset AddrA, AddrB, AddrW, A, B, Din, write);  
    reg [15:0] R0, R1, R2, R3;
```

```
    always @(AddrA) begin  
        case (AddrA or R0 or R1 or R2 or R3)  
            0: A = R0;  
            1: A = R1;  
            2: A = R2;  
            3: A = R3;  
        endcase  
    end  
endmodule
```

+ The equivalent
always block for B

Restricted FSM Implementation Style


- Mealy machine requires two always blocks
 - register needs posedge CLK block
 - input to output needs combinational block
- Moore machine can be done with one always block
 - e.g. simple counter
 - ***Not a good idea for general FSMs***
 - Can be very confusing (see example)
- Moore outputs
 - Share with state register, use suitable state encoding

Problem 4 – Design a “Steppable” Clock

A clock generator:



Mode 0 : clk is free-running, 1/2 sysClk frequency

Mode 1 : clk is stopped, step causes one pulse on clk

 


Problem 4 – Design a “Steppable” Clock

Draw a state diagram – start with Mode 1 (step mode)

  

 
Problem 4 – Design a “Steppable” Clock

Draw a state diagram – start with Mode 1 (step mode)





State Assignment?

Since clk is a Moore output, share it with a state bit

 

 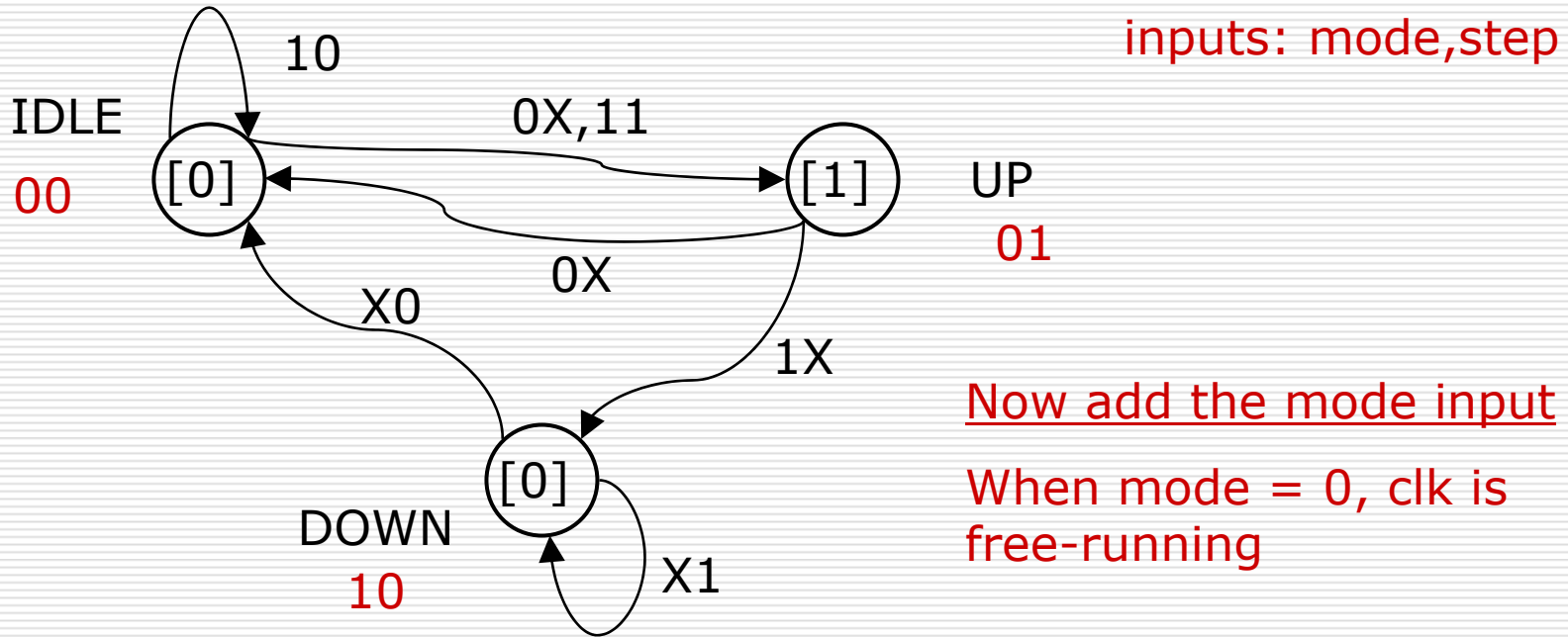Problem 4 – Design a “Steppable” Clock

Draw a state diagram – start with Mode 1 (step mode)



Verilog for "Steppable" Clock (state reg)

```
module stepClk (sysClk, mode, step, clk);
```

```
  input sysClk, mode, step;          output clk;
```

```
  parameter IDLE=0, UP=1, DOWN=2;    // Use names!
```


```
  reg [1:0] state, nxtState;
```

```
  assign clk = state[0];             // clk output shared with state
```

```
  always @(posedge sysClk) begin
```

```
    state <= nxtState;
```

```
  end
```

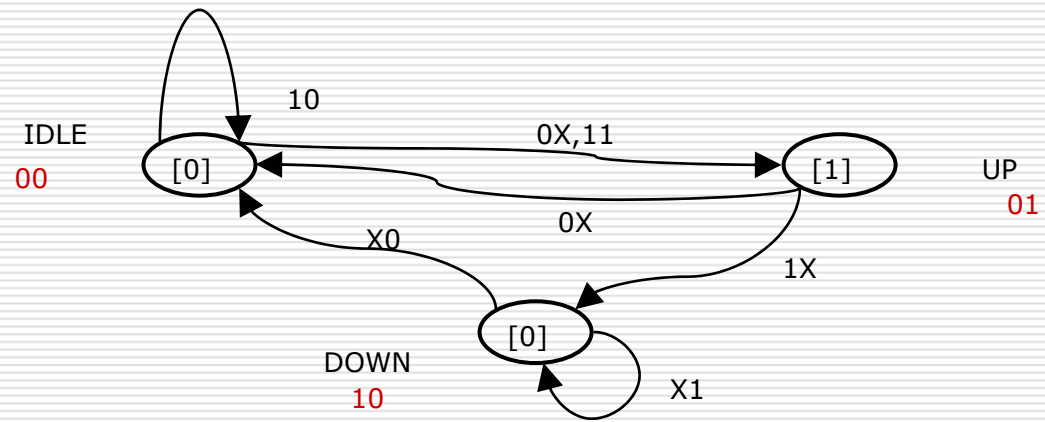

Verilog for "Steppable" Clock (functions)

```
module stepClk (sysClk, mode, step, clk);  
  input sysClk, mode, step;          output clk;  
  parameter IDLE=0, UP=1, DOWN=2;
```

```
  always @(state or mode or step) begin
```

```
    nxtState = state;                // Default (what if we leave out??)
```

```
    case (state)
```

```
      IDLE : if (~mode | step) nxtState = UP;
```


```
      UP :   nxtState = DOWN;
```

```
      DOWN : if (~mode) nxtState = UP;
```

```
             else if (~step) nxtState = IDLE;
```

```
    endcase
```

```
  end
```

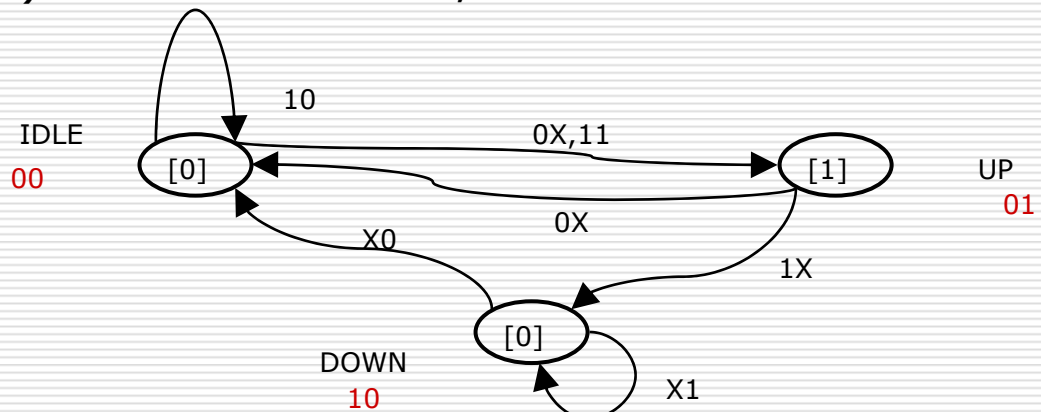

Verilog for "Steppable" Clock (functions)

```
module stepClk (sysClk, mode, step, clk);
  input sysClk, mode, step;          output clk;
  parameter IDLE=0, UP=1, DOWN=2;


---


  always @(state or mode or step) begin
    nxtState = state;                // Default (does this matter?)
    case (state)
      IDLE : if (~mode | step) nxtState = UP;
      UP   : nxtState = DOWN;
      DOWN : if (~mode) nxtState = UP;
            else if (~step) nxtState = IDLE;
      default: nxtState = 2'bX;      // Does this matter?
    endcase
  end
```

Problem 5 : Data Switch


Two input data streams enter the switch, one item per clock

Each contains an address (addrA, addrB) which indicates which output port they want

The switch sends each to the desired output port


If they contend, then the switch treats them fairly

valid outputs indicate if there is a message for that output

 

Problem 5 : Data Switch

There is a control and data circuit.
Design the data circuit first.

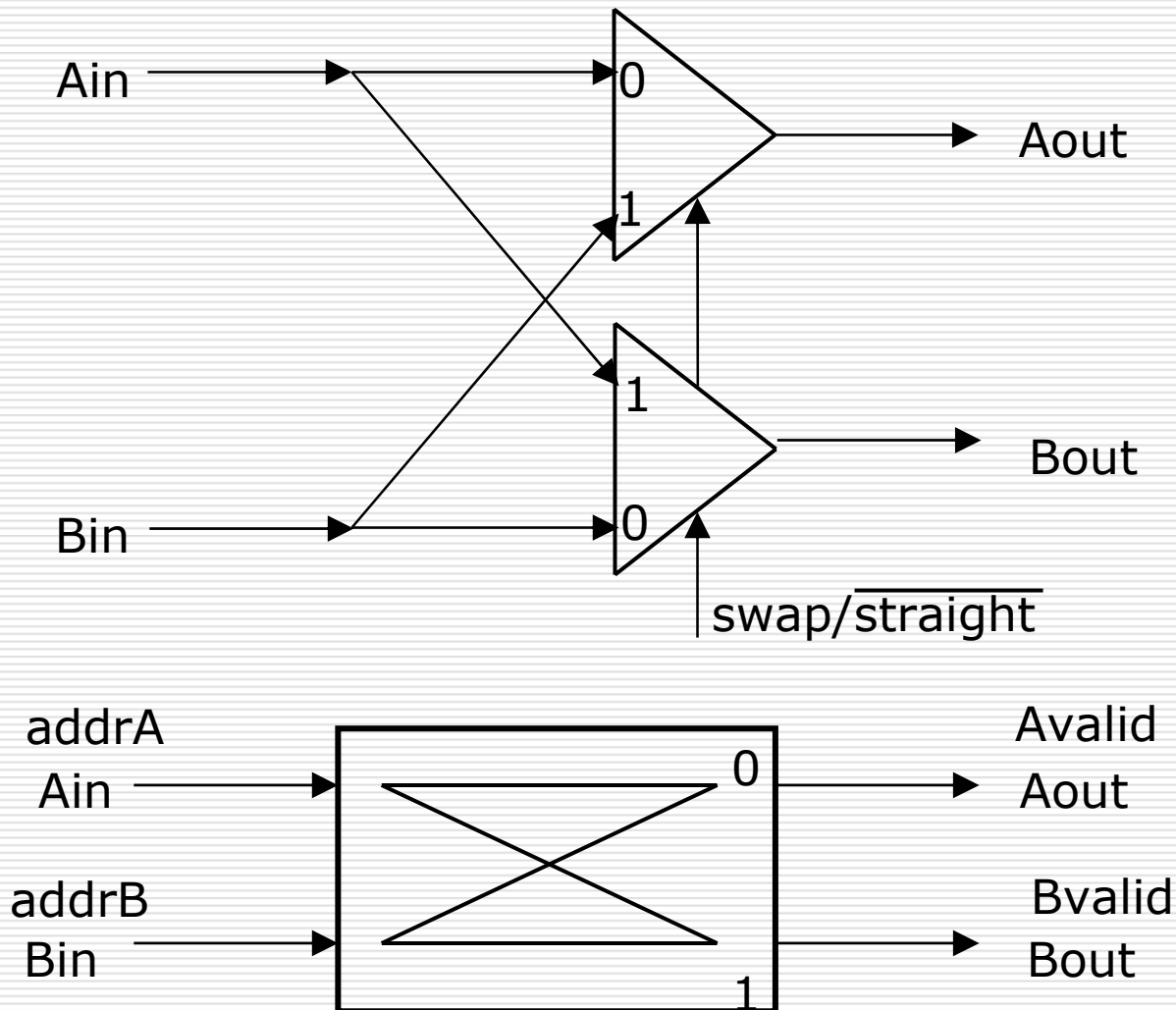


Problem 5 : Data Switch Verilog for data circuit:

```
input  [15:0] Ain, Bin;  
output [15:0] Aout, Bout;  
reg  swap;           // Internal Control signal
```

```
assign Aout = swap ? Bin : Ain;
```


```
assign Bout = swap ? Ain : Bin;
```

 

Problem 5 : Data Switch Verilog for data circuit:

```
input  [15:0] Ain, Bin;      // Add reg declaration
output [15:0] Aout, Bout;   // for always block!
reg  swap;                  // Internal Control signal
```


```
always @(Ain or Bin or swap) begin
  if (swap) begin
    Aout = Bin; Bout = Ain;
  end else begin
    Aout = Ain; Bout = Bin;
  end
end
end
```

 

Problem 5 : Data Switch Verilog for data circuit:

```
input  [15:0] Ain, Bin;  
output [15:0] Aout, Bout;  
reg swap; // Internal Control signal
```

```
always @(Ain or Bin or swap) begin  
    Aout = Ain; Bout = Bin; // Default  
    if (swap) begin  
        Aout = Bin; Bout = Ain;  
    end  
end
```

 

Problem 5 : Data Switch


Now design the control

AddrA,AddrB/swap

If we have addrA, addrB and swap, then we can compute Avalid and Bvalid:

```
assign Avalid = (addrA == swap);
```

```
assign Bvalid = (addrB != swap);
```


 


Problem 5 : Data Switch

Now design the control:

AddrA,AddrB/swap

Mealy! We forward the data **this** clock cycle

  

Problem 5 : Data Switch Verilog

```
module switch (clk, reset, Ain, addrA, Bin,
              addrB, Aout, Avalid, Bout, Bvalid);
  input clk, reset;
  input [15:0] Ain, Bin;
  input addrA, AddrB;
  output [15:0] Aout, Bout;
  output Avalid, Bvalid;
  reg swap; // Control signal
  assign Aout = swap ? Bin : Ain;
  assign Bout = swap ? Bin : Bin;
  assign Avalid = (addrA == swap);
  assign Bvalid = (addrB != swap);

  parameter APRI=0, BPRI=1; // State names
  reg state, next_state;
  always @(posedge clk) begin
    if (reset) state <= APRI;
    else state <= next_state;
  end

  always @(*) begin
    next_state = state;
    swap = 0;
    case (state)
      APRI: begin
        swap = addrA;
        if (addrA == addrB) nextState = BPRI;
      end
      BPRI: begin
        swap = ~addrB;
        if (addrA == addrB) nextState = APRI;
      end
    endcase
  end
endmodule
```

