 


CSE 370 Spring 2006

Introduction to Digital Design

Lecture 3: Boolean Algebra



Last Lecture

- Binary and other bases
- Negative binary numbers
- Switches/CMOS

Today


- CMOS
- Basic Boolean Functions
- Boolean Algebra

Administrivia

- Hand in Homework 1: Homework 2 on the web this afternoon.
- Lab 2 is on the web, you might want to start the tutorial before you lab session.
- Office hours change:
Adrienne Wang W 1-3pm in 003 Allen Center

Switching Networks

 - Switch settings determine whether a conducting network to a light bulb
- Larger computations?
 - Use a light bulb (output) to set other switches (input)
 - Example: Mechanical relay



conducting path composed of switches closes circuit

current flowing through coil magnetizes core and causes normally closed (nc) contact to be pulled open

when no current flows, the spring of the contact returns it to its normal position


Transistor Networks

- Relays no more: slow and big
- Modern digital electronics predominately uses CMOS technology
 - MOS: metal-oxide-semiconductor
 - C: complementary (both p and n type transistors arranged so that power is dissipated during switching.)


MOS Transistors

■ MOS transistors have three terminals: drain, gate, and source

 
■ Act as switches: if the voltage on the gate terminal is (some amount) higher/lower than the source terminal then a conducting path will be established between the drain and source terminals.



MOS Networks

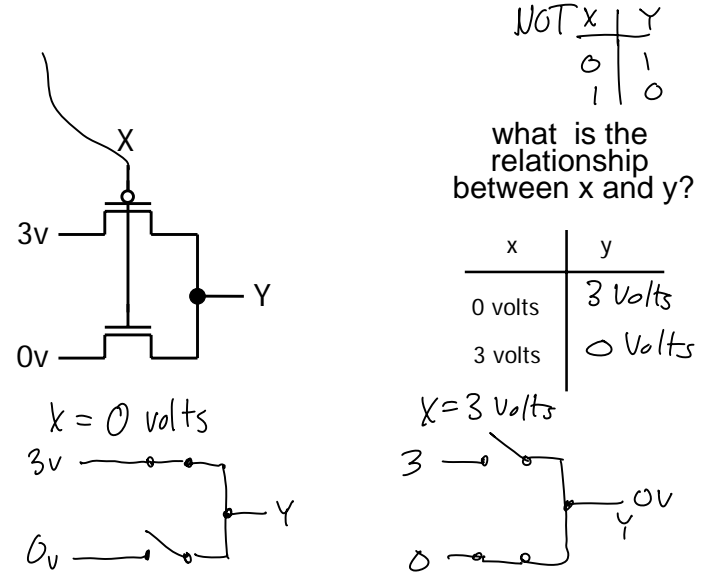

Two Input Networks

 

what is the relationship between x, y and z?

x	y	z1	z2
0 volts	0 volts	3V	3V
0 volts	3 volts	3V	0V
3 volts	0 volts	3V	0V
3 volts	3 volts	0V	0V
0	0	1	1
0	1	1	0
1	0	1	0
1	1	0	0

Handwritten notes: NAND, NOR

2 to 1 Boolean Functions

There are 16 possible two bit input one bit output

$2^4 = 16$

$X \rightarrow \square \rightarrow F$

16 possible functions (F0-F15)

X	Y	F0	F1	F2	F3	F4	F5	F6	F7	F8	F9	F10	F11	F12	F13	F14	F15
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Handwritten labels for functions: X and Y, X, Y, X xor Y, X or Y, X = Y, not Y, not X, X nand Y, not (X and Y).

(General: k input bits, one output bit: 2^k such functions)

Costs

- 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
- X (F3) and Y (F5): require 0 switches, output is one of inputs ←
- X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
- X nor Y (F4) and X nand Y (F14): require 4 switches
- X or Y (F7) and X and Y (F1): require 6 switches
- X = Y (F9) and X ⊕ Y (F6): require 16 switches

NOTs, NANDs, NORs cost the least

NOT, NOR, NANDS, Oh My!

- Can we implement all logic functions from NOT, NOR, NANDs?
- Example: Implementing NOT(X NAND Y)
 - is the same as implementing (X AND Y)
- In fact we can implement a NOT using a NAND or a NOR:

$$\text{NOT}(X) = X \text{ NAND } X \quad \text{NOT}(X) = Y \text{ NOR } Y$$
- In fact NAND and NOR can be used to implement each other:

$$X \text{ NAND } Y = \text{NOT}(\text{NOT}(X) \text{ NOR } \text{NOT}(Y)) \quad \text{NORs}$$

$$X \text{ NOR } Y = \text{NOT}(\text{NOT}(X) \text{ NAND } \text{NOT}(Y))$$
- To sort through the mess of what we have created we will construct a mathematical framework: Boolean Algebra

Boolean Algebra

■ A set of elements B together with a two binary operations, addition, {+}, and multiplication, {•} which satisfy the *axioms*:

- B contains at least two nonequal elements $B \times B \rightarrow B$
- ✓ (closure) For every a,b in B
 - a+b is in B
 - a•b is in B
- ✓ (commutative) For every a,b in B
 - a+b=b+a
 - a•b=b•a
- ✓ (associative) For every a,b,c in B
 - (a+b)+c=a+(b+c)
 - a•(b•c)=(a•b)•c
- ✓ (identity) There exists identity elements for + and •, such that for every a in B
 - a+0=a
 - a•1=a
- ✓ (distributive) For every a,b,c in B
 - a+(b•c)=(a+b)•(a+c)
 - a•(b+c)=(a•b)+(a•c)
- ✓ (complement) For each a in B there exists an element a' in B, such that a+a'=1 and a•a'=0

A Boolean Algebra

- A Boolean Algebra:
 - the set B={0,1}
 - binary operation + = logical OR
 - binary operation • = logical AND
 - complement ' = logical NOT
- These satisfy the above axioms
- We will often deal with variable representing an element from the set:

Example: $(X+Y)•(X+Z)$


$$(X \text{ OR } Y) \text{ AND } (X \text{ OR } Z)$$

$$\begin{aligned} 0+0 &= 0 & 0' &= 1 \\ 0+1 &= 1 & 0 \cdot 1 &= 0 \\ 1+0 &= 1 & 1 \cdot 0 &= 0 \\ 1+1 &= 1 & 1 \cdot 1 &= 1 \end{aligned}$$

Boolean Functions


■ Boolean Function

 - function from k input bits to one output bit



- All such functions can be represented by a truth table

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

Boolean Functions and Algebra

- All Boolean Functions can be represented by an expression in Boolean Algebra using ANDs, ORs, and NOTs:

2 bit

X	Y	F	$X' \cdot Y$	$X \cdot Y'$	$X'Y + XY'$
0	0	0	0	0	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

terms

$X' \cdot Y' \cdot Z$

$X' \cdot Y \cdot Z'$

$X \cdot Y \cdot Z$

$F = X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y \cdot Z$

$F = X' \cdot Y + X \cdot Y'$

Universality of NAND/NOR

- All Boolean Functions can be represented by an expression in Boolean Algebra using ANDs, ORs, and NOTs.

But we can express AND, OR, and NOT in terms of NAND:

$X' = X \text{ NAND } X$

$X \text{ AND } Y = (X \text{ NAND } Y)'$

$X \text{ OR } Y = (X' \text{ NAND } Y')$

But we can express AND, OR, and NOT in terms of NOR:

$X' = X \text{ NOR } X$

$X \text{ OR } Y = (X \text{ NOR } Y)'$

$X \text{ AND } Y = (X' \text{ NOR } Y')$

Duality

- All Boolean expressions have logical duals
- Any theorem that can be proved is also proved for its dual
- Replace: \cdot with $+$, $+$ with \cdot , 0 with 1, and 1 with 0
- Leave the variables unchanged

Example: $X+0=0$ is dual to $X \cdot 1=1$


$X+0=X$ $X \cdot 1=X$

Do not confuse Duality with de'Morgan's theorem.

$X+0=X$

↓ ↓ ↓ ↓ ↓

$X \cdot 1=X$

 

Axioms and Theorems

- | | | |
|---------------------|---|---|
| 1. Identity: | $X + 0 = X$ | Dual: $X \cdot 1 = X$ |
| 2. Null: | $X + 1 = 1$ | Dual: $X \cdot 0 = 0$ |
| 3. Idempotent: | $X + X = X$ | Dual: $X \cdot X = X$ |
| 4. Involution: | $(X')' = X$ | |
| 5. Complementarity: | $X + X' = 1$ | Dual: $X \cdot X' = 0$ |
| 6. Commutative: | $X + Y = Y + X$ | Dual: $X \cdot Y = Y \cdot X$ |
| 7. Associative: | $(X+Y)+Z=X+(Y+Z)$ | Dual: $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$ |
| 8. Distributive: | $X \cdot (Y+Z) = (X \cdot Y) + (X \cdot Z)$ | Dual: $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$ |
| 9. Uniting: | $X \cdot Y + X \cdot Y' = X$ | Dual: $(X+Y) \cdot (X+Y') = X$ |
| 10. Absorption: | $X + X \cdot Y = X$ | Dual: $X \cdot (X + Y) = X$ |
| 11. Absorption2: | $(X + Y') \cdot Y = X \cdot Y$ | Dual: $(X \cdot Y') + Y = X + Y$ |
| 12. Factoring: | $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$ | Dual: $X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$ |

Axioms and Theorems

13. Consensus: $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$
 Dual: $(X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$
14. DeMorgan's Law: $(X + Y + \dots)' = X' \cdot Y' \cdot \dots$
 Dual: $(X \cdot Y \cdot \dots)' = X' + Y' + \dots$
15. Generalized DeMorgan's Laws: $f'(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)$

Notice the DeMorgan is not Duality: Duality is not a way to rewrite an expression, it is a meta-theorem.

16. Generalized Duality:
 $f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$

Proving Theorems

- $F = X \cdot Y + X' \cdot Y' = X$
- Example 1: Prove the uniting theorem-- $X \cdot Y + X \cdot Y' = X$
- | | | |
|-----------------|---|--------------|
| Distributive | $X \cdot Y + X \cdot Y' = X \cdot (Y + Y')$ | (8) |
| Complementarity | $= X \cdot (1)$ | $Y + Y' = 1$ |
| Identity | $= \underline{X}$ | |

- Example 2: Prove the absorption theorem-- $X + X \cdot Y = X$
- | | |
|--------------|---|
| Identity | $X + X \cdot Y = (X \cdot 1) + (X \cdot Y)$ |
| Distributive | $= X \cdot (1 + Y)$ |
| Null | $= X \cdot (1)$ |
| Identity | $= \underline{X}$ |

Activity

- Example 3: Prove the consensus theorem--
 $(XY) + (YZ) + (X'Z) = XY + X'Z$

Exercise

- Example 3: Prove the consensus theorem--
 $(XY) + (YZ) + (X'Z) = XY + X'Z$

Complementarity $XY + YZ + X'Z = XY + (X + X')YZ + X'Z$
 Distributive $= XYZ + XY + X'YZ + X'Z$

Use absorption $\{AB + A = A\}$ with $A = XY$ and $B = Z$

$$= XY + X'YZ + X'Z$$

Rearrange terms $= XY + X'ZY + X'Z$

Use absorption $\{AB + A = A\}$ with $A = X'Z$ and $B = Y$

$$\underline{XY + YZ + X'Z = XY + X'Z}$$

Proving Theorems

- Prove by using "Perfect Induction" also called "Enumeration"
- Cumbersome for very large expressions

$(X + Y)' = X' \cdot Y'$
 NOR is equivalent to AND
 with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
 NAND is equivalent to OR
 with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Logic Simplification

- Use the axioms to simplify logical expressions
 - Why? To use less hardware

- Example: A two-level logic expression

$$\begin{aligned} Z &= A'BC + AB'C' + AB'C + ABC' + ABC \\ &= AB'C + AB'C' + A'BC + ABC' + ABC && \text{rearrange} \\ &= AB'(C + C') + A'BC + AB(C' + C) && \text{distributive} \\ &= AB' + A'BC + AB && \text{comp.} \\ &= AB' + AB + A'BC && \text{rearrange} \\ &= A(B' + B) + A'BC && \text{distributive} \\ &= A + A'BC && \text{comp.} \end{aligned}$$

$B' + B = 1$
 $A' \cdot 1 = A'$

Absorption #2D $\{(X \cdot Y) + Y = X + Y\}$ with $X = BC$ and $Y = A$

$$Z = A + BC \quad \checkmark$$

Example: Full Adder

- 1-bit binary adder



Cin	A	B	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth table

Boolean express

$$S = A'B'Cin + A'BCin' + AB'Cin' + ABCin$$

$$Cout = A'BCin + AB'Cin + ABCin' + ABCin$$

Simplification of Carry Out

$$\begin{aligned} \text{Cout} &= A'BCin + AB' Cin + ABCin' + ABCin \\ &= A'BCin + AB' Cin + ABCin' + \overline{ABCin} + ABCin \\ &= A'BCin + ABCin + AB' Cin + \overline{ABCin'} + ABCin \\ &\Rightarrow (A'+A)BCin + AB' Cin + ABCin' + ABCin \\ \text{associative} &= \underline{(1)}BCin + AB' Cin + ABCin' + ABCin \\ &= BCin + AB' Cin + ABCin' + ABCin + ABCin \\ &= BCin + AB' Cin + ABCin + ABCin' + ABCin \\ &= BCin + A(\underline{B'+B})Cin + ABCin' + ABCin \quad \text{idempotent} \\ &= BCin + A(\underline{1})Cin + ABCin' + ABCin \\ &= BCin + ACin + AB(\underline{Cin'+Cin}) \quad \text{distribut} \\ &= BCin + ACin + AB(\underline{1}) \\ &= \underline{BCin + ACin + AB} \end{aligned}$$