 


CSE 370 Spring 2006 Introduction to Digital Design

Lecture 15: Sequential Verilog



Last Lecture

- Latches
- Flip-flops

Today

- Timing Methodology
- Sequential Verilog

Administrivia

- Turn in HW#5
- Lab #6 on the web

Quiz #2


Quiz #2

Timing methodologies


- Rules for interconnecting components and clocks
 - guarantee proper operation of system when strictly followed
- Approach depends on building blocks used for memory elements
 - we'll focus on systems with edge-triggered flip-flops
 - found in programmable logic devices
 - many custom integrated circuits focus on level-sensitive latches
- Basic rules for correct timing:
 - (1) correct inputs, with respect to time, are provided to the flip-flops
 - (2) no flip-flop changes state more than once per clocking event

Timing methodologies (cont'd)

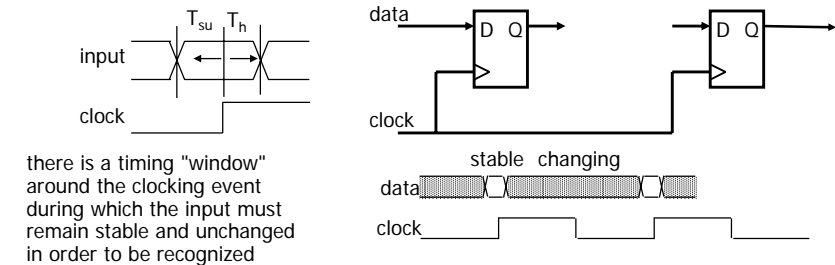- Definition of terms
 - clock: periodic event, causes state of memory element to change can be rising edge or falling edge or high level or low level
 - setup time: minimum time before the clocking event by which the input must be stable (T_{su})
 - hold time: minimum time after the clocking event until which the input must remain stable (T_h)



Comparison of latches and flip-flops

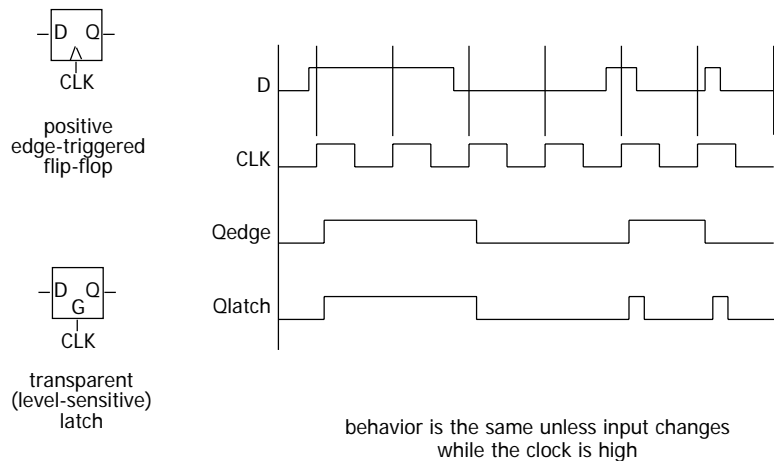


Comparison of latches and flip-flops (cont'd)

Type	When inputs are sampled	When output is valid
unclocked latch	always	propagation delay from input change
level-sensitive latch	clock high (T_{su}/T_h around falling edge of clock)	propagation delay from input change or clock edge (whichever is later)
master-slave flip-flop	clock high (T_{su}/T_h around falling edge of clock)	propagation delay from falling edge of clock
negative edge-triggered flip-flop	clock hi-to-lo transition (T_{su}/T_h around falling edge of clock)	propagation delay from falling edge of clock

Typical timing specifications

 
- Positive edge-triggered D flip-flop
 - setup and hold times
 - minimum clock width
 - propagation delays (low to high, high to low, max and typical)



all measurements are made from the clocking event (the rising edge of the clock)


Cascading edge-triggered flip-flops

 - Shift register
 - new value goes into first stage
 - while previous value of first stage goes into second stage
 - consider setup/hold/propagation delays (prop must be > hold)



Cascading edge-triggered flip-flops (cont'd)

 - Why this works
 - propagation delays exceed hold times
 - clock width constraint exceeds setup time
 - this guarantees following stage will latch current value before it changes to new value



timing constraints guarantee proper operation of cascaded components

assumes infinitely fast distribution of the clock

Variables

- wire
 - Connects components together
- reg
 - Saves a value
 - Part of a behavioral description
 - Does **NOT** necessarily become a register when you synthesize
 - May become a wire
- The rule
 - Declare a variable as reg if it is a target of an assignment statement
 - Continuous assign doesn't count

Sequential Verilog

- Sequential circuits: Registers & combinational logic
 - Use positive edge-triggered registers
 - Avoid latches and negative edge-triggered registers
- Register is triggered by “posedge clk”

```
module register(Q, D, clock);  
  input  D, clock;  
  output Q;  
  reg   Q;  
  
  always @(posedge clock) begin  
    Q = D;  
  end  
endmodule
```

Example: A D flip-flop

A real register. Holds Q between clock edges

always block

- A procedure that describes a circuit's function
 - Can contain multiple statements
 - Can contain *if*, *for*, *while*, *case*
 - Triggers at the specified conditions
 - *begin/end* groups statements within *always* block

```
module register(Q, D, clock);  
  input  D, clock;  
  output Q;  
  reg   Q;  
  
  always @(posedge clock) begin  
    Q = D;  
  end  
endmodule
```

always example

```
module and_gate(out, in1, in2);  
  input  in1, in2;  
  output out;  
  reg   out;  
  
  always @(in1 or in2) begin  
    out = in1 & in2;  
  end  
endmodule
```

Not a real register!!
Holds assignment in
always block

The compiler will not synthesize
this code to a register, because
out changes whenever *in1* or *in2*
change. Can instead simply write
wire out, in1, in2;
and (out, in1, in2);

specifies when block is executed
i.e. triggered by changes in *in1* or *in2*

Incomplete trigger or incomplete assignment

- What if you omit an input trigger (e.g. *in2*)
 - Compiler will insert a register to hold the state
 - Becomes a sequential circuit — **NOT** what you want

```
module and_gate (out, in1, in2);  
  input  in1, in2;  
  output out;  
  reg   out;  
  
  always @(in1) begin  
    out = in1 & in2;  
  end  
endmodule
```

A real register!! Holds *out*
because *in2* isn't specified
in *always* trigger

2 rules:

- 1) Include all inputs in the trigger list
- 2) Use complete assignments
 - ⇒ Every path must lead to an assignment for *out*
 - ⇒ Otherwise *out* needs a state element

Another way: Use functions

■ Functions for combinational logic

■ Functions can't have state

```
module and_gate (out, in1, in2);
  input      in1, in2;
  output    out;

  assign out = myfunction(in1, in2);
  function myfunction;
    input in1, in2;
    begin
      myfunction = in1 & in2;
    end
  endfunction
endmodule
```

Benefits:

- Functions force a result
- ⇒ Compiler will fail if function does not generate a result
- ⇒ If you build a function wrong the circuit will not synthesize.
- If you build an always block wrong you get a register

if

■ Same as C *if* statement

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel;    // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y;              // target of assignment

  always @(sel or A or B or C or D)
    if (sel == 2'b00) Y = A;
    else if (sel == 2'b01) Y = B;
    else if (sel == 2'b10) Y = C;
    else if (sel == 2'b11) Y = D;
endmodule
```

- ⇒ Single *if* statements synthesize to multiplexers
- ⇒ Nested *if/else* statements usually synthesize to logic

if (another way)

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel;    // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y;              // target of assignment

  always @(sel or A or B or C or D)
    if (sel[0] == 0)
      if (sel[1] == 0) Y = A;
      else Y = B;
    else
      if (sel[1] == 0) Y = C;
      else Y = D;
endmodule
```

case

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel;    // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y;              // target of assignment

  always @(sel or A or B or C or D)
    case (sel)
      2'b00: Y = A;
      2'b01: Y = B;
      2'b10: Y = C;
      2'b11: Y = D;
    endcase
endmodule
```

- case* executes sequentially
- ⇒ First match executes
- ⇒ Don't need to break out of *case*
- case* statements synthesize to muxes

case (another way)

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel; // 2-bit control signal
input A, B, C, D;
output Y;

assign out = mymux(sel, A, B, C, D);
function mymux;
input [1:0] sel, A, B, C, D;
begin
case (sel)
2'b00: mymux = A;
2'b01: mymux = B;
2'b10: mymux = C;
2'b11: mymux = D;
endcase
end
endfunction
endmodule
```

Note: You can define a function in a file
Then *include* it into your Verilog module

default case

```
// Simple binary encoder (input is 1-hot)
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
case (A)
8'b00000001: Y = 0;
8'b00000010: Y = 1;
8'b00000100: Y = 2;
8'b00001000: Y = 3;
8'b00010000: Y = 4;
8'b00100000: Y = 5;
8'b01000000: Y = 6;
8'b10000000: Y = 7;
default: Y = 3'bx; // Don't care about other cases
endcase
endmodule
```

If you omit the *default*, the compiler will
create a latch for Y
⇒ Either list all 256 cases
⇒ Or use a function (compiler will
warn you of missing cases)

case executes sequentially

```
// Priority encoder
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
case (1'b1)
A[0]: Y = 0;
A[1]: Y = 1;
A[2]: Y = 2;
A[3]: Y = 3;
A[4]: Y = 4;
A[5]: Y = 5;
A[6]: Y = 6;
A[7]: Y = 7;
default: Y = 3'bx; // Don't care when input is all 0's
endcase
endmodule
```

Case statements execute sequentially
⇒ Take the first alternative that matches

for

```
// simple encoder
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment
integer i; // Temporary variables for program
reg [7:0] test;

always @(A) begin
test = 8b'00000001;
Y = 3'bx;
for (i = 0; i < 8; i = i + 1) begin
if (A == test) Y = i;
test = test << 1; // Shift left, pad with 0s
end
end
endmodule
```

for statements synthesize as
cascaded combinational logic
⇒ Verilog unrolls the loop

Verilog *while/repeat/forever*

- *while* (expression) statement
 - execute statement while expression is true
- *repeat* (expression) statement
 - execute statement a fixed number of times
- *forever* statement
 - execute statement forever

Blocking and non-blocking assignments



- Blocking assignments ($Q = A$)
 - Variable is assigned immediately
 - New value is used by subsequent statements
- Non-blocking assignments ($Q <= A$)
 - Variable is assigned after all scheduled statements are executed
 - Value to be assigned is computed but saved for later
- Example: Swap

```
always @(posedge CLK)          always @(posedge CLK)
begin                            begin
    temp = B;                    A <= B;
    B = A;                       B <= A;
    A = temp;                    end
end
```

Blocking and non-blocking assignments

```
reg B, C, D;
always @(posedge clk)
begin
    B = A;
    C = B;
    D = C;
end
```
  
```
reg B, C, D;
always @(posedge clk)
begin
    B <= A;
    C <= B;
    D <= C;
end
```



Swap

- The following code executes incorrectly
 - One block executes first
 - Loses previous value of variable

```
always @(posedge CLK)          always @(posedge CLK)
begin                            begin
    A = B;                       B = A;
end                                end
```

- Non-blocking assignment fixes this
 - Both blocks are scheduled by posedge CLK

```
always @(posedge CLK)          always @(posedge CLK)
begin                            begin
    A <= B;                       B <= A;
end                                end
```

Parallel versus serial execution

■ `assign` statements are implicitly parallel

■ “=” means continuous assignment

■ Example

```
assign E = A & D;
```

```
assign A = B & C;
```

■ **A** and **E** change if **B** changes

■ `always` blocks execute in parallel


■ `always @(posedge clock)`

■ Procedural block internals not necessarily parallel

■ “=” is a blocking assignment (sequential)

■ “<=” is a nonblocking assignment (parallel)

 ■ Examples of procedures: `always`, `function`, etc.



Synthesis examples

```
wire [3:0] x, y, a, b, c, d;
```

```
assign apr = ^a;
```

```
assign y = a & ~b;
```

```
assign x = (a == b) ?  
    a + c : d + a;
```

