 


CSE 370 Spring 2006 Introduction to Digital Design

Lecture 18: Moore and Mealy Machines



Last Lecture


- Finite State Machines

Today

- Moore and Mealy Machines


Counter/shift-register model

 - Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - next state
 - function of current state and inputs
 - outputs
 - values of flip-flops




General state machine model

 - Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - next state
 - function of current state and inputs
 - outputs
 - function of current state and inputs (Mealy machine)
 - function of current state only (Moore machine)



State machine model (cont'd)

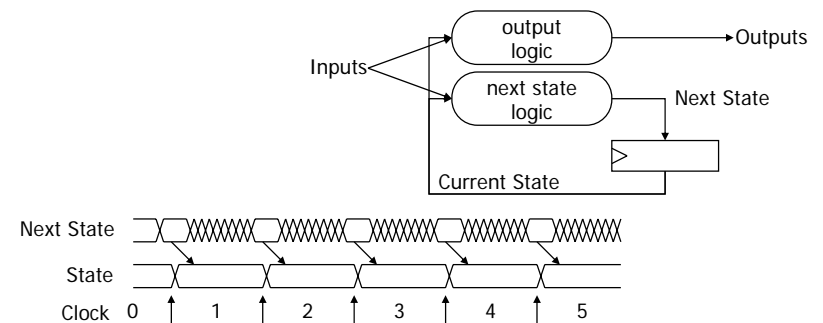- States: S_1, S_2, \dots, S_k
- Inputs: I_1, I_2, \dots, I_m
- Outputs: O_1, O_2, \dots, O_n
- Transition function: $F_s(S_i, I_j)$
- Output function: $F_o(S_i)$ or $F_o(S_i, I_j)$




Comparison of Mealy and Moore machines


- Mealy machines tend to have less states
 - different outputs on arcs (n^2) rather than states (n)
- Moore machines are safer to use
 - outputs change at clock edge (always one cycle later)
 - in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback may occur if one isn't careful
- Mealy machines react faster to inputs
 - react in same cycle – don't need to wait for clock
 - in Moore machines, more logic may be necessary to decode state into outputs – more gate delays after clock edge

Comparison of Mealy and Moore machines (cont'd)


■ Moore

 

■ Mealy

 


■ Synchronous Mealy

 


Specifying outputs for a Moore machine

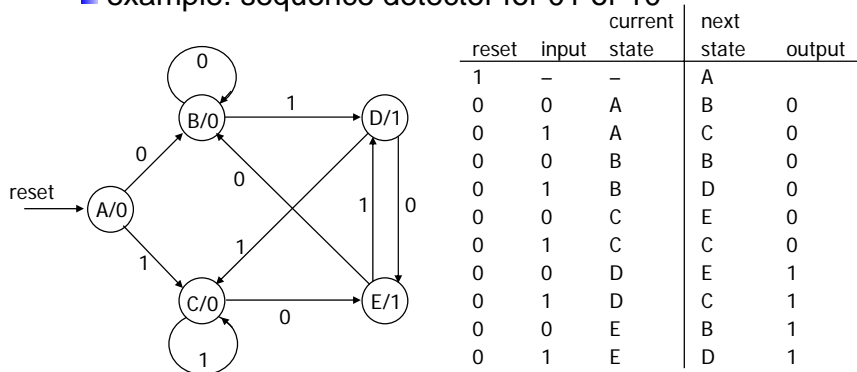- Output is only function of state
 - specify in state bubble in state diagram
 - example: sequence detector for 01 or 10




Specifying outputs for a Mealy machine

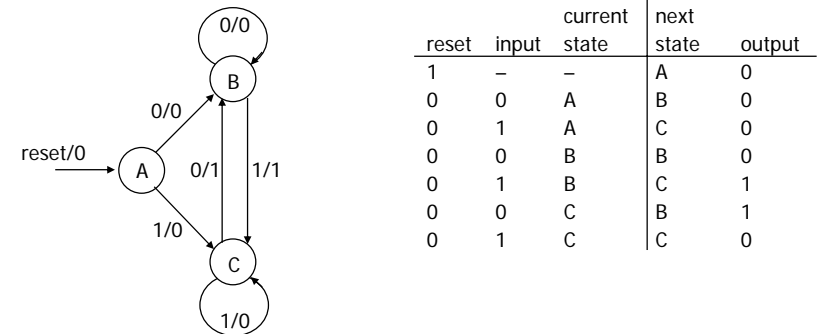- Output is function of state and inputs
 - specify output on transition arc between states
 - example: sequence detector for 01 or 10




Registered Mealy machine (really Moore)

 - Synchronous (or registered) Mealy machine
 - registered state AND outputs
 - avoids 'glitchy' outputs
 - easy to implement in PLDs
- Moore machine with no output decoding
 - outputs computed on transition to next state rather than after entering
 - view outputs as expanded state vector



 
Example: vending machine

- Release item after 15 cents are deposited
- Single coin slot for dimes, nickels
- No change



 
Example: vending machine (cont'd)

- Suitable abstract representation
 - tabulate typical input sequences:
 - 3 nickels
 - nickel, dime
 - dime, nickel
 - two dimes
 - draw state diagram:
 - inputs: N, D, reset
 - output: open chute
 - assumptions:
 - assume N and D asserted for one cycle
 - each state has a self loop for N = D = 0 (no coin)



 Example: vending machine (cont'd)

- Minimize number of states - reuse states whenever possible



present state	inputs		next state	output
	D	N		open
0c	0	0	0c	0
	0	1	5c	0
	1	0	10c	0
	1	1	-	-
5c	0	0	5c	0
	0	1	10c	0
	1	0	15c	0
	1	1	-	-
10c	0	0	10c	0
	0	1	15c	0
	1	0	15c	0
	1	1	-	-
15c	-	-	15c	1

symbolic state table


Example: vending machine (cont'd)

Uniquely encode states

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	-	-	-
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	-	-	-
1	1	-	-	1	1	1

Example: Moore implementation

Mapping to logic

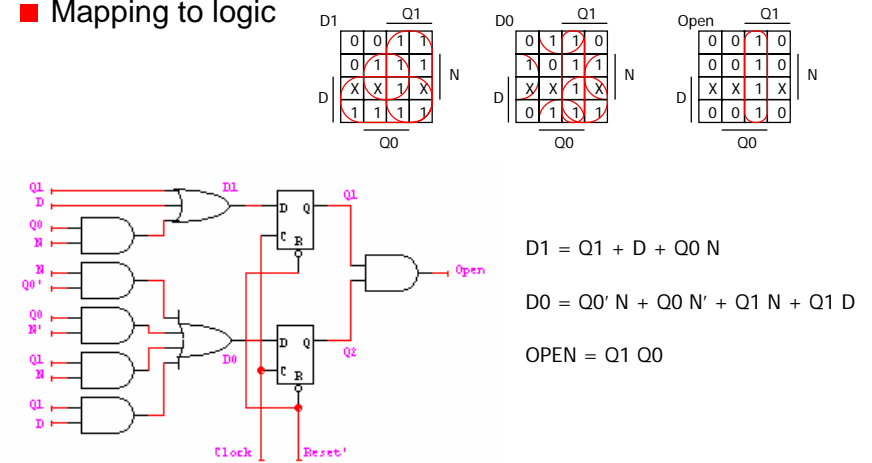

Example: vending machine (cont'd)

One-hot encoding


present state				inputs		next state				output
Q3	Q2	Q1	Q0	D	N	D3	D2	D1	D0	open
0	0	0	1	0	0	0	0	0	1	0
				0	1	0	0	1	0	0
				1	0	0	1	0	0	0
				1	1	-	-	-	-	
0	0	1	0	0	0	0	0	1	0	0
				0	1	0	1	0	0	0
				1	0	1	0	0	0	
				1	1	-	-	-	-	
0	1	0	0	0	0	0	1	0	0	0
				0	1	1	0	0	0	0
				1	0	1	0	0	0	
				1	1	-	-	-	-	
1	0	0	0	-	-	1	0	0	0	1

$D0 = Q0 D' N'$
 $D1 = Q0 N + Q1 D' N'$
 $D2 = Q0 D + Q1 N + Q2 D' N'$
 $D3 = Q1 D + Q2 D + Q2 N + Q3$
 $OPEN = Q3$

Equivalent Mealy and Moore state diagrams


Moore machine

outputs associated with state

 


Mealy machine

outputs associated with transitions

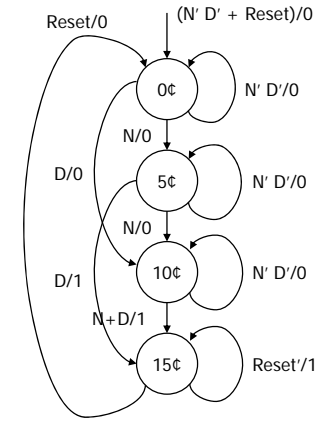

Example: Mealy implementation

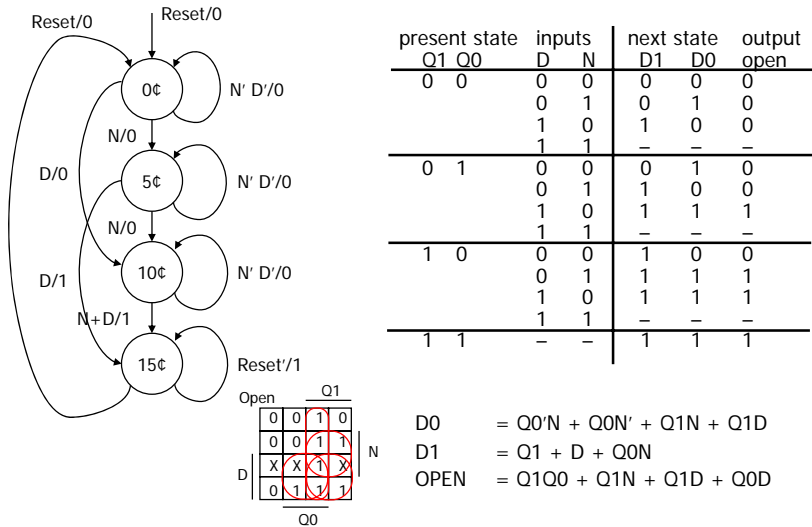


Example: Mealy implementation

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$


$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$

 make sure OPEN is 0 when reset
- by adding AND gate




Vending machine: Moore to synch. Mealy

 - OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D) = Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$



Vending machine: Mealy to synch. Mealy



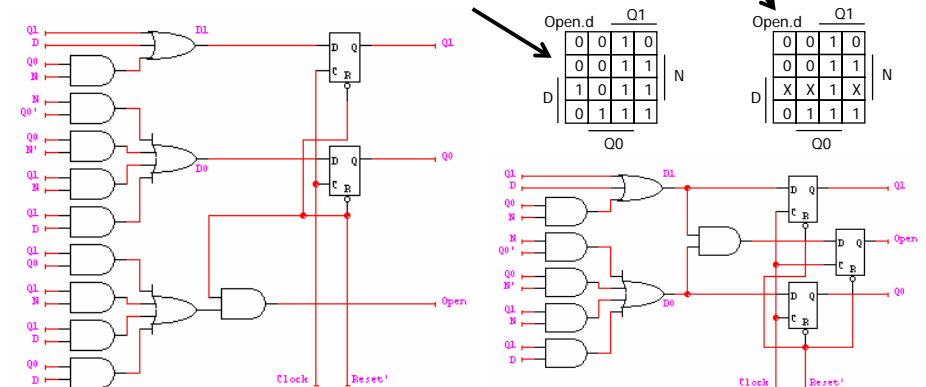
- $OPEN.d = Q1Q0 + Q1N + Q1D + Q0D$
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D) = Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$



Mealy and Moore examples

- Recognize A,B = 0,1


- Mealy or Moore?

   

Mealy and Moore examples (cont'd)

- Recognize A,B = 1,0 then 0,1

- Mealy or Moore?


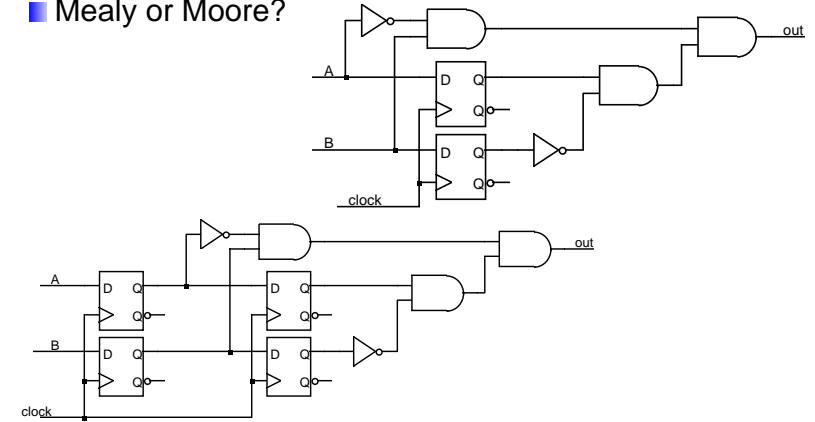


HDLs and Sequential Logic

- Flip-flops
 - representation of clocks - timing of state changes
 - asynchronous vs. synchronous
- FSMs
 - structural view (FFs separate from combinational logic)
 - behavioral view (synthesis of sequencers – not in this course)
- Data-paths = data computation (e.g., ALUs, comparators) + registers
 - use of arithmetic/logical operators
 - control of storage elements

  Example: reduce-1-string-by-1

- Remove one 1 from every string of 1s on the input



Verilog FSM - Reduce 1s example

Moore machine

```


module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;

  parameter zero = 2'b00;
  parameter one1 = 2'b01;
  parameter twos = 2'b10;

  reg out;
  reg [2:1] state; // state variables
  reg [2:1] next_state;

  always @(posedge clk)
    if (reset) state = zero;
    else state = next_state;

```

 

state assignment
(easy to change,
if in one place)

Moore Verilog FSM (cont'd)

```

always @(in or state)
  case (state)
    zero:
      // last input was a zero
      begin
        if (in) next_state = one1;
        else next_state = zero;
      end
    one1:
      // we've seen one 1
      begin
        if (in) next_state = twos;
        else next_state = zero;
      end
    twos:
      // we've seen at least 2 ones
      begin
        if (in) next_state = twos;
        else next_state = zero;
      end
  endcase

```

crucial to include
all signals that are
input to state determination

note that output
depends only on state

```

always @(state)
  case (state)
    zero: out = 0;
    one1: out = 0;
    twos: out = 1;
  endcase
endmodule

```

Mealy Verilog FSM


```

module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables
  reg next_state;

  always @(posedge clk)
    if (reset) state = zero;
    else state = next_state;

  always @(in or state)
    case (state)
      zero: // last input was a zero
        begin
          out = 0;
          if (in) next_state = one;
          else next_state = zero;
        end
      one: // we've seen one 1
        if (in) begin
          next_state = one; out = 1;
        end else begin
          next_state = zero; out = 0;
        end
    endcase
endmodule

```

 

Synchronous Mealy Machine

```

module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables

  always @(posedge clk)
    if (reset) state = zero;
    else
      case (state)
        zero: // last input was a zero
          begin
            out = 0;
            if (in) state = one;
            else state = zero;
          end
        one: // we've seen one 1
          if (in) begin
            state = one; out = 1;
          end else begin
            state = zero; out = 0;
          end
      endcase
  end
endmodule

```

Finite state machines summary

- Models for representing sequential circuits
 - abstraction of sequential elements
 - finite state machines and their state diagrams
 - inputs/outputs
 - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
 - deriving state diagram
 - deriving state transition table
 - determining next state and output functions
 - implementing combinational logic
- Hardware description languages