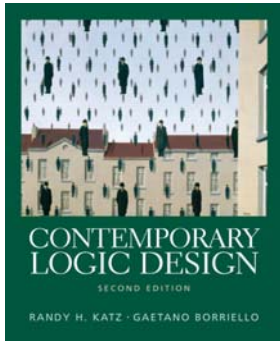


# CSE 370 Spring 2006

## Introduction to Digital Design

### Lecture 21: Ant Brain FSM



#### Last Lecture

- FSM Technologies

#### Today

- A larger FSM example

## Administrivia


- Turn in Homework #7
- Lab 8,9 on the web
- Lab 8 due at end of following lab session
- Lab 9 due on last day of class

## Overview

- Last lectures
  - Finite-state machines
    - Example: A sequence detector FSM
    - Example: A vending machine FSM
- Today
  - A bigger example
    - Ant-brain FSM

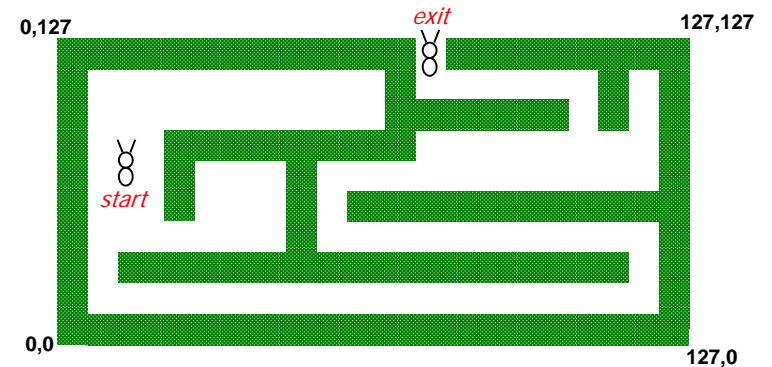
## Ant in a maze

- Electronic ant, electronic maze
  - Design the ant



 
## Example: ant brain (Ward, MIT)

- Sensors: L and R antennae, 1 if in touching wall
- Actuators: F - forward step, TL/TR - turn left/right slightly
- Goal: find way out of maze
- Strategy: keep the wall on the right




## Example: ant brain (special case 1)

- Left (L) Antenna touching the wall

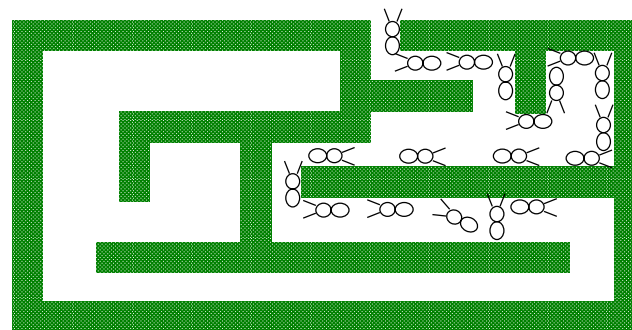


## Example: ant brain (special case 2)

- Ant Lost

 


## Example: ant brain (special case 2)

- Ant Lost (another example)

 

## Ant behavior

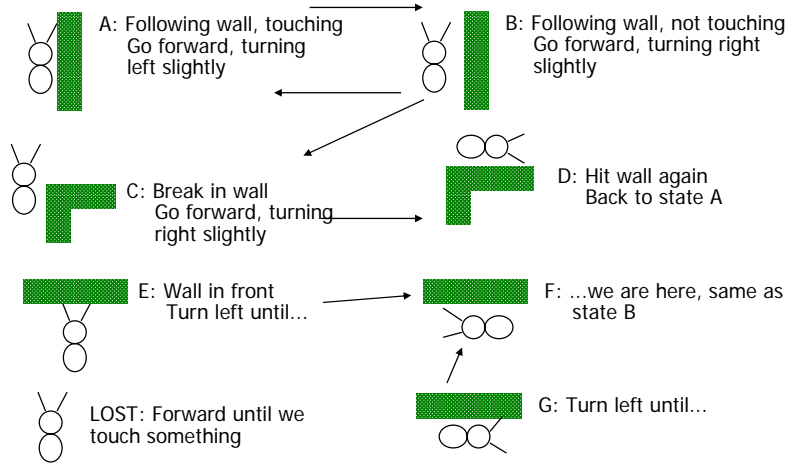

## Goal: Find a way out of maze

### Sensors on L and R antennae

■ Sensor = "1" if touching wall; "0" if not touching wall

■ L'R' ≡ no wall

■ L'R ≡ wall on right

■ LR' ≡ wall on left

■ LR ≡ wall in front

■ \*\*\* ≡ exit

### Movement:

■ F ≡ forward one step

■ TL ≡ turn left 90 degrees

■ TR ≡ turn right 90 degrees

## Notes & strategy


### Notes

- Maze has no islands
- Corridors are wider than ant
- Don't worry about startup
- Assume a Moore machine
- Assume D flip-flops

### Strategy

- Partition your design into datapath and control
- Keep the wall on the right

## The ant's behavior

 

## The maze

- Virtual maze
  - 128 × 128 grid
    - Stored in memory
    - 16384 8-bit words
  - YX is maze addresses
    - X is the ant's horizontal position (7 bits)
    - Y is the ant's vertical position (7 bits)
  - Each memory location says
    - 00000001 ≡ No wall
    - 00000010 ≡ North wall
    - 00000100 ≡ West wall
    - 00001000 ≡ South wall
    - 00010000 ≡ East wall
    - 00100000 ≡ Exit

Can have multiple walls  
Example: 00001100  
⇒ Walls on South and East

## Where do you start???

# Don't look ahead


## What you need

- An FSM for the ant
  - 3 outputs
    - Go forward
    - Turn left
    - Turn right
- Two 7-bit registers for X and Y
  - With preload, increment, decrement
- A register to hold the ant's heading
- Logic to convert memory data to antennae info

## Recommendations

- 7-bit counters for X, Y
  - Move horizontally: Increment or decrement X
  - Move vertically: Increment or decrement Y
- Shift register for heading
  - N: 0001
  - W: 0010
  - S: 0100
  - E: 1000
  - Rotate right when ant turns right
  - Rotate left when ant turns left
- Combinational logic for antennae decoder


# Partition the design

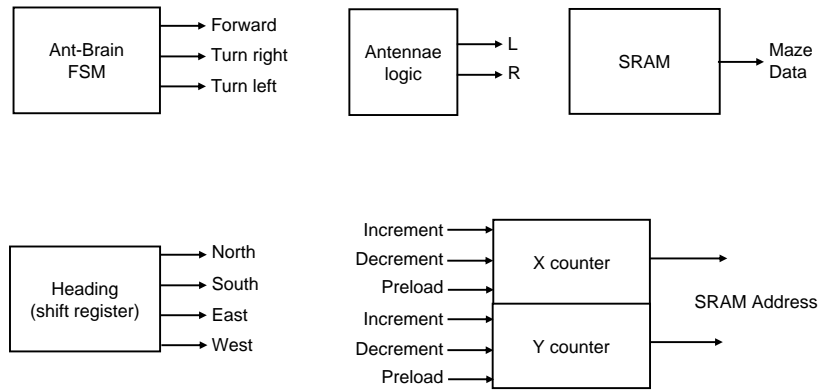

# Design the ant-brain FSM

1. State diagram and state-transition table
2. State minimization
3. State assignment (or state encoding)
4. Minimize next-state logic
5. Implement the design

# Step 1a: State diagram

 

# Step 1b: State-transition table

Exit	State	L	R	Next State	Output
1	Reset				
0	S0	0	0	S0	F
		0	1	S1	F
		1	0	S3	F
		1	1	S3	F
0	S1	0	0	S2	F
		0	1	S1	F
		1	0	S3	F
		1	1	S3	F
0	S2	0	0	S0	TR
		0	1	S0	TR
		1	0	S0	TR
		1	1	S0	TR
0	S3	0	0	S1	TL
		0	1	S1	TL
		1	0	S3	TL
		1	1	S3	TL

## Step 2: State minimization


- Two states are equivalent if they cannot be distinguished at the outputs of the FSM
  - The outputs are the same for any input sequence
- Two conditions for two states to be equivalent
  - 1) Outputs must be the same in both states
  - 2) Machine must transition to equivalent states for all inputs
- Any equivalent states in our state diagram?

## Step 3: State encoding


Exit	X Y	L R	X <sup>+</sup> Y <sup>+</sup>	F TL TR
1	Reset			
0	0 0	0 0	0 0	1 0 0
	0 0	0 1	0 1	1 0 0
	0 0	1 0	1 1	1 0 0
	0 0	1 1	1 1	1 0 0
0	0 1	0 0	1 0	1 0 0
	0 1	0 1	0 1	1 0 0
	0 1	1 0	1 1	1 0 0
	0 1	1 1	1 1	1 0 0
0	1 0	0 0	0 0	0 0 1
	1 0	0 1	0 0	0 0 1
	1 0	1 0	0 0	0 0 1
	1 0	1 1	0 0	0 0 1
0	1 1	0 0	0 1	0 1 0
	1 1	0 1	0 1	0 1 0
	1 1	1 0	1 1	0 1 0
	1 1	1 1	1 1	0 1 0

S0  $\wedge$  00  
 S1  $\wedge$  00  
 S2  $\wedge$  10  
 S3  $\wedge$  11

## Step 4: Minimize the logic

 

## Step 5: Implement the design

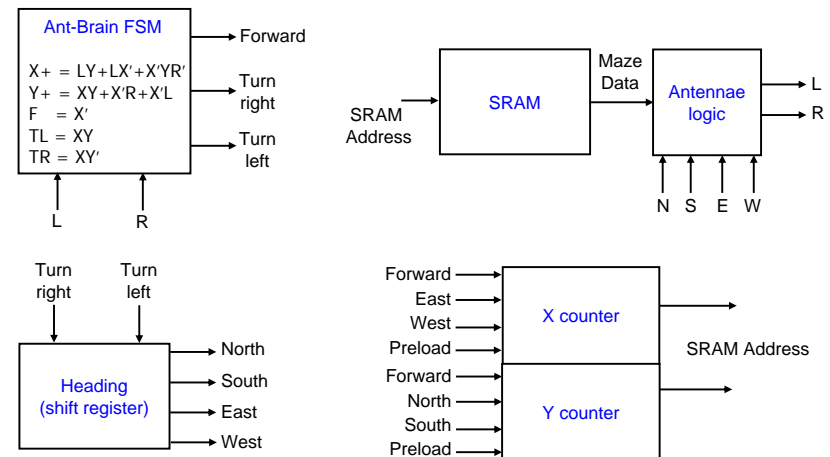

## Antennae logic

### ■ Each memory location says

■ 00000001 ≡ No wall

■ 00000010 ≡ North wall (NW)

■ 00000100 ≡ West wall (WW)

■ 00001000 ≡ South wall (SW)

■ 00010000 ≡ East wall (EW)

■ 00100000 ≡ Exit

Logic for right antennae

$$R = NW(N + W) +$$

$$WW(W + S) +$$

$$SW(S + E) +$$

$$EW(E + N)$$

Logic for left antennae

$$L = NW(N + E) +$$

$$WW(W + N) +$$

$$SW(S + W) +$$

$$EW(E + S)$$

### ■ The ant can be heading

■ N: 0001

Gate count:

4 2-input ORs

■ W: 0010

8 2-input ANDs

■ S: 0100

2 4-input ORs

■ E: 1000

## What we left out...

### ■ Crumbs in cell

■ Ant eats crumbs in every cell it visits

■ Writes crumb file back to SRAM

■ Read crumb file, for future display on monitor

### ■ Need a memory controller

■ A state machine to talk to the SRAM

### ■ Need to deal with startup, exit states