

# Lecture 3: All Hail George Boole

CSE 370, Autumn 2007  
Benjamin Ylvisaker

---

## Where We Are

- Last lecture: Binary numbers & arithmetic
- This lecture: Boolean algebra
- Next lecture: Playing around w/ Boolean functions
- Homework 1 due Wednesday at the beginning of class
- Lab 1 this week. Read it before the session starts!

## Boolean Logic/Algebra

- Notation for writing down precise logical statements (in propositional logic)
- Primitives: true, false, variables
- Connectives: NOT, AND, OR, IMPLIES, ...
- (Almost) all memoryless digital circuits can be seen as Boolean algebra expressions

## Why Do We Care?


- Understanding Boolean logic helps us design “simpler” circuits, both by hand and automatically
- $((A \text{ AND } B) \text{ OR } (\text{NOT } A \text{ AND } B)) \text{ AND } A$
- Equivalent to:  $A \text{ AND } B$

## Lots of Alternative Notations


- I will mostly use:
  - $\neg A$  for NOT A
  - $A+B$  for A OR B
  - $A \cdot B$  for A AND B
- Book lists all of the common notations

## From Expressions to Gates


- NOT A

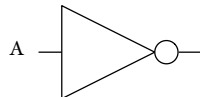

- A OR B

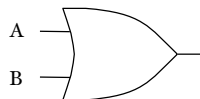

- A AND B

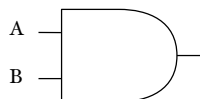

# The Useful Theorems

- Several slides of statements of basic facts about Boolean algebra
- Every theorem comes with a “dual”

## 0 and 1

- $X+0=X$                        $X \cdot 1=X$
- $X+1=1$                          $X \cdot 0=0$

## Idempotence

- $X+X=X$                          $X \cdot X=X$

# Involution

- $\neg\neg X = X$

# Complementarity

- $X + \neg X = 1$

$$X \cdot \neg X = 0$$

# Commutativity

- $X + Y = Y + X$

$$X \cdot Y = Y \cdot X$$

## Associativity

$$\begin{aligned} \bullet (X+Y)+Z &= X+(Y+Z) & (X \cdot Y) \cdot Z &= X \cdot (Y \cdot Z) \\ &= X+Y+Z & &= X \cdot Y \cdot Z \end{aligned}$$

## Distributivity

$$\bullet X \cdot (Y+Z) = (X \cdot Y) + (X \cdot Z) \quad X + (Y \cdot Z) = (X+Y) \cdot (X+Z)$$

## Some Simplifications

$$\begin{aligned} \bullet (X \cdot Y) + (X \cdot \neg Y) &= X & (X+Y) \cdot (X+\neg Y) &= X \\ \bullet X + (X \cdot Y) &= X & X \cdot (X+Y) &= X \\ \bullet (X+\neg Y) \cdot Y &= X \cdot Y & (X \cdot \neg Y) + Y &= X+Y \end{aligned}$$

## Prove Simplification 1

- $(X \cdot Y) + (X \cdot \neg Y) \neq X$        $(X + Y) \cdot (X + \neg Y) \neq X$ 
  - By distributivity
- $X \cdot (Y + \neg Y) \neq X$        $X + (Y \cdot \neg Y) \neq X$ 
  - By complementarity
- $X \cdot 1 \neq X$        $X + 0 \neq X$ 
  - By identity
- $X = X$        $X = X$

## Prove Simplification 2

- $X + (X \cdot Y) \neq X$        $X \cdot (X + Y) \neq X$ 
  - By identity
- $(X \cdot 1) + (X \cdot Y) \neq X$        $(X + 0) \cdot (X + Y) \neq X$ 
  - By distributivity
- $X \cdot (1 + Y) \neq X$        $X + (0 \cdot Y) \neq X$ 
  - By identity
- $X \cdot 1 \neq X$        $X + 0 \neq X$ 
  - By identity
- $X = X$        $X = X$

## Prove Simplification 3

- $(X + \neg Y) \cdot Y \neq X \cdot Y$        $(X \cdot \neg Y) + Y \neq X + Y$ 
  - By simplification 2
- $(X + \neg Y) \cdot ((Y + \neg Y) \cdot Y) \neq X \cdot Y$        $(X \cdot \neg Y) + ((Y \cdot \neg Y) + Y) \neq X + Y$ 
  - By associativity
- $(X + \neg Y) \cdot (Y + \neg Y) \cdot Y \neq X \cdot Y$        $(X \cdot \neg Y) + (Y \cdot \neg Y) + Y \neq X + Y$ 
  - By distributivity
- $((X \cdot Y) + \neg Y) \cdot Y \neq X \cdot Y$        $((X + Y) \cdot \neg Y) + Y \neq X + Y$ 
  - By distributivity
- $(X \cdot Y \cdot Y) + (\neg Y \cdot Y) \neq X \cdot Y$        $(X + Y + Y) \cdot (\neg Y + Y) \neq X + Y$ 
  - By associativity, idempotence and complementarity
- $(X \cdot Y) + 0 \neq X \cdot Y$        $(X + Y) \cdot 1 \neq X + Y$ 
  - By operations with 1 and 0
- $X \cdot Y = X \cdot Y$        $X + Y = X + Y$

## DeMorgan's law (or theorem)


- $\neg(X+Y) = \neg X \cdot \neg Y$        $\neg(X \cdot Y) = \neg X + \neg Y$

## Duality


- A Boolean function is just an expression with a name and a "parameter list" of variables used in the expression
  - $f(A,B,C) = (A \cdot B) + C$
- The dual of a function (written  $f(A,B,C)^D$ ) is the function with  $\cdot$ 's and  $+$ 's swapped and 1's and 0's swapped
  - $f(A,B,C)^D = (A+B) \cdot C$
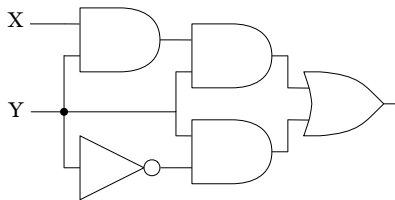
## A Bigger Circuit Diagram


- $(X \cdot Y \cdot Y) + (\neg Y \cdot Y)$



## Real Circuits Can Hurt You

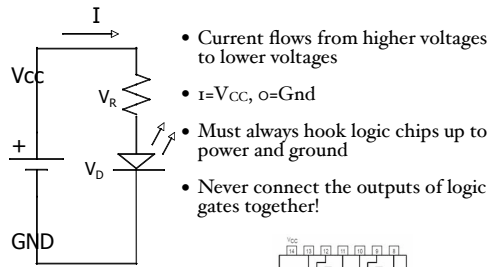

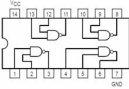- Current flows from higher voltages to lower voltages
- $I = V_{CC}$ ,  $O = GND$
- Must always hook logic chips up to power and ground
- Never connect the outputs of logic gates together!



## Thank You for Your Attention

- Read the lab assignment before you show up for your session!
- Continue reading the book
- Continue homework 1